AUTO TRANSFORMERS

# The Wireless World

6D

## THE PRACTICAL RADIO & TELEVISION JOURNAL

Thursday, May 4th, 1939.

SIDDON BLACKEEN LIBRARY

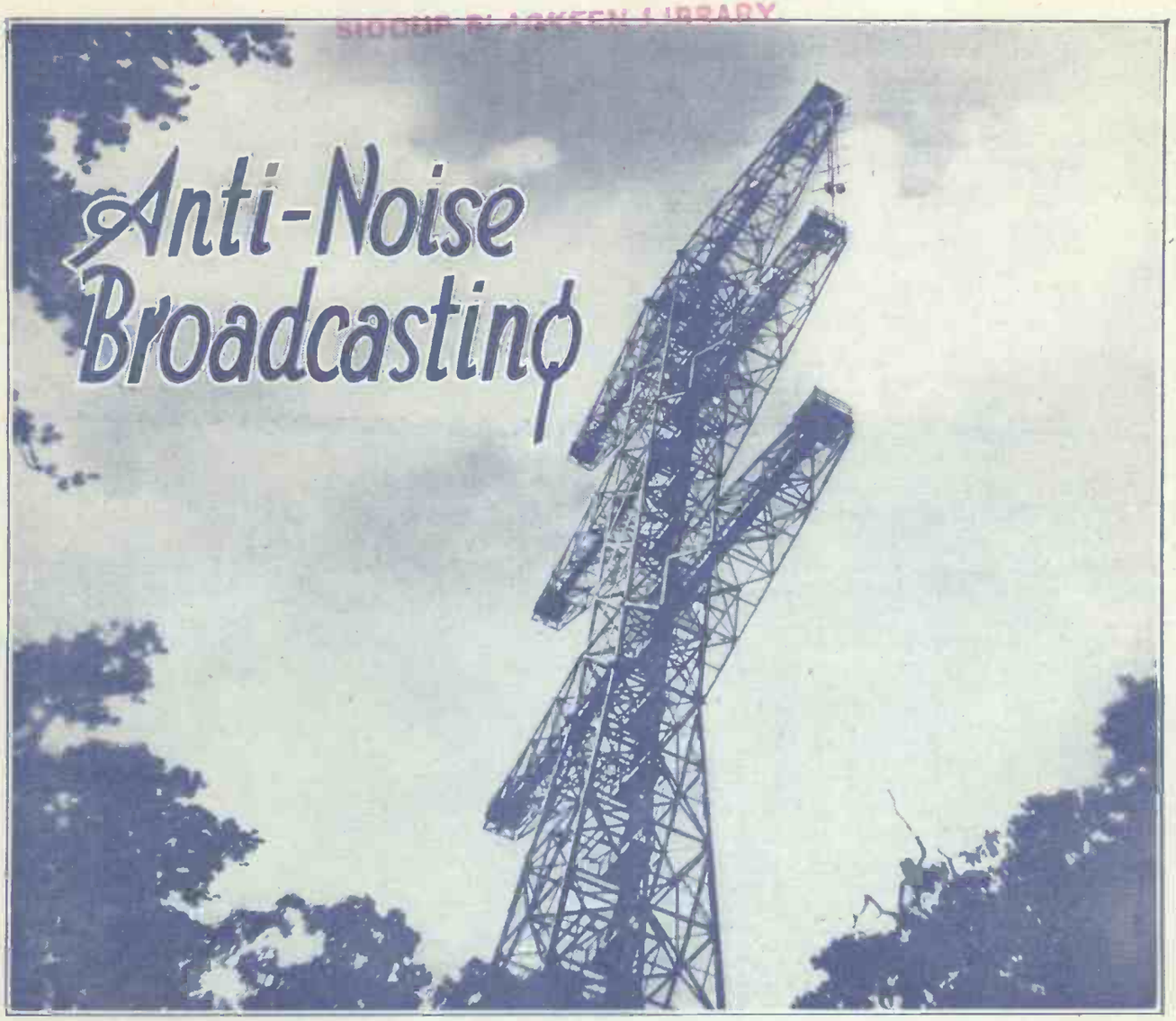


No. 1,027. Vol. XLIV. No. 18.

*Copyright. Registered as a Newspaper for transmission in the United Kingdom. Entered as Second Class at the New York, U.S.A., Post Office.*

An inexpensive **PRECISION** Instrument

# The D.C. AVOMINOR

Regd. Trade Mark.

**ELECTRICAL MEASURING INSTRUMENT**

This instrument provides precision testing facilities at a truly modest cost. Incorporating a fully jewelled moving-coil movement and a 2½-ins. scale, it permits accurate readings of milliamps., volts and ohms, with ranges adequate for the majority of normal circuit, battery and resistance tests. The total resistance of the meter is 100,000 ohms; full scale deflection of 300v. or 600v. is obtained for a current consumption of only 3mA. and 6mA. respectively.

*In case, complete with leads, interchangeable crocodile clips and testing prods; and with comprehensive instruction booklet.*

**45/-**

DEFERRED TERMS IF DESIRED

**13 RANGES**

**CURRENT**
0- 6 milliamps
0- 30 milliamps
0-120 milliamps

**VOLTAGE**
0- 6 volts
0- 12 volts
0-120 volts
0-240 volts
0-300 volts
0-600 volts

**RESISTANCE**
0- 10,000 ohms
0- 60,000 ohms
0-1,200,000 ohms
0-3 megohms

BRITISH MADE.

• *Write for fully descriptive pamphlet*

*Sole Proprietors & Manufacturers.*
**The Automatic Coil Winder & Electrical Equipment Co., Ltd.**
Winder House, Douglas Street, London, S.W.1. *'Phone: Victoria 3404/7.*



# B.I.
## RADIO MATERIALS

We have had a long experience in the manufacture of all kinds of Cables and Wires, Aluminium Sheets and Strips, Static Condensers, Insulators and Iron Work, Telephone Cords and Copper Earthing Rods, for Radio use. Write for Radio Materials catalogue describing these and other B.I. manufactures.

**BRITISH INSULATED CABLES LTD.,**
*CABLE MAKERS AND ELECTRICAL ENGINEERS,*
**PRESCOT, LANCS. Tel. No. PRESCOT 6571**



# The ELECTRICAL REVIEW

*The Complete Technical Journal*

Practical articles on all aspects of electricity supply and utilisation — industrial, commercial and domestic. Latest news of the electrical industry and developments. Advertisement pages form a comprehensive buyers' guide.

*Contents of May 5th Issue :—*

**DISTRIBUTION IN SOUTH WALES**
South Wales Power Company electricity supply system.

**BOILER-WATER TREATMENT**
A review of softening methods by a works chemist.

**NEW ZEALAND**
Account of electrical development; views on trade prospects.

**SWITCHGEAR PRODUCTION**
Illustrated description of a factory at Banbury.

**NEWS AND COMMENTS**

EVERY FRIDAY 6d. Subscriptions: United Kingdom £1 14 8 Canada £1 12 6 Other Countries £2 1 6 per annum, post free.

**ELECTRICAL REVIEW LTD.**
**Dorset House, Stamford Street, London, S.E.1**



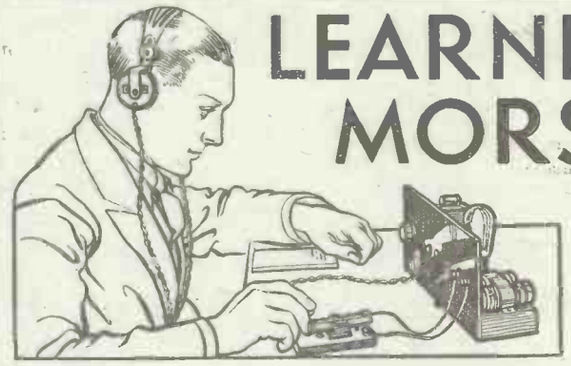

# LEARNING MORSE

AN EASY METHOD OF MASTERING THE INTERNATIONAL SIGNAL CODE

*Published from the Offices of* The **Wireless World** ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1

**6D NET**
**BY POST 7d.**



*THE*

# WIRELESS ENGINEER

The Journal for Professional Engineers and Advanced Wireless Experimenters

Monthly **2/6 net.**

Annual Subscription **32/- post free.**

ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1

W.W.2

The Wireless World
THE PRACTICAL RADIO JOURNAL
29th Year of Publication

No. 1027. THURSDAY, MAY 4TH, 1939 VOL. XLIV. No. 18

Proprietors : ILIFFE & SONS LTD.

Editor :
HUGH S. POCOCK.

Editorial,
Advertising and Publishing Offices :
DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1.

Telephone : Waterloo 3333 (50 lines).
Telegrams : "Ethaworld, Sedist, London."

COVENTRY : 8-10, Corporation Street.
Telegrams : "Autocar, Coventry." Telephone : 5210 Coventry.

BIRMINGHAM :
Guildhall Buildings, Navigation Street, 2.
Telegrams : "Autopress, Birmingham." Telephone : 2971 Midland (5 lines).

MANCHESTER : 260, Deansgate, 3.
Telegrams : "Iliffe, Manchester." Telephone : Blackfriars 4412 (4 lines).

GLASGOW : 26B, Renfield Street, C.2.
Telegrams : "Iliffe, Glasgow." Telephone : Central 4857.

PUBLISHED WEEKLY. ENTERED AS SECOND CLASS MATTER AT NEW YORK, N.Y.

Subscription Rates :
Home and Canada, £1 10s. 4d. ; other countries, £1 12s. 6d. per annum.

*As many of the circuits and apparatus described in these pages are covered by patents, readers are advised, before making use of them, to satisfy themselves that they would not be infringing patents.*

## CONTENTS

| | Page |
|---|---|
| *Editorial Comment* | 407 |
| *Auto Transformers* | 408 |
| *Single-knob Sensitivity Adjustment* | 410 |
| *Frequency Modulation Again* | 411 |
| *Cheap Valve Voltmeter* | 413 |
| *The Radio Compass* | 414 |
| *Television Programmes* | 416 |
| *Modern Insulating Materials—II* | 417 |
| *News of the Week* | 419 |
| *Murphy Television Receiver A56V: Test Report* | 422 |
| *Aircraft Wireless* | 424 |
| *Television Topics: Linear Saw-tooth Oscillator* | 425 |
| *Unbiased* | 426 |
| *The AVC Characteristic* | 427 |
| *Random Radiations* | 428 |
| *Recent Inventions* | 430 |

# *EDITORIAL COMMENT*

## Wire or Wireless?

### *Feeding the Television Relays*

IT would appear that the Radio Manufacturers' Association's offer to bear any financial loss consequent on extension of the television service to the Birmingham area has been generally misunderstood. In a supplementary statement subsequently issued by the Association the details are elaborated, and it is made clear that the offer is confined to reimbursing those concerned for the cost, in the event of the experiment proving unsuccessful, of a wireless link for supplying the proposed Midland transmitter with modulation from the London television headquarters.

It is rightly stressed in the R.M.A. statement that the transmitting station itself will in any case be required sooner or later, and so there is no real excuse for delay in beginning construction. The transmitter that would be built can in no sense of the word be described as experimental, and it would be equally suitable for operating with picture signals supplied either by co-axial cable or a radio link.

Sir Noel Ashbridge, Chief Engineer of the B.B.C., has expressed himself publicly as being in favour of cables for television extensions, as he considers that they provide a neater and more workmanlike solution of the problem, and, above all, one that does not occupy valuable space in the ether. Although it may sound like heresy to admit it in a wireless journal, this is an opinion with which one cannot disagree, at any rate as applied to the permanent system that will, we may be sure, eventually supply the whole of this country with a television service. But for experimental extensions in the early stages the wireless link seems to have much in its favour; its cost is considerably less than that of a cable and it is certainly more flexible.

In the opinion of the technical advisers of the R.M.A. there are no unsurmountable obstacles to the use of wireless, and this opinion is endorsed by Mr. Ralph R. Beal, Research Director of the Radio Corporation of America, who recently said: "R.C.A. engineers are confident that American cities will be linked by means of automatic radio relays, employing ultra-high frequencies. The practicability of such relays has been proved by exhaustive experiments."

If this country is to retain the lead it has gained something must be done quickly, and, from this point of view, the outstanding attraction of the wireless method of distribution is that it can be installed more quickly than cables.

## Battery Portables

### *The "All-dry-cell" Type*

*ALTHOUGH* America was slow in taking up the self-contained battery-fed portable receiver, she has, in one important detail, made amends for her tardiness. As described by a correspondent on another page, the latest American portables are equipped with dry-cell low-tension batteries.

We have for some time urged the use of this form of LT supply for broadcast receivers—and other apparatus—that is intended solely for intermittent and occasional use. Of course, over long periods of operation the accumulator remains the most effective and by far the most economical source of current, in spite of the improvement that has taken place in the better type of dry cell.

# Auto Transformers

## THEIR OPERATION EXPLAINED

By N. PARTRIDGE

*THE main features of an auto transformer are explained in this article and it is then shown that a considerable saving in cost can be effected when conditions permit the use of components of this kind.*

THE auto transformer is a much maligned piece of apparatus. When recommending such an instrument, it is not at all unusual to be met by the retort: "Oh, I want a proper transformer, not a tapped choke." Remarks of this sort are nothing short of libellous. Not only is the auto directly descended from the greatly respected double-wound transformer, but it is an amazingly energetic offspring. It will handle more power, weight for weight, than its revered ancestor could contemplate without acquiring a feverish temperature and other symptoms of distress.

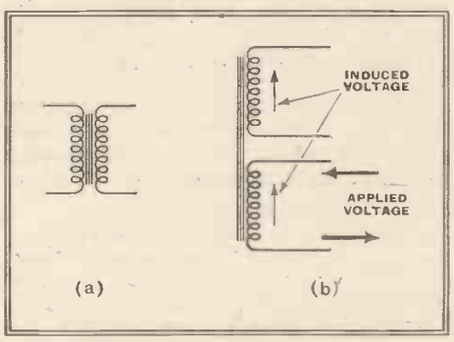


Fig. 1.—Two ways of symbolising a double-wound transformer ; (a) is the more usual way but that of (b) serves better to follow the explanation given in the text.

Fig. 1(a) shows the usual diagram representing a double-wound transformer. In order to make the ensuing discussion more readily understandable, we will redraw it in the form of Fig. 1(b). There is no reason why both windings should not be drawn on the same side of the core, and this proceeding involves less mental readjustment when we join the windings together and thus make an auto of it.

Suppose the primary, which we will assume is the lower winding in the diagram, is rated at, say, 100 v., 1 a., i.e., 100 watts. The DC resistance of this winding would be a matter of only 2 to 3 ohms. Yet, when 100 v. AC is applied (the secondary remaining open circuited) only quite a small current flows. On the face of it, Ohm's Law appears to be in error!

The explanation is that as soon as an alternating current passes round a coil it sets up an alternating magnetic flux in the iron core of the transformer. This in turn induces an opposing voltage in the coil which tends to prevent current from flowing. The state of affairs can be pictured by looking at the arrows in Fig. 1(b). The heavy external arrows indicate the applied voltage at any instant, while the light arrow suggests the internally generated voltage. These two are pushing in reverse directions and almost cancel each other. The induced EMF is always slightly smaller than the applied voltage owing to losses and the inefficiency of the magnetic circuit, and, therefore, a small no-load current flows from the external supply.

It is not necessary for the reader to worry about the technicalities of how all these things come to pass, but it is extremely important to thoroughly understand that an opposing voltage *is* generated within the winding, and that it is this voltage that prevents a heavy current from flowing.

Since both the windings on our imaginary transformer are wound upon the same magnetic core, it is reasonable to expect that if a voltage is induced in one it will also be induced in the other. Such, indeed, is the case, as the application of a voltmeter to the open-circuited coil will readily prove. The induced voltage is found experimentally (and can be proved theoretically) to be proportional to the number of turns on the coil. In other words, a definite voltage is induced in each turn of the winding, and the total voltage exhibited by the coil will be the voltage per turn multiplied by the number of turns.

When the mains are applied to the primary of a transformer, everybody knows that the various secondaries become "alive." But we have just discovered a vital point that normal experience does not reveal, namely, the direction of the voltage. The induced EMF in the secondary is always in the reverse sense to that of the voltage applied to the primary. If the secondary circuit be completed through a suitable load, current will flow through the winding in such a direction as to oppose the magnetising effect of the small no-load primary current. As soon as this occurs the back voltage in the primary falls and the primary current consequently increases (see Fig. 2).

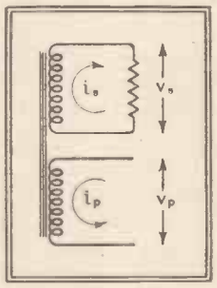


Fig. 2.—The induced secondary current in a double-wound transformer flows in the opposite direction to the primary current.

Were this a serial story it would be a suitable moment to terminate the episode at this juncture, with the secondary doing its best to demagnetise the core, and the primary speedily drawing excess current in a desperate effort to hold its own. However, the sequel must be divulged at once and, as is not unusual with these things, it is somewhat disappointing. The invariable result of the struggle is a draw. The excess primary current ends up by exactly balancing the demagnetising effect of the secondary current, and the small initial primary current that flowed in the no-load condition continues its monotonous occupation of producing an alternating magnetic flux in the core.

### Primary Current

It will be noted that the primary current (on load) consists of two parts. Namely, the magnetising or no-load current and the load current. The former is only a small percentage of the latter in a well-designed component, and can be left out of one's calculations so long as its presence is not entirely forgotten. Henceforth we will ignore its existence.

The magnetising effect of a current passing round a coil is proportional to the current multiplied by the number of turns in the coil. Since, under load, primary and secondary always balance one another magnetically, it follows that

$$i_p T_p = i_s T_s \quad \ldots \quad (1)$$

where $T_p$ and $T_s$ are the turns on the primary and secondary windings, and $i_p$ and $i_s$ are the corresponding currents. It has already been stated that the voltages of the windings are proportional to the turns and, therefore, it follows that

$$i_p V_p = i_s V_s \quad \ldots \quad (2)$$

which is to say that the watts put into the primary equal the watts going out of the secondary. This condition would be substantiated if iron and copper losses were

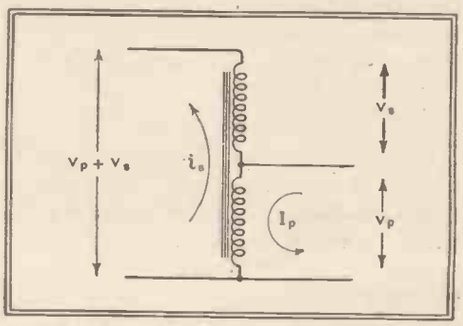


Fig. 3.—By connecting primary and secondary in series it becomes an auto transformer.

**Auto Transformers—**

non-existent, and it is approximately true in practical experience if the transformer is a good one.

Having understood the general principles of transformer action, it is easy to grasp what occurs when the windings are auto connected. Fig. 3 shows the transformer of Fig. 2, arranged in auto fashion with $v_p$ and $v_s$ the original primary and secondary voltages. Under the new scheme the total output voltage becomes $(v_p + v_s)$ since the windings are joined together with their induced voltages in the same sense. $I_p$ and $i_s$ represent the load current drawn from the mains and that passing through the secondary load. Note carefully that $I_p$ is *the current drawn from the mains* and *not* necessarily the current passing through the primary section of the winding.

### Current in Auto Transformer

A critical examination of Fig. 3 will reveal that while the upper section of the winding, i.e., the original secondary, carries the secondary load current ($i_s$), the lower section, i.e., the original primary, carries both the input load current ($I_p$) and also the secondary current ($i_s$). These two currents are in reverse directions and the true current passing through the conductors of the primary winding is $(I_p - i_s)$. If we can show that $(I_p - i_s) = i_p$ the transformer will function quite happily because the currents carried by the upper and lower

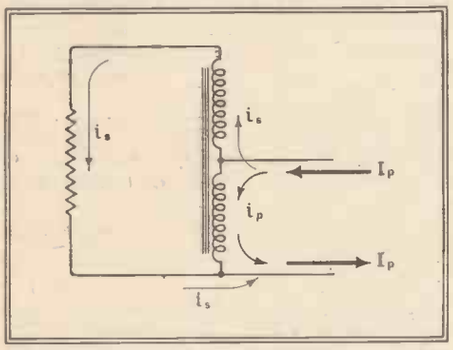


Fig. 4.—The current flow and voltages in an auto transformer are shown here.

sections of the winding will be the same as they were originally, although the output has been increased from $i_s\ v_s$ to $i_s\ (v_p + v_s)$ watts.

The proof is not very difficult. For a condition of equilibrium we know that a state of "magnetic balance" must exist between the two sections of the winding. The demagnetising effect of the secondary is proportional to $i_s\ T_s$ and the magnetising effect of the primary is $(I_p - i_s)\ T_p$. It follows that

$$i_s\ T_s = (I_p - i_s)\ T_p \quad \ldots\ldots\ldots\ldots (3)$$

Earlier it was shown that "magnetic balance" resulted when $i_p\ T_p$ equalled $i_s\ T_s$ (see equation 1). Thus by substituting in equation (3) we conclude that

$$i_p\ T_p = (I_p - i_s)\ T_p$$

and if both sides are now divided by $T_p$ we achieve our object by proving that:—

$$i_p = I_p - i_s \quad \ldots\ldots\ldots\ldots\ldots\ldots (4)$$

A common sense method of visualising what happens without fussing around with algebraical symbols is illustrated in Fig. 4. The load current drawn from the mains ($I_p$) splits into two parts when it reaches the transformer at the junction of the two windings. One part turns to the right and becomes the secondary load current ($i_s$), while the remaining part ($i_p$) goes to the left through the lower or primary winding. Hence $i_p = I_p - i_s$ as before. These two currents, $i_p$ and $i_s$ having completed their various journeyings, link up again on leaving the transformer and proceed home to the local power station as one ($I_p$).

Having elucidated the problem of how an auto works, the solution should not be discarded in the manner of a finished crossword puzzle. The fact that $i_p$ equals $I_p - i_s$ can be extremely useful and transformer manufacturers who know about it can often save a lot of money by its conscientious application. A few examples will make this clear.

*Example* 1.—Input voltage 200 V, output 230 V; 300 watts. The input current will be 300 divided by 200 which equals 1.5 amps, and the output current is 300 divided by 230 which equals 1.305 A. Current through the common portion of the winding becomes $1.5 - 1.305 = 0.195$ amp. (see Fig. 5 (a)). The apparent wattage of each section of the winding is: $200 \times 0.195 = 30 \times 1.305 = 39$ watts.

It follows that this 300-watt auto transformer could be assembled on a core that would accommodate only 40 watts if double-wound.

*Example* 2.—Input voltage 115V; output 230 V, 80 watts.

The input current will be 80 divided by $115 = 0.695$ amp., and the output current 80 divided by 230 $= 0.3475$ amp. Current through the common portion of the winding becomes $0.695 - 0.3475 = 0.3475$ amp. (see Fig. 5 (b)). The apparent wattage of each section of the winding is: $115 \times 0.3475 = 115 \times 0.3475 = 40$ watts.

Again the core required will be one capable of handling 40 watts when double wound. Note that when the transformation ratio is 2 : 1 the current through both sections of the winding is the same, and hence the same gauge of wire can be used throughout. This is the practice adopted for autos designed to operate between the 100 to 120 V and the 200 to 250 V ranges.

*Example* 3.—Input 230 V, output 4 V, 40 watts.

The input current is 40 divided by 230, which is 0.174 amp., and the output current is 10 amps. $(40 \div 4)$. The current through the common portion of the winding is therefore $10 - 0.174 = 9.826$ amps., and the apparent wattage of each portion of the winding is:—

$$226 \times 0.174 = 4 \times 9.826 = 40 \text{ (approx.)}$$

It is evident from the above calculations that the saving is greatest when the input and output voltages are of the same order, i.e. when the transformation ratio approaches unity. In fact, when the ratio *is* unity the transformer vanishes and is not wanted at all whatever the power! At the other end of the scale, Example 3 indicates that little advantage is to be gained by auto connecting when the ratio is large. A point that might well be mentioned here is that for the purpose of preliminary calculations it does not matter which way the auto transformer is working, i.e. stepping up or down. This will influence only the small allowance that should be made in the final design for the voltage dropped in the windings.

The photograph shown in Fig. 6 brings out in a striking manner the economy that can be effected by the use of properly de-

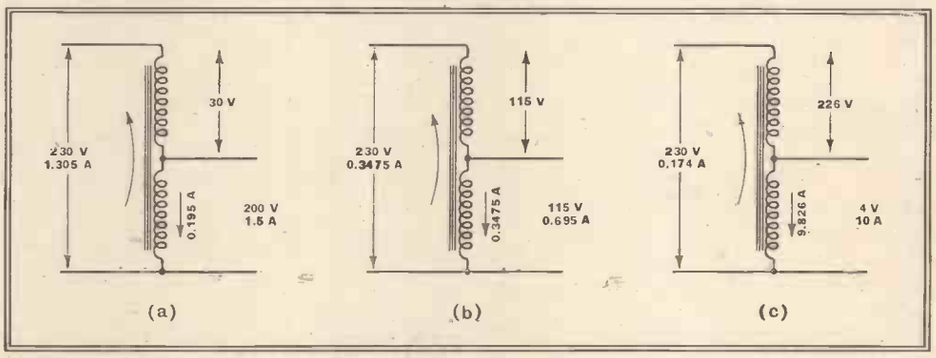


Fig. 5.—Three examples of auto transformer; the method of calculating current distribution is explained in the text.

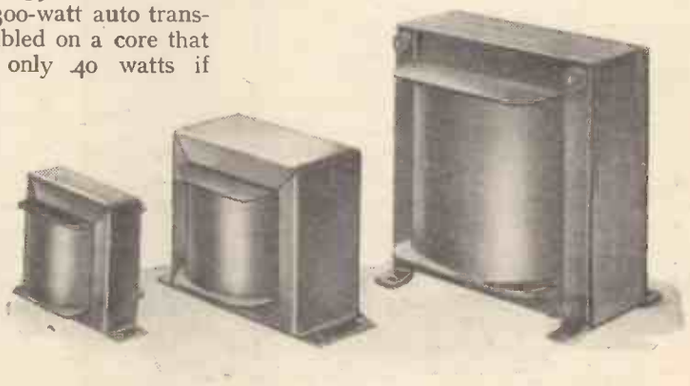

Fig. 6.—All these transformers handle the same wattage but the smallest and medium-size models are auto-wound. The largest weighs 29½ lb., the medium-size one 12 lb. and the smallest 3¼ lb.

**Auto Transformers—**

signed auto transformers. Each of the three transformers illustrated is rated at 500 watts and the complete electrical de-

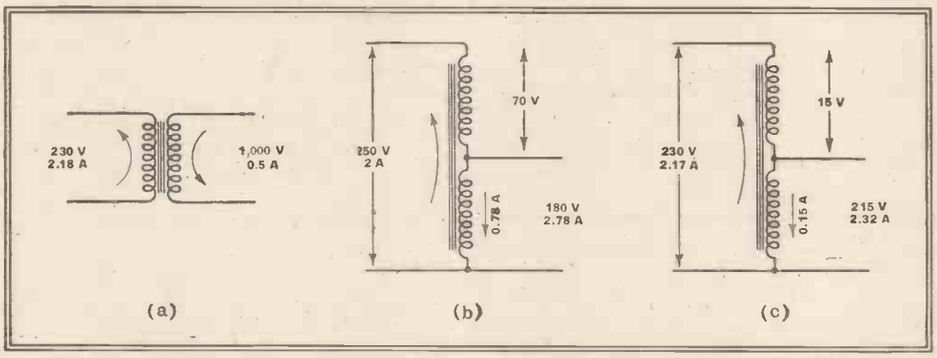


Fig. 7.—Voltages and currents of the three transformers illustrated in Fig. 6 (a) the large model, (b) the medium-size one and (c) the smallest.

tails are indicated in Fig. 7. Were the two smaller items double wound they would have been the same size as the large one. The reader can verify his understanding of the foregoing by calculating from the information given in Fig. 7 what wattage could be accommodated on the two smaller transformers if they were double wound. The answer is approximately 140 and 33 watts.

# Single-knob Sensitivity Adjustment

## COUPLING DEVICE FOR CONTROL SPINDLES

IT is nearly always found necessary to provide two controls for simple TRF receivers to enable, on the one hand, excessive input from strong local transmitters to be cut down, and, on the other, to provide adequate sensitivity for the reception of very weak stations.

In the interests of simplicity, it is highly desirable that these two controls should be operated from the same knob. This can be achieved by means of:—

(1) a three-electrode differential condenser;
(2) a tapped potentiometer;
(3) concentric knobs;
(4) two controls ganged together.

Methods (1) and (2) have various technical disadvantages, and method (3) is not a complete solution. Method (4) may have the following disadvantages:—

(*a*) Undue space may be taken up in attempting to couple two standard components.
(*b*) To overcome disadvantage (*a*) it will be necessary to design special controls having a common spindle.
(*c*) Unless components of special design are used both controls will operate simultaneously, whereas it is desirable that one should complete its travel before the second comes into effect. Further, the second should be brought near zero before the first commences to reduce the input.

A mechanism has been evolved which overcomes these three difficulties. It is simple in operation and takes up very little space.

It couples two spindles, mounted in parallel planes, in such a manner that the

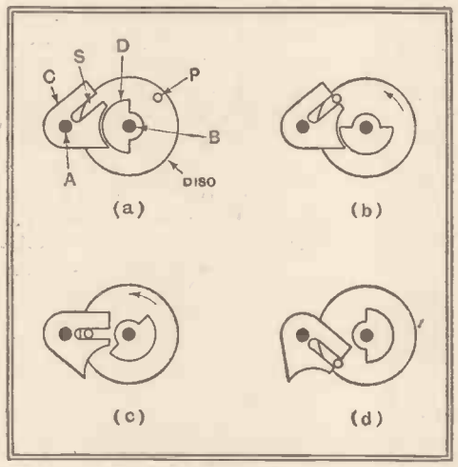


Showing different stages in the operation of the coupling mechanism described in the text. The coupling would be suitable for linking, say, an RF gain potentiometer and a reaction condenser in a simple "straight" receiver.

first control moves to maximum before the second advances considerably, and remains at maximum while the second continues on its travel towards maximum. On returning the second control to minimum the first control does not start to decrease until the second has almost reached a minimum value itself. The mechanism is shown in the accompanying sketch in four positions in order to make clear the principle of operation.

The two controls have spindles A and B respectively. On spindle A a cam is mounted, having a slot S. On spindle B a cam and disc are mounted. A pin P is fixed to the disc. The knob is mounted on the spindle B. At (*a*) both controls are shown at maximum. On rotating the knob in an anti-clockwise direction the spindle B moves towards minimum, and at a point near minimum the pin P enters the slot S. Spindle A then starts to move. This is only possible due to the fact that the cam face C at this point ceases to lock with cam D, as indicated at (*b*). In diagram (*c*) spindle B has moved nearer to minimum and spindle A has completed half its travel. At the point when the pin is about to leave the end of the slot, spindles A and B have both reached minimum. Throughout these movements both spindles remain interlocked either by the slot and pin or the cam surfaces, and stops at minimum and maximum of control B prevent the pin P from leaving the slot S.

# PROBLEM CORNER—18

**An extract from Henry Farrad's correspondence, published to give readers an opportunity of testing their own powers of deduction :—**

All Hallows School,
Berkhamsted.

Dear Henry,

During the hols. my people were having a refrigerator put in ready for the summer, and as it made quite a row in the domestic radio I thought I would have a shot at suppressing it. I wanted to use the smallest coils possible, but the current-carrying capacity question then arose. As I haven't an AC ammeter I tried working it out from the house meter, and although the coils I got should be all right I find they get quite hot. Would you mind checking over my line of thought, because I can't see anything wrong with it?

The meter is marked "900 revs per kWH," and the voltage is 240. When the fridge is on (and nothing else) it does two revs in exactly one minute. That would be 120 revs in an hour, so the watts ought to be $\frac{1{,}000 \times 120}{900}$, which I think is just over 133. So the current ought to be $\frac{133}{240}$, which I make to be 0.55 amp. Seeing that the thing doesn't run continuously I should have thought coils advertised to carry half an amp would have been quite good enough, wouldn't you? Or have I slipped up somewhere?

Yours ever,
Tony.

*Has he? And, if so, where?* *Turn to page 416.*

## "The Wireless Engineer"

THE properties and advantages of a new "all-glass" valve construction are given in the May issue of *The Wireless Engineer*, which is published at 2s. 6d. and is obtainable from booksellers or from the Publishers, Dorset House, Stamford Street, London, S.E.1. Among other articles in this issue is one in which the input impedance of self-biased amplifiers is discussed.

Editorial comment is made on an apparatus recently introduced in Germany for the direct measurement of the "quality" of coils. A monthly feature of *The Wireless Engineer* is the Abstracts and References section, compiled by the Radio Research Board, in which is given abstracts of the articles on wireless and allied subjects published in the World's technical press.

# Frequency Modulation Again

## ANTI-NOISE BROADCASTING AND HOW IT WORKS

By "CATHODE RAY"

TWO years ago[1] I had something to say about the Armstrong frequency modulation system. It was not new even then, but it is only in the last month or two that it has attained the supreme rank of "front-page stuff," as the lay Press has it. I am not now attempting to compete with the well-known organs of journalism in the matter of picturesqueness of description or the wealth of imagination with which they decorate these highly technical matters, but perhaps the tendency for this enthusiasm to lead to a loss of proportion needs some corrective. For example, the solution of some great technical problem that has exercised the minds of the experts for a generation is much more likely to qualify for the status of "front-page stuff" if an unimportant by-product of the thing happens to cause tabby cats to turn light blue and refuse fish. To appreciate the really important features of a technical achievement it is generally necessary to know something about the subject, and the lay writer suffers from the handicap of being unable to assume even the desire for knowledge except of the most superficial kind.

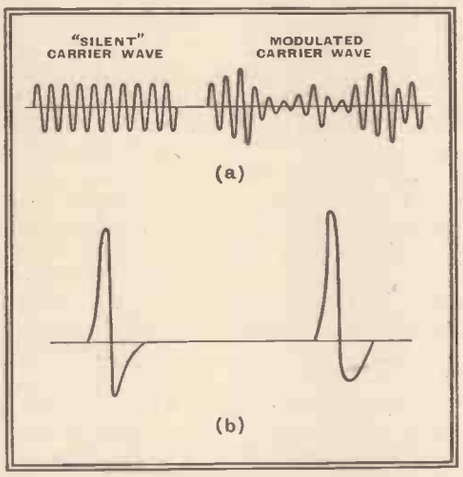


Fig. 1.—The waveforms of (a), an ordinary broadcasting station and (b) noise.

### The Basic Problem

My readers, on the other hand, probably know already that the problem in radio nowadays is not so much how to get the "signal" across as how to exclude "noise." "Noise" in this sense means interference due to a great variety of causes—atmospherics, disturbances caused by electrical appliances, other stations, valve and circuit fluctuations, and so on. It isn't an ideal term, I know, but the American "static" is far worse (*static* means "at rest"). Put concisely, signal/noise ratio is more important than signal strength. If it were not for noise, the range of even a low-power transmitting station would be almost unlimited. If you have ever worked an extremely—one might perhaps say *excessively*—sensitive receiver you will have realised that almost every station in the world can be brought in, but only a few of them are worth having. On a thundery day it may be that only the local station is clear of noise; perhaps not even the local station.

Hitherto, the method of tackling this problem has been to use brute force. The power of the largest broadcasting stations, which used to be 1½ kW, has gone up in turn to 5, 10, 25, 50, 100, 120, 150, and even 500, in the attempt to keep above the rising flood of noise. Of course, this tends to increase the interference trouble. Already one of the 500 kW fellows—Cincinnati — has been told to come down to a more reasonable level.

The main object of frequency modulation is to cut through the noise without excessive power. It has been demonstrated that a frequency modulation station of, say, 1 kW, gives as good a service as an amplitude modulation station of perhaps 20 kW or more. Why? Well, it is not at all easy to see exactly, but some idea can be got by considering how "noise" affects a receiver of the ordinary type. Looking at Fig. 1, (a) shows a typical sample of the waveform received from a broadcasting station. The sound is conveyed by variations in the *amplitude* of the carrier wave; in other words, it is amplitude-modulated. Most of the noises have waveforms something like (b); often much stronger than the transmitter's wave, but very short-lived. The effect of these sudden blows is to jerk the tuned circuits of the receiver into oscillation at whichever frequency they are tuned. The signal amplitude is therefore disturbed, and besides the broadcast programme one hears crackles and bangs.

Now contrast the reception of a frequency-modulated station. The receiver is of a special design, and is arranged to be unresponsive to variations in amplitude. So ordinary stations and noise are not heard. At least, not nearly so much. The transmitter sends out a carrier wave of constant strength, and the sound is imposed on it by causing its frequency to vary to and fro around the normal frequency. The receiver is designed to translate these frequency variations back into sound.

That is a very rough and ready explanation. Actually, there is very much more in Armstrong's system. It would be possible theoretically to convey a programme with only a small variation in frequency, but the discrimination against noise would then be small, too. To get the full benefit of the method the frequency is made to vary over a wide band—about 60,000 cycles each side of normal. That covers the space allotted to about a dozen ordinary broadcasting stations, so a frequency-modulated station has to be treated like a television station and pushed into the ultra-short wave department where a hundred kilocycles or so doesn't matter very much.

### The Methods Compared

Those who have forgotten my previous article on frequency modulation, or never read it, may be a bit confused about the difference between these two methods of modulation, knowing that the common or amplitude modulation system also covers a band of frequencies. That is quite true. Any elementary textbook on radio explains how a variation in amplitude of a constant-frequency wave, as shown in Fig. 1 (a), is equivalent to the combination of a constant amplitude wave and waves of slightly different frequencies (the "sidebands"). But here is the distinction—in such a system the difference in

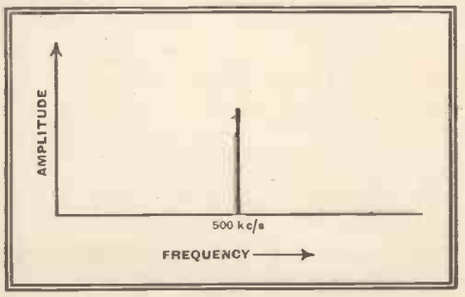


Fig. 2.—Amplitude/frequency diagram of a silent carrier wave transmitting at 500 kc/s.

[1] "Noise," January 15th, 1937.
"Frequency Modulation," July 16th, 1937.

**Frequency Modulation Again—**

frequency between the original carrier frequency and these sidebands is fixed by the frequency of the modulation; whereas in frequency modulation the frequency of the carrier wave itself fluctuates, to an extent that has nothing to do with the frequency of the modulation. It sounds very confusing in words, I'm afraid, but the idea is easy to grasp from simple diagrams representing the result of broadcasting a 1,000-cycle tuning note on a 500-kc carrier wave. In either system the unmodulated carrier wave would be represented as in Fig. 2—a single fixed frequency. In the common AM system the effect of varying the amplitude at a frequency of 1,000 c/s is to produce two more waves, differing 1,000 c/s from the carrier (Fig. 3). A strong sound is shown by (a), a weak one by (b). In FM the frequency of the carrier is varied to and fro 1,000 times a second (Fig. 4). The extent of the variation corresponds to the strength of the sound, so strong and weak are again shown by (a) and (b) respectively. Suppose now that the frequency of the modulation—that is to say, of the sound that is heard—is raised to 2,000 c/s; the effect in Fig. 3 is that the two outside vertical lines spread out twice as far from the centre line, whereas in Fig. 4 there is no visible change, but the line has to be imagined to vibrate to and fro twice as many times per second.

The above simple explanation is rather misleading, because it would lead one to suppose that a frequency-modulated station could be made to operate within a narrower band of frequencies than an A-M station. In fact, even the experts thought so at one time, until a certain Mr. Carson proved mathematically that the frequency band covered by a transmitter could never be less than twice the greatest modulation frequency; which put a permanent end to hopes of packing stations closer together in the frequency scale. However, that is not what Armstrong was after.

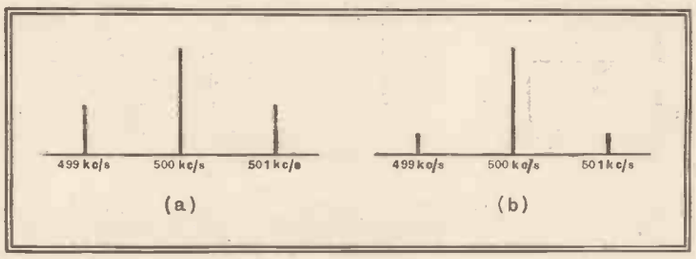


Fig. 3.—The same carrier wave as in Fig. 2 when modulated by a 1,000 c/s note, (a) strong, (b) weak.

### High-Power Tests

In his most recent demonstrations he used two ultra-short wave transmitters; one high-power station, 40 kW on 42.8 Mc/s (just about half-way between the Alexandra Palace sound and vision frequencies), and a low-power station, 0.6 kW, on the still higher frequency of 110 Mc/s (about $2\frac{3}{4}$ metres). The first *ought* to be pretty good, of course, being of far higher power than any other ultra-short wave station in the world, though less than the average medium-wave "main" broadcasting station; and it has been received consistently at 275 miles distance. But at 50 miles even the low-power station gives results better than ordinary broadcasting stations a hundred times more powerful, at the same distance, the superiority being more marked the worse the conditions of noise prevailing at the receiving station.

Another advantage is that there is a further saving at the transmitter due to the very nature of the modulation. As the amplitude is kept constant the transmitter does not have to be designed to cope with the peaks of amplitude that occur in amplitude modulation, and which for a given average radiated power necessitate far larger and more expensive valves, power plant, etc. Then, for the same reason—constancy of amplitude—there is no objection to the use of "Class C" amplification in the output stage of the transmitter, giving a higher power efficiency than the methods that are generally necessary for really high quality in amplitude modulation. Still another point in favour of FM, so far as the transmitter is concerned, is that no drastic results follow if there is accidental over-modulation. With the AM transmitters the control engineers have to be extremely vigilant in preventing the audio signal supplied to the transmitter for modulation from exceeding a certain amount. Not only would it cause distortion, but it might lead to serious and expensive damage and breakdown. In a demonstration of the Armstrong system the modulation was increased up to nearly six times the normal limits, and there was not even noticeable distortion up to three times. Much smaller increases would be absolutely fatal in AM.

On the other side of the balance sheet, the system is far more complicated, and about 50 valves are used in the preliminary stages. That may sound a lot, but remember the 1,079-valve *receiver* I referred to a few weeks ago. And, although they are at the transmitting end, these preliminary valves can be small receiving types, and it would not be uneconomical to duplicate the whole system for guarding against breakdown. The original oscillation is at 200 kc/s (same as Droitwich long-wave station); and modulation is introduced at this stage, producing a small shift in *phase*, that is to say, a fraction of each cycle. The carrier frequency is then multiplied time after time till it reaches 12,800 kc/s; it is whisked back to 891.6 kc/s by a frequency-changer stage as in a superhet; and then multiplied again until it reaches the final 42,800 kc/s. By the time all this has been done the modulation is 120,000 c/s wide (60,000 each side of normal). Then the power is amplified in several stages up to the full output.

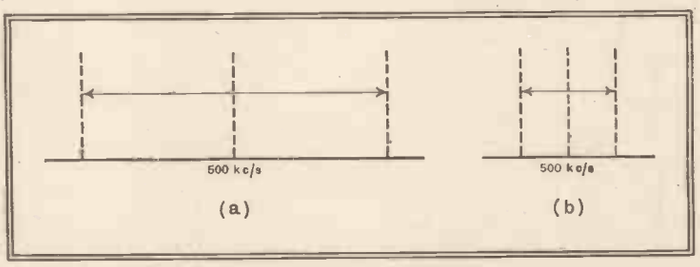


Fig. 4.—Diagrams, corresponding to Fig. 3, for a frequency modulation transmitter.

At the receiver there is no constructional advantage; in fact, it seems inevitable that it must be rather more complicated and costly than an AM receiver. From information available, however, it does not look as if the extra cost need be out of proportion to the increase in performance. This advantage in performance consists, first, as I said, of cutting out most of the noise. Listeners at the demonstrations were greatly impressed by the dead quiet background. The other thing that impressed them was the extremely high fidelity of the reproduction. This was made possible by working in the ultra-short waveband, allowing frequencies up to 15,000 c/s without the interference that would be inevitable at 50-mile range in the medium band. Of course, that is no monopoly of frequency modulation; any ultra-short wave station can be allowed to spread enough to take in the highest programme frequencies. But, with AM, the wider the band the more liable to noise, whereas the opposite applies to FM of the Armstrong brand; and a lot of the naturalness of reproduction was stated to be due to the complete absence of background. So FM can be said to improve the quality actually attainable under working conditions at a distance from the transmitter.

***Our cover illustration shows the aerial tower of Major Armstrong's experimental frequency-modulated station at Alpine, New Jersey. The radiating system, relatively insignificant in size as compared with the tower, can just be seen between the extremities of the upper and intermediate arms.***

The one type of interference that has been found to break through—though much less badly than with AM—is car ignition, because, as ill-luck would have it, this is the type of interference that FM is least effective against, as well as being by far the most vicious on USW.

Well, it would be very nice to have some FM stations for the quality merchants to practise on, but the B.B.C. will have their hands full for some time to come develop-

**Frequency Modulation Again—**

ing the television service, and are not likely to put up stations that would be of no use to existing receivers. On the other hand, it seems hardly likely that such a worked-out invention will be allowed to lapse. One must certainly congratulate Armstrong and his co-workers on their achievement in the face of all previous theoretical assumptions and established precedent.

By the way, seeing that the Alexandra Palace station is systematically received in U.S.A., is it not time that somebody reported the much more powerful Armstrong station over here? Given a suitable receiver, the FM characteristics ought to give good reception.

# Cheap Valve Voltmeter

## SIMPLE WIDE-RANGE MEASURING INSTRUMENT USING A DIODE

By
HUMFREY ANDREWES, B.Sc., A.M.I.E.E.
and F. A. LOWE

TO the serious experimenter, a valve voltmeter of fairly wide voltage range and reasonable accuracy is a very necessary instrument. It has an enormous number of uses, for both audio- and radio-frequency measurements. Unfortunately, many voltmeters of a suitable type are expensive. With a view to producing a valve voltmeter of sufficient accuracy for the normal needs of the experimenter, and which may be easily constructed and calibrated, the instrument described below has been designed.

Perhaps the simplest voltmeter to construct is the leaky grid or anode-bend triode type. The anode current, or rather the change in anode current, is a measure of the AC voltage aplied to the grid of the triode and usually this involves the use of a calibration chart or curve. Anyone who has used this type of meter knows that, although great accuracy can be obtained, the calibration curve can be a great nuisance and unless permanently fastened to the meter in some way, has a nasty habit of getting lost. In any event if great accuracy is not required and speed is important a direct reading meter saves a great deal of time.

The writers, therefore, have overcome these difficulties by designing a meter, having a reasonable input impedance, with which any alternating voltage from between 1 volt to 300 volts can be easily read directly on the scale of the meter.

To make the instrument as simple as possible a 2-volt triode is used connected as a diode. A diode of the type used for rectification in superheterodynes, or for supplying AVC was not used, as it was found that the zero space current is too high.

The most expensive item in all instruments of this type is usually the meter used to read the current flowing through the diode. To obtain a fairly wide range at a reasonably high input impedance it was decided to use a meter having a maximum reading of 50 microamperes.

The particular instrument used is obtainable at a low price and has the required accuracy; it is a Leslie Dixon 0-50 microammeter. The circuit diagram of the voltmeter is shown in Fig. 1 and the photographs show the completed instrument. It will be seen that it is self-contained and very compact.

An exterior view of the instrument.

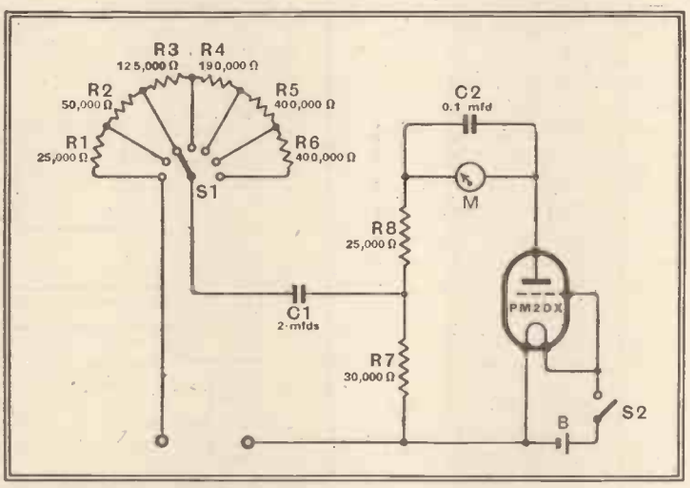


Fig. 1.—The voltmeter itself is of fixed range and a wide variety of input voltages is catered for by the input potentiometer, which is controlled by the 7-way switch S1.

A Mullard Type PM2DX valve is used, but any valve having similar characteristics may, of course, be employed. It will be noted from an examination of Fig. 1 that the control grid is connected to the positive end of the filament. This is done to reduce the standing space current. It was found that with the grid connected to the anode the space current was about 5 microamps, but with the connections as shown this value dropped to about 1 microamp.

The ranges of the meter illustrated are as follows: 5, 10, 20, 50, 100, 200, 300 volts maximum, using a seven position switch, but these may, of course, be altered to suit individual requirements. As the meter is scaled 0-50, no calibration curve is necessary and the voltage reading is obtained by multiplying by a simple factor. It was found that the readings were accurate to about plus or minus 5 per cent. using standard resistances.

Calibration, that is to say, checking the accuracy of the ranges, was carried out at 50 c/s using an Avometer, and it is felt that this is probably the best method.

The frequency characteristic of the instrument is good and the writers feel confident that in view of its extreme simplicity the time and money spent on its construction will be well repaid.

Apart from the general uses at radio-frequency the meter is suitable for all audio-frequency work and, of course, for checking valve heater voltages.

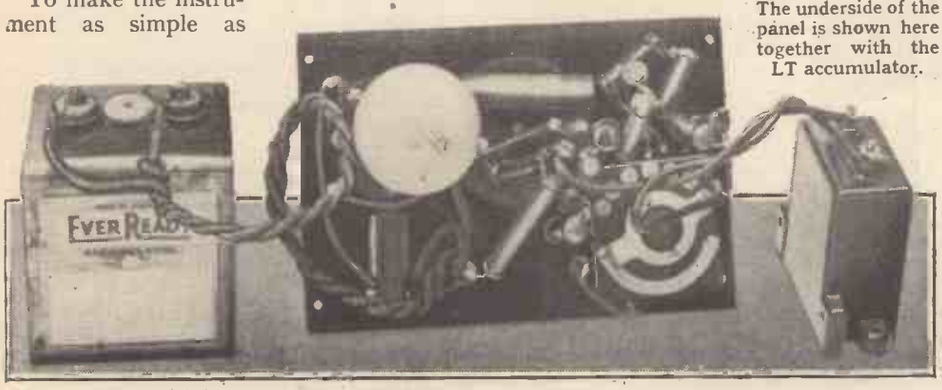


The underside of the panel is shown here together with the LT accumulator.

# The Radio Compass

*DESCRIBING the principles of operation of specialised direction-finding instruments, largely used on aircraft, in which visual or aural indication of bearing (or deviation from course) is given more or less automatically and without the usual "searching" process.*

## Elaborations of the Direction-finder Principle

AN expression which has been used rather freely to describe any automatic method of direction-finding which claimed to be an improvement on the ordinary frame aerial appears at the head of this article. It was applied, for instance, to the early rotating beam transmitter which radiated first a "start" signal and then a timed sequence of impulses at successive points of the compass, so that a distant navigator could ascertain his bearings with the help of a stop-watch. As far back as 1920, the U.S.A. Navy installed a receiving set which was officially called a radio-compass though, in fact, it was little more than a convenient form of the well-known frame-and-open-aerial combination that has the merit of indicating "sense" as well as direction.

More recently directional systems have been developed in which two overlapping beams (one modulated with dots and the other with dashes) mark out a definite path or "guideway" for air navigation. The machine is flown along the centre line of overlap, where the dots and dashes merge into a sustained or unbroken note. At first the pilot had to depend upon a pair of headphones to distinguish the starboard "dots" and the port "dashes" from the continuous note which told him he was keeping on his proper course. Subsequently, the headphones were replaced by visual indicators which showed him automatically the extent and direction of any deviation from the straight path. This kind of installation—also known as a radio-compass—is representative of the more modern type of instrument, which is usually designed for work in the air where quick results and automatic action are of the first importance.

Generally, it consists of a small frame aerial maintained in constant rotation at a speed sufficiently high to keep the indicator steady, whether the latter is a centre-zero meter possessing a certain amount of inertia, or a cathode-ray tube depending on a persistence-of-vision effect. In some cases the aerial is positively driven, whilst in others the effect of physical rotation is secured by a method of switching which leaves the aerial stationary.

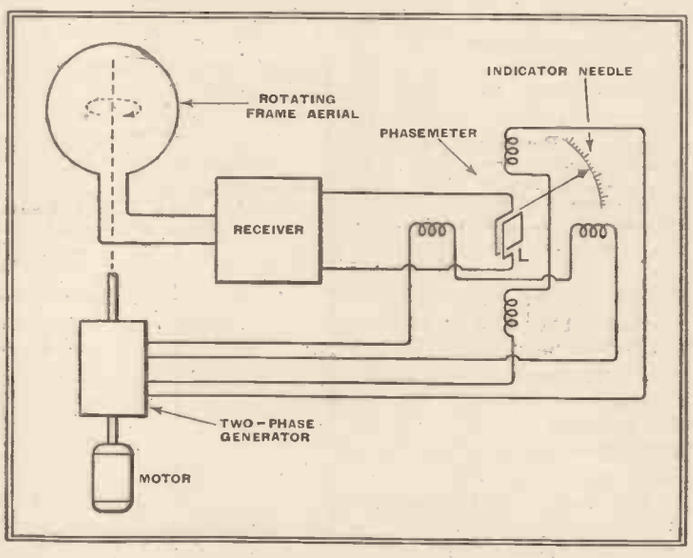


Fig. 1.—Simplified diagram of a single-frame radio compass.

When a single frame aerial is constantly rotated, at a speed of, say, five revolutions a second, the received signal strength rises to a maximum each time the plane of the aerial cuts across the line of the distant transmitter; this will occur twice in the course of each complete revolution. Similarly, there are two points of minimum signal strength, where the phase of the pick-up is also reversed. The resulting current is therefore sinusoidal, with a low-frequency "amplitude" variation of 10 cycles a second, and so long as the machine keeps on a straight course towards the transmitter, the maxima and minima will always repeat themselves at the same points on the circle of rotation. In other words, both the frequency and phase of the signal current remain constant.

But if the machine changes course the point in the circle of rotation at which the aerial picks up maximum signal strength will follow suit. That is to say, the phase of the pick-up current shifts by an amount which depends upon the change in direction. This phase-shift, which can be measured by comparison with a second current of constant frequency and unvarying phase, then gives a direct indication of the new bearing of the distant transmitter.

As shown in Fig. 1, the frame aerial is driven by a motor through reduction gearing, and the local "reference" current is supplied from a two-phase motor mounted on the same spindle. After the phase of the reference current has been centred about the fore-and-aft line of the machine it is supplied to the field coils of the phasemeter or indicator, whilst the pick-up current from the aerial is fed through the receiver into the pivoted search coil L.

The reference current produces a constantly rotating field in which the coil L seeks to set itself so as to link with maximum flux at the moment when the signal

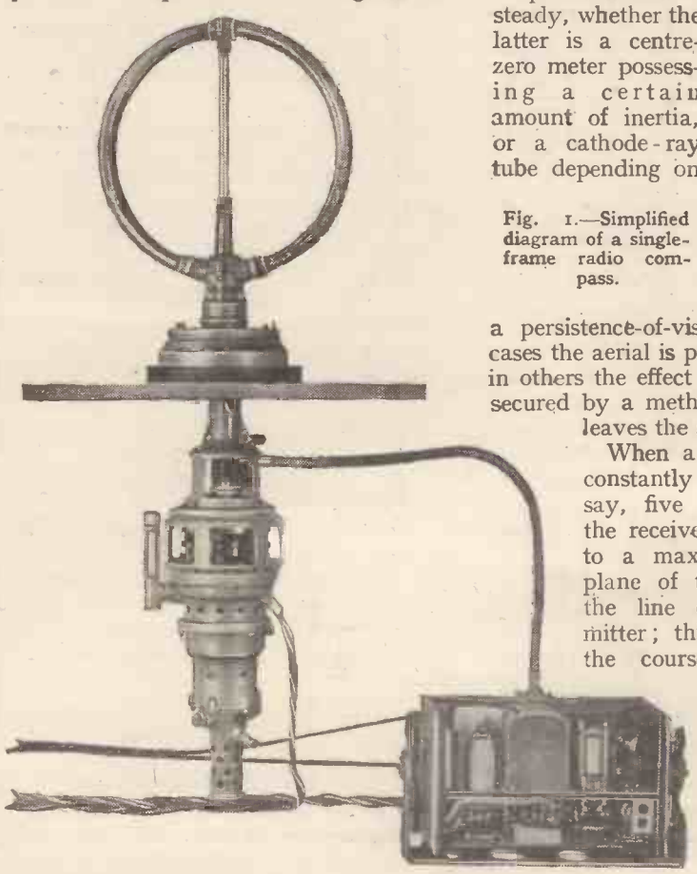

A direct-reading aircraft direction-finder produced by Standard Telephones and Cables.

**The Radio Compass—**

current is greatest. If the transmitter is located along the fore-and-aft line of the machine, this will occur when the needle points to zero, but for any other position of the transmitter the coil L must move in one direction or the other to a point where both the flux and the current are in phase. The needle will then show the bearing of the transmitter relatively to the fore-and-aft line of the machine.

Fig. 2 (a) shows another direct-reading instrument in which the rotating frame F is combined with a vertical aerial A to produce the well-known "heart-shaped" curve of Fig. 2 (b). This gives only one point of maximum and one point of minimum signal strength, so that it is free from the usual 180 deg. ambiguity of the single frame. The indicator is operated by reversing the pick-up current each time the aerial passes through the fore-and-aft line of the machine and balancing the currents collected on one side of the reversing switch against those collected on the other side.

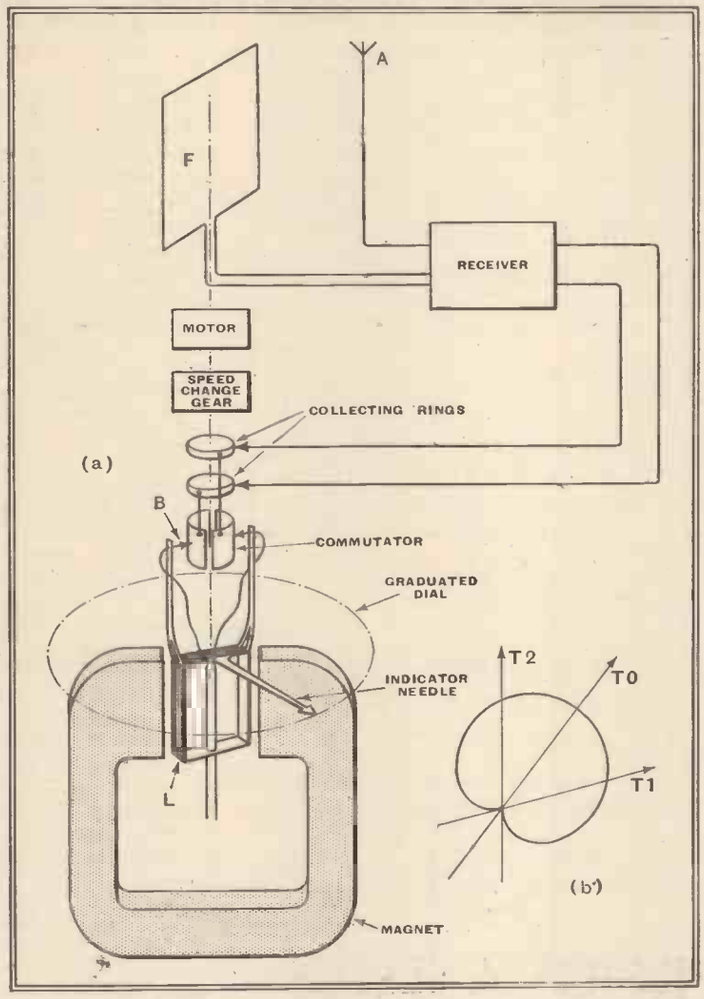


Fig. 2.—Rotating frame radio compass giving indication of sense. Diagram (b) explains its action.

The frame is rotated by a motor, which also drives the reversing switch or commutator (and its collecting rings) at double speed. The signal pick-up from both aerials is first combined in the receiver and the output is fed to the collecting rings of the commutator. The indicator needle is carried by a galvanometer coil L, which swings about a pivot between the poles of a magnet and is fed with current from the commutator through brushes B.

### Operation of Indicator

If the beacon transmitter is situated along the fore-and-aft line of the machine, that is, in the direction marked *To* in Fig. 2 (b), the commutator will collect exactly equal currents on both sides of the reversal point and the indicator needle remains at zero. But if the machine is heading in a different direction, such as T1 or T2, the commutator (which is fixed relatively to the fore-and-aft line) no longer collects equal currents. For the position T2 the excess current will tend to rotate the coil L clockwise, whilst in the position T1 the conditions are reversed. In both cases, however, the torque is such as to urge the needle towards the "maximum" position *To*, that is, towards the line of the distant transmitter, so that the indicator shows the angle which this bearing line makes with the flight of the aeroplane.

In Fig. 3 the aerial system is kept stationary and the critical bearing line is ascertained by a method of switching—an arrangement which is particularly suitable for use when "homing" or flying directly on to a distant beacon. The frame aerial F is connected to the top grid of a pentode valve, and the output from this valve is combined with the pick-up from the vertical aerial A and fed to the receiver, where it produces a "heart-shaped" response. The two lower grids of the pentode are back-coupled at L so as to generate a local oscillation having a frequency of, say, 100 cycles a second. The output from the receiver is also fed back at L1.

### Valve-controlled Switching

The local oscillation produces the effects shown in detail in Fig. 4, where curve 1 represents the RF signals picked up by the non-directional aerial A, whilst 2 and 3 show the signals picked up by the frame aerial on two opposite sides of its critical minimum position. The phase of the current in a frame aerial reverses as it passes through this point, so that whilst curve 2 is shown in phase with the non-directional signals, curve 3 is drawn in phase-opposition. Curve 4 is the low-frequency oscillation produced in the circuit L, and curve 5 shows how it is modulated, through the pentode valve, by the frame signals. The signals from the non-directional aerial A do not pass through the pentode, and therefore remain unaltered, but curves 6 and 7 show their effect on the signals received by the frame according as the latter points to one side or other of the critical bearing line. In one case the two signals reinforce each other, whilst in the other they are in opposition.

The meter M is adjusted by a potentiometer P until the needle points to zero, when the normal current from the middle grid (which forms the anode of the local-oscillator part of the valve) passes through the output resistance R. The needle will then be deflected to one side or other of

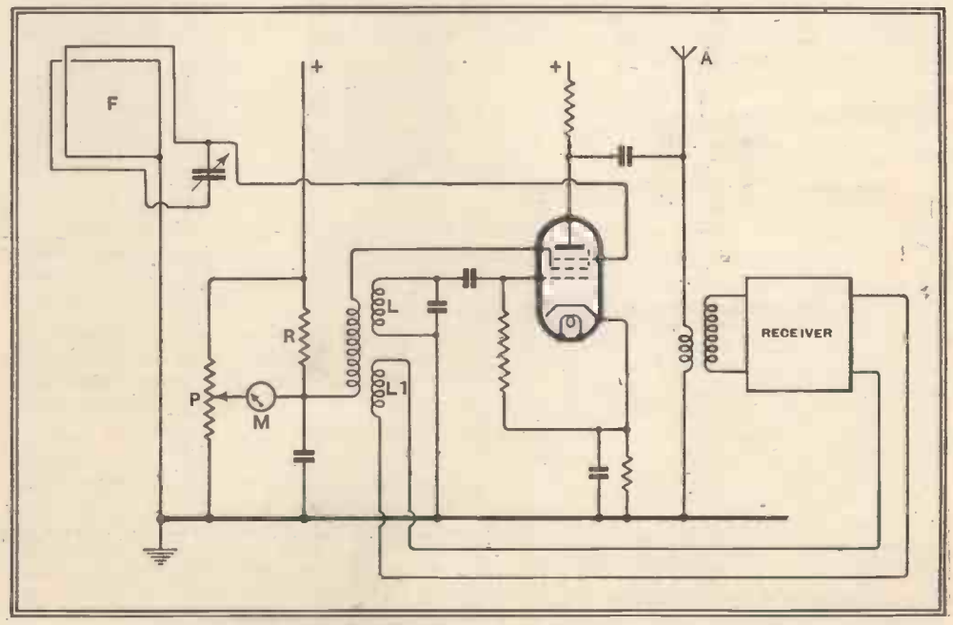


Fig. 3.—Homing compass with high-speed switching and fixed frame.

**Radio Compasses—**

the zero as the frame aerial is turned to the right or left of the critical bearing line.

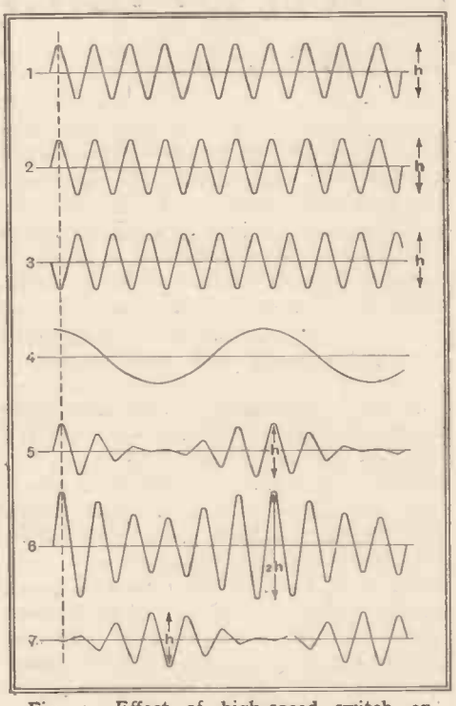


Fig. 4.—Effect of high-speed switch on received signals.

As the frame aerial is usually mounted on the fuselage so that it is fixed relatively to the fore-and-aft line of the aeroplane, the indicator will show automatically any deviation from the straight-line course when the machine is "homing" on to a beacon station. Preferably, the signals are fed to two different pentode valves which operate in the manner just described to light up separate port and starboard glowlamps if the machine yaws to one side or other of its proper path.

In Fig. 5 two fixed frame aerials A, B, mounted at right-angles to each other, are used to secure a similar result. The strength of signal picked up at any instant by each aerial depends upon its setting relatively to the distant beacon, just as in the well-known Bellini-Tosi arrangement. As shown, both aerials are coupled to an

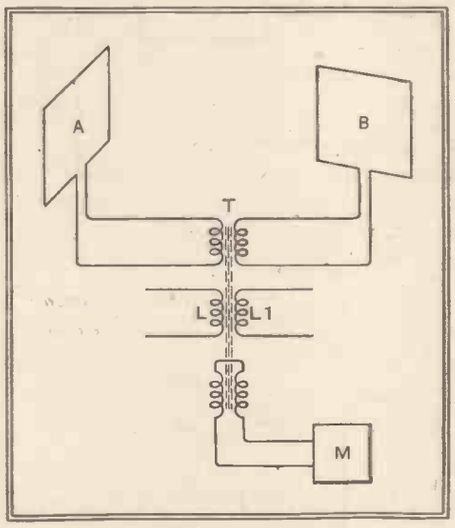


Fig. 5.—Non-rotating crossed frame compass.

iron-cored RF transformer T, to which a locally generated modulating current of, say, 100 cycles, is supplied through coils L, L1. In this instance the local current must be fed in quadrature to correspond with the right-angled setting of the two aerials.

The local current varies the permeability of the iron core of the common transformer, and so modulates the incoming signal at that frequency before the latter is fed in phase to the meter M. Here the signal current is compared with the locally generated current, which is also supplied directly to the meter in order to serve as a reference. Any difference in phase between the two currents will then force the indicator needle to set itself, in the manner already explained, so as to indicate the bearing of the distant transmitter.

---

**Electro-Acoustics.** By Prof. Erwin Meyer. 117 pages, 84 illustrations, including 24 half-tones. G. Bell and Sons, Ltd. Price 10s.

THE title and list of contents (I. Physical and Physiological Foundations. II. Electro-Acoustical Measurements. III. Microphones and Loud Speakers. IV. Sound Recording Technique, and Electrical Music. V. Architectural Acoustics) suggest that this might be yet another standard text-book on a subject which, long neglected, is now reasonably well served by general text-books for the student.

The contents list is certainly familiar, but the treatment, while it retains enough well-known theory to give continuity, makes frequent excursions into those fascinating by-ways which the originality of Dr. Meyer and his co-workers at the Institute für Schwingungsforschung, Berlin, and other investigators in Germany, have opened up.

There is a strong bias towards experimental methods and many useful hints for those engaged in acoustic measurements, particularly in connection with architectural acoustics. The principle underlying the measurement of velocity amplitude in gramophone records by optical methods is explained in detail, as are the analysis of sounds of short duration by the Gruzmacher grating and the Freystadt spectrometer.

On the subject of loud speakers there is some very useful information concerning baffles, which suggests that interference patterns may still exist even when the radiation from the back of the cone is absorbed; also a comparison of transient measurements at different parts of the frequency scale.

Electrical musical instruments are discussed with much interesting data on electrical pianos.

This is altogether a stimulating work and one which naturally supplements the recognised text-books on acoustics. F. L. D.

---

# TELEVISION PROGRAMMES

Sound 41.5 Mc/s Vision 45 Mc/s

THURSDAY, MAY 4th.

**3,** Stanley Holloway in "Eastern Cabaret," with Browning and Starr and Hari Sin Bey, compère. **3.45,** 239th edition of Picture Page.

**9,** Edward Cooper and Patricia Leonard in "Order to View," No. 3. **9.45,** Gaumont-British News. **9.55,** 240th edition of Picture Page. **10.25,** News.

FRIDAY, MAY 5th.

**3-4.30,** "On the Spot," the play by Edgar Wallace. Cast includes Arthur Gomez, Percy Parsons and Joan Miller.

**9,** "London Wall," a play by John van Druten. Cast includes Lewis Stringer, Barbara Couper and Nadine March. **10.30,** News.

SATURDAY, MAY 6th.

**12-12.45,** The Departure from London of The King and Queen on their State Visit to Canada, the United States, and Newfoundland. Television cameras will be situated outside Buckingham Palace and at Waterloo Station.

**3,** A Gershwin programme by Eric Wild and his Band. **3.25,** Cartoon Film. **3.30,** Punch and Judy show by Frank Worth. **3.40,** British Movietonews. **3.50,** "In Our Garden,"—C. H. Middleton.

**9,** "Eastern Cabaret" (as on Thursday at 3 p.m.) **9.55,** Gaumont-British News. **10.5,** Wyndham Goldie in "Five at the George," a ghost play by Stuart Ready. **10.30,** News.

SUNDAY, MAY 7th.

**3,** Pas Seul. **3.15,** Cartoon Film. **3.20,** "Early Days," Film. **3.30,** "Anna Janska, The Bolshevik Empress," by George Bernard Shaw. **8.50,** News. **9.5,** Friends from the Zoo. **9.20,** Cartoon Film. **9.25-10.50,** The Hungarian State Ballet from the Adelphi Theatre in "Hungarian Rhapsody."

MONDAY, MAY 8th.

**3-4.30,** "London Wall," (as on Friday at 9 p.m.)

**9,** Starlight—Peggy Wood. **9.10,** Salute to America," a picture of life across the Atlantic. **9.45,** Gaumont-British News. **9.55,** Black and White Boxing Demonstration. **10.15,** Bridge Demonstration by a team of International Women Players. **10.30,** News.

TUESDAY, MAY 9th.

**3,** Renée Houston and Donald Stewart in Cabaret, with Charles Harrison and Afrique. **3.40,** Gaumont-British News. **3.50,** "Looking for a House." Pearl Binder describes her trials with the help of drawings.

**9,** O.B. from the stage of the Coliseum. **10,** The Right Hon. R. B. Bennett, K.C.—Speaking Personally. **10.10,** "A Game of Cut-Throat," a "telecrime." **10.35,** News.

WEDNESDAY, MAY 10th.

**3,** "Order to View" (as on Thursday at 9 p.m.). **3.45,** Cartoon Film. **3.50,** British Movietonews.

**9,** Talk by Frank Lloyd Wright, the American architect. **9.10,** Starlight—Ivor Moreton and Dave Kaye. **9.20,** Cartoon Film. **9.25,** Week ends in the Country. **9.45,** Gaumont-British News. **9.55,** "Castle in Spain," a programme of dances to music by Albeniz and Granados, with Sidonie Goossens, harp. **10.30,** News.

---

## HENRY FARRAD'S SOLUTION

(See page 410)

YES, Tony has slipped up. As he mentions an AC ammeter, presumably the mains are AC, and he is wrong in supposing that watts in an AC circuit are equal to volts×amps. In an inductive load such as a refrigerator motor the actual power is only a fraction of volts×amps, this fraction being known as the power factor. Supposing the power factor to be 0.5, the current would be 1.1 amp, which would produce *four* times as much heat in the suppressor coils as the current Tony bargained for, because heat is proportional to the square of the current.

# Modern Insulating Materials

## Part II.—CERAMICS: THEIR PROPERTIES AS INSULATORS AND DIELECTRICS

By L. HARTSHORN, D.Sc.

IT is well known that ceramics in the raw state take the form of a clay, which can be moulded to shape while wet, dried without change of shape (although usually with some shrinkage), and finally hardened or vitrified by heating to a very high temperature.

China clay or kaolin is a hydrated compound of alumina and silica. The clay used for the manufacture of ordinary porcelain is a fine-grained mixture of this material with quartz and felspar (which is a complex compound of potash, alumina and silica). The felspar acts as a flux by combining at the high temperature with a certain proportion of the other materials to form a glass, which softens at a much lower temperature than the other constituents and, therefore, serves to bind them together into a coherent mass. Thus the final product may be regarded as a mass of microscopically small crystals bonded together by thin films of glass.

It is interesting to note that these materials are the inorganic equivalent of the organic plastics: the one material consisting of an agglomeration of tiny mineral crystals bonded by thin glassy films, and the other particles of wood or cellulose fibre bonded by an organic resin. The analogy even extends to the method of fabrication, for ceramic components may be made by dry dust pressing as well as by the wet plastic process. Both materials owe their industrial importance in greater part to the fact that such moulding processes lend themselves so well to mass production. Large ceramic components can also be made by a process of casting.

The importance of the new ceramics to the radio industry is due to the wide range of their electrical properties. It is obvious that the electrical properties of ceramics will vary very considerably with the nature and relative proportions of their crystalline and glassy components. The recent successes of the ceramic technologist in producing materials which are so admirably suited to certain radio applications are due to the fact that he has succeeded in bonding certain mineral crystals having the desired electrical properties with the minimum quantity of glassy material.

Glasses, except those like fused quartz which are of very high melting point, are electrically inferior to these mineral crystals, and therefore the proportion of readily fusible glassy component must be kept small. It is, however, equally important that the material shall be impervious to water. The whole mass must be thoroughly bonded or "vitrified," and not porous. These conditions are evidently to some extent conflicting, and it is therefore perhaps not surprising that nominally the same ceramic materials vary considerably in quality. Nevertheless, all the new materials mark a great advance on ordinary "electrical porcelain."

*ONE of the most remarkable developments in insulating materials in recent years has been the increasing use of ceramics in the radio industry. Not only are these materials very stable mechanically, but they can be blended to give a wide range of dielectric properties*

The new materials may be divided into groups according to their principal crystalline constituent. The first group is the steatite group, in which the principal constituent is magnesium silicate. These materials are specially valuable where low dielectric loss (and, of course, great mechanical strength and permanence) are the main considerations, e.g., for coil formers. They are made from steatite (soapstone) or talc, both hydrated forms of magnesium silicate, with a small proportion of, say, kaolin and felspar (a potassium alumino-silicate) to form the glassy binder. Glasses containing the alkali metals are of relatively high power factor, since they contain sodium or potassium ions which give rise to electrolytic conductivity. Thus by the use of fluxes other than felspar the losses may be made even smaller. Examples of these materials are "Frequentite," "Calit," and "Calan." They have a dielectric constant of about 6, and power factors ranging from about 0.001 to 0.002 at frequencies of the order of 10 Mc/s.

It should be mentioned that ordinary electrical porcelain is also made from steatite, but the proportions of clay and felspar used in its manufacture are greater than those in the high-frequency ceramics. Manufacture is correspondingly easier, but the power losses are of a higher order. Steatite materials have also been used for many years for special experimental work in which insulation capable of withstanding very high temperatures is required. For such purposes the material is moulded approximately to the shape required and given a preliminary firing, after which it is strong enough for the final shaping by turning, drilling, tapping, etc. The component is then fired at a higher temperature to complete the vitrification.

For certain applications, such as coil formers used in the construction of constant-frequency oscillators, the smallness of the thermal coefficient of expansion is the main criterion, and for such work materials in which the main crystalline constituent is cordierite $2MgO, 2Al_2O_3, 5SiO_2$ have been found advantageous. These may be regarded as developments of the steatite materials, in which some of the steatite is replaced by alumina.

A completely different class of ceramics is that in which the principal constituent is rutile, a crystalline form of titanium dioxide, which is remarkable for its very high dielectric constant. It has been known for thirty years or more that the dielectric constant of rutile has the very

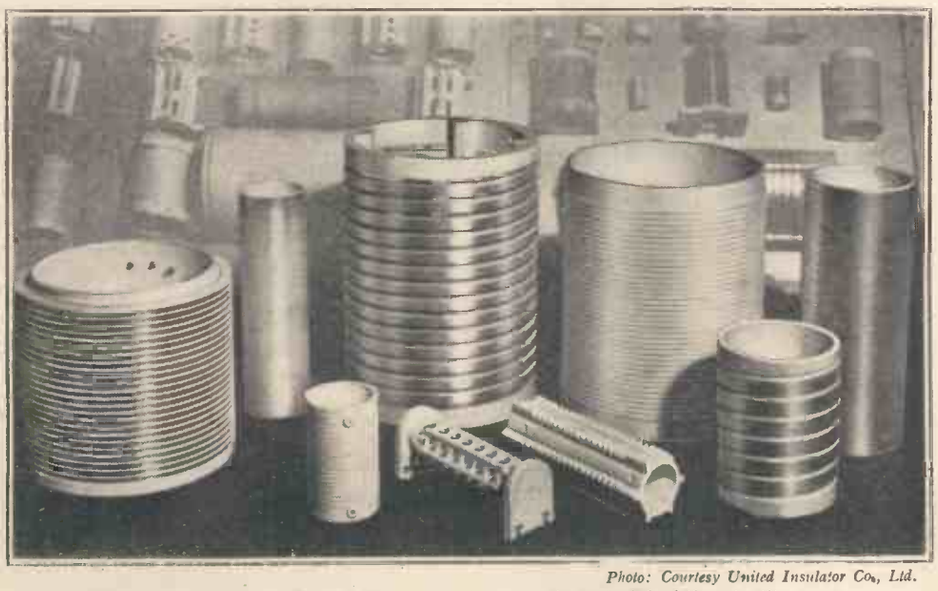

Photo: Courtesy United Insulator Co., Ltd.

Fig. 4.—Coil formers made from "Calit," a ceramic material of the steatite group.

**Modern Insulating Materials—**

large value of 170 for fields in the direction of the axis of the crystal and about 90 in a perpendicular direction, but only quite recently has it been discovered that ceramics consisting mainly of rutile can be commercially produced, and that not only have they the high dielectric constant of rutile, but also a fairly low power factor at radio frequencies. They are, therefore, specially valuable for the construction of small fixed condensers. Unlike mica, such materials require no mechanical protection. It is only necessary to take a small disc of the material and deposit metal films on two opposite faces, and the condenser is complete.

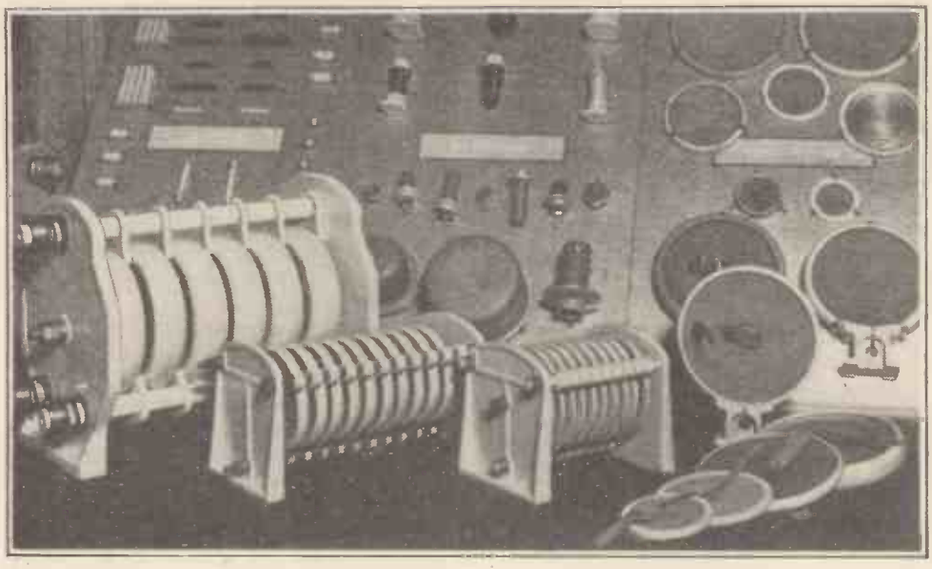

*Photo: Courtesy United Insulator Co., Ltd.*

Fig. 5.—Condensers made of ceramic material of the rutile group.

The earlier materials of this kind had dielectric constants varying from 20 to 100 according to the proportion of rutile, but more recently the very high dielectric constants have been dispensed with in order to secure certain other properties. Constancy of capacity with rise of temperature is obviously of considerable importance, for variations in working temperature are often considerable, and it is important that these shall not cause appreciable changes of capacitance. The temperature coefficient of capacitance of a good small air condenser may be no more than 0.003 per cent. per 1 deg. C., but for materials consisting mainly of rutile the coefficient is negative and amounts to about 0.07 per cent.

### Power Factor at RF and AF

For the steatite materials the coefficient is positive, so that by using mixtures of the two kinds, ceramics with a dielectric constant of about 10 and a negligibly small coefficient may be produced. Another disadvantage of the earlier ceramics of the rutile group was that the power factor, although very low at very high frequencies, tended to become high at lower frequencies. This disadvantage has been overcome in rutile ceramics by combining the titanium dioxide with an alkaline earth to form a titanate. An example is "Tempa S." in which the principal crystalline constituent is magnesium titanate. This material has a dielectric constant of about 16, and when perfectly dry a power factor which may be as low as 0.0005 at audio-frequencies and 0.0001 at radio-frequencies. In addition its temperature coefficient of capacity is almost negligible.

When it is remembered that these remarkable electrical properties are combined with a very high degree of permanence of linear dimensions and excellent thermal properties, it will be clear that the various short-wave components now manufactured from these materials constitute a great advance on previous practice. There is, however, still one fly in the ointment, and that is that all the ceramics have an affinity for water. They may be no more porous than glass when properly vitrified, but they appear to have the power of absorbing an appreciable amount of water from the atmosphere. This does not greatly affect their properties at very short wavelengths, but is apt to be serious at the lower frequencies. In practice steps are taken to ensure that as far as possible the materials are used in the dry condition. Thus small condensers are almost invariably protected by a coating of some kind of varnish after drying.

Probably a great part of the moisture is held by the material in the form of a surface film, and it is therefore very important that the surface should be kept clean and not handled, for dirty water has a much greater conductivity than clean water. A few dirty finger-marks on the surface of the ceramic insulator of a standard laboratory condenser will often cause a serious deterioration of its properties, especially at the lower frequencies. The same is true of fused silica. If the ceramic industry is able to overcome this disadvantage it will probably be able to supply us with the ideal insulating material.

Meanwhile the polystyrene resins hold a decided advantage on this particular point. Not that these two groups of materials are to be regarded as merely competitors. The flexibility of the resins is as valuable in its own way as the rigidity of the ceramics, and all radio experimenters will find many uses for both classes of material.

## CLUB NEWS

### *Aldershot and District Radio Society*

**Headquarters:** 41, Grosvenor Road, Aldershot, Hants.
**Hon. Sec.:** Mr. H. Atthill, "Ardvarney," College Road, Farnham, Surrey.

The first general meeting of the society, held on April 6th, opened with a junk sale. Morse practice is held at each meeting, and, in addition, certain transmitting members are giving slow morse "over the air" at stated times. The club hopes to arrange a visit to the local telephone exchange and a visit to view the apparatus at the local cinema. A field day is also to be held.

The next meeting will be held in the first week of May.

### *Bethnal Green Radio Club*

**Headquarters:** The Institute, 224, Bethnal Green Road, Bethnal Green, London, E.2.
**Meetings:** Tuesdays and Thursdays at 8 p.m.
**Hon. Sec.:** Mr. L. Bard, The Institute, 224, Bethnal Green Road, Bethnal Green, London, E.2.

The club devotes its Tuesday meetings to the theoretical side of radio engineering. Lectures are usually accompanied by a demonstration of apparatus. Thursday evenings are given over to practical constructional work. A morse class is also held on Thursday evenings.

This club is additional to those given in the directory of wireless societies, published in *The Wireless World* of April 6th.

### *International Short-wave Club*

**Headquarters:** R.A.C.S. Hall, Cavendish Grove, Wandsworth Road, London, S.W.8.
**Hon. Sec.:** Mr. A. E. Bear, 100, Adams Gardens Estate, London, S.E.16.

On April 21st Mr. M. Raymond gave a lecture and demonstration arranged by Baird Television, Ltd., a Baird Type T18 model being used for the purpose.

The society has erected a 50ft. mast on the roof of its headquarters. The mast is a wooden structure, and provision is made for a television dipole and also for short-wave reception and transmission. Experiments in transmitting are at present being carried out on a dummy aerial circuit (call sign 2CLR) prior to going on the air.

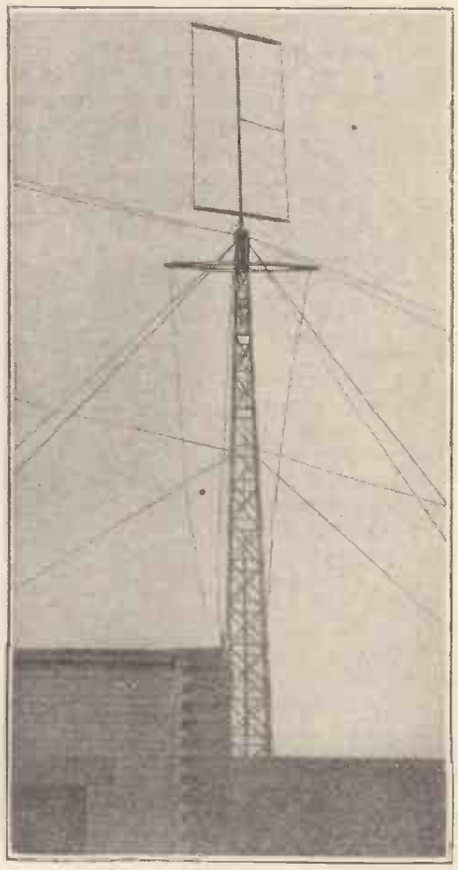

The new aerial system installed at the headquarters of the International Short-wave Club (London Chapter).

# NEWS OF THE WEEK

## ECONOMISING IN METAL

**New Methods of Set Construction**

THE full effect of the German Four-Year Plan and the order to economise in the use of metals which have to be imported from foreign countries will be felt for the first time when next season's receivers are put on the German market.

One hundred and thirty metric tons of iron will be saved on every hundred thousand sets manufactured by the introduction of a new type of vertical presspahn chassis and some twenty-eight metric tons by the replacement of the iron loudspeaker cradle by one of wood.

Until now, twenty - five grammes of precious metal were required for superhet wavechange switch contacts, but in future only six grammes will be used. Instead of fitting small alloy rivets to the bronze contact spring of wavechange switches an ultra-thin coating is pressed on to it, and flat and pointed contacts are produced by simply pressing out part of the strip. Further to save metal the thickness of the covering has been reduced from 0.04 mm. to 0.01 mm. without, it is stated officially, ill-effects on the life of the switch!

As tin has to be imported, the amount used is to be reduced to a minimum by employing the welding process instead of soldering in all cases where this is possible, and also, by decreasing the percentage of tin in the solder to forty. The introduction of a new method of making coil cans by the cold-spray method will result in a saving of 74 per cent. in imported metals.

Further saving is effected by the use of artificial silk covered Litz and by substituting home-grown flax thread in the place of the cotton used for tying the ends of the coils.

It is stated in the official report that the changes will in no way lower the quality of receivers.

## EMPIRE DAY PROGRAMME

MESSAGES of loyalty and devotion to the Crown from all parts of the United Kingdom will be heard on Empire Day, May 24th, in the programme arranged by the Canadian Broadcasting Corporation, beginning at 7.15 p.m., B.S.T., and concluding with the voice of the King speaking from Winnipeg at 8 p.m.

The honour of supplying a contribution in the name of England rests with a boy from the training ship H.M.S. *Conway*.

## RADIOLYMPIA, 1939

**Some Features : Televiewers' Corridor, Technical Section, Model Factory and Television Equipped Amphitheatre**

THE chairman of the Radio Manufacturers' Association Exhibition Committee, Lt.-Col. G. D. Ozanne, outlined in a message to overseas buyers the main features of this year's Radio Exhibition, which is to be held at Olympia from August 23rd to September 2nd. It would appear that the Show is to surpass all others, for, he says: "It will reflect the predominant position which radio, after seventeen years of existence, has won for itself in the life of the nation and the individual."

Every effort is being made to bring before the public the advantages of 1940 receivers, and to impress upon listeners throughout Great Britain, what they are missing by using old and obsolete receivers. Readers of *The Wireless World* will be pleased to know that a technical section is being incorporated this year.

Last year's decision to drop the Radiolympia Theatre has been reversed, and what is to be known as the Amphitheatre equipped with television cameras will be built. It will be possible to relay shows given on the stage to television receivers on the stands as well as to a "televiewers' corridor."

A complete model factory, with moving conveyor showing the assembly and testing of receivers, is proposed for erection in the annexe. With the object of showing the part played by wireless in the Services, special features are being arranged by the Royal Navy, the Army and the R.A.F. A cinema, showing films of wireless interest, will be erected in the smaller hall.

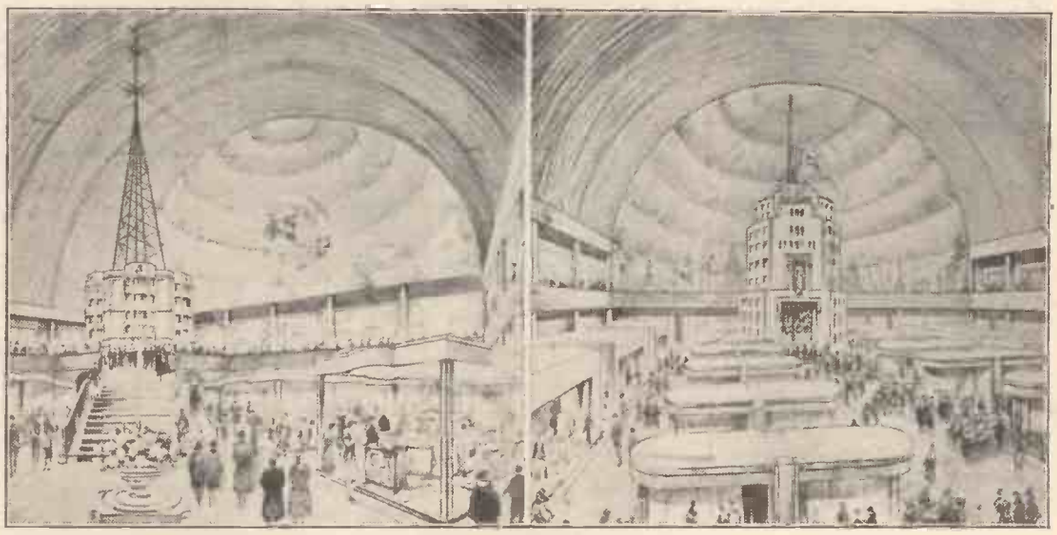

SYMBOLIC FEATURES of the Exhibition, at the east and west ends of the main hall, will be reproductions of part of Alexandra Palace, complete with replica of the television aerial, and Broadcasting House.

## C.B.S. TELEVISION

**B.B.C. Adviser Sails for New York To-day**

MR. GILBERT SELDES, Television Director of the Columbia Broadcasting System, and Mr. D. H. Munro, B.B.C. Television Productions Manager, sail for New York on the s.s. *Georgic* to-day.

Mr. Seldes has been in London since April 26th making a brief study of television production technique at Alexandra Palace, and Mr. Munro, as previously stated, is being lent to the C.B.S. for the purpose of assisting in the setting up of a New York "Alexandra Palace."

Speaking in New York recently on British television and the arrangement whereby advice should be sought from the B.B.C., Mr. Seldes said:

"Munro is ranked among the world's foremost authorities in the field of television. Our joint observations and discussions will help us to find the methods which will prove useful and applicable to our American production and audience. England is far advanced in the matter of television production technique, but each country must develop its own methods, material and style of production. It is only background technique which remains universal."

## LEARNING MORSE

**Two Methods of Study**

MANY readers have written asking how they can learn morse in the minimum of time in order to fit themselves for the various defence services for which this knowledge is required. There is, of course, no royal road to acquiring this knowledge, and it is solely a matter of steady and consistent practice, but much time can be saved by adopting the correct methods.

Much help in this direction can be obtained by a study of the recently published handbook "Learning Morse," and by constructing the morse practice set described therein. It cannot be too strongly emphasised that skilled operating is largely a question of knowing, and instantly recognising, the rhythm associated with each letter. In the handbook, aids to memorising the code are so devised that the learner is automatically guided along the right path. "Learning Morse" is issued by the publishers of *The Wireless World*, and costs 6d. (by post 7d.).

The best method of acquiring proficiency is, naturally, to enlist the services of somebody who is already a proficient telegraphist, but this can seldom be done. It is not always convenient for two learners to get together for mutual assistance, although this should be done if possible. The lone learner can, however, do much by himself with the aid of a morse practice set.

Another useful aid to learning the code is the gramophone. A set of three instructional record-

News of the Week—

ings have been prepared by Mr. C. E. Masters, who is an Instructor of Signals to the R.A.F. Volunteer Reserve. These records contain messages at a speed as low as two words per minute and ranging up to 30 words per minute. The records cost 2s. 6d. each, or 7s. for the set of three, and can be obtained from Mr. Masters at Orchard House, Finchampstead Road, Wokingham, Berks.

## B.B.C. REVENUE

**Statement in the House of Commons**

THE Assistant Postmaster-General, Sir Walter Womersley, replied non-committally in the House of Commons last week to a suggestion that the B.B.C. should receive the whole of the revenue from wireless licences.

He said that from the total of £36,000,000 derived from receiving licences since the inception of the broadcasting service, the Post Office had retained about £4,000,000 to cover its expenses, the B.B.C. had been paid about £22,300,000, and the Exchequer had retained about £9,700,000.

Under present arrangements the amount accruing to the Corporation to cover all broadcast services represented about 81 per cent. of the total licence receipts, while the Post Office retained 9 per cent. for its expenses and the Exchequer received approximately 10 per cent.

## NORWEGIAN STATIONS

**Geographical Considerations**

WITH the recent addition of two new 100-kW Regional transmitters, the Norwegian state broadcasting organisation, Norsk Rikskringkasting, now controls a network of seventeen stations with an aggregate aerial power of 360 kW. Fourteen of these stations have been erected since 1933, when the broadcasting organisation was taken over by the State.

The comparatively large number of broadcasting stations in Norway is necessitated by the shape and nature of the country, which has also necessitated the extensive use of wire links, and the technical staff of the Norsk Rikskringkasting has become expert in long-distance line transmission. The longest HF cable is 2,160 km (1,350 miles), which relays the programme from Oslo to Vadso in North Norway.

The new 5-kW short-wave transmitter at Jeloy has, since May 1st and until further notice, ceased normal broadcasting, as it will be required for telegraphic purposes during the summer. Its place is being taken by the former 1-kW station at Jeloy.

## GERMAN AMATEURS

**Licensing Regulations**

THE position of German amateur transmitters has now been defined by the introduction of a new law. Any full German citizen may now apply for a transmitting licence provided he is over eighteen, a member of the official amateur organisation and that the police give their permission. He will, of course, have to pass a technical examination.

So far as listening is concerned the amateur is limited to broadcasting and amateur transmissions. Should an operator hear other services, he must keep the very existence of these services secret.

Transmission is restricted to telegraphy, and the maximum aerial power is 50 watts, except in special cases, where 100 watts is permitted. Amateurs are allowed to transmit within the following bands: 3.5-3.6, 7-7.3, 14-14.4 and 28-30 Mc/s.

The cost of a transmitting licence is the same as that of the receiving licence, Rm.2 per month, which licence also permits the use of any receivers belonging to the transmitter.

The operation or even the mere possession of a secret unlicensed transmitter renders the culprit liable to fifteen years' penal servitude. If the station is operated seditiously against the Party it is a crime of high treason, which is punishable by the death penalty or a long term of imprisonment according to the degree of malice.

THIS KNAPSACK TRANSMITTER was used for the first time in a B.B.C. transmission during the English Amateur Golf Championship at Birkdale last Saturday. The equipment enables a commentator to move freely about at a sports meeting or in the street, while the low-power radiations from the portable transmitter are picked up by an O.B. van parked in the vicinity.

## TELEVISION SOUND

**Audio-Frequency Equipment at Alexandra Palace**

SOME interesting information about the sound accompaniment to television was disclosed in a paper by Messrs. Turnbull and Clark (Electric and Musical Industries, Ltd.), which was discussed last night at the Institution of Electrical Engineers.

It goes without saying that full advantage has been taken of the high carrier frequency to extend the range of audio-frequency response (the overall characteristic of the system is flat within ± 2 db from 40 to 10,000 cycles) but in the authors' opinion it is the extremely low harmonic distortion, particularly at the low-frequency end of the scale, which is the foundation of the superior sound quality from Alexandra Palace. Over the complete programme channel under normal working conditions the third harmonic at 40 c/s is only 0.66 per cent. and at 1,000 cycles, less than 0.15 per cent. This has been accomplished by the extensive use of triodes with high anode loads and negative feed-back in the amplifiers.

The microphones used are of the pressure and velocity types. The former is the well-known E.M.I. moving-coil microphone with balsa wood diaphragm. The velocity microphone is a comparatively new design with a stretched, uncorrugated ribbon about 1 inch long and 0.00005 inch thick.

The intensity of the radio-frequency field surrounding the audio apparatus at A.P. has brought its own problems which have been solved by individual screening of all early stages in amplifiers and the inclusion of separate tuned RF filters in the heater, cathode, grid and anode leads of each valve.

## EUROPEAN LISTENERS

**Saturation Point Approaches**

STATISTICS issued by the International Broadcasting Union show that although the number of European registered licensees, now totalling 35,130,000, shows a substantial expansion, it is noticeable that the percentage rate of increase over the whole continent is slackening with the approach of saturation point.

On the accepted basis of three and a half listeners to each set, the potential audience reaches nearly 123,000,000.

The following summary published in *The Birmingham Post* indicates the percentage rate of approximate increase in those countries where pronounced advances have been made in listening during the past year:

| | |
|---|---|
| Poland | 18 per cent. |
| Greece | 30 per cent. |
| Lithuania | 31 per cent. |
| Estonia | 35 per cent. |
| Bulgaria | 37 per cent. |

Due to the inauguration of a new high-powered station at Ankara, the number of wireless licence holders in Turkey has been more than doubled during the year. Germany's estimated total, including Czecho-Slovakia, is 12,300,000. Italy by the annexation of Albania is not expected to derive more than 2,000 additional listeners—bringing her total to over a million.

The total number of wireless licences in force in Great Britain and France is now 8,968,600 and 4,957,886 respectively.

## NEW YORK WORLD'S FAIR

**Sound System in the British Pavilion**

AMONG the features of the British Pavilion at the World's Fair, which opened in New York last Sunday, will be the showing of films portraying conditions and life in England. The Department of Overseas Trade, who were responsible for the British Pavilion, have installed sound and picture projection apparatus manufactured by British Thomson-Houston.

The B.T.H. sound system uses soundheads which incorporate a drive, hitherto used only on recording cameras, in which the film is passed round a drum driven by electromagnetic means to ensure as smooth propulsion as possible, the minimum of film wear and constancy of film path at the point where the track is scanned by the optical system. Another feature is that the sound amplifier includes automatic volume expansion.

## MAKING COMPLETE BROADCASTERS

EVERY senior member of the B.B.C. staff is being given an opportunity to become a technician. The summer course of the Staff Training Department includes certain lectures which can be attended by Corporation officials whether or not they are undergoing the course.

The technical lectures coming within this category give a complete survey of the essentials of radio transmission, ranging from elementary electricity and magnetism to the functions of a modern transmitter. Microphones, studio acoustics, mixing and control units, recording, television and short- and medium-wave transmission are all made the subjects of lectures.

## 214 METRES

### Wavelength for a Hypothetical Station

HAVING secured a share in the wavelength of 214 metres for the hypothetical relay transmitter at Norwich, the B.B.C. is not likely to leave the wavelength vacant. The new Montreux Plan comes into operation on March 4th, 1940, and after that date the 214-metre wavelength will be a plum ripe for picking by any predatory transmitter in search of a niche in the ether, for the remaining stations sharing this wavelength are all very low powered.

If the Norwich relay cannot be completed by then, there is a distinct possibility that the wavelength will be temporarily adopted by another British transmitter. Nearby European stations will find the "number engaged."

## HOW A VALVE WORKS

### A Novelty at the World's Fair

TO show visitors to the New York World's Fair what goes on inside a triode valve and the effect of a magnetic field on a stream of electrons flowing through a vacuum, the engineers of the Westinghouse Electric and Manufacturing Company have built a triode 27 inches high and 7 inches in diameter. It is similar to a standard radio valve except that it has a filament and a grid on each side of the anode so that the action of the electrons is visible from both sides.

The surface of the anode is coated with a fluorescent material so that wherever electrons impinge on the anode a green colour shows. By changing the negative biasing of the grid the stream of electrons to the anode can be varied from zero to the maximum of which the valve is capable.

By placing a permanent magnet near the valve the electron stream can be deflected, thereby showing the effect of the magnetic field on the stream.

The circuit used is similar to that in an ordinary AF amplifier, AC at sixty cycles being applied to the grid. The valve output is connected to a loud speaker and the volume corresponds to the area of the green glow on the anode of the valve.

OUTSIZE IN RECEIVING VALVES, built to show visitors to the World's Fair how the electrons move.

## FROM ALL QUARTERS

### New Empire Telegraph Service

A FURTHER stage in the progressive policy of Cable and Wireless for cheapening Imperial communications was introduced last Monday, when a new service of Empire social telegrams was inaugurated. It is now possible to exchange such telegrams within most parts of the British Empire at a flat rate of 5s. for twelve words, plus 5d. for each additional word. To mark the inauguration of the service, telegrams were despatched free on the opening day, May 1st.

### News from China

WE are still open to receive, for forwarding to China, reception reports of the Chinese Central Broadcasting Administration's station at Chungking, Szechwan. This 35-kW Marconi station, which transmits under the call-sign XGOY on 25.21 metres (11.9 Mc/s) from 10.30 a.m.-4.30 p.m. and from 9.30-11.20 p.m. G.M.T., is also radiating a transmission from an aerial directed on North America on 16.85 metres (17.8 Mc/s) from 2 to 3.30 a.m. under the call-sign XGOX. News is now broadcast in English four times during the day at 2.50 and 11.20 a.m. and 2 and 10.50 p.m. G.M.T.

### Licence Free

THE Danish State Broadcasting Organisation has issued an order which exempts foreign visitors from holding a Danish radio licence to cover the use of portable wireless sets or permanently installed receivers in motor cars or yachts.

### Increase of Power

WHILE the Finnish medium-wave transmitter at Viborg is having its aerial power increased from 10 to 20 kW, a stand-by transmitter of 1 kW is operating in its place.

### Producing an Electric Charge

SIR AMBROSE FLEMING, D.Sc., F.R.S., the ninety-year-old father of the thermionic valve, read his thirty-seventh paper to the members of the Physical Society last Friday. It dealt with a new method of creating electrification by silica powder falling on a perforated metal sheet, whereby the metal becomes electrified positively and the insulating powder negatively.

### Swiss SW Link

WITH the inauguration of a new short-wave station Switzerland now has direct communication with the U.S.A. Hitherto she has been dependent upon relaying facilities via England.

### South African Ground Stations

A FURTHER five aerodromes, bringing the total to twenty, are to be equipped by the South African Post Office with "Standard" transmitting, stand-by and DF stations. The transmitters are combined short- and medium-wave sets having outputs of 250 watts for telegraphy and 80 watts for carrier telephony. The change-over between four pre-set wavelengths is easily effected. The DF equipment in each case is a Standard Adcock Type R.4 direction finder with goniometer and receiver installed some 600 feet from the aerials.

### Import Restrictions

IN accordance with an order issued by the Norwegian Department of Commerce, no complete wireless receiver or components of foreign makes may be imported without a special licence. This order does not apply to single loud speakers.

### Change of Wavelength

BODO, the Norwegian long-wave transmitter, has changed its wavelength to 1,186 metres and Kristianssand has changed to 476.9 metres.

### DF Lightship

THE lightship *Abertay*, recently launched for the Dundee Harbour Trustees, will be equipped with Marconi wireless telephone equipment for ship-to-shore communication, and a Marconi radio beacon transmitter.

### Navigational Science

A PRIZE of £25 is offered by the Council of the Royal Society of Arts to any person who may bring to their notice an invention, publication, diagram, etc., which, in the opinion of the judges, is considered to be an advancement in the science or practice of navigation, proposed or invented by himself between January 1st, 1934, and December 31st, 1939. This prize is offered under the Thomas Gray Memorial Trust, which was established as a memorial to Thomas Gray, C.B., who was for many years assistant secretary to the Board of Trade (Marine Department). The objects of the trust are "The advancement of the science of navigation and the scientific and educational interests of the British Mercantile Marine."

### The Australian Trend

THERE are 1,100,000 wireless sets in use in Australia and nearly 650,000 telephones for a population of fewer than 7,000,000.

### Radio Relays

ACCORDING to a report issued by the Finnish Post Office relay systems appear to be unpopular in that country. The total number of subscribers to the system amounts to only 970.

HER MASTER'S VOICE (with apologies to H.M.V.). Zoe, an Alsatian belonging to the Alexandria (Sydney) police force, has been trained to act upon the wirelessed commands of her master which are conveyed to her by a small receiving set strapped to her back.

### Legal Actions Broadcast: A New Method

THE B.B.C. is watching with interest an experiment now being carried out at Poste Parisien. Important trials are being broadcast, not direct from the police courts, but by reconstructions in the studio. Skilled reporters provide verbatim accounts of the trials and the "parts" of prosecutor, defendant and witnesses are taken by actors at the microphone.

### Conversazione to I.E.E. Overseas Members

A CONVERSAZIONE and reunion of members of the I.E.E. from overseas is being arranged to take place in the Institution building, Savoy Place, London, W.C.2, on Tuesday evening, June 13th. Members from overseas who will then be in England and would like to be present are asked to communicate with the secretary immediately on their arrival in England.

### By Any Other Name . . . .

"MIKE" has long been the recognised abbreviation for microphone. In America the television camera is known as an "Ike" (Iconoscope).

### Shocks for "Mikes" and "Ikes"?

MR. S. C. H. DAVIS, of our sister-journal, *The Autocar*, is lending his ancient Léon Bollée car, of 1898 vintage, for the television O.B. from the Crystal Palace race-track on May 19th. Precautions will be taken to shield the microphones while the veteran vehicles are being started up. Emitron cameras have also to be protected against sudden shocks.

Test Report

# MURPHY A56V

## Television Receiver (15 Valves + 3 Rectifiers) for Alexandra Palace Sound and Vision Only - - Price £30

IT is safe to say that the majority of prospective viewers already possess a good broadcast receiver, and if they have grown to know its little tricks of tuning and tone control and are satisfied with its quality of reproduction, they may not like the idea of having to accept a new instrument as make-weight in the new television set.

The Murphy A56V is as much a self-contained receiver as television is a self-contained service, and it can, if required, be installed in a different room from the existing broadcast set so that the two can be used simultaneously.

Murphy Radio have already had experience of building a television receiver (the A42V) without restriction as to cost. Most of the economies they have effected in the A56V are the result of the better valves which are now available and of the acceptance of a slightly smaller picture size.

***Circuit.***—The di-pole aerial feeder is tapped directly into the tuned aerial circuit preceding the single stage of RF amplification, which is transformer-coupled to the frequency-changer. The inherent damping in the tuned circuits associated with the RF stage is sufficient to cover both sound and vision signals without tuning. There is a pre-set gain control for areas of medium signal strength consisting of a variable cathode bias resistance. In areas of strong signal strength this is hardly sufficient to prevent the formation of a vertical pattern on the picture due to cross-modulation between sound and vision channels, and an additional input attenuator becomes necessary. The makers, through their service agents, are able to fit an accessory with the required attenuation when the receiver is installed.

Tuning is effected by varying the oscillator frequency. The triode section of the frequency-changer is arranged as a Colpitts circuit with inductance tuning by means of an adjustable metal plunger. The normal oscillator frequency is 40.75 Mc/s, giving intermediate frequencies for sound and vision of 750 kc/s and 4.25 Mc/s respectively.

The sound receiver is similar in general design to that of the A46 broadcast receiver, but has a wider bandwidth in the IF stage to take advantage of the good quality available from Alexandra Palace and to allow for a possible drift in the oscillator frequency. The double-diode-triode second detector supplies undelayed AVC to the IF valve and also acts as first AF stage before the output tetrode. Negative feed-back is incorporated in this stage.

Three stages of IF amplification are used in the vision receiver with a gain (contrast) control consisting of a variable cathode resistance in the first two stages. A tuned filter is connected in the cathode circuit of the first stage to introduce negative feed-back at the frequency at which break-through of the sound channel may be experienced. A diode rectifier follows the vision IF amplifier and feeds the single-stage vision amplifier, the anode of which is connected directly to the control grid of the cathode-ray tube. This ensures that the DC component will be retained under all conditions. The brightness control takes the form of a potentiometer in the cathode circuit of the cathode-ray tube.

Segregation of the synchronising impulses is effected by a double-diode valve fed from the cathode circuit of the vision amplifying stage.

Saw-toothed currents for the magnetic deflection of both line and frame time bases are generated by gas-filled triodes in conjunction with tetrode power amplifiers. An interesting method of ensuring linearity in the working stroke of the time bases has been devised and is dealt with

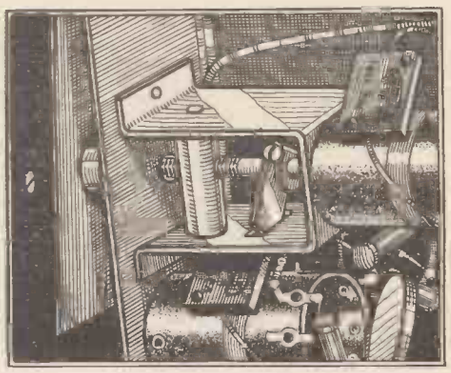

The adjusting screw for varying the inductance of the oscillator circuit is fitted with a tongue working in a slot which limits the movement to about three turns.

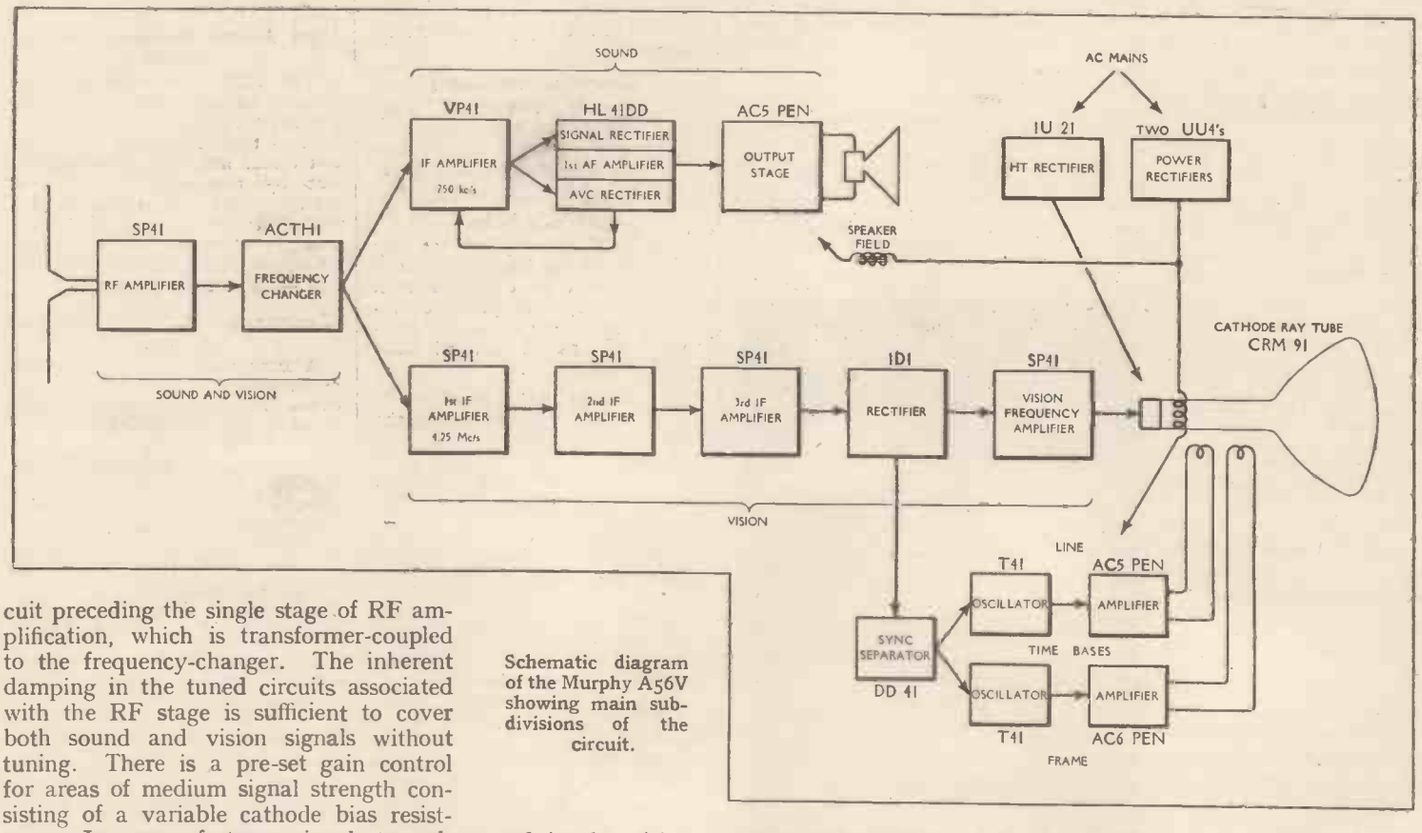


Schematic diagram of the Murphy A56V showing main subdivisions of the circuit.

**Murphy A56V—**

in "Television Topics" in another part of this issue.

The power consumption of any television set is considerably greater than that of a broadcast receiver, and in this case two rectifiers with strapped anodes are used for full-wave rectification of the main power supply. After one stage of smoothing the current divides, one branch going through the loud-speaker field for extra smoothing, to the sound and vision receivers, the other through the focusing coil to the time bases. Suitable decoupling is provided to prevent interaction between the various circuits.

High tension of 4,700 volts for the anode of the cathode-ray tube is derived from a separate mains transformer and a half-wave rectifier valve with a cathode of large heat capacity to delay the application of the HT voltage until the remaining circuits have warmed up. To prevent damage to the screen after the set has been switched off and while a charge remains on the HT reservoir condenser, the mains switch is provided with contacts which increase the cathode bias resistance of the tube to limit the beam current. Once the set has been switched off it should not be switched on again until the HT rectifier cathode has had a reasonable chance to cool down.

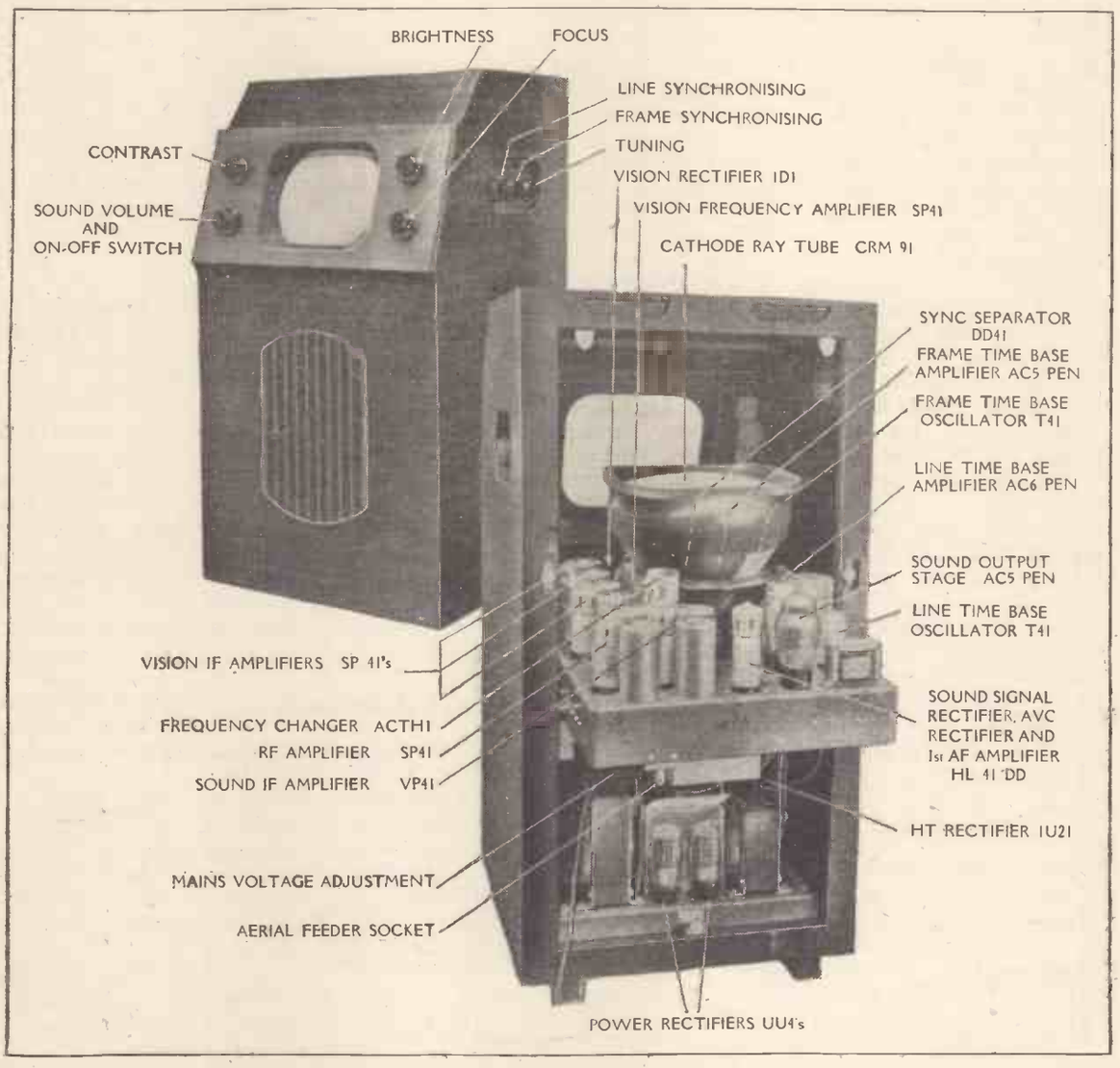


**Principal controls of the Murphy A56V and view with chassis lowered into the horizontal position to show arrangement of valves and mounting of the cathode-ray tube.**

***Performance.***—The instrument was tested at a distance of six miles from Alexandra Palace on a di-pole aerial erected well clear of surrounding buildings. The signal strength was above the optimum for satisfactory operation and the makers supplied an input attenuator to eliminate the cross-modulation between the sound and vision signals.

We were very much impressed by the reserve of brightness in the picture, which enabled it to be viewed in comfort in daylight. The contrast control was well able to cope with the corresponding adjustment required of it, and all the controls of the instrument are notable for their wide range. The line and frame synchronising controls are not critical, and once set require no further attention.

Focusing is sharp and uniform up to the edges of the picture. The focusing control required much less attention than was expected in view of the fact that it is magnetic. By the time the valves had warmed up and the synchronising controls had been properly adjusted, the focusing coil current was sufficiently stable to hold its setting for the remainder of the transmission period.

Definition is excellent and the breaking up of the lines into closely spaced dots due to some break through of the vision intermediate frequency is not at all objectionable and gives the effect of a half-tone reproduction.

A 10in. moving-coil loud speaker of the type used in the Murphy A38 receiver is employed in the sound channel and quite easily reveals the superior quality associated with transmissions from the Alexandra Palace studios.

There are rather more than the usual number of tappings on the mains transformer as the set is more sensitive to changes of HT volts than an ordinary broadcast receiver. Errors of adjustment may be suspected if the picture is too wide or too narrow. Normally a picture size of 7½in. by 6in. is obtained, and this is an admirable compromise for the range of viewing distances and the number of the audience which can be comfortably accommodated in the average living-room.

***Constructional Details.***—The end of the tube is framed in a moulded black rubber mask which is fitted over the tube itself. The chassis as a whole is hinged and in its normal position all components under the base are readily accessible. By removing two screws the chassis may be lowered into a horizontal position for valve or tube inspection.

The cathode-ray tube passes through a hole in the chassis and the wiring of vision frequency and time base circuits is thereby reduced to a minimum. This method of construction enables a very compact cabinet to be designed as well as facilitating adjustment and servicing. All connections to the chassis, including those to the controls on the side of the cabinet, are flexible, and it is possible to work the set in the horizontal position.

***Summary.***—The A56V very happily fills the gap between the larger and more expensive combined television and radio receivers and the cheap table models with small tubes. In size, brightness and

**Murphy A56V—**
quality the picture is much nearer the performance of the former than the latter class of instrument. The controls are as easy to work as they are simple in appearance. In relation to the circuit specification, the quality of components and the performance, the price is very reasonable, and appears to have been fixed in advance for future quantity production.

# AIRCRAFT WIRELESS

## Keeping Pace with Modern Aeronautical Developments

IN the days before broadcasting commenced, and in the early days of broadcasting itself, we were accustomed to listen for aircraft wireless mainly on a wavelength of 900 metres, but as in other spheres of wireless communication, aircraft has now "gone short wave." The necessity for long-distance communication is partly responsible for this, but there are other conditions peculiar to flying which have played an important part in the matter. These points and also a great deal of other interesting data concerning problems which beset the designer of aircraft wireless were discussed in a paper recently read before the Institution of Electrical Engineers by N. F. S. Hecht.

At one time the only aerial known aboard an aeroplane was the long trailing wire, usually of some 200 or 300ft. in length. There were always certain difficulties connected with this device, but none of an insuperable nature until really high-speed aircraft were developed. The result of speed was that the aerial was trailed almost completely horizontally instead of taking up the familiar downward curve. It thus lost practically all its vertical component, this resulting in a very serious reduction of range; in addition it became very liable to foul the aircraft structure.

### The Aerial Problem

The above difficulties led designers to consider the question of fixed aerials stretched over or under the fuselage. As the latter formed the wireless counterpoise or earth, the effective height of the aerial was very restricted, being less than two feet in the case of small aircraft. The use of long and medium waves, therefore, became no longer possible with any degree of efficiency, although it should be mentioned that they are still employed to some extent and in certain circumstances by large aircraft and flying boats. In such aircraft medium waves are used up to about 300 miles, short waves being employed at greater distances, and it is quite a common arrangement for a trailing aerial to be employed for the short distance medium wave transmissions, a change being made to a fixed aerial for long-distance SW work.

In recent years the practice has been adopted of using dipoles connected through the usual matching transformers and transmission line. Frequently arrangements are made to use this type of aerial on medium waves by connecting the dipoles so that they act as the two limbs of a T aerial. Aircraft aerials are subject to a great deal of vibration and, in addition, at high altitudes are liable to ice-formation. Both these factors are liable to cause breakages, and special measures are taken to counteract them. Ice-formation on insulators is another enemy to efficient wireless communication which has had to be tackled by designing protective cowls for these components, and by other measures.

Another serious effect of aerial vibration, apart from mechanical strain, is that, in the case of short-wave CW working, excessive frequency wobble is produced. Although mechanical measures such as shock absorbers were sufficient to relieve the ordinary physical strain, no great improvement in the matter of frequency wobble was brought about until self-oscillators and direct aerial coupling were abandoned in favour of the master-oscillator system, which designers, at one time, showed a great reluctance to adopt in view of the necessity of keeping down bulk and weight.

### Interference Elimination

Noise is one of the bugbears of the air, and considerable research has been directed towards producing suitable designs of helmets containing microphones and earpieces. It is necessary that the helmets should be efficient for their purpose without bringing in their train other troubles not directly connected with wireless. Perhaps some idea of the difficulties that have had to be overcome will be had when it is stated that in certain aircraft the noise level at the operator's unprotected ear reaches a value of 135 phons or one million times that observed in the carriage of an express train. Some difficulty was experienced in preventing the microphone picking up and transmitting aeroplane noise along with speech. This was tackled by arranging to restrict the audio-frequency range to as great an extent as possible compatible with speech intelligibility. Actually it was found that if frequencies below 700 c/s and above 2,500 c/s were eliminated, speech intelligibility was still maintained satisfactorily and the transmission of unwanted noises greatly reduced.

With regard to purely electrical noise generated in the aircraft itself, it need hardly be said that all the well-known anti-interference measures are extensively used. Among the electrical noises peculiar to aircraft are those due to the existence of bad electrical contact between rubbing parts such as cross-over points in straining wires, and such-like. In some cases the cure has been effected by careful bonding although, in the case of the wires already mentioned, insulating acorns have had to be used to keep them permanently apart.

Another point of interest is the provision of soft-iron cases for headphones in order to prevent interference with the magnetic compass. Prior to the adoption of soft iron, deviations up to about 20 deg., with the headphones at a distance of 18in., were experienced. Soft iron cases reduced this to 1 deg. at 6in. The soft iron cases are moulded into an insulated covering to prevent the wearer receiving a shock through some accidental connection with high voltage circuits, and for the same reason a mica disc is placed over the iron diaphragm.

### Fire Precautions

Fire is an ever-present danger in aircraft, and remarkable care is taken to use adequately insulated cables and components, and to carry out very careful bonding. The accumulator circuits have been found to be the most likely source of fire owing to excessive surface leakage over acid-splashed areas, and much protective work has been done by the provision of unspillable and splash-proof accumulators and by fitting insulating separators between the latter and the containing crates. Lightning is, contrary to popular opinion, comparatively innocuous, and it has been found that little need be done beyond a careful "earthing" of the aerial when in a storm area.

Lowered atmospheric pressure at high altitudes is a frequent cause of trouble due to corona losses over the surfaces of insulators and at sharp points. Long leakage surfaces and the avoidance, as far as possible, of excessively sharp points are the remedies adopted. The lowered temperature of the upper atmosphere can, however, cause serious frequency drift due to contraction of certain components. Transmitting inductances are the chief offenders, and a goodly measure of improvement was obtained by the use of copper tubing shrunk on to heavy supports built up of a homogeneous material, but better results were had by the use of bi-metallic conductors, silver and copper being the principal metals used. The most obvious cure for this trouble is the employment of crystal oscillators, although it means the use of several of them in order to cover different wavebands.

In recent years the receiver has been coupled to the common transmitting/receiving aerial by means of a small condenser of high insulation. The transmitter is permanently connected to the aerial, and thus the aircraft transmitter can be automatically set to the frequency of the ground transmitter as the operator tunes in the signal from the latter. This ensures accurate setting of the transmitter, without the necessity of carrying a wavemeter.

# Television Topics

## LINEAR SAW-TOOTH OSCILLATOR

NOT the least of the difficulties encountered in the design of television equipment is the attainment of a linear saw-tooth waveform for scanning. Whatever form of time-base oscillator is employed it is usual to adopt a resistance-capacity charging circuit, and it is commonly arranged on the lines shown in Fig. 1. Here a gas-triode oscillator is shown, but other types can be used.

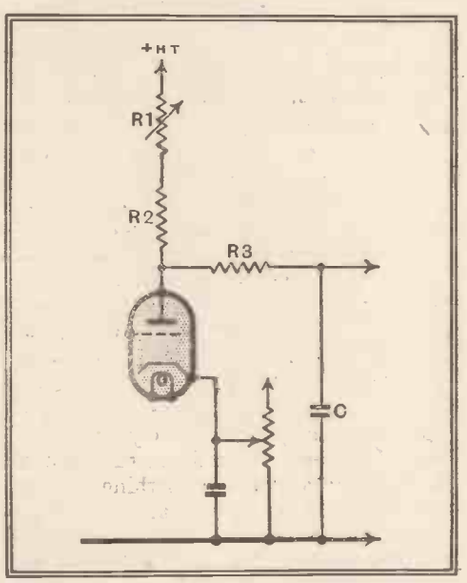


Fig. 1.—The conventional gas-triode saw-tooth oscillator.

When the valve is non-conductive the condenser C charges from the HT supply through R1, R2, and R3, and the voltage across it rises exponentially. The sync pulse at length arrives, and changes the grid potential in a positive direction; the valve becomes conductive, and the condenser discharges through R3 and the valve resistance. These are so low in value that the discharge time does not exceed about one-tenth of the charging time. R3, in fact, is only included to limit the discharge current to a safe value for the valve.

The voltage waveform across C is of the form shown exaggerated in Fig. 2 (a), whereas it should be linear as in (b). In practice, exponential charging is satisfactory if the amplitude of saw-tooth voltage is small enough in relation to the HT voltage, for the initial portion of an exponential curve is nearly linear. It is desirable that the saw-tooth amplitude should not exceed 7 per cent. of the HT voltage.

There is usually no difficulty with electrostatic deflection, because the HT supply is of the order of 1,000 volts, and it is rare for more than 50 volts amplitude to be needed. With magnetic deflection, however, the HT supply is generally only about 300 volts, so that no more than 20 volts amplitude of saw-tooth waveform can be secured.

Now this is generally too small. In the first place, the amplifier often needs a greater input, especially if negative feedback is used, and, secondly, saw-tooth oscillators usually operate much more regularly when giving a reasonably large output than when the output is small. It is not uncommon to find, therefore, that the oscillator is made to give an output of 30 volts or so, and that the curvature of the waveform is corrected by designing the following amplifier to introduce an equal and inverse curvature.

This is by no means as easy as it sounds, and a particularly interesting method of overcoming the difficulty has been adopted in the Murphy A56V and A58V receivers reviewed elsewhere in this issue. Correction is used, but it is obtained in the saw-tooth oscillator itself and not in the amplifier.

The arrangement for the line oscillator is shown in Fig. 3. It will be seen that it is the same as Fig. 1, but the charging condenser is split into two parts, C1 and C2, and an extra resistance R4 and condenser C3 are added. The output is taken across C2 and C3.

The operation is most easily followed by starting, with the condensers charged to their normal maxima, at the instant the gas-triode becomes conductive. All condensers then start to discharge for the fly-back. C1 and C2 in series discharge rapidly through R3 and the valve resistance, but C3 can discharge relatively slowly because of the high time-constant C3 R4. Actually, C1 and C3 are of the same order of capacity, and R4 is several hundred thousand ohms.

When C1 and C2 are discharged to their normal minimum and the valve becomes non-conductive, C3 is by no means discharged. C1 and C2 then start to charge again through R1 and R2, but as the voltage across C3 is greater than that across C1, C3 still continues to discharge, and C1 takes its discharge current which thus helps to charge C1. The voltage across C1 is rising, and that across C3 is falling, and they at length become equal; the discharge of C3 then ceases. After this the voltage across C1 exceeds that across C3, with the result that C3 starts to charge again.

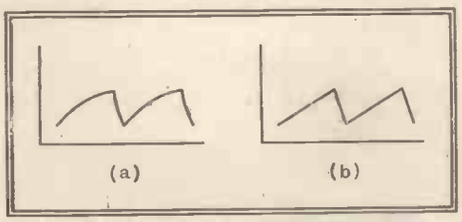


Fig. 2.—The usual exponential waveform is shown exaggerated at (a) and the ideal linear waveform at (b).

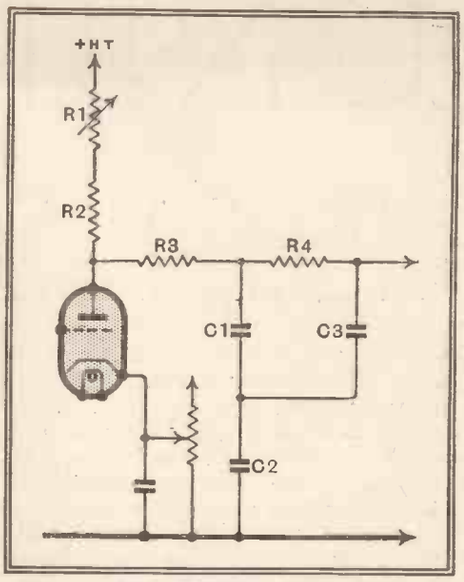


Fig. 3.—The oscillator circuit used in Murphy receivers is shown here.

The result of this is that while there is a more or less normal exponential saw-tooth wave across C2, there is a semi-circular wave across C3, as shown in Fig. 4 (a) and (b) respectively. The output voltage is the sum of the voltages across C2 and C3, and takes the linear form Fig. 4 (c).

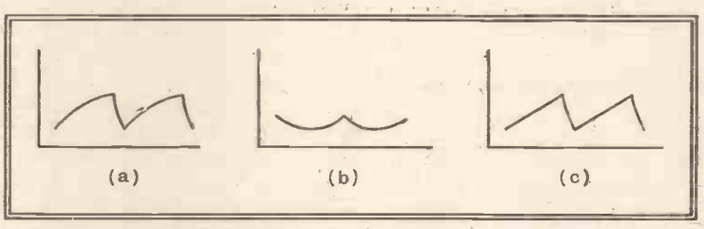


Fig. 4.—The usual exponential waveform (a) is obtained across C2 of Fig. 3 and the semi-circular wave (b) across C3. The output wave (c) is linear and is the sum of (a) and (b).

Of course, there are limits to the amount of correction it is possible to apply. There is still a maximum set to the output obtainable with reasonable linearity, but this is considerably higher than with the simple circuit of Fig. 1.

In the frame oscillator Murphy Radio use a similar circuit, but the values are so chosen that there is a large amount of over-correction. This is done to compensate for the distorting effect of the finite inductance of the output transformer in conjunction with the impedance of the deflecting coil. At frame frequency this is largely resistive.

# UNBIASED

## By FREE GRID

### A Maritime Mishap

EASTER is now a thing of the past, and it is no fault of the P.M.G. that I'm not in the same boat. Boat is certainly the most appropriate word to use as it was actually in a boat that I nearly came to a sad and watery end. I am very keen on DF work and have been experimenting on and off for a very considerable period and enjoying the hospitality of a friend's yacht for this purpose. Needless to say, I used the Easter recess for the purpose of furthering my experiments.

I almost invariably use the carrier of the 500 kW. Moscow No. 1 station on which to test my gear, as this station is on the air for most of the twenty-four hours. I have spent several week-ends experimenting in the crowded waters of the Solent, achieving such a marked degree of success that I have been able to navigate blindfold, and have amazed some ships' captains by passing right under the bows of their vessel during the densest fog, and, in some cases, calling forth vituperation from them, as sailors are very superstitious folk and they probably mistook me for the Flying Dutchman, or some other ghostly visitant.

During the Easter week-end, however, I found myself all at sea in more senses than one as the carrier of the Moscow station gave bearings at almost all points of the compass, and before I knew where I was, I found myself ashore, and my name and address were being taken by a bucolic constable for allowing my bowsprit to collide with a car on the King's Highway. It was only when I returned to London and talked the matter over with the Editor of this journal that I tumbled to what I feel sure was the cause of the trouble.

A collision on the King's Highway.

As you will have seen in *The Wireless World*, the G.P.O. are to use the Moscow wavelength for one of their wretched wired wireless transmissions, and, although this service has not started yet, experimental work undoubtedly has. Some time ago the G.P.O. announced that they proposed to experiment in the Southampton area, and although this project was nipped in the bud at the time, it is obvious that some dirty work has been going on. Small as is the radiation of these overhead telephone lines there is no means of stopping it altogether, and it must be remembered that to get the Moscow carrier I was using a DF receiver of very great sensitivity indeed.

### An International Conspiracy

I DARE say that, in common with myself, a great many of you suffer from extreme reluctance to get out of bed in the morning. It is, of course, a malady which affects both young and old and is especially virulent at this time of the year when we know that all the clocks are an hour fast, and that, by a Government subterfuge, we are all being forced to get up an hour earlier than usual. However, the malady has become so acute with me this year that I consulted a doctor upon the matter, and to my surprise he informed me that his surgery is daily crammed with patients who are suffering from the same complaint.

By pure chance I believe I have got on the track of the cause of it all, and have incidentally unearthed an international conspiracy of the first magnitude to increase the burden of our lot. I happen to have staying with me a retired ship's captain who, through sheer force of habit, insists on shooting the sun and stars at all hours of the day and night in order to ascertain his position. To his surprise, no less than my own, he made the startling discovery that my house was not always in the same place, a considerable variation in longitude being noticeable at different periods of the 24 hours.

Naturally, I questioned the accuracy of his calculations and made a point of calling into consultation some yachtsmen of my acquaintance. They at first derided the captain's statements and ascribed them to the effects of strong drink, but, later, when they reluctantly consented to check them over with their own sextants they made the amazing discovery that not only my house but those in every other locality were oscillating violently from east to west. As everybody knows, in order to determine longitude it is necessary to have a precise knowledge of the time, but, in these days of wireless time signals and frequency-controlled AC mains clocks, this presents no difficulty.

Now, it is the very fact that the question of accurate time is in such an apparently unassailable position that has made me doubt it. By careful observations I have discovered that all our watches and "clockwork" clocks are gaining heavily in the daytime and losing at night. Even so, I might have accepted the explanation that ordinary clocks are notoriously erratic, but, as far as I can find out from the fitful bursts of sunshine we get in this country, our sundials are also varying from hour to hour, and I am only waiting for sunnier days to come along to confirm my theory that there is an international conspiracy afoot to get more work out of us by the simple expedient of slowing down the frequency of AC mains—and, therefore, the clocks which they control—in the daytime and speeding them up at night, so giving us longer working hours and shorter sleeping time.

After all, the AC mains clock is so ubiquitous nowadays that it is simple for a thing like this to be done. At present this is only a theory, but I am hoping that you will assist me in gathering the necessary evidence to expose this vast time-robbing conspiracy to which, of course, the authorities who are responsibe for the wireless time signals must be party.

An amazing discovery.

### An Unscrupulous Selling Dodge

THIS Budget business is all very vexing to a person of a methodical turn of mind like myself. During the few days preceding it I had been at great pains to discover, through certain sources known to me, whether any wireless taxes were to be imposed. As a result of the information I received—and for which, incidentally, I paid a tidy sum of money—I laid in a considerable stock of valves and HT batteries, which I learned were to be the subject of excise duties. It now appears that the rumour was deliberately promulgated by certain unscrupulous valve and battery manufacturers. The result is that I have a considerable stock of batteries and valves for which I can have no possible use for some time to come. I do not mind the valves so much, as, after all, they will keep, but it is very different with batteries. I met with a blank and uncompromising refusal when I approached the dealer from whom I had bought them, asking him to take them back into stock.

# The AVC Characteristic

## AN AID TO RECEIVER TESTING

By M. G. SCROGGIE, B.Sc., A.M.I.E.E.

*DESCRIBING a method of plotting the AVC curve of a receiver that gives much useful information with regard to general performance and also affords a check on the correctness of the design in various directions.*

WHEN testing a receiver by means of a signal generator to find out if all is well, it is usual to check the sensitivity at various frequencies, and perhaps also the selectivity. It does not seem to be generally realised, however, that one of the most informative tests is taking an AVC curve. Perhaps this is because when taken by the commonly prescribed method it is *not* very informative. The official instructions are to adjust the output of the signal generator, modulated the usual 30 per cent., to 1 volt (which is impossible with many good generators), and to set the volume control of the receiver so that a quarter of the rated maximum output is delivered. Leaving the volume control at this position, the signal is then successively reduced and the corresponding outputs noted. Fig. 1 is a curve taken in this way.

There is nothing in such a curve to show what the output of the receiver is with a given signal strength and volume control setting. The latter is unspecified. No indication is given of the correctness or otherwise of the AVC delay voltage. For the sensitivity at that frequency it is necessary to look up other data. The lower part of the curve is often difficult to measure owing to the smallness of the output. But before making other criticisms it would be better to explain the method used with complete satisfaction by the writer throughout the last six years. It is carried out in the reverse order. The volume control is turned right over to maximum. If any output is shown, due to internally generated "noise," before the generator is connected, the amount is noted. Next the signal is applied, beginning from zero. The strengths in microvolts required to give outputs of 1, 3, 10, 30, 100, etc., milliwatts is recorded. To be midway between 1 and 10 on a logarithmic scale the intermediate point should really be $\sqrt{10}$, but in this sort of work 3 is near enough for the error to be immaterial. Weak signals are measured with the volume control at maximum, which is the easiest and most accurate condition. It also corresponds to working conditions; and it automatically covers the sensitivity test, another piece of information omitted from the official scheme.

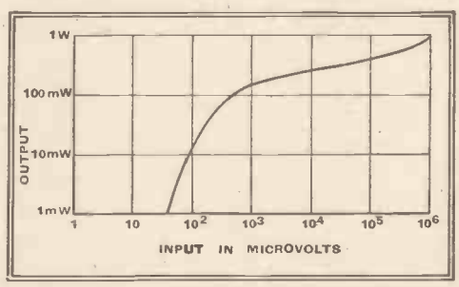


Fig. 1.—Typical AVC characteristic as measured at a frequency of 1,000 kc/s by the descending signal strength method.

If the test were continued to the end with the volume control at maximum, in most receivers the results would be vitiated by overloading of the output stage. To avoid this, when an output somewhere in the region of a quarter of the nominal maximum is reached it is reduced to one-tenth by adjustment of the volume control. If necessary this is repeated, perhaps more than once, at higher inputs. This process, although it corresponds much more closely to the way the receiver is actually used, appears to provide the only possible argument for advocates of the other method of test, on the supposition that it involves more work than moving the range switch of the output meter. In practice this argument has no weight, because by moving the range switch one stud back with one hand and simultaneously keeping the deflection constant by moving the volume control with the other, the adjustment is a matter of perhaps 2 seconds. And instead of giving a vague result, the volume control setting is definitely known throughout the test, and the signal level can be traced through the receiver and the figures used for checking the correct operation of all the stages. Thus there is actually economy of effort.

The results for the receiver concerned in Fig. 1 might be entered like this:—

| Output : mW measured | Output : mW plotted | Input : μV |
|---|---|---|
| 2 | 2 | 0 |
| 3 | 3 | 14 |
| 10 | 10 | 22 |
| 30 | 30 | 30 |
| 100 | 100 | 47 |
| 300 } 30 } | 300 | 70 |
| 100 | 1,000 | 120 |
| 300 } 30 } | 3,000 | 270 |
| 100 | 10,000 | 1,800 |
| 300 | 30,000 | 360,000 |

The two places where brackets are used are, of course, the points at which the volume control was readjusted.

The figures in the second column show the output power that would be given if overloading of the audio-frequency section did not take place.

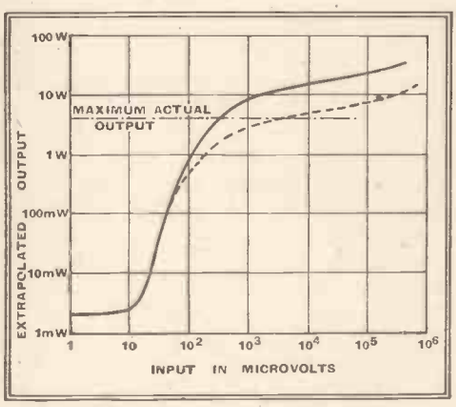


Fig. 2.—AVC characteristic, again taken at 1,000 kc/s, obtained by the ascending signal strength method. Valuable information on the design is revealed, including the desirability of reducing the delay voltage to alter the characteristic to the position shown by the dotted line.

When plotted they give Fig. 2. Although superficially very similar to Fig. 1 resulting from the alternative method of test, the only information that can be derived from Fig. 1 is that the AVC takes control at about 30 μV input and above that is quite up to average effectiveness for a normal type of receiver with 3 controlled stages; whereas the following additional information is given by Fig. 2:—

(1) The output power corresponding to any signal strength and volume control setting. For example, a 10-millivolt signal modulated 30 per cent. and with the volume control set at one quarter voltage (one sixteenth in power) would give an output of about 1 watt. Modulated 60 per cent., and neglecting distortion, the output would be 4 watts, but as the nominal output for this receiver is 3½ watts there would be some overloading. The remaining threequarters of the volume control would merely intensify the overloading. The only signals for which volume control maximum could be tolerated are those that are so weak as to be below the point where AVC operates. Therefore, the greater part of the volume control range is useless, due to excessive AVC delay voltage. A more satisfactory result would be given by dropping the flat part of the curve to the dotted position.

(2) The approximate decrease in delay voltage required is given by the square root of the power ratio between the full and dotted lines. In Fig. 2 the power is to be reduced to about a third, so if the

**The AVC Characteristic—**

present delay voltage is 6 it should be reduced to $\frac{6}{\sqrt{3}}$, or 3.5. This calculation is more accurate with high level detection, where the delay voltage is considerably greater and more nearly equal to the peak voltage at the detector.

(3) A check is given on the design. Suppose the audio amplifier requires 2.5 volts peak to give full output: that corresponds to $\frac{2.5 \times 100}{30} = 8.3$ volts IF peak (modulated 30 per cent.) applied to a perfect detector, or $\frac{8.3}{0.8} = 10.4$ volts, assuming 80 per cent. detector efficiency. The AVC voltage corresponding to that output should, therefore, be a little less than 10.4 minus the delay voltage.

(4) The sensitivity can be seen to be 35 $\mu$V for 50 mW output. If there are three AVC-controlled stages and an AF stage, this is not very good at 1,000 kc/s.

(5) The lower part of the curve is obtainable, because it is measured at volume control maximum, unlike the other method of test (Fig. 1) in which it was necessary to cut down the power to one-seventieth throughout the whole range of signal strength. It is often not convenient to measure outputs smaller than about 1 mW., and even if the meter is sensitive enough there is a likelihood of error due to hum. The lower part of the curve is of special interest when testing a receiver with QAVC. If the slope is not practically vertical, due to instant throwing off of the muting, there is a likelihood of weak-signal distortion.

(6) The 2-mW noise output is recorded. This is definitely excessive for the type of set that it appears to be, and in conjunction with the poor sensitivity suggests insufficient aerial coupling.

For these reasons, then, and from extensive practical experience, the second method of test is strongly recommended. The resulting characteristic contains so many clues to the performance of the receiver that it is well worth including as a routine test in the laboratory at least. For large quantities it might be quite practicable to rig up an automatic cathode-ray tester, which if operated at a fixed cyclical speed would, in addition, show up abnormalities in the AVC time constant as a departure from the normal separation of upgoing and downcoming curves.

## New McMichael Receivers

THE same cabinet has been adopted for the Model 391 and Model 398 AC and battery 4-valve superheterodynes. It is larger than the average table model and the specification includes many features not to be found in the low-priced categories. The "Clear-curve"

tuning scale has been designed for easy reading from any angle, and an improved four-position tone control combines variable selectivity in the IF circuits with controlled negative feedback in the AF stages. The price of the Model 391 is £12 5s., and of the Model 398 £11 5s., less batteries.

# Random Radiations

By "DIALLIST"

## U.S.A. Television Starts

BY the time that you read this, at least one regular service of television broadcasts will have started in the United States, for the N.B.C. had long been planning to make its bow by televising the opening of the World's Fair at New York. When I say "a regular service" I'm thinking only of the 441-line, 50-frame system, which will be the standard in the U.S.A.; actually, services of a more or less experimental kind with varying number of lines and frames have been carried on for some little time in different parts of the country. The Don Lee station, W6XAO, has, for instance, been running daily 300-line broadcasts on 45 Mc/s (vision) and 49.75 Mc/s (sound) for several months at Los Angeles. This station is quite a giant amongst the smaller plants, for its vision output is rated at a whole kilowatt; there are not a few which range between 15 and 125 watts.

## A Useful List

Though I knew that plans had been made to start television broadcasts in America, I'd no idea that there were so many stations contemplated or already in being until I saw the list in the May *Radio News*. It contains 19 stations already licensed and three which have applied for permits. Some of these, however, are of minute power output, whilst others, classed as portables, are apparently meant to provide the radio link for television O.B.s. Still, if we eliminate these and allow only the stations to rank whose vision output rating is one kilowatt or more, the list remains quite an imposing one. Here it is: W3XEP (30 kW), Camden, N.J.; W2XBS (12 kW), New York; W2XB (10 kW), Schenectady, N.Y.; W3XE (10 kW), Philadelphia; W2XAX (7.5 kW), New York; W1XA (3 kW), Bridgeport, Conn.; W6XAO (1 kW), Los Angeles, Cal.; W9X2V (1 kW), Chicago; W2XDR (1 kW), Long Island City, N.Y. I haven't included the 1.5 kW W9XG of West Lafayette, Indiana, because its wavelength of 150 metres doesn't appear to indicate high definition.

The wavelengths (yes, they *are* shown as wavelengths and not as frequencies) appearing in the list are all very much shorter than ours. For most of the higher-powered stations the vision and sound channels are in the neighbourhood of 6½ and 4 metres respectively. The 10-kilowatt W2XB, though, is to use channels close to 4½ metres for both sound and vision. To the portable stations and radio links still shorter wavelengths are assigned. W3XAD is to work on about 2½ metres, W2XBT on 3 for vision and 1¾ for sound, W3XP on 1½ and W2XD on 1.4. It will be extraordinarily interesting to see what kind of service areas these very short wavelengths give.

## Funny if it Weren't So Sad

WE'RE making a little progress in the anti-interference campaign; but it's slow, regrettably slow. In 1937 a standard specification was published for apparatus that could be considered as not interfering with wireless reception. It was then announced that a mark would be registered and placed on apparatus that conformed to the standards. Now, nearly two years later, the mark *has* been registered, and a very pretty design it is. But only "in due course" (and you know what that means!) will apparatus sporting the mark become available. Time, it is said, must be allowed for manufacturers to dispose of their existing stocks; in other words, vast numbers of interference-producing apparatus must be unloaded on to the public and installed by it in its homes before the campaign can begin! The whole business would be laughable if it wasn't so sad. Why in the name of fortune have the manufacturers built up these stocks when they knew two years ago that the mark was coming along?

## Portables Booming in U.S.A.

SOME months ago I reported, if you remember, that America had discovered the portable wireless set, which was then being advertised over there as the latest and greatest discovery in radio. I now hear from a friend in America that the portable has definitely caught on in the States. It didn't do so years ago when an accumulator had to be used for filament heating. I don't quite know why, though possibly Americans, used to mains receivers, couldn't be bothered with an LTB or "A battery," as they call it, which required periodic recharging. The introduction of the low-consumption filament in battery valves, which now makes it possible to use a single dry cell in place of the accumulator, has changed all that. If the LTB runs down, replacements can be obtained anywhere, and it is only a matter of a couple of minutes to have the old one removed and another put into the set in its stead. I can quite understand the point of view of those who would not touch the portable when it required an accumulator, but welcome it with open arms (and purses) now that it can get all that it needs from dry cells. There is something so beautifully neat and clean about the almost foolproof dry cell.

## Always Useful

Not that I object myself to an accumulator in a portable set—provided, of course, that it is either unspillable or of the jelly-acid type. Ever since there were portables (and they go back a good few years now) I've always had one by me and I wouldn't be without it. In my home I have aerial and earth points in three rooms. I suppose I ought to have taken leads to the bedrooms as well; but one so seldom wants wireless

in a bedroom in the ordinary way that it didn't seem worth while. It's simpler and far less trouble, anyhow, to rely on the portable to bring the programmes into bedrooms in times of illness and convalescence. And then when you're going away for a holiday a light and compact portable is easily taken with the rest of the luggage. You're quite sure too, that it will work when you get to your destination, whereas you can't be certain that a mains set will, even though it be of the AC/DC type. Before now I've struck such unexpected snags as supplies with a voltage of 100 or so, to say nothing of noisy DC mains or AC with a periodicity of 25 cycles.

## The Wavelengths

IT doesn't look as if the channels allotted at the Montreux Conference would have any very adverse effects on the service areas of our home stations. Two channels show increases in wavelength: Droitwich goes up from 1,500 to 1,511 metres and the London, Northern and Scottish Nationals from 261.1 to 262.9 metres. All of the other wavelengths are shorter, the biggest drops being suffered by the West Regional and Penmon (373.1 to 344.4 metres), the London Regional (342.1 to 327.5 metres), Northern Ireland (307.1 to 285.4 metres) and the Midland Regional (296.2 to 276 metres). But wavelength decreases should be more than offset by the promised increases in power; in fact, they may in one way prove beneficial by compelling the B.B.C. to get down to its programme of improving and rebuilding stations sooner than it would otherwise have done. It's perhaps a little hard on the radio industry that it has been decided to introduce the new plan next March. Set makers will have to decide whether to print the names on their tuning dials in the old positions this autumn and include free issues of new dials in the spring, or to anticipate the Plan by arranging their dials according to its provisions when their new models appear.

## Europe's Listeners

THE figures showing the numbers of licensed radio listeners in all European countries which were recently published by the I.B.U. make interesting reading. They show that for the whole continent the increase during 1938 was actually very nearly as great as in the previous year. There is naturally some slowing up in the rate in countries such as France and our own, which are in sight of the saturation point. But against that may be set the notable speeding up of the expansion of listeners' numbers that occurred in Italy (25 per cent.), Finland (27 per cent.), Romania (25 per cent.), Estonia (35 per cent.) and Turkey (110 per cent.). The fact that Turkey's listeners more than doubled their numbers was no doubt due to the opening of the high-power long-wave station at Ankara. Wireless in Italy seems at last to have turned the corner, though the 25 per cent. increase means an addition of only 200,000 to her listeners. At the end of the year Italian licences still totalled less than one million, despite the fact that the country has for some time had one of the largest and most efficient broadcasting systems in Europe.

# Accessories and Components

### WILLIS WORLD CLOCK

THE junior model of the Willis World Clock, which shows at any instant the time in the principal countries and on any of the standard meridians, is now available in skeleton form for incorporation in receiving sets. The hour dial revolves anti-clockwise and carries a red sector showing the part of the world which is broadcasting its evening programmes. A subsidiary hand gives the time to the nearest minute.

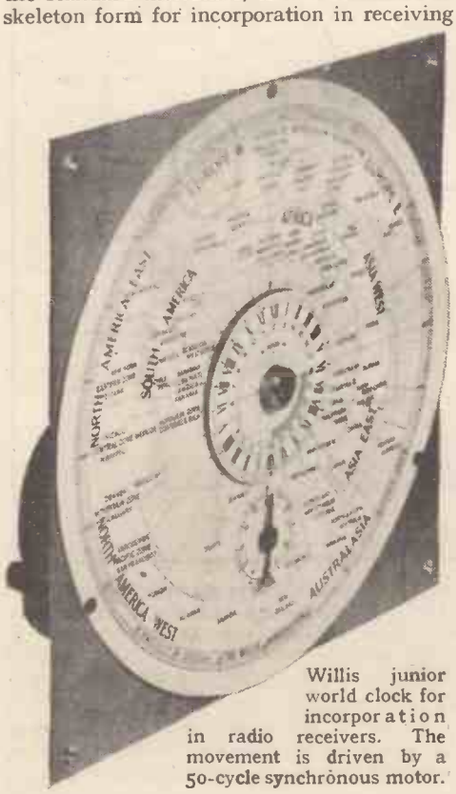


Willis junior world clock for incorporation in radio receivers. The movement is driven by a 50-cycle synchronous motor.

The makers are J. H. Willis and Co., Ipswich Road, Norwich, and the price of the movement without case is £1 18s. 2d.

### TAYLOR SIGNAL GENERATOR

THE specification of this instrument includes most of the features to be found in the more expensive standard signal generators. It has a frequency coverage of 100 kc/s to 46 Mc/s divided into six ranges calibrated in frequency. On five of the ranges, i.e. up to 23 Mc/s, the fundamental of the RF oscillator is used and on the sixth the first harmonic.

Variable internal modulation at 400 c/s up to 50 per cent. is provided, and a switch enables an external source of AF to be used. The 400 c/s internal supply is also available for testing amplifiers and the modulation control then functions as an output volume control.

The metal case measures only 12in. × 8in. × 6in. External leakage is negligible for all practicable purposes. A screened output lead is supplied and a special lead having the characteristics of a dummy aerial is available at an extra charge of 7s. 6d. The 400 c/s output is taken from a telephone jack, and a pilot lamp is fitted to show whether the power supply is reaching the instrument.

The RF output is controlled by a continuously variable attenuator marked "Microvolts" 0-10, and a separately screened multiplier increases the output in decade steps up to 0.1 volt. There are intermediate stops which should be ignored between the marked settings. No calibration chart is supplied, but the output

Taylor Model 60 all-wave signal generator.

approximates to the settings of the attenuator except on the "F" range, where the harmonic is much weaker.

A check on the AF output showed the maximum voltage on open circuit to be about 1¼ volts. Most of the variation is in the first half of the volume control. The pitch is constant when the oscillator is used as a source of AF, but varies about a semitone over the range of the control when modulating the RF circuit.

The RF calibration is within the reading accuracy of the scales, which are from 2¼ to 3½ inches in diameter. The 400 c/s waveform is good and the instrument can be recommended for circuit alignment and the comparison of receiver performance. At 10 guineas it is not expensive. The makers are Taylor Electrical Instruments, Ltd., 77-77a, Queen Victoria Street, London, E.C.4.

### RESISTANCES FOR CATHODE-RAY CIRCUITS

ALTHOUGH not new, the multiple resistance elements made by Erie Resistor, Ltd., Carlisle Road, The Hyde, London, N.W.9, are being put forward as possible substitutes for the lengthy and often exposed string of resistors usually fitted in television receivers to discharge the high voltage smoothing condensers.

The resistor illustrated measures 2½ inches overall and is only 1¼ inches in diameter. It has a resistance of 20 megohms and will withstand 5,000 volts without flash-over.

Erie multiple high voltage resistor for cathode-ray HT circuits.

The resistance elements are in the form of rings which are separated by flanged ceramic formers and connected non-inductively. Any number of units may be assembled up to a total length of 18 inches, and the elements are of two types: Size A, 1¼ inches diameter, 1,000 volts per ring, 3½ watts per inch length; and Size B, ¾ inch diameter, 600 volts per ring and 1¼ watts per inch length.

Their compactness and safety will commend them to manufacturers who realise that ordinary broadcast receiver standards of insulation are in the nature of a makeshift when applied to the high-tension side of television receivers.

# Recent Inventions

The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from Specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.

***Brief descriptions of the more interesting radio devices and improvements issued as patents will be included in this section.***

### ELECTRON-MULTIPLIERS

THE ordinary type of electron-multiplier has a very high output impedance—approaching infinity—so that it is impossible to deliver power efficiently from it to, say, a loud speaker or other low-impedance load.

According to the invention, this difficulty is overcome by making the last target electrode so that its emissivity is not uniform, but varies in a predetermined manner from point to point of its surface. This has the effect of making the characteristic curve of the device less steep and of providing a long straight-line "slope" over which the device can be operated.

As shown in the figure, the main electron stream passes from one target electrode T to the next in a series of curved paths, the current being increased in intensity at each stage by secondary emission. The last target T1 is not uniformly emissive, as are the others, but a part of it (shown clear in the inset diagram) is coated with a more highly emissive material than the parts shown shaded.

Under working conditions the stream will either fall mostly towards the right-hand side of the target, where the emissivity is greatest, or else mostly towards the left-hand side, where the emissivity is less, according to the output voltage on the collecting electrode O. In this way the effective impedance is made dependent upon the "sensitivity design" of the target T1.

*Marconi's Wireless Telegraph Co., Ltd., and G. B. Banks. Application date July 15th, 1937. No. 498843.*

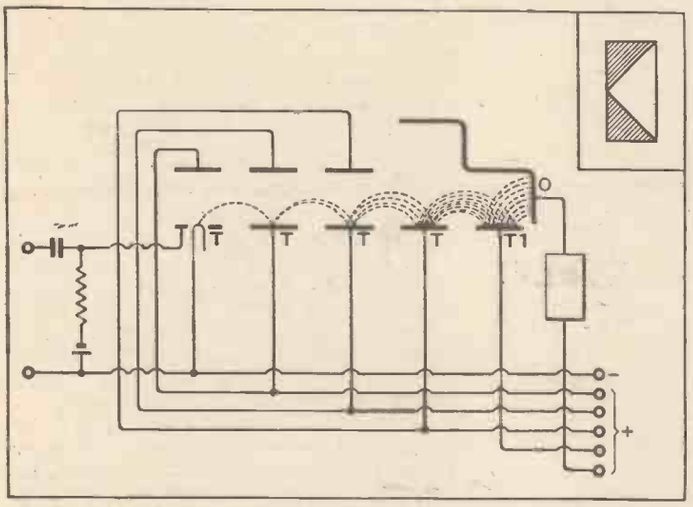


Decreasing the output impedance of an electron multiplier by means of a special construction of the final target electrode (shown in the inset).

o o o o

### DIRECTIONAL AERIAL SYSTEMS

TWO spaced aerials, coupled in opposition to a common receiver, will pick up maximum signal strength from a transmitter which is in line with them, but will give minimum signal strength if the transmitter is situated at right-angles to this line. The well-known Adcock aerial consists of two such pairs of spaced aerials arranged crosswise.

According to the invention, three or more such pairs of aerials are arranged symmetrically around the circumference of a circle, each pair being coupled to the corresponding field winding of a radio-goniometer, or to the similarly arranged deflecting plates of a cathode-ray indicator. This improves the sensitivity of the aerial system, and therefore adds to its effective range, and is used as an alternative to increasing the aerial height—which is undesirable in the case of an aerodrome installation. The operation of the system in direction-finding is also less dependent upon the accurate balancing of each pair of aerials, particularly as regards phase.

*Standard Telephones and Cables, Ltd., and C. F. A. Wagstaffe. Application date July 9th, 1937. No. 498417.*

### LOUD-SPEAKER "TONE-CONTROL"

IN a highly selective receiver, the band width of the intermediate-frequency circuits may be made so narrow that the sounds from the loud speaker are accompanied by rustling and hissing noises, probably due to the production of overtones by the valves and to spurious vibrations in the speaker diaphragm.

According to the invention, such noises are prevented by applying a "compensation" device to the loud speaker.

The drawing shows part of a superhet receiver, including the IF band-pass coupling A, and the usual AF tone-controls comprising capacity C and inductance L. Both couplings are ganged to a series of movable shutters S, which serve to close the sound-apertures in the speaker diaphragm to a greater degree as the band-pass coupling is tightened up, or as the tone-controls C and L are brought into operation. The shutters slightly reduce the volume of sound, but are stated to keep the higher and lower frequencies in the correct proportion to produce a pleasing effect, free from disagreeable overtones.

*N. V. Philips Gloeilampenfabrieken. Convention date (Germany) May 10th, 1937. No. 499108.*

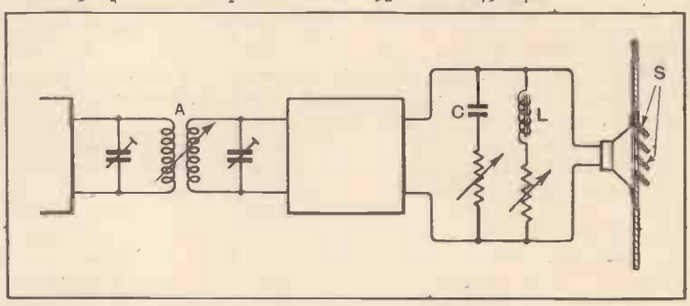


Combined electrical and acoustic tone-control.

o o o o

### PRODUCING SYNCHRONISING IMPULSES

THE invention relates to means for producing synchronising impulses at the end of each scanning line in a television transmitter. Although the method is of general application, it is illustrated in connection with a rotating disc scanner D and a cinema film F.

Light from an aperture O in the rotating disc is focused on to the film by means of lenses L, L1, and passes through the film to energise a photo-electric cell P, which is coupled to the signal amplifier A. As the ray reaches the end of each scanning line, it falls on to an inclined mirror M, from which it is reflected along the dotted line path on to an auxiliary photo-electric cell P1. The cell P1 is connected to an impulse amplifier A1 in opposite polarity to that in which the primary cell P is conected to the signal amplifier A. The EMF produced by the impact of the reflected ray on the cell P1 thus produces a negative synchronising impulse at the end of each line of radiated signals.

*Radio-Akt. D. S. Loewe. Convention date (Germany) July 16th, 1936. No. 498841.*

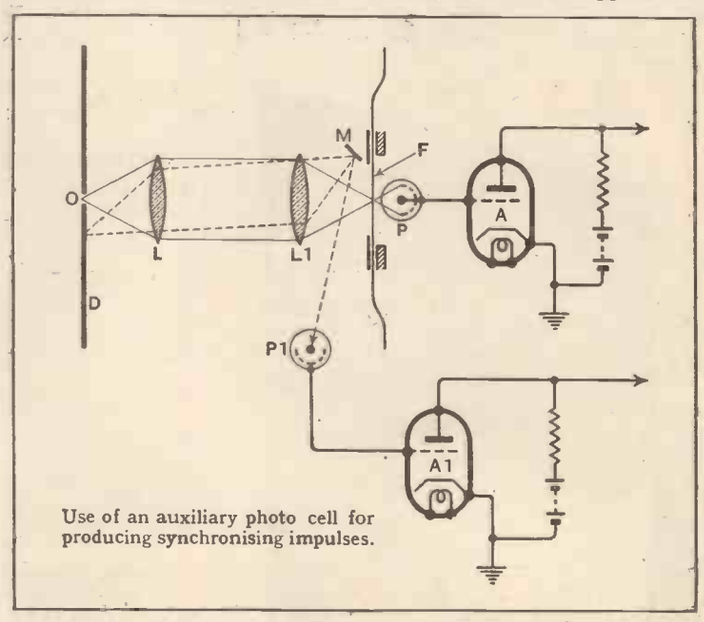


Use of an auxiliary photo cell for producing synchronising impulses.

### MAKING MOSAIC-CELL SCREENS

A BUNDLE of fine aluminium wires, equal to the number of picture-points required on the screen, and coated with aluminium oxide, is firmly bound with metal rings, and is then cut up into thin slices, each of which forms the basis of the screen.

To complete its preparation, the surface of each slice is first etched so that the ends of the wires are slightly eaten away, leaving a corresponding number of small cups or recesses, surrounded by the projecting edges of the original insulating layer. The cupped wires are then made photo-sensitive by treatment with silver and cæsium vapour. The aluminium oxide insulation may be further covered with a layer of graphite, which serves to screen the wires electrically from one another.

*Radio-Akt. D. S. Loewe. Convention date (Germany) June 16th, 1936. No. 498672.*

# TROPHY communications GEAR

IN a nutshell, the phenomenal success of TROPHY short-wave receivers and accessories is due to (1) the amazing increase in the number of short-wave enthusiasts. (2) Unbeatable TROPHY performance. (3) Reasonable prices. (4) Preference for ALL-BRITISH. The importance of short-wave communications these days is appreciated most by TROPHY owners... Prove it for yourself. See about your TROPHY now.

## PRESELECTOR for your present set

For use with any TROPHY receiver or in front of any mains or battery operated superhet or straight instrument. Two low-noise R.F. pentodes are employed giving increased range, selectivity, signal strength and considerable image suppression, factors of sufficient importance to merit the use of the TROPHY PRESELECTOR with any existing receiving gear. 3 controls—combined R.F. Gain, On-Off Switch, Band Switch and Tuning. Complete in black crackle finish steel cabinet size 11 x 9 x 9 ins., aligned and ready for use. TERMS: 11/9 down and 12 monthly payments of 11/7.

**£6.15s.**

- ★ 2-stages using EF8 valves.
- ★ 5 Bands—7 to 550 metres.
- ★ S/M tuning—800° in 1° steps.
- ★ Frequency calibrated scale.
- ★ Self-powered for AC 200/250 volts.

● TROPHY 12 months' guarantee includes valves

## AT A GREAT SAVING

... these TROPHY Best Sellers are also available on Easiest Terms.

**TROPHY 6** New Junior A.C. communication model. 6 valves—all octal types. 10-550 metres complete coverage. Two-dial electrical band spreading. Switched AVC and BFO. Pitch control. Send-Receive switch. Built-in speaker. 'Phone jack. Amazing performance, amazing value. TROPHY Guarantee .. .. .. **9½ GNS.**

**TROPHY 3** A.C. and Battery 3-valvers for operation on 6 to 550 metres using self-locating inductors. Metre calibrated scale. Built-in speaker. 'Phone jack. Supplied complete in cabinet with coils for 12-52 metres. BATTERY model, £5/15/0. A.C. model, 6 Gns. Extra coils for complete coverage add 16/9 to cash prices **£5 15 0**

**STEEL CABINET** TYPE T8. Now available at the request of experimenters. In appearance as illustration below, lift-up lid but supplied with extra heavy gauge undrilled separate steel panel. Sufficiently robust for all classes of gear. Pleasing black crackle finish. Size 17¾" × 9½" × 12" deep. Required special packing and part carriage 3/6 extra. Cash or C.O.D. only .. .. **21/-**

## WIRELESS WORLD Pilot Kit Service

Still available, all kits for receivers designed by this journal including the following:

- Pretuned Receiver
- Stand-By (Portable) 3
- Short-Wave A.C.3
- Communication Receiver
- Straight Six
- 2RF Straight set

*Detailed price lists FREE*

## TROPHY 8

A.C. communications-type receiver. 8 valves. Wave-range 7-550 metres. R.F. on all five bands. Continuous band-spreading. AVC, BFO, Send and Receive switches. 'Phone jack and sockets for using separate speaker. Pleasing cabinet as illustrated. The performance of this set rivals many American similar types offered in this country at double the price. Aligned and ready for use. TERMS: 15/6 deposit and 18 monthly payments of 15/6.

**12 GNS.**

**PLEASE SEND** for complete Short-wave and Broadcast Radio Chassis lists.

**PETO SCOTT Co. Ltd.** 77 (WW 15) CITY ROAD, LONDON, E.C.1 *Clissold 9875*
41 (WW 15) HIGH HOLBORN, W.C.1 *Holborn 3248*

---

# CERAMIC H.F. INSULATORS

Low Power Loss
No Leakage Loss
Completely Cyclic
Secularly Stable
Range of Permittivities

*Fixed and variable Condensers, High Stability Inductance Coils, Coil Formers, Mouldings, Rods, Tubes and all components for H.F. Work.*

**UNITED INSULATOR Co LTD**
**12-16, LAYSTALL ST., LONDON, E.C.1**
Telephone Terminus 4148-9 Telegrams Cabinet Smith London

UIC

---

# MODERN MINSTREL TOURS

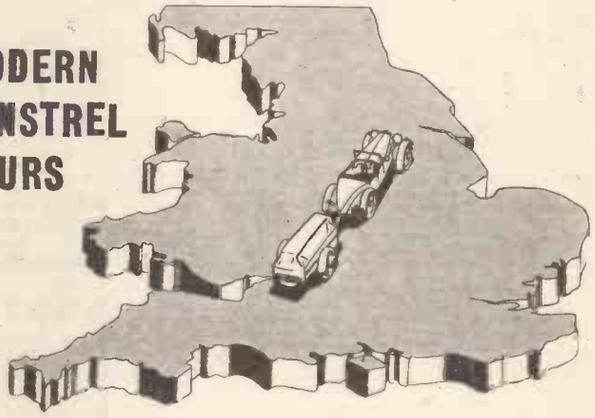

Our thanks to all those enthusiasts and societies who have offered to act as hosts under our modern minstrel scheme. Responses have come from Lincoln to South Wales, from Hastings to Manchester. Good!—but we want to fill in intermediate points.

How those musical evenings are enjoyed! Requests for repeat visits are the sure evidence of that.

The idea is simple—a series of demonstrations (ideally at places 30 miles apart), taking place in the home of any enthusiast who permits us to invite a few others from our mailing list, and who accommodates our engineer for the night.

Such tours increase our experience with the light coil twin diaphragm under practical working conditions, and enable direct comparisons with other speakers to be made.

Do you wish to be host or visitor? If host, kindly advise distance to nearest garage.

Don't miss the opportunity. Perhaps a friend will oblige if you cannot.

Please write NOW and help us to make our plans.

VOIGT
VOIGT PATENTS LTD

THE COURTS, SILVERDALE, LONDON, S.E.26
*Tel.: SYDenham 6666*
Regd. Office: 22, Castle Street, E.C.1.

# CLASSIFIED ADVERTISEMENTS

## NOTICES

THE CHARGE FOR ADVERTISEMENTS in these columns is

12 words or less, 3/- and 3d. for every additional word.

Each paragraph is charged separately and name and address must be counted.

SERIES DISCOUNTS are allowed to Trade Advertisers as follows on orders for consecutive insertions, provided a contract is placed in advance, and in the absence of fresh instructions the entire "copy" is repeated from the previous issue: 13 consecutive insertions 5%, 26 consecutive, 10%; 52 consecutive, 15%.

ADVERTISEMENTS for these columns are accepted up to FIRST POST on MONDAY MORNING (previous to date of issue) at the Head Offices of "The Wireless World," Dorset House, Stamford Street, London, S.E.1, or on SATURDAY MORNING at the Branch Offices, 8-10, Corporation Street, Coventry; Guildhall Buildings, Navigation Street, Birmingham, 2; 260, Deansgate, Manchester, 3; 26B, Renfield Street, Glasgow, C.2.

Advertisements that arrive too late for a particular issue will automatically be inserted in the following issue unless accompanied by instructions to the contrary. All advertisements in this section must be strictly prepaid.

The proprietors retain the right to refuse or withdraw advertisements at their discretion.

Postal Orders and Cheques sent in payment for advertisements should be made payable to ILIFFE & SONS Ltd., and crossed & Co. Notes being untraceable if lost in transit should not be sent as remittances.

All letters relating to advertisements should quote the number which is printed at the end of each advertisement and the date of the issue in which it appeared.

The proprietors are not responsible for clerical or printers' errors, although every care is taken to avoid mistakes.

## NEW RECEIVERS AND AMPLIFIERS

R.

C.

TELEPHONE: Holborn 4631.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1, by offering brand new receivers, maintain their reputation as the leading Mail Order House for surplus radios.

BRITISH Belmont 8-valve Plus Magic Eye All-wave A.C. Superhet Chassis, 4 wave bands, 2 short medium and long, fitted latest Mullard octal base American type valves. Brief specification: Short wave 6-18 metres (covers television sound), short wave 2, 18-50 metres, medium band 200-550 metres, long 900-2,000 metres; valve combination 6K7 Pre H.F., 6J7 oscillator, 6J7 mixer, 6K7 I.F., 6Q7 (DDT) detection, A.V.C. and first L.F., two 6F6s, parallel output, 5Y3 rectifier, plus 6G5 Magic Eye visual tuning, handsome dial, station names etched on glass, controls 2-speed tuning, volume and on-off, combined variable tone control and selectivity switch, wave change plus gramo. switch; size of chassis 13½in.×10in.×3in.; supplied complete with valves, escutcheon, knobs, but less speaker, £5/19/6 each; complete receiver in handsome walnut cabinet, details as above, complete with speaker, £7/7.

DECCA 6-valve 3-waveband Battery Chassis, fitted complete with Mazda and Osram valves, QPP output; these chassis give a sparkling performance on all wavebands, and are the product of a well known manufacturer, complete with valves, £3/3 each; complete receiver in handsome walnut cabinet, details as above, complete with speaker, £3/19/6 each.

LISSEN 5-valve Plus Magic Eye All Wave A.C. Superhet, three separate scales operated by wave-change switch, fitted in magnificent walnut table cabinet, triode output, fitted ring valves throughout, brand new in carton; our price £5/19/6.

LISSEN 5-valve All Wave A.C. Superhet, fitted in upright walnut table cabinet, brand new in carton; £5/5.

LISSEN 4-valve 2 Wave A.C. Superhet, fitted in modern oblong type walnut cabinet, brand new, in carton; £4/4.

LISSEN 5-valve All Wave Battery Superhet, Class B output, fitted in handsome walnut table cabinet, complete but less batteries, brand new in carton; £3/17/6.

LISSEN 4-valve All Wave Battery Superhet, as above, but pentode output; £3/15.

ALL the Above Fitted Ring Valves Throughout.

SEE Our Advertisement under Components.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1. Telephone: Holborn 4631. [8380

## ARMSTRONG'S NEW HEADQUARTERS

After many years at our old premises in Camden Town we have moved our Offices, Show Rooms and Development Department to a modern building centrally situated in

**WARLTERS ROAD, HOLLOWAY, N.7**
**(Adjoining Holloway Arcade).**

which is conveniently reached by bus or tube from any part of London.

We take this opportunity of sincerely thanking the vast number of "Wireless World" readers whose consistent custom it has been our pleasure to receive for so many years.

Incidentally, this is the seventh year we have advertised in the "Wireless World" *without a break*. The facilities afforded by these larger premises will enable us to give the same personal attention and service to our constantly growing list of customers, as we have given in the past.

We shall be glad to see you in our new "Home" where you can hear, in comfort, demonstrations of any or all the latest Armstrong Models.

Send for Illustrated Catalogue of our full range, which includes the following outstanding chassis.

**MODEL AW125PP . Price £17.17.0**
**12-V. ALL-WAVE RADIOGRAM CHASSIS**

5 wavebands, 12-550 continuous, 1,000-2,000 m., R.F. Pre-Amplifier, 2 I.F. stages with Variable Selectivity. Manual R.F. gain control and 10 watts R.C. coupled Triode P.P. output.

Every worthwhile modern refinement has been incorporated in the design of this chassis.

**MODEL AW93PP . Price £10.10.0**
**9-V. ALL-WAVE RADIOGRAM CHASSIS**

3 wavebands, R.F. Pre-amplifier, 3 stages of A.V.C. and 8 watts R.C. coupled Triode P.P. Output.

Specially designed for those requiring particularly good quality reproduction.

*All communications to be addressed to*

**ARMSTRONG MANUFACTURING CO.,**
**WARLTERS ROAD, HOLLOWAY, LONDON, N.7**
**(Adjoining Holloway Arcade).**

*Telephone: NORth 3213.*

**EASY TERMS *by* L.R.S**
ON ALL
**ARMSTRONG CHASSIS**

MODEL AW125PP - - - 12-VALVE ALL-WAVE RADIOGRAM CHASSIS
Cash 17 Gns. or £2 with order and 12 monthly payments of - - - - - - - - - - £1.8.0
MODEL AW93PP - - - 9V. ALL-WAVE RADIOGRAM CHASSIS - - Cash 10 Gns. or 21/- with order and 12 monthly payments of 17/-
(See *Armstrong Advt. above*)

Send for details of the 11 Armstrong Models and our CONVENIENT TERMS.

*Estd: —1925* THE *'Phone NATional 6828*
**LONDON RADIO SUPPLY COMPANY**
11·OAT LANE·NOBLE ST·LONDON·E.C.2

**Pamphonic AMPLIFIERS**

Pamphonic Reproducers Ltd. (*Associated with PYE Ltd.*)
45, St. Pancras Way, London, N.W.1.
'Phone: EUSton 1727.

## NUMBERED ADDRESSES

For the convenience of private advertisers, letters may be addressed to numbers at "The Wireless World" Office. When this is desired, the sum of 6d. to defray the cost of registration and to cover postage on replies must be added to the advertisement charge, which must include the words Box 000, c/o "The Wireless World." All replies should be addressed to the Box number shown in the advertisement, c/o "The Wireless World," Dorset House, Stamford Street, London, S.E.1. *Readers who reply to Box No. advertisements are warned against sending remittances through the post except in registered envelopes: in all such cases the use of the Deposit System is recommended, and the envelope should be clearly marked "Deposit Department."*

### ☞ DEPOSIT SYSTEM

Readers who hesitate to send money to advertisers in these columns may deal in perfect safety by availing themselves of our Deposit System. If the money be deposited with "The Wireless World," both parties are advised of its receipt.

The time allowed for decision is three days, counting from receipt of goods, after which period, if buyer decides not to retain goods, they must be returned to sender. If a sale is effected, buyer instructs us to remit amount to seller, but if not, seller instructs us to return amount to depositor. Carriage is paid by the buyer, but in the event of no sale, and subject to there being no different arrangement between buyer and seller, each pays carriage one way. The seller takes the risk of loss or damage in transit, for which we take no responsibility. For all transactions up to £10, a deposit fee of 1/- is charged; on transactions over £10 and under £50, the fee is 2/6; over £50, 5/-. All deposit matters are dealt with at Dorset House, Stamford Street, London, S.E.1, and cheques and money orders should be made payable to Iliffe & Sons Limited.

SPECIAL NOTE.—Readers who reply to advertisements and receive no answer to their enquiries are requested to regard the silence as an indication that the goods advertised have already been disposed of. Advertisers often receive so many enquiries that it is quite impossible to reply to each one by post. When sending remittances direct to an advertiser, stamp for return should also be included for use in the event of the application proving unsuccessful.

## NEW RECEIVERS AND AMPLIFIERS

*

*

DEGALLIER'S "Challenger Radio Corporation."

SEND 2d. Stamp for Handsome Illustrated Catalogues Telling of our Superb Range of Receivers; direct public sales policy (saves you 40%), most exceptional value on the market, from a T.R.F. Midget at £3/5 to a 19-valve general purpose receiver, 6 bands, with two P.A. speakers, at 30 gns.; 6-page brochure of *Wireless World* report on this set is available; car radio; any known American valve, all 5/6 each; if interested ask for particulars of American samples at less than cost; even samples covered by usual guarantee; also American P.A. Speakers and Cabinets. Hours business 11 a.m. until 9.30 p.m.

DEGALLIER'S, 31, Craven Terrace, London, W.2. Paddington 6492. Nearest point Lancaster Gate Tube Station. [8382

FREE, Radio Handbook and Summer Call Book, with new Hallicrafters Sky Buddy, which covers 10-metre band, has electrical band spread, BFO, A.V.C. Phone Jack, complete coverage to 550 metres, great job; all in £10.

RADIOGRAPHIC, Ltd., 66, Osborne St., Glasgow, C.1. [8372

## RECEIVERS AND AMPLIFIERS
### CLEARANCE, SURPLUS, ETC.

BANKRUPT Bargains.—Brand new 1938 Philco Model 847 Empire 8, finest 8v. all-wave superhet available, exceptional short wave performance, 4 W.B., in maker's sealed carton, with guarantee, list price 29 gns.; cash price £13/13; send 1½d. stamp for list of other bargains.—261-3, Lichfield Rd., Aston, Birmingham. [8376

## USED SETS FOR SALE

### McMURDO

McMURDO Silver Masterpiece V, in special solid oak cabinet, 20 valves, 5 wavebands, 18in. speaker, a magnificent instrument, all as new, cost £95; accept £27/10.—Harris, Caterham 250. [8410

### MIDWEST

MIDWEST Receivers, a few demonstration models, chassis complete with speaker and valves, 18-valve superhet., A.C. mains, 6 wavebands, 4-valve push-pull, 12½ gns.; 14-valve ditto, 5 wavebands, 11 gns.; 11-valve ditto, 10 gns.; all guaranteed perfect condition.—Electro Mechanix, 27, Lisle St., London, W.C.2. [8414

### PILOT

PILOT 10-valve Set, 4½-2,000 metres, perfect; £16, offers.—Langley's Library, Deeside, Brighton. [8403

## VORTEXION 50 W AMPLIFIER
## £15 in Chassis Form

VORTEXION, LTD., are making a new 50 W amplifier which is offered at £15 as a chassis with valves and plugs, or at £20 complete in black leatherette-covered cabinet with Collaro turntable, piezo-electric pick-up and shielded microphone transformer.

A pair of matched 6L6's with 10 per cent. negative feed-back is fitted in the output stage, and the separate HT supplies to the anode and screen have better than 4 per cent. regulation, while a separate rectifier provides bias.

The 6L6's are driven by a 6F6 triode connected through a driver transformer incorporating feed-back. This is preceded by a 6N7, electronic mixing for pick-up and microphone. The additional 6C5 operating as first stage on microphone only is suitable for any microphone. A tone control is fitted, and there is an eight-section output transformer whereby any output from 4 to 30 O may be matched and yet deliver the full response (20-18,000 C/S) to the loudspeakers.—*Vortexion, Ltd., 182 The Broadway, Wimbledon, S.W.19. 'Phone: LIBerty 2814.*

*Said Peter Augustus De Wet,*
*"I've found out what's wrong with this set.*
*For all it's requiring*
*Is just a rewiring,*
*And this time, with FLUXITE you bet!"*

**See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for 30 years in Government works and by leading engineers and manufacturers. Of Ironmongers—in tins, 4d., 8d., 1/4 and 2/8.**
**Ask to see the FLUXITE SMALL-SPACE SOLDERING SET—compact but substantial—Complete with full instructions, 7/6.**
**Write for Free Book on the art of "SOFT" SOLDERING—and ask for leaflet on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE.**

**TO CYCLISTS!** Your wheels will NOT keep round and true unless the spokes are tied with fine wire at the crossings AND SOLDERED. This makes a much stronger wheel. It's simple—with FLUXITE—but IMPORTANT

## THE FLUXITE GUN

is always *ready* to put *Fluxite* on the soldering job instantly. A little pressure places the right quantity on the right spot and one charging lasts for ages. Price 1/6 or filled 2/6

ALL MECHANICS *WILL* HAVE

# FLUXITE

IT SIMPLIFIES *ALL* SOLDERING

FLUXITE LTD., Dept. W.W., DRAGON WORKS, BERMONDSEY ST., S.E.1

## USED SETS FOR SALE

### R.M.E. 69

COMBINATION R.M.E.69, D.B.20, one cabinet; one month old, cost £55; £45, or near offer.—Kennedy, Rushmere, Weedon Rd., Northampton. [8401

### W.W. QUALITY AMPLIFIER

"W.W." Quality Amplifier, 12 watts, with valves, new, unused; £7/10.—127, Broadway, Cricklewood. [8402

## CAR RADIO

CROSLEY Push-button 1939 10 guinea Models, 5½ gns.; aerials, overheads, police type, etc., from 8/6; trade enquiries solicited.—Shippers, 18, Corporation St., Manchester. [0622

FINEST American Twin Running-board Aerials, completely rubber covered, maximum signal pick-up, minimum noise, easy mounting, now only 17/6 pair complete; handsome chromium roof aerials, to mount straight or "vee," complete, 15/-; immediate despatch, carriage paid; cash with order or c.o.d.

WIRELESS SUPPLIES UNLIMITED, Essex House, Stratford, E.15. Maryland 3191. [0577

## PUBLIC ADDRESS

VORTEXION P.A. Equipment.

IMITATED, but unequalled.

WE Invite You to a Demonstration.

A.C.-D.C. Dance Band Amplifier, 10 watts output, complete in case, with moving coil microphone, speaker and cables, weight 22lb.; 12 gns.

A.C.-20 15-20-watt Amplifier, 30-18,000 cycles, independent mike and gram., inputs and controls, 0.037 volts required to full load, output for 4, 7.5, and 15 ohms speakers or to specification, inaudible hum level; ready for use; 8½ gns., complete.

C.P. 20, 12-volt battery and A.C. mains model, as used by R.A.F., output as above; 12 gns.

A.C.20, in portable case, with Collaro motor, Piezo pick-up, etc., £14; C.P.20 ditto, £17/17.

50-WATT Output 6L6s, under 60-watt conditions, with negative feed back, separate rectifiers for anode screen and bias, with better than 4% regulation, level response, 20-25,000 cycles, excellent driver, driver transformer and output transformer matching 2-30 ohms impedance electronic mixing for mike and pick-up, with tone control, complete with valves and plugs; £15.

COMPLETE in Case, with turntable B.T.H. Piezo pick-up and shielded microphone transformer, £20.

80-WATT Model, with negative feed back; £25, complete.

120-WATT Model, with negative feed back; £40, complete.

250-VOLT 250 m.a. Full Wave Speaker, field supply unit; 25/-, with valve.

ALL P.A. Accessories in Stock; trade supplied.

VORTEXION, Ltd., 182, The Broadway, Wimbledon, S.W.19. 'Phone: Lib. 2814. [8241

ALEXANDER BLACK, Ltd.—Consult us on sound installations, temporary or permanent; booklet on request.—55, Ebury St., S.W.1. Sloane 6129. [0597

PUBLIC Address Contractors Can Hire P.A. Vans, loud-speakers, microphones and equipments of all types from Hire Dept., Grampian Reproducers, Ltd., Kew Gardens, Surrey. Tel.: Richmond 1175-6-7. [0618

SLIGHTLY Used Goodmans P.A. Horn Speaker and Junior Auditorium Unit, cost £10 and £3/2/6, 55/- and 25/- respectively; Hunt's condenser and resistor tester, £5, cost £11/5; also mikes, cable, etc.; write for list.—50, Carpenter Rd., Birmingham, 15. [8393

## NEW MAINS EQUIPMENT

VORTEXION Supply G.P.O., B.B.C., L.P.T.B. Why not you?

ALL Models Super Shrouded, primaries screened and tapped, 200-250v., filaments C.T.

ANY Model Fitted 5v. or 6.3v. Filaments if Required.

500-0-500 150 m.a., 4v. 4a., 2.5a., 4v. 2a., 4v. 2a., 4v. 2a., 35/-; 400 or 350v., same price.

500-0-500 120 m.a., 4v. 4a., 4v. 2.5a., 4v. 1-2a., 4v. 1-2a., 28/-; 400v. or 450v., same price.

425-0-425 150 m.a., 4v. 8-10a., 4v. 2.5a., 4v. 1a., 4v. 1a., 32/-.

350-0-350 120 m.a., 4v. 4a., 4v. 2.5a., 4v.1-2a., 21/-; with extra 4v. 6a., 25/-.

350-0-350 75 m.a., 4v. 2.4a., 4v. 1-2a.; 18/-.

250-0- 250 60 m.a., 4v. 2-4a., 4v. 1-2a.; 15/-.

AUTO Transformers, 100-120 to 200-240v., 80 watts, 11/-; 120 watts, 14/6; 200 watts, 21/-; 250 watts, 25/-; 300 watts, 28/-; 500 watts, 47/6.

W.W. Q.A. Output Transformer; 21/-.

MICROPHONE Transformers, in heavy magnetic shielding; 12/6.

CHOKES.—30h. 60 m.a., 7/6; 7-13h. 120 m.a., 12/6; 30h. 150 m.a., 15/-; 25h. 150 m.a., 21/-.

TRANSFORMERS and Chokes to Any Specification.

CAR Battery Charger, 6 and 12v., 1½ to 2 amperes; 30/- complete.

VORTEXION, Ltd., 182, The Broadway, Wimbledon, London, S.W.19. Telephone: Liberty 2814. [8412

GRAMPIAN REPRODUCERS LTD. 1002

**MEMORANDUM**

From Chief Research Engineer.
To. All Sound Engineers.
Date. 27-4-39

Results of final tests on
High Velocity Projector Speaker
Unit Type P.V.H.
show this model to be ideal for rough usage - outdoor work. Maximum results from minimum input. Audible at 2 miles. Normally rated at 10 watts, will handle peak powers of 18 and 35 watts (according to size of horn). Efficiency approximately 45%, 2½ times that of usual horn speaker embodying cone unit. Will project speech ¼ mile with only 6 watts loading. Specially suitable for noisy conditions. Entirely weatherproof - unaffected

GRAMPIAN REPRODUCERS LTD / CONTINUATION

by damp or heat. Response curve smooth in critical region between 200 and 2,000 C.P.S. falling off slightly at 5,000 C.P.S. but steadily increasing above 7,000 C.P.S.
Construction is unique. Diaphragm of moulded, seamless bakelite is fitted with copper, (NOT aluminium) speech coil. Difficulty of connecting lead-out wires to usual aluminium coil thus avoided. Accessibility a special feature. Diaphragm can be centred or replaced by even a semi-skilled person in less than five minutes. Recommended to cover large areas or where excessive noise has to be overcome.

Prices:
With straight 42 in. Horn 11 Gns.
With "Diska" Co-axial Horn 12 Gns

# GRAMPIAN
REPRODUCERS LTD.
KEW GARDENS SURREY
PHONE RICHMOND 1175

*"Foundations of Wireless," Second Edition. 4s. 6d. net. Post free 4s. 11d.*

## NEW LOUD-SPEAKERS

SINCLAIR Speakers for all types.—Alma Grove, Copenhagen St., N.1. [0603

BAKERS.—New corner horn speakers for realistic reproduction; leaflets free.—Bakers Selhurst Radio, South Croydon. [8369

## LOUD-SPEAKERS

### SECOND-HAND, CLEARANCE, SURPLUS, ETC.

ROLAS, for 6/11; G12's, 47/6; ½d. stamp for lists.—Shippers, 18, Corporation St., Manchester. [0606

VAUXHALL UTILITIES, 163c, Strand, W.C.2.—Rola G12 P.M. speakers, 62/6; G12 energised, 50/-; with transformers, brand new. [8385

BARGAIN!—Epoch new £14/14 energised speaker, 45/-; Rola J90, in cabinet, £1/1.—Levene, 1, Bushey Rd., West Ham, E.13. [8415

HARTLEY TURNER Speakers, energised and permanent magnets, as new; 50/- each.—Crouch, 11, Dingle Close, Sea Mills, Bristol. [8404

BAKERS.—Famous super power speakers at half price; as solely specified for "Wireless World" Quality receiver.—Bakers Selhurst Radio, South Croydon. [8370

3,000 Speakers from 5/6 each, P.M. and energised 4in. to 14in., including several Epoch 18in.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0591

EPOCH "Domino" Speaker, with rectifying equipment and additional smoothng choke and condenser, perfect condition; demonstration; £4.—Seymour, 3, Fulbrooke Rd., N.19. [8395

SIX B.T.H. Cinema Speakers, 1,100 ohms, 100-volt field, 8in. cone, 15 ohms speech coil, with 64in. oak horns, handle 10-15 watts; £3 each, carriage forward.—Ward, 46, Farringdon St., London, E.C.4. Telephone: Holborn 9703. [0629

EPOCH 18in., rebuilt, any field, £5; with A.C. equipment, £2 extra; Epoch 14in. mains energised, 70/-; fitted A.C., 30/- extra; several 10in., 12in., and 15in. energised and P.M.s, from 20/-.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0628

## LOUD-SPEAKER CONVERSIONS

BAKERS.—Triple cone conversions immensely improve reproduction from any speaker; price 29/6.—Bakers Selhurst Radio, South Croydon. [8371

## TELEVISION

EDISWAN 10in. Electrostatic Tube, used 300 hours for oscillograph work only, £3/10; Bosch 7in. electrostatic tube, brand new and unused, £4.—S. West, Worlingham, near Beccles, Suffolk. [8392

## TRANSMITTING APPARATUS

A.C.S. RADIO, specialists in short-wave apparatus, communication receivers, including Hallicrafters, National and R.M.E. transmitting equipment, valves and components.—Send for free catalogue to A.C.S. Radio, 16, Gray's Inn Rd., W.C.1. Holborn 9894-5. G2NK. Technical Manager. [0550

G5NI.—The oldest and largest distributors of amateur equipment, transmitting and receiving; short-wave catalogue, 1½d.; G5NI 70-page Manual, 7½d., post free; authorised direct distributors for Collins, National, R.M.E., Thordarson, Hammerlund, Bliley, Taylor, Eimac, etc., etc.—44, Holloway Head, Birmingham. [0531

## CABINETS

A CABINET for Every Radio Purpose.

CONVERT Your Set into a Radiogram at Minimum Cost; surplus cabinets from noted makers under cost of manufacture (undrilled); 30/- upwards; motors at wholesale prices.

"FIT-A-GRAM" Cabinet, 31×17×15; 21/-.

UNDRILLED Table Console and Loud-speaker Cabinets, from 3/6.

INSPECTION Invited; photos loaned to country customers.

H. L. SMITH and Co., Ltd., 289, Edgware Rd., W.2. Tel.: Pad. 5891. [0485

CLEARANCE Sale!! — Radiogram and television cabinets; prices slashed! 10 gns. worth for 50/-! 5 gns. worth for 20/-!—Write, wire, 'phone or call. Cameo Co., 23, Denmark St., W.C.2. (Tem. 5900.) [8353

## DYNAMOS, MOTORS, ETC.

D.C.—A.C. Convertors, motors, all voltages, for sale and wanted.—Easco, 18w, Brixton Rd., S.W.9. [0558

E.D.C. Alternator, 230 D.C., 230 A.C., 120 watts; £5 or nearest.—Retreat, Brownedge, Buxton. [8398

ALL Types of Rotary Converters, electric motors, battery chargers, petrol electric generator sets, etc., in stock, new and second-hand.

A.C.-D.C. Conversion Units for Operating D.C. Receivers from A.C. Mains, 100 watts output, £2/10; 150 watts output, £3/10.

WARD, 46, Farringdon St., London, E.C.4. Tel.: Holborn 9703. [0518

ELECTRADIX Rotary Converters for A.C. Radios on D.C. mains; alternators 50 to 500 cycles; mains motors and motor generators for 1 to 600 cells; petrol engines and switchgear.—218, Upper Thames St., London, E.C.4. [0619

## RECORDING EQUIPMENT

ALL Recording Discs and Materials in Stock; tracker units, £4/7/6; recording motors, £3/17/6.—Write for further details, Will Day, Ltd., 19, Lisle St., W.C.2. [0595

## APRIL the THIRTEENTH

**BETTER THE DAY**
**BETTER THE DEED**

To follow up our advertisement of April 27th, asking you to let us "TRANSFORM" your reproduction with the 036 Output Transformer, may we draw your attention to the article entitled "Phase Splitting in Push Pull Amplifiers" (*April 13th—"Wireless World."*)

The author states that the overall frequency response of the latest "Wireless World" Quality Amplifier circuit is within plus or minus 0.6 db from 20 to 20,000 cycles including the output transformer.

This was, of course, the

**SOUND SALES TYPE 036**

mentioned in the text,

**THUS SUBSTANTIATING OUR CLAIMS**

May we send YOU our latest catalogue and technical manual of other components, and complete Amplifiers with equally good characteristics? PRICE 6D.

*Specified by the Experts*

**SOUND SALES**

MARLBOROUGH RD., UPPER HOLLOWAY, LONDON, N.19. LIMITED.

*(Contractors to the G.P.O., etc.)*
*Tel.: Archway 1661/2/3*

Hours of Business—
Monday to Friday, 8.30 a.m. to 6 p.m.
SATURDAYS CLOSED

## M·R· SUPPLIES

*for Exclusive Modern Bargains*

**G.E.C. SCHOOL or HOSPITAL RECEIVERS.** Universal A.C./D.C. superheterodyne in fine oak cabinet, 20in. by 12½in. by 8½in. Laboratory-built far above commercial standards. Officially approved for school broadcasting and ideal for all communal or domestic reception in Hospitals, Hotels, Institutes, Clubs and the Home. Multi-matching output for four or five speakers or 400 pairs 'phones. Tunes 200/2,000 metres (station names). Brand new in makers' own transport cases. (Listed £22.) We offer 32 only at £7/10/- each.

**G.E.C. POWER PACKS** (or A.C. Eliminators). 100/250 v. A.C. delivering 250 v. D.C. 55 m.a. Ideal for Preliminary Amplifier, Radio Stage or Receiver, Field Excitation, etc. Sturdily made with impregnated chokes and transformer in steel cabinet 8in. by 8in. by 5½in., with Osram U10 Rectifier. Circuit diagram with each. (Originally listed £6/1/6.) Very remarkable offer, 22/6 each (28 only).

**G.E.C. GRAMOPHONE PICKUPS.** Fine response—very large output. Comparable to any popular armature pickup on market to-day and better than most. Resulting from internal G.E.C. policy we are able to offer the last of these 18/6 pickups, complete with arm, at only 6/6 each.

**G.E.C. PORTABLE PROJECTOR SPEAKERS,** comprising 15-watt P.M. M/coil unit mounted on 50in. air column folded horn, all contained in leatherette-covered cabinet, 18in. by 15in. by 14in., 10 only at £4 each.

**G.E.C. STANDARD RACK PANELS.** Heavy gauge crystallined steel, 19in. long, with brackets. Opening cut for controls. P.A. contractors please note—normally difficult to obtain, 5/9 each.

**G.E.C. 1576 MICROPHONE TRANSFORMERS** for all carbon mikes. Fully shrouded, 4in. by 4in. by 2½in., with plug-type terminals (list 21/-) 6/6 each.

**AMPLIFIER CABINETS,** with motor-board for playing desk. Strongly made in fine walnut finish, corners reinforced. Stay hinges to lift-up lid. Panel opening 12½in. by 4½in. Overall size of cabinet, 17in. by 17in. by 13½in., fitted bronze locking hasps, removable grilled panel at rear and carrying handles. Sketch on request. (Cost 35/-.) 60 only at 15/6 each.

**ROTHERMEL de Luxe TWEETERS.** New 30/- senior model, handling 6 watts. Essential for high-fidelity reproduction, 25 only at 19/6 each.

**ISMAY (Blue Spot) ENERGISED M/COIL SPEAKERS,** 8in., with transformer, fields 1,000, 2,000 to 5,000 ohms (we send nearest to requirements). Well made, fine response, handle 8 watts, 9/6.

**MINIATURE P.M. SPEAKER UNITS** (M/Coil). Only 3in. dia., 15 ohms imp. Perfect M/Coil Mikes, ideal for intercommunication, 9/11.

**EDISWAN "Tungar" BATTERY CHARGERS,** as new. 200/250 v. A.C. Delivery 5 amps. at 30 volts, capacity 60 cells. In steel cabinet with ammeter. (List, £12/12/-.) Last few at £5/10/- each. Leaflet on request.

**PANEL AMMETERS,** 2in. dia. Precision A.C./D.C. Readings 0/1.5, 0/3, 0/5 and 0/10 amp. Ideal for chargers, transformer tests, etc. Any one, 5/6.

**DRAWING INSTRUMENTS.** Precision-made sets, brand new, about one-third list price. Complete set of 12 pieces (including 3 spring bows, half-set and dividers) in velvet-lined case, 9/11. Also super set, 14/6, and student's set (8 pieces), 6/6.

**ELECTRIC CLOCK MOVEMENTS** (Synchronous). Acclaimed by hundreds of customers during the past four years as the finest obtainable. Machine-cut gears, long-life bearings, drive from 2 to 15in. hands. 200/250 v. 50 cycles, 16/6. (These are guaranteed two years and will give lifetime of service.)

**OUTPUT TRANSFORMERS.** Two remarkably fine offers. (A) Made to exact "W.W." spec. All ratios from 11.5/1 to 75/1 with C.T. for P.P., weight 7½ lbs., 26/-. (B) Super high-fidelity model (see "W.W." of 6th April). Response quite flat 20 to 20,000 c/s (really amazing performance). Ratios on each, 18/1, 24/1, 36/1 and 72/1 (with P.P.). No better O/transformer is possible, 37/6.

Send stamp for latest supplementary bargain list.

**M.R. SUPPLIES, 68, New Oxford Street, London, W.C.1.** *(Telephone MUSeum 2958)*

## VALVES

ALL Types of American Tubes in Stock of Impex and Arcturus makes, at competitive prices.

WE Can Also Supply a Full Range of Guaranteed Replacement Valves for Any British, non-ring, American or Continental type at an appreciably lower price.

SEND for Lists of These, and also electrolytic condensers, line cords, resistances, etc.

CHAS. F. WARD, 46, Farringdon St., London, E.C.4. Tel.: Holborn 9703. [0452

SPECIAL 3in. Cathode Ray Tubes, hand, vacuum green screen, 37/6; or with Agnadag coating, £2, guaranteed; every American valve in stock, of course; new valve manuals, 1/6.

RADIOGRAPHIC, Ltd., 66, Osborne St., Glasgow, C.1 [8351

AMERICAN Valves, first grade, by leading makers, guaranteed, popular types; standard base 5/6, octal base 6/6; 6L6G, 7/6.—General Radio Distributors, 309, Falloden Way, N.W.11. [0626

2/9.—R.C.A. American valves, 50 popular types; also National Union, Hytron; also British non-ring valves; cheapest in Britain; ½d. stamp for revised lists.—Shippers, 18, Corporation St., Manchester [0607

METROPOLITAN RADIO SERVICE.—Special offer: American valves, in makers' cartons, 3/- each; Octals, 3/6 each; American valves, first grade in all types; trade supplied.—1021, Finchley Rd., N.W.11. Speedwell 3000. [0436

## TEST EQUIPMENT

C. RAY Oscilloscope, 3in. screen, with linear amplified time base, balanced or unbalanced by panel switching, vertical amplifier, terminals direct to plates if required, complete with 5 valves and Mullard C.R. tube, in metal case with carrier, specification equivalent to conventional £40 outfits, brand new condition; 15 gns.—S. West, Worlingham, near Beccles, Suffolk. [8391

## NEW COMPONENTS

RADIO Components, all makes in stock; complete range of Bulgin and Eddystone short wave parts; American valves specialists; all goods cash with order; post free; established 20 years.—C. Noyes, 163, Shepherd's Bush Market, London, W.12. [8346

## COMPONENTS

### SECOND-HAND, CLEARANCE, SURPLUS, ETC.

PREMIER SUPPLY STORES.

PLEASE See Our Displayed Advertisement on page 7. [0488

LONDON'S CENTRAL RADIO STORES.

SPECIAL Bargain Offers.—Wego 4 mfd. 2,000 vw, 7/6; ex R.A.F. wavemeters with H.F. buzzer, 7/6 each; buzzers only, 2/6; Muirhead 1 mfd. 2,000 v.w., 2/-; B.I. 4 mfd. 450v. A.C. working, 2/-; 0.1 and 0.25 mfd. 1,000 v.w., 1/6; Geni-E-Motor 12 volt in, 285 D.C. output at 60 m.a., 45/-; Decca mike trans., 80:1 ratio, 1/9; Philips mains trans. 280.0.280v. 80 M.A., 4v. 2½a., 4v. 5a., 100 to 250 volts input; 3/6.

CONTACT Cleaner, 2/6 per tin; American valves, Cambridge type 18, output pentode, 2/6; 83v. Rectifier, 3/6; 1 meg. volume controls, 1/6; 50ft. coils 18G tinned copper wire, 1/3 per coil; set of trimming tools, 10 in set, 7/6; Ferranti microphone transformers, 60:1 ratio; 2/6.

T.C.C. 0.5 450 v.v., 3d.; Ferranti 2½in. moving coil meters, 500 micro amps., 25/-; 1 m.a. with rectifier, 35/-; 500 micro amps. with rectifier, 50/-; 250 volts, 1,000 ohms, per volt, 25/-; 5 amps. thermal, 35/-; one only A.C./D.C. circuit tester, 55/; 250 micro amps. with rectifier, 45/-. All above in new condition and guaranteed. Many more bargains for callers only.

LONDON'S CENTRAL RADIO STORES, London's Only Walk Round Radio Store, 23, Lisle Street, Leicester Square, London, W.C. Telephone: Gerrard 2969. [8418

RYALLS RADIO, 280, High Holborn, London, W.C.1, offer new goods, post free.

ELLIPTICAL Speakers, Celestion, suitable Ekco replacements, 750 and 1,250 ohms, less transformers, speech 25 ohms, new, handle 8 watts, carry up to 120 m.a.; 5/6 each.

SPECIAL Offer of New Ferranti Transformers, AF5cs, OPM6c, B5 chokes, 12/6; AF5, OMP6, AF6c, OPM16c, 8/9; AF17c, B2 chokes, 6/9; OPM8 (15-1), AF10, B8 chokes, OPM1c, 4/9; all each.

GARRARD AC Induction Type AC7a Gramophone Motors, with pick-ups complete, 200-250v., 12in. turntable and unit plate, auto. stop, speed regulator, new; 32/6 each.

WEARITE 110 k.c. I.F.'s with Top Trimmers, 1/6 each; sets band pass air core superhet coils, ex Halycon, screened chassis type, 4/9 set five; 110 kc. with coil details.

B.I. Tubular 4mf. 200v., 6d. each or 4/- dozen; B.I. 0.05, 1/3 dozen, 7/9 gross; B.I. 0.25 mf. tubulars, 2/- dozen, 4/6 per three dozen.

SPEAKERS, pairs, brand new, elliptical cone speakers, made by first class firm, quality of reproduction outstanding, push-pull pentode transformer, fields 325 ohm for smoothing choke, 8,600 as bleeder, circuit available, handle 10-15w.; 14/- pair.—Ryalls Radio, see above. [8374

FOR Disposal Below Cost, quantity of new receivers, amplifiers, feeder units, chokes, condenser banks, Ferranti and other transformers, etc.; state requirements; write, 'phone or call.—W. T. Rickards, 17, Heathfield Rd., King's Heath, Birmingham. [8390

*"Radio Laboratory Handbook," Price 8s. 6d. net. Post free 9s.*

## COMPONENTS—SECOND-HAND, CLEARANCE, SURPLUS, ETC.

RADIO CLEARANCE, Ltd.,

63, High Holborn, W.C.1. Holborn 4631.

PRESS Button Assembly, comprising compact unit size 6in.×6in.×2in., complete with six press buttons and manual trimmer for balancing circuits, complete with ten silver mica capacitators; ideal for adapting existing receiver for press button tuning; 9/11 each.

SET of 4 Skeleton Type All-wave Coils (manufacturers type unshielded), comprising oscillator coil, wave trap, broadcaster aerial coil and short wave coil with circuit; 2/6 set of 4.

EARPHONES by Standard Telephones, 2,000 ohms resistance; 5/11 per pair.

AMERICAN Press Button Car Radios, 6- and 12-volt models, manual tuning plus 6 press buttons, medium wave only, 6 gns.; medium and long, £6/15.

CAR Aerials, running board type, 8/6; chromium roof type, 11/6.

***

T.C.C. New Range of Compact Electrolytic Condensers, as follows:—

T.C.C. 8 Mfd. Tubular Electrolytic, wire ends, 500 volt working, 600 volt surge; 1/6 each.

T.C.C. 8 Mfd. Midget, wire ends, size 2½in.×1½in., 500 volt working, 600 volt surge; 1/6 each.

T.C.C. 8 plus 8 4-lead Midget Electrolytics, 500 volt working, 600 volt surge; 2/9 each.

T.C.C. 1 Mfd. Tubular, wire ends; 1/- each.

T.C.C. Bias Condensers:—50 mfd. 12 volt, 1/-; 25 mfd. 25 volt, 1/-; 25 mfd. 50 volt, 1/3; 50 mfd. 25 volt, 1/3; 50 mfd. 50 volt, 1/6.

***

WEARITE Mains Transformers, standard for the season and exclusive to us, made to strict electrical standards, wire end type, all windings centre tapped, screened primaries, tapped inputs, 200-250 volts, screw adjustment.

TYPE R.C.1, 250-0-250, 80 m.a. 4 volts 2.5 amp., 4 volts 4.5 amp.; 9/6 each.

TYPE R.C.2, 350-0-350, 120 m.a. 4 volts 2.5 amp., 4 volts 5 amp.; 11/- each.

TYPE R.C.3, 350-0-350, 150 m.a. 4 volts 2.5 amp., 4 volts 2 amp. 4 volts 5 amp.; 12/6 each.

R.C.4 500-0-500, 150 m.a., 4 volts 2 amp., 4 volts 2 amp., 4 volts 2.5 amp., 4 volts 5-6 amp.; 19/6 each.

TYPES R.C.1. and R.C.2 Drop Through Type, capped.

TYPES R.C.3 and R.C.4 Upright Mounting Type, fully shrouded.

WEARITE Auto Transformers, type R.C.5, fully shrouded, input 100-110 volts, output 200-250 volts, 100 watts; 12/- each.

***

PLESSEY Slow-motion Drives.

TYPE 1841-1125, size of dial 5in. square; 2/- each.

TYPE 1393, size of dial 4×5; 1/10 each.

TYPE 1510, size of dial 4×5; 1/10 each.

TYPE 2077, clock face dial, separate indications, size of dial 5×5 (R. and minute-hand type), geared; 4/6 each.

TYPE 2806, size of dial 3×3, overall height 8in.; 1/3 each.

TYPE 1825, size of dial 5½×1¾; 1/3 each.

ALL Above With Plain Unprinted Scales Only.

***

CRYSTAL Pick-up, high grade American, bronze finish complete with arm; £1/5 each.

STANDARD Octal Base Valve Holders; 4d. each.

AMERICAN Valve Holders, best quality, 4-, 5-, 6-, and 7-pin; 3d. each.

CLIX 5-pin Chassis, 3d. each; Clix 7-pin chassis, 4d. each; Bulgin S.P.S.T. twist switch, 9d. each; Bulgin D.P.D.T. twist switch, 1/- each.

T.C.C. Paper Tubular Condensers, all sizes up to 0.1, 5d. each, 4/6 doz.; 0.25 ditto, 7d. each; 0.5, 10d. each.

POLAR N.S.F. 1 Watt Resistances; 3½d. each, 3/- doz.; all sizes up to 2 meg.

MAINS Smoothing Chokes, Wearite unshrouded, fitted wire ends:—30 henry 80 m.a., 500 ohms, 7/6 each; 40 henry 150 m.a., 500 ohms, 10/6 each.

AMERICAN Valves.—Complete range of Raytheon 1st Grade stocked; competitive prices consistent with quality; write for lists.

***

LISSEN Valves, brand new, boxed, as follows:—H2, L2, 2/- each; BB.220A, 3/11 each; SGV, SG 215, 3/11 each.

RADIO CLEARANCE Bargains Continued in Third Column.


# 'Skyrod' gives

## GOOD RECEPTION with set inside a refrigerator

Here's how an ordinary Belling-Lee 'SKYROD' Aerial installation was tested under extremely bad conditions by a radio dealer—with astonishing results. Read in the letter below how this terrible interference was conquered and reception improved—then go along to your own dealer's and hear for the first time the performance of which a modern receiver is capable.

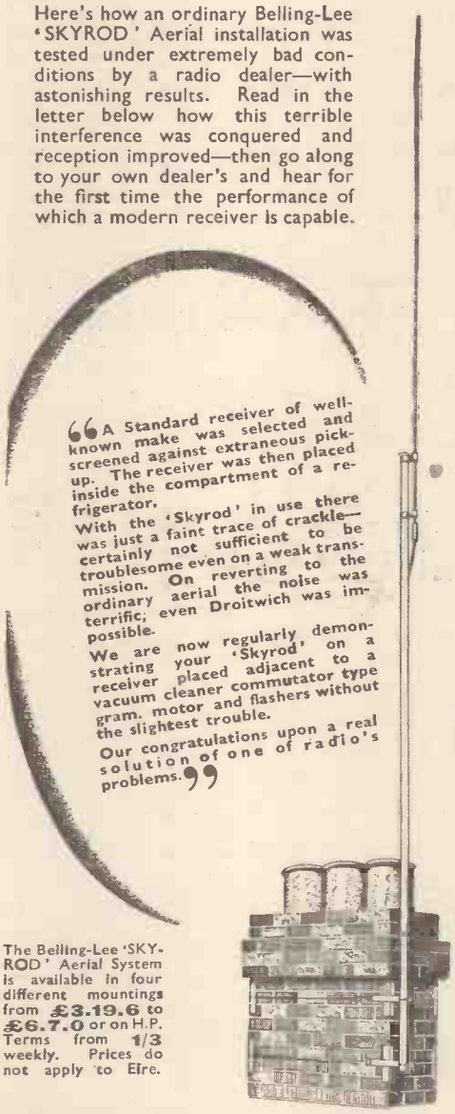


The Belling-Lee 'SKYROD' Aerial System is available in four different mountings from **£3.19.6** to **£6.7.0** or on H.P. Terms from **1/3** weekly. Prices do not apply to Eire.

The BELLING-LEE 'SKYROD' AERIAL SYSTEM

BELLING & LEE LTD.,
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX

7345


## COMPONENTS—SECOND-HAND, CLEARANCE, SURPLUS, ETC.

RADIO CLEARANCE, Ltd., continuing bargains in components, etc.

***

CENTRALAB Volume Controls Available as Follows, with switch, long spindle:—1,000, 5,000, 10,000, 25,000, 50,000, 100,000, 250,000, 2/- each.

G.E.C. Relays, make and break type, 3,300 ohms; 4/- each

100 Watt Auto Transformers, 100-250 volts reversible, wire end type; 5/11 each.

***

STANDARD Telephone Mains Transformer, Type 1, input 200-250 volt, output 250v. 40 m.a., 4 volt 2.5 amp.; 2/6 each.

TYPE 2, input 200-250 volt, output 250 volt 200 m.a., 4 volt 2.5 amp.; 3/- each.

TYPE 3, input 200-250 volt, output 200 volt 500 m.a., 4 volt 4 amp.; 5/6 each.

HELLSEN 8 mfd. Cardboard Electrolytics, 450 volt working, wire end; 1/- each.

CONDENSER Block, four, 0.05 mfd., metal cased, 500 volt working; 1/9 each.

TYPE 4 Smoothing Choke, 500 m.a. 100 ohms 12 henrys; 8/6 each.

CONDENSER Block, two, 6 mfd., 2.1 mfd., metal cased, 500v. wkg.; 2/3 each.

METAL Safety Case with Base and 2 Valve Holders, size 7½×6in.×5¼in.; 2/6 each; finished brown crackle.

METAL Safety Case with Base and 2 Valve Holders, size 12½in.×8¾in.×5¾in.; 3/6 each; finished brown crackle.

32 M.f.d. 400 volt working, can type wet electrolytic; 1/6 each.

16 M.f.d., 450 volt working; 1/- each.

ALL Orders to the Value of 5/- Post Free; postage must be enclosed with orders for less than 5/-; enquiries 1½d. stamp if reply expected. Hours of business: Week-days, 9 a.m. to 7 p.m.; Saturdays, 9 a.m. to 1 p.m. Postal rates apply to the United Kingdom only, orders for Ireland and abroad must include sufficient postage to cover whatever the value of same.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1. Telephone: Holborn 4631. [8413

VAUXHALL UTILITIES, 163a, Strand, W.C.2.—Ask for free list; metal rectifiers, HT10, 10/-; HT9, 9/-.

VAUXHALL.—Hivac valves, all types; full range of pick-ups, from 11/-.

VAUXHALL.—T.C.C. dry, 8mfd., 2/6; 600v. aluminium containers; T.C.C. 600 v. dry, cardboard containers, 8mfd., 1/9. [8386

COLLARO A.C./D.C. Record-changers, 200-250, plays eight 10in. or 12in. records, mixed, also incorporates repeater and rejector; limited quantity, £5/5, in sealed cartons.

GARRARD. A.C. Motors, Model A.C.6, enclosed type with automatic stop, 110-250 volts, 30/-, carr. pd.; sealed cartons.

MARCONI K25 Pick-up, unused and boxed; 14/-.

HENRY'S, 72, Wellington Ave., Stamford Hill, N.15. Stamford Hill 2907. [8216

SOUTHERN RADIOS Bargains.—Sale now proceeding of hundreds of bargain lines, goods previously advertised still available.—Southern Radio, 46, Lisle St., London, W.C.1. Gerrard 6653. [8236

MAINS RADIO DEVELOPMENT Co. Can Now Offer Immediate Delivery of Transatlantic All-wave Tuning Packs. Stamp for details. Carriage paid by return, immediate delivery, telephone Tudor 4046, call mornings. Stamp for list 226.

AMAZING Opportunity.—Fifty N.S.F. marked and coloured coded resistors. ½, 1 and 2 watt, wire ends. 20 good sizes in every parcel of 50 resistors; 2/6 per 50 only.

TUBULAR Condensers.—400 volt working, wire ends, best make. 0.0001-0.05 mfd., 4d.; 0.1 mfd., 4d.; 0.25, 0.5 mfd., 6d.

CLIX Unused Chassis Valve-holders, 5-pin, 7-pin, 3d. each. All American sizes, 6d. each. Best sleeving, 1½d. yard.

CENTRALAB Latest Potentiometers, long spindle, unused. All sizes, 5,000 ohms. to 2 megohm, 2/-; with mains switch, 2/3.

FIRST-GRADE Boxed American Tubes, guaranteed, 4/- each; octals, 4/6; T.C.C. dry metal 8 mfd., 600 volt, 2/3.

POLAR MIDGET Latest Three-gang Condensers, screened, trimmers, ¼in. spindle, 0.0005 mfd., 100 k/c tracker (perfect straight two-gang), 2/6.

DUBILIER Mica Tag Condensers, 0.00005, 0.0001, 0.0002, 0.0003, 0.0005 mfd., 3d.; 2/6 dozen.

ERIE One Watt, colour coded, unused resistors, any size, 50 ohms to 5 megohm, your selection, 3d.; 2/6 dozen. Two watt, 6d.

MAINS RADIO DEVELOPMENT Co., 4-6 Muswell Hill Road, London, N.6. Tudor 4046. [8394

### Wanted

WE Buy for Cash All Types of Modern Second-hand Radio Sets and Accessories, test meters, parts, etc. We pay more than any other dealer. Part exchanges. Bring, send or will call.—University Radio, Ltd., 238, Euston Rd., London, N.W.1. 'Phone: Euston 3810. [8366

*"Wireless Direction Finding," Third Edition. Price 25s. net. Post free 25s. 9d.*

# ELECTRADIX

**3/9 MILLIAMMETERS.**—New. Where the job calls for something simple without calibration for tuning or galvo for testing. Back of panel type, as illus., 8 m.a. full scale. Great Bargain at 3/9 post free.
**MILLIAMMETERS.**—Moving coil. 5, 10, 25, 50, 500 m.a., in various sizes, from 2½in. to 8in. dia. Switchboard Meters, 3 to 8in. dial, all ranges.
**PANEL MOV. COIL MICRO-AMMETERS.**—Distortion in receivers may be caused by a few micro-amps. of grid current detected by Lesdix sensitive moving coil micro-ammeters reading ½ m. m.a. to 50. 1,000 ohm coils, bakelite case, flush panel, 2½in. dial, 40/-. Relay small Mov. Coil working on 50 micro-amps., 60/-.

**SILVERTOWN** Portable Tester. Combines Wheatstone Bridge, Galvo shunts and ratios, as new, £8. G.P.O. Plug-in Bridge Resistance Boxes, to 8,000 ohms, 60/-.
**SULLIVAN MARINE REFLECTING GALVANOMETERS,** as used by the Cable Co's. Cheap.
**DIX-MIPANTA VEST POCKET TESTER.** — A wonderfully versatile moving-iron multi-range meter for service on A.C. or D.C. jobs. No projecting terminals. THREE ranges of volts: 0-7.5, 0-150, 0-300. Used for MILLIAMPS. reads: 12½ m.a. and 75 m.a. In black bakelite case. Measures only 2½in. by 2¼in., with pair of test leads and plugs. Leaflet "N" gives full information. 19/6.

**VIBRATOR BATTERY SUPERSEDER,** with metal rectifier, for H.T. from your 2-volt battery. 3 output volt tappings. A boon to those who are not on the mains. Reduced from £3 15s. to sale price 37/6.
**HEADPHONES.** Light weight. 2,000 ohms, 4/6. Single high res. carpieces, 2/6. Sullivan 120 ohm W.D. model. Aluminium body and headbands. Maker's price to-day, 15/-. Our price, 2/9 per pair. Pocket double headphones, W.D. type for portable sets, 2/6 pair.

**RELIABLE DISC RECORDING.** Electric Feigh set for use on your radiogram. Quick detachable ball-bearing gear box, tracker and traverse rod with tone arm, pick up and diamond cutter, worth £3 10s. Quite new. Sale, 37/6. Blank discs, 3/3 doz.
**METERS** of all ranges and sizes in stock from millivolts to 12,000 volts or micro-amps. to 1,000 amps.
**MORSE INKER** Tape Strip Recorders; portable or table. Cheap. Wheatstone Strip Hand Perforators, 15/-. Paper Tape for Morse and Wheatstones, green or white, 6d. reel. Brass Tape Reels in mahogany case, 2/6.
**TELEPRINTER TELEGRAPH.**—G.P.O. Model for Typewriter transmission. Electrically operated, in new condition, beautiful work. Cost £50. Sale, £4. Few complete Wheatstone Code Transmitters.

**PARCELS** of useful oddments for the Experimenter who wants a junk-box of Coils, Magnets, Wire, Chokes, Condenser, Switches, etc., mostly ex-W.D. parts worth a lot more than 10 lbs. 7/-, or 7 lbs. for 5/-. post free. British Isles only.

BARGAIN SALE LIST "W" FREE ON REQUEST.
*MOTORS. Our well-known low-priced Dynamos, Motors and Motor-driven appliances for D.C. and A.C. 50 cycle supply are a special line. Fractional horse-power Motors for driving small lathes, blowers, drills, polishers, cine projectors, etc.*

**ELECTRADIX RADIOS**
218, Upper Thames Street, London, E.C.4
*'Phone: Central 4611*

*FOR INEXPENSIVE ACCURACY....*

# TAYLORMETER

**70 RANGES**
**BRITISH MADE**
SIZE 10"x7"x5"

MODEL 80A.
2,000 Ohms per volt A.C. and D.C.
**10 GNS.**
LOW DEPOSIT EASY TERMS AVAILABLE

This precision built Universal Meter with its sturdy 4½" Moving Coil movement covers D.C. volts 0.002—2,000; A.C. Output/volts 0.2—2,000. D.C. Current 10μA—20 Amps; A.C. Current 10μA—5 Amps. Resistance 0.1 Ohms—5 megohms. Output —18 to +60 DB. at the touch of two switches. Although unusually low in price the TAYLORMETER is extremely reliable, sensitive and accurate.

FILL IN AND POST THIS COUPON NOW.

To TAYLOR ELECTRICAL INSTRUMENTS LTD.
45, Foubert's Place, Regent St., London, W.1
Please send me full details of the TAYLORMETER.
Name.....
Address.....
W.W.10


## REPAIRS AND SERVICE

"SERVICE with a Smile."

AMERICAN Valves, spares, linecords, rewinds; repairers of all types of American and British receivers.—F.R.I., Ltd., 22, Howland St., W.1. Museum 5675. [0434

LOUD-SPEAKER Repairs. British, American, any make, 24-hours service; moderate prices.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0590

GUARANTEED Repairs Any Transformers, choke, motor armature, converter, dynamo, etc.; keenest prices, immediate quotation, prompt dependable service.—See below.

L.T.P. (LONDON TRANSFORMER PRODUCTS, Ltd.), Willesden, N.W.10. Willesden 6486 (3 lines). [6892

BAKERS.—Take advantage of 15 years' experience; send your next speaker repair, any make, to Bakers Selhurst Radio, South Croydon. [8372

MAINS Transformer Service. Repairs, rewinds, or construction to specification of any type, competitive prices and prompt service.—Sturdy Electric Co., Dipton, Newcastle-on-Tyne. [0516

METROPOLITAN RADIO SERVICE.—Guaranteed repairs to American and British receivers; American valves, service parts and rewinds; trade supplied.—1021, Finchley Rd., N.W.1. Speedwell 3000. [0435

SCOTT-SESSIONS REPAIR SERVICE.—All types of receivers overhauled, rebuilt, repaired, including American communication sets, W.W. Monodials, All-wave Super-Seven. Variable Selectivity IV., etc.

SCOTT-SESSIONS REPAIR SERVICE, popular for 15 years from Land's End to John-o-Groats; van collection London area; immediate, courteous and skilled attention to every instruction.

SCOTT-SESSIONS REPAIR SERVICE. Exchange Works, Muswell Hill, N.10. Tudor 4101-2. [7497

REPAIRS to Moving Coil Speakers a Speciality; cones and coils fitted, fields altered; prices, including eliminators, quoted; loud speakers, 4/-; L.F. and output transformers, 4/-, post free; guaranteed satisfaction; trade invited, estimates free; prompt service.—Loud-Speaker Repair Works, 5, Balham Grove, London. Battersea 1321. [0394

## SITUATIONS VACANT

AIR MINISTRY.

DIRECTORATE of Scientific Research.

APPLICATIONS are Invited for an Appointment as Designer at Bawdsey Research Station, Bawdsey Manor, Woodbridge, Suffolk.

CANDIDATES Should Have Had a Good Training in Electrical Engineering, with several years' drawing office experience in the design of radio equipment, and must be capable of preparing working drawings for production purposes from rough sketches or laboratory models; adaptability to follow rapid experimental development of a wide variety of novel radioelectric, mechanical and mathematical appliances is essential.

SCALE of Salary £350-£18-£500 per annum.

THE Appointment will be Non-pensionable in the First Instance.

APPLICATION Should be Made on a Form to be obtained by letter, quoting reference C.93, enclosing stamped addressed envelope, from the Superintendent, Bawdsey Research Station, Bawdsey Manor, Woodbridge, Suffolk, to whom it should be returned not later than the 12th May, 1939. [8408

CROWN Agents for the Colonies.

COLONIAL Government Appointments.

APPLICATIONS from Qualified Candidates are Invited for the following post:—

WIRELESS Technician Required for the Post Office (Engineering Department), Hong Kong, for three years, with possible permanency. Salary £310, rising to £470 a year. Free passages and quarters and leave on full pay. Candidates, aged 23-26, must possess the Postmaster General's first class certificate in Radiotelegraphy; have had three years' seagoing experience, and some experience in workshop and servicing practice.

APPLY at Once by Letter, stating age, whether married or single, and full particulars of qualifications and experience, and mentioning this paper, to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M/8408. [8411

SERVICE Engineer, over 22, drive car; state wages required, experience, to: Box 9606, c/o *The Wireless World*. [8400

RADIO Engineers Required for the Development of Mass-produced Broadcast Receivers; previous experience in a similar capacity essential.—Write in confidence full particulars of experience, age and salary required, to the Personnel Manager, Kolster-Brandes, Ltd., Footscray, Sidcup. [8405

VACANCY Exists for a Television Engineer experienced in the design and production of modern television receivers. Good prospects for the right man.—Apply in confidence, stating age, experience and salary required, to the Chief Engineer, Beethoven Electric Equipment, Ltd., Chase Rd., London, N.W.10. [8407

DRAUGHTSMAN Required by Large Electrical Engineering Firm in the Midlands, preferably with experience in design of short wave radio transmission equipment, or similar electrical apparatus.—Reply, with full particulars of age, education, experience and salary required, Box 9394, c/o *The Wireless World*. [8344


# RADIOMART

G5NI (BIRMINGHAM) LTD.

**THE SHORT-WAVE SPECIALISTS**

**SPECIAL OFFER !!!**
Fully shrouded Transformers by America's largest manufacturer. While they last.
All 230 v. primary and fully impregnated.

| | |
|---|---|
| T28708—375/375 v. 150 m/A., 6.3V5A. 2.5V5A. 5V3A. | 15/- |
| T19610—350/350 v. 150 m/A., 2.5V6A. 2.5V2A. 5V3A. | 12/6 |
| T7236—375/375 v. 120 m/A., 6.3VCT. 4A. 5V3A | 10/6 |
| T7326—350/350 v. 100 m/A., 6.3VCT. 3A. 5V3A | 8/6 |
| T7307—350/350 v. 80 m/A., 6.3VCT. 3A. 5V3A | 7/6 |
| T7000—320/320 v. 80 m/A., 6.3V4A. 5V3A | 7/6 |
| T6025—320/320 v. 80 m/A., 2.5V6A. 5V3A | 7/6 |
| T464919—10V4A Primary Tapped 110—250 v. | 5/6 |
| T1113AB—110/230 v. 500 watt Auto Transformer | 29/6 |

The following chokes are interleaved and impregnated.

| | |
|---|---|
| T7007—250 m/A., 135 ohms. 20-8 Hy., cadmium shrouded | 12/6 |
| T7007A—150 m/A., 250 ohms, 30-12 Hy., cadmium shrouded | 12/6 |
| 100 m/A., 20 Hy., 500 ohms, unshrouded | 4/11 |
| 60 m/A., 15 Hy., 250 ohms | 1/11 |

**HEAVY DUTY TRANSFORMER** for models, bells, etc., 6 v. 3 a., 2/3. 4 mf., 1,500 v. test 500 v. wkg. oil filled condensers, 2/-.
**HEAVY DUTY** Mains Transformer, worth 45/-. 350-350, 150 m/A., 4 v. 2.5 a. CT, 4 v. 6 a., CT, 12/6; 300-300 v., 80 m/A., 4 v. 3 a., CT, 4 v. 2 a., CT, 6/6. Moving Coil Speech Transformers, 1/11.
**GANG CONDENSERS** with Airplane Dial, 8 and 80-1. Cost 35/-. Few only, 4/11. Utility, 7/6. Microdials, 3/9.
**W.B. 8in. PERMANENT MAGNET SPEAKERS AT ONE-THIRD COST** Extension Type (no Transformer), 8/11. Standard Type (with Transformer), 10/6. Energised 8", 1,200 ohms with Transformer, 6/11.
**PUSHBACK** Wire, 6 yds., 6d., heavy, 9d. Resin-cored Solder, 6ft., 6d.; Screened Flex, single, 6d. yd.; twin, 9d. yd. Assorted Solder Tags, 6d. packet. Humdimmers, 6d. each.
Centralab pots, all sizes, 1/6; switched, 2/-; tubular glass fuses, 2d. Milliammeters, 0-25 m.a., upwards, 5/9; Super, 6/9.
**OUR NEW 66-PAGE MANUAL,** packed full of valuable information. Post Free, 7½d.
**THE NEW RAYMART CATALOGUE** shows dozens of New Short-wave Components and is yours for 1½d. post free.
**VALVES.**—A complete range of replacements, showing a saving of over 50 per cent. Quotations on receipt of types required. Quantity Discounts to Service Engineers. TRADE enquiries for communication equipment solicited.

**RADIOMART** *Telephone: MIDland 3251.*
G5NI (Birmingham) Ltd.
44, HOLLOWAY HEAD, BIRMINGHAM



**DIRECT SOUND RECORDING**

**PYRAL**
AND
**NEOCIRE**
ACETATE DISCS
can now be obtained from the suppliers of the well-known
'Simplat' Blanks, Apparatus and Accessories
PYRAL DISCS from 8d. upwards
**V. G. MANUFACTURING CO. LTD.**
GORST ROAD, LONDON, N.W.10
*'Phone: WILLESDEN 1632/3*



# WELBURN 12 WATT AMPLIFIER

Built of heavy, 16 S.W.G., steel and finished Grey and Chromium, this high-gain sound amplifier is completely self-contained.

Only 0.008 v. is necessary to develop full output while 15% Negative Feed-Back and a symmetrical output transformer are used. The output power is conservatively rated at 12 watts, and a level response is combined with linear amplification.

*Full details on request.*

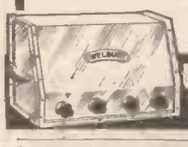

RETAIL PRICE **£14**

**WELBURN RADIO LTD.**
QUEENSWAY, TEAM VALLEY
GATESHEAD-ON-TYNE



**NO A.R.P. SHELTER is COMPLETE WITHOUT a**

# UNIVERSAL 3 VALVE BATTERY SET

with British Ring Valves Detector. L.F. and Power, and W.B. Permanent Magnet Moving Coil Speaker. In Walnut Cabinet, as illus. A real station getter and fully guaranteed.

**22/6** *CARRIAGE PAID.*

.0005 2 Gang Condensers..... 2/- each
.0005 3 Gang Condensers..... 3/6 each
Magnum Multi Contact Switches..... 1/3 each
American Valve Screens ..... 4d. each
*POST FREE.*

**UNIVERSAL, 8 & 10, Brown Street, MANCHESTER, 2**
*'Phone: Deansgate 5009.*

SPADE TERMINALS For Every Purpose

The range of CLIX terminals include Spade, Panel, Pin, "All-in," Heavy Wiring Keyhole and Hook types, every one of which can be depended upon for perfect contact.

Small No. 414 ..... 1½d.
Large No. 415 ..... 2d.
Heavy Wiring No. 416 3d.
Keyhole No. 418 ..... 2d.
Hook No. 419..... 2d.
*Usual colours and engravings*

**SPADE TERMINALS** are fitted with collars to prevent acid creep and a special slide to give positive metal-to-metal contact. The Heavy Wiring type has a large insulator to take wires up to 3/16" without stripping or joints.

*Send for Clix Radio and Electrical Catalogue - Post free.*

CLIX

*British Mechanical Productions Ltd, 79a, Rochester Row, London, S.W.1.*

THE INSTITUTE OF WIRELESS TECHNOLOGY
(Founded in 1925. Incorporated).
**PROFESSIONAL MEMBERSHIP**
**The advantages of professional membership are open to all qualified wireless engineers.**
*Full information, with syllabus, may be obtained from the Secretary, Institute of Wireless Technology, 4, Vernon Place, Southampton Row, London, W.C.1. 'Phone: Holborn 4879.*

# BRIGHTER PHOTOGRAPHY

By DAVID CHARLES, F.R.P.S.

The carefully arranged chapters cover the whole field from the choosing of a camera to developing and printing the finished picture. Details of the various photographic materials on the market are given, and there are important sections dealing with Focusing, Aiming the Camera, Photographic Groups, Lighting and Exposing.

In addition there are over one hundred and sixty illustrations, each numbered and each conveying a really useful hint.

Price 2/6 net. By post 2/9

ILIFFE & SONS, LTD.
Dorset House, Stamford Street, London, S.E.1

W.W.40

Cage Birds and Aquaria World
The weekly journal for all who keep Canaries, British Hybrids or Foreign Pet Birds.
EVERY FRIDAY 2d. W.W.98
Specimen copy of recent issue free on request from The Publisher (W.W.), Dorset House, Stamford St., London, S.E.1


## SITUATIONS VACANT

SKILLED Laboratory Assistant Required for work on the development of radio receivers; thorough practical and theoretical knowledge essential. Junior assistant also required for simple routine measurements.—Reply by letter, giving full details of qualification and experience, to Employment Dept., Murphy Radio, Ltd., Welwyn Garden City. [8406

## SITUATIONS WANTED

YOUNG Engineer (radio technician), 23, spent one year at University laboratory, excellent theoretician, speaks good English, seeks situation.—Reply Stephen Singer, Budapest, 62, P.O.B.166. [8416

## MISCELLANEOUS

CHEAP Printing.—1,000 billheads, 3/6; sample free.—Creteway Press, 18, Buxted, Sussex. [8180

PHOTO-ELECTRIC Cells, brand new; 15/- each.—Universal, 221, City Rd., London, E.C.1. [8370

G.P.O. Engineering Dept (no experience required); commencing £3/13 per week; age 18-23; excellent prospects; free details of Entrance Exam. from B.I.E.T. (Dept. 574), 17-19, Stratford Place, London, W.1. [8396

EVERY Radio Dealer Who is Not a Regular Reader of "The Wireless and Electrical Trader" should send his trade card at once for a specimen copy and full details of the "Trader" Services. "The Wireless and Electrical Trader" has the widest influence, the largest weekly circulation, and is read by all the leading manufacturers and traders Trade only, 15/- per annum, post free.—Published at Dorset House, Stamford St., London, S.E.1. [0615

"ENGINEER'S Guide to Success" Shows How to Qualify in Television Radio Engineering and Servicing, sound recording, wireless communication, etc., by studying at home with the T.I.G.B. Write to-day for this Great Guide—free—which gives full particulars, contains the world's widest choice of engineering courses—over 200—and alone gives the regulations for qualifications such as A.M.I.E.E., A.M.I.R.E., A.M.I.T.E., A.M.I.W.T., C. and G., etc. Training until successful guaranteed.—The Technological Institute of Great Britain, 82, Temple Bar House, London, E.C.4. (Founded 1917. 20,000 successes.) [8409

## FINANCIAL PARTNERSHIPS

PARTNER Wanted for Radio Service Business in London; good organising ability essential; capital £250, or would consider sale; write for appointment to: Box 9615, c/o *The Wireless World*. [8417

## PATENTS

"PRACTICAL Hints on Patents," free on application.—The Imperial Patent Service, First Avenue House, High Holborn, W.C.1. Preliminary consultation free. [0481

## TUITION

RADIO Training.—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0611

MORSE Code Easily Learnt by Gramophone Records; all speeds; also correspondence courses; particulars, stamp.—Masters, Orchard House, Wokingham. [8397

WIRELESS.—Complete training. Marine, Broadcast and Television. Posts waiting. Mod. fees. Boarders taken. Approved college, prosp.—Dept. W., London Radio College, Grove Park Rd., London, W.4. (Chi. 3244.) [0580

WIRELESS Careers; increased salaries and pensions make radio a profitable and interesting profession; we train students for all branches and guarantee appointments; Britain's leading Colleges; boarders accepted; write for free prospectus.—Wireless College, Colwyn Bay, or Wireless College, Calmore, Southampton. [8373

## BUSINESSES AND PROPERTY FOR SALE, TO BE LET, OR WANTED

TO Let.—Shop, parlour and room, 24 King's College Rd., Hampstead, N.W.3. No opposition. Particulars.—Apply Boden, Swiss Cottage. [8399

NEED for Radio and Cycle Dealer on Large New Estate. Main road position. Success assured. No premium.—Apply Fairway Homes, Mutton Lane, Potters Bar. Tel.: 931. [8371

"THE Wireless and Electrical Trader" is an essential part of the equipment of every Wireless Trader; its pages reflect the very latest turn of trade events, and it is read by all the leading dealers and manufacturers, for particulars of businesses offered or wanted. By subscription to the trade only, 15/- per annum, post free.—Send your trade card for specimen copy to Dorset House, Stamford St., London, S.E.1. [0614

## BOOKS, INSTRUCTION, ETC.

AMERICAN Valve Data.—The new 200-page Raytheon Valve Data Book gives full characteristics and applications of all types of American valves; invaluable to all servicemen; post free 2/3; abroad 3/-.—Leonard Heys, 36, Henry St., Blackpool. [0594

"THE Wireless World" Diary for 1939 contains 77 pages of facts, formulæ and general information of the kind that is always wanted but is difficult to follow. Also a list of the most important European Broadcasting Stations and short-wave stations of the world. Twelve pages of circuit diagrams of receivers, amplifiers and units.—By post 1/7 from Iliffe & Sons, Ltd., Dorset House, Stamford St., London, S.E.1.

"FOUNDATIONS of Wireless." By A. L. M. Sowerby, M.Sc. Second edition. An elementary textbook on receivers. Deals fully with the construction of wireless sets, valves, and the process of detection. Price 4/6 net. By post 4/11, from Iliffe and Sons, Ltd., Dorset House, Stamford Street, London, S.E.1.


# PREMIER ★ RADIO ★

**Premier Short-Wave Kits.**

Complete to the last detail including all Valves and coils, as well as theoretical and wiring diagrams and lucid instructions for building and working. Each kit is supplied with a steel Chassis and Panel and uses plug-in coils to tune from 13 to 170 metres.
1 Valve Short-Wave Receiver or Adapter Kit ... 17/6
1 Valve Short-Wave Superhet Converter Kit ... 20/-
1 Valve Short-Wave A.C. Superhet Converter Kit 22/6
2 Valve Short-Wave Receiver Kit ... ... ... 25/-
3 Valve Short-Wave Screen Grid and Pentode Kit 58/6
**PREMIER U.S.A. QUARTZ TRANSMITTING CRYSTALS.** 7 mc Band, 10/- each, with Calibration Certificate. Enclosed holder and Base, 3/-.
**PREMIER SHORT-WAVE COILS,** 4- and 6-pin types, 13-26, 22-47, 41-84, 78-170 metres, 1/9 each, with circuit. Special set of S.W. Coils, 14-150 metres, 4/- set, with circuit. Premier 3-band S.W. coil, 11-25, 19-43, 38-80 metres. Suitable any type circuit, 2/6.
**ULTRA S.W. COILS,** 4-10 metres Wound silver plated Wire. Mounted on Trolitul base. Inside diam. coils ¾", 3, 4, 5, 6 or 7 turns, complete with base, 1/- each.
**UTILITY** Micro Cursor Dials, Direct and 100.1 Ratios, 3/9.
**PREMIER** Short-Wave Condensers, all-brass construction, with **Trolitul** insulation. 15 mmf., 1/6; 25 mmf., 1/7; 40 mmf., 1/9; 100 mmf., 2/-; 160 mmf., 2/3; 250 mmf., 2/6.
**TROLITUL DOUBLE SPACED TRANSMITTING CONDENSERS.** 15 mmf., 2/9; 40 mmf., 3/6; 100 mmf., 4/-; 160 mmf., 4/6.
**NEW TROLITUL SPLIT STATOR CONDENSERS,** 50×50 mmf., 10/6.
**COIL FORMERS,** 4- or 6-pin low-loss, 1/- each.
**AMERICAN VALVES.** We hold the largest stocks of U.S.A. tubes in this country and are sole British Distributors for **TRIAD** High-grade American Valves. All types in stock. Standard types, 5/6 each. All the new Octal Base tubes at 6/6 each, 210 and 250, 8/6 each.
**EUROPA MAINS VALVES,** 4 v. A.C. Types, A.C./HL., A.C./L., A.C./S.G., A.C./V.M.S.G., A.C./H.P., A.C./V.H.P., A.C./P., and 1 watt D.H. Pentodes, all 4/6 each. A.C./Pens., I.H., 5/6; A.C./P.X.4, 6/6; Oct. Freq. Changers, 8/6; Double Diode Triodes, 7/6; Triode H. ex. Freq. Ch., 8/6; Tri. Grid Pen., 10/6; 3½-watt D.H. Triode, 7/6. 350 v. and 500 v. F.W. Rect., 5/6. 13 v. 2 amps. Gen. Purpose Triodes, 5/6; H.F. Pens. and Var.-Mu. H.F. Pens., Double Diode Triodes, Oct. Freq. Changers, 7/6 each. Full-wave and Half-wave Rectifiers, 5/9 each.

**MATCHMAKER UNIVERSAL MODULATION TRANSFORMERS**
Will match any modulator to any R.F. load. 50 watts, 17/6; 150 watts, 29/6; 300 watts, 49/6.
**MATCHMAKER UNIVERSAL OUTPUT TRANSFORMERS.** Will match any output valves to any speaker impedance. 11 ratios from 13 : 1 to 80 : 1. 5-7 watts, 13/6; 10-15 watts, 17/6; 20-30 watts, 29/6. Send for full details.

**PREMIER MOVING COIL METERS**
**Guaranteed Accuracy within ± 2 per cent.**

| Model 21. 3in. sq. case. | | Model 311. 3½in. round case | |
|---|---|---|---|
| 0–1 m/A. ... ... | 13/6 | 0–1 m/A. ... ... | 22/6 |
| 0–10 m/A. ... ... | 17/6 | 0–10 m/A. ... ... | 20/- |
| 5–50 m/A. ... ... | 17/6 | 0–50 m/A. ... ... | 20/- |
| 0–100 m/A. ... ... | 17/6 | 0–100 m/A. ... ... | 20/- |
| 0–250 m/A. ... ... | 17/6 | 0–250 m/A. ... ... | 20/- |

**Model 311.** 0–1 m/A. movement, with calibrated scale, volts-ohms-m/A., 25/-.
**VOLTAGE MULTIPLIER RESISTANCES,** guaranteed accuracy ± 2 per cent. All standard ranges, 1/3 each.
**TAPPED SHUNT** to provide readings of 5 m/A., 25 m/A., 250 m/A., and 1,000 m/A., 5/6.
**PREMIER AC/DC MOVING IRON METERS.** 2½ in. diam. Flush Mounting. All ranges. 10 ma., 30 ma., 50 m.a., 100 ma., 250 m.a., 500 ma., 5/9 each.
**AMMETERS.** 1, 3, 5, 10 or 30 amps., 5/9 each.

**PREMIER 1939 HIGH FIDELITY AMPLIFIERS**
**A New Complete Range of 7 High Fidelity P.A. Amplifiers for A.C. or A.C./D.C. Mains operation.**

| | Kit of Parts with Valves. | Completely Wired and Tested. |
|---|---|---|
| 3-watt A.C. Amplifier ... | £2 0 0 | £2 15 0 |
| 3-watt A.C./D.C. „ ... | £2 0 0 | £2 15 0 |
| 6-watt A.C. „ ... | £5 5 0 | £6 0 0 |
| 8–10-watt A.C./D.C. „ ... | £4 10 0 | £5 5 0 |
| 15-watt A.C. „ ... | £5 15 0 | £7 0 0 |

Black Crackle Steel Cabinet 15/- extra.

**PREMIER MIKES.**
**REISZ PATTERN.** Transverse Current, High Grade, large Output Unit. Fine Frequency Response 45-7,500 cycles 20/- each.
**MOVING COIL MIKES.** High class P.M. Unit. Frequency Response 90-5,200 cycles, 42/- each.
**MIKE TRANSFORMERS,** 5/- each.
**MIKE STANDS.** Table, 7/6 each, Folding Portable, 15/-. Adjustable Floor, 22/6.

*Send for full details.*

Orders 5/- and over sent Post Free. Under 5/- please add 6d. Postage.

**Have you had our 1939 Catalogue, Handbook and Valve Manual? 90 pages of Radio Bargains and Interesting Data. Price 6d.**

**ALL POST ORDERS TO: Jubilee Works, 167, Lower Clapton Road, London, E.5.** *Amherst 4723*
**CALLERS TO: Jubilee Works, or our NEW PREMISES, 169, FLEET STREET, E.C.4.** *Central 2833*
**or 50, High Street, Clapham, S.W.4.** *Macaulay 2381.*


*"Handbook of Technical Instruction for Wireless Telegraphists." Price 21s. net. Post free 21s. 9d.*

## INDEX TO ADVERTISEMENTS


| | PAGE |
|---|---|
| A.C.S. Radio | |
| Air Ministry | |
| Air Service Training, Ltd. | |
| Ambassador Radio Works | |
| Anglo-American Radio (& Motors), Ltd. | |
| Armstrong Manufacturing Co. | 2 |
| Automatic Coil Winder Co., Ltd. | Inside Front Cover |
| Belling & Lee, Ltd. | 5 |
| Birmingham Radiomart G5N1 | 6 |
| British Centralab, Ltd. | |
| British Institute of Engineering Technology | |
| British Insulated Cables, Ltd. | Inside Front Cover |
| British McMurdo Silver Co., Ltd., The | |
| British Mechanical Productions, Ltd. | 7 |
| British Thomson-Houston Co., Ltd., The | |
| Capstan Cigarettes | |
| Chloride Electrical Storage Co., Ltd. | |
| Cosmocord, Ltd. | |
| Degalliers | |
| Edison Swan Electric Co., Ltd. | |
| Electradix Radios | 6 |
| Evrizone Radio & Television Co., Ltd. | |
| Fluxite, Ltd. | 3 |
| General Electric Co., Ltd. | |
| Grampian Reproducers | 3 |
| Hartley Turner Radio, Ltd. | |
| Henley, W. T., Telegraph Works Co., Ltd. | |
| Institute of Wireless Technology | 7 |
| International Correspondence Schools | |
| Jackson Bros. (London), Ltd. | |
| Lockwood Casework Co. | |
| London Radio Supply Co. | 2 |
| Marconi-Ekco Instruments, Ltd. | |
| McCarthy, H., Ltd. | |
| M.R. Supplies | 4 |
| Pamphonic Reproducers, Ltd. | 2 |
| Partridge, N. | |
| Peto-Scott Co., Ltd. | 1 |
| Player's Cigarettes | |
| Premier Supply Stores | 7 |
| Quartz Crystal Co. | |
| Savage, W. Bryan, Ltd. | 6 |
| Sound Sales, Ltd. | 4 |
| Taylor Electrical Instruments, Ltd. | 6 |
| United Insulator Co., Ltd. | 1 |
| Universal Electric | 6 |
| Varley, Ltd. | |
| V.G. Manufacturing Co. | 6 |
| Voigt Patents, Ltd. | 1 |
| Vortexion, Ltd. | 3 |
| Welburn Radio, Ltd. | 6 |



Third Edition Revised by O. F. BROWN, B.Sc.

*The* ELEMENTARY PRINCIPLES *of* WIRELESS TELEGRAPHY *and* TELEPHONY

*by* R. D. BANGAY

PRICE 7/6 net

by post 8/-

*From all leading Booksellers or direct from the Publishers*

The standard book of instruction for wireless beginners and students. The style is clear and simple and attention is given to the theoretical elements of electricity and magnetism: to the dynamo: and to the properties of waves. A leaflet which gives full particulars of the volume, including a synopsis of the chapters, will be sent on request.

ILIFFE & SONS LIMITED, DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1 W.W.9.

*FOURTH EDITION* *Revised and Enlarged with 50 Additional Pages*

WIRELESS SERVICING MANUAL

By W. T. COCKING

(*of "The Wireless World"*)

**The most complete book of reference of its kind. A reliable practical guide for amateur and professional**

The present Edition of the "Wireless Servicing Manual" brings the material of the book right up to date and includes an additional chapter on television receivers which is practically the only source of servicing information available on this subject.

Testing apparatus is fully dealt with and the methods of locating and curing faults in receiving equipment are explained.

Ganging, Automatic Volume Control, Instability, Distortion, Mains Hum, Whistles, Local Interference and Aerials, are all separately treated.

The reference material, including base-connections for British, Continental and American Valves, and the various colour codes for components, has been extended and revised.

***BOUND IN CLOTH BOARDS***
***SIZE 7½ ins. × 5 ins.***
***288 Pages***

**5/- net.** By post 5/5

**Issued in conjunction with "THE WIRELESS WORLD" and Published by the Proprietors:—**

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

W.W.20.


Printed in England for the Publishers, Iliffe and Sons Ltd., Dorset House, Stamford Street, London, S.E.1, by The Cornwall Press Ltd., Paris Garden, Stamford Street, London, S.E.1. "The Wireless World" can be obtained abroad from the following: France: W. H. Smith & Son, 248, Rue Rivoli, Paris; Hachette et Cie, Rue Réaumur, Paris, and branches; Messageries Dawson, 4, Pue de Faubourg Poissoniere, Paris. Belgium: W. H. Smith & Son, 71-75, Boulevard Adolphe Max, Brussels. Australia: Gordon & Gotch, Ltd., Melbourne (Victoria), Sydney (N.S.W.), Brisbane (Queensland), Adelaide (S.A.), Perth (W.A.), and Launceston (Tasmania). New Zealand: Gordon & Gotch, Ltd., Wellington, Auckland, Christchurch and Dunedin. India: A. H. Wheeler & Co., Bombay, Allahabad and Calcutta. Canada: Imperial News Co., Toronto, Winnipeg and Vancouver; Benjamin News Co., Montreal; Gordon & Gotch, Ltd., Toronto. South Africa: Central News Agency, Ltd.; Wm. Dawson & Sons (S.A.), Ltd., Cape Town. United States: The International News Co., New York.

*—Third Edition of*

# WIRELESS DIRECTION FINDING

**BY R. KEEN, B.Eng.**

**A BOOK OF INSTRUCTION AND REFERENCE FOR ENGINEERS, TECHNICIANS, TELEGRAPHISTS AND OTHERS ENGAGED OR INTERESTED IN THE USE OF DIRECTIVE WIRELESS TELEGRAPHY FOR THE NAVIGATION OF SHIPS AND AIRCRAFT**

The third edition of this well-known book deals with the principles of Wireless Direction Finding and gives an account of the circuits and apparatus used in its application to navigation. The Adcock Aerial has a separate chapter covering its principles together with much information on its installation and performance. Further chapters are included on Shore, Ship and Aircraft installations as well as a special section on the choice of a suitable site for the Aircraft Ground D.F., with Adcock Aerials.

Engineering students and research engineers will find useful references to a selected list of some 600 of the more important contributions to the literature of D.F.

**800 pages 550 illustrations**

**PRICE 25/- net By post 25/9**

*From leading Booksellers or direct from the Publishers:*

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

*Sixth Edition* *Revised and Enlarged*

# HANDBOOK of TECHNICAL INSTRUCTION for WIRELESS TELEGRAPHISTS

by H. M. DOWSETT
(M.I.E.E., F.Inst.P., M.Inst.R.E.)

**This standard handbook is planned primarily for the use of wireless operators, whether prospective or actual. It is virtually a complete theoretical course for students wishing to qualify for the Postmaster-General's Certificate of Proficiency.**

CONTENTS INCLUDE:

The Electric Charge and the Condenser—The Condenser in Practice—Direct Current and Ohm's Law—Scalar and Vector Quantities and Curve Plotting—Primary Batteries—Accumulators—Magnetism—Electro Magnetism—Self-Induction—Dynamo Electric Machines—Measuring Instruments—Switchboards and Switchgear—Alternating Current Effects, and Vector Diagrams—Alternating Current Fundamental Formulae—Alternating Current Generators, Alternating Current Motors and Transformers—Damped Oscillations—Commercial Types of Spark Transmitter—Aerials and Radiation—Simple Receiver Circuit and Crystal Detector—Thermionics and the Various Applications of the Valve—Depth Sounding—Valve Transmitters—Wavemeter and Transmitter Adjustment—Theory of Valve Receiver Circuits—Valve Receivers—Short Wave Aerials and Apparatus—Marine Direction Finders—Marine Audio Relay Service—Distress Call Apparatus—Lifeboat and Emergency Outfits—Trawler Apparatus—Maintenance of Marine Radio Installations and Possible Faults.

NOW ON SALE PRICE 21/- By post 21/9
Foreign Postage 22/-.

*Obtainable from leading booksellers or direct from the Publishers:*

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

# DAILY SKETCH
# NEWS - PICTURES HAVE MADE HISTORY

History is being made every day of these stirring years. The DAILY SKETCH news-pictures—most vivid, most compelling, most complete of any published in the daily press of Great Britain—show you history in the making.

DAILY SKETCH pictures have made history in themselves by proving that, for the first time, newspaper photographs can outlive the passing interest of a glance at the breakfast table. So powerful and so widespread has been their appeal that put on exhibition, they have continued to draw crowds in all parts of the country a year after the events they portrayed took place.

Be well informed on the world in which you live. *See* the important events everywhere as they happen. See the pages of important news-pictures in the DAILY SKETCH every morning.

# DAILY SKETCH

*All the News and Pictures Fit to Print*

BIDCUP BLACKFEN LIBRARY.

BY-PASS CONDENSERS: New Ideas

# The Wireless World

6D.

## THE PRACTICAL RADIO & TELEVISION JOURNAL

Thursday, May 11th, 1939.

No. 1,028. Vol. XLIV. No. 19.

Copyright. Registered as a Newspaper for transmission in the United Kingdom. Entered as Second Class at the New York, U.S.A., Post Office.

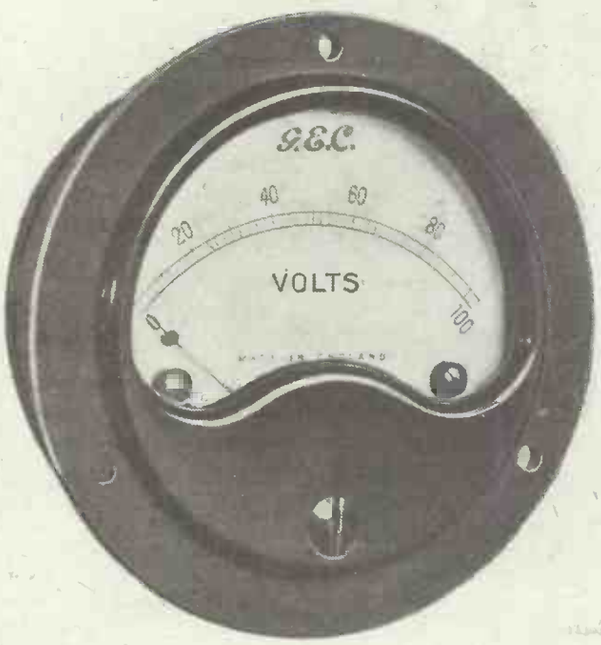


G.E.C.
REGD. TRADE MARK

# ACCURATE MEASUREMENT

Accurate measurement, the essential of progress, necessitates the use of good instruments, and nowhere is this more important than in radio.

Good instruments can be designed and produced consistently only as the result of great experience in experiment and research extending over many years.

Salford Electrical Instruments Ltd. have been making first quality instruments for half a century, and our products are to be seen in constant use in Power Houses, Test Rooms and Laboratories all over the world.

Instruments in sizes from 2" upwards are available for almost every electrical measurement. The 2½" flush or projecting types are specially suited for radio purposes, and may be supplied as:—Milliammeters, Microammeters, Ammeters, and Voltmeters, D.C. and A.C.

Portable types are also made in most of these ranges. For H.F. measurements a range of Valve Voltmeters is available.

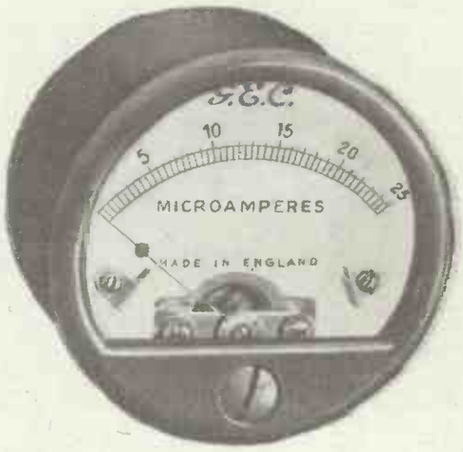


*Please write for descriptive list S.27, and state particular instruments in which you are interested.*

## SALFORD ELECTRICAL INSTRUMENTS LTD.

**PEEL WORKS, SALFORD, 3.** *Telephones: BLAckfriars 8888 (3 lines)* *Telegrams and Cables: "SPARKLESS, MANCHESTER."*

**PROPRIETORS: THE GENERAL ELECTRIC Co. Ltd., OF ENGLAND**

The Wireless World
THE PRACTICAL RADIO JOURNAL
29th Year of Publication

No. 1028. THURSDAY, MAY 11TH, 1939. VOL. XLIV. No. 19.

Proprietors : ILIFFE & SONS LTD.

Editor :
HUGH S. POCOCK.

Editorial,
Advertising and Publishing Offices :
DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1.

Telephone : Waterloo 3333 (50 lines).
Telegrams : "Ethaworld, Sedist, London."

COVENTRY : 8-10, Corporation Street.
Telegrams : "Autocar, Coventry." Telephone : 5210 Coventry.

BIRMINGHAM :
Guildhall Buildings, Navigation Street, 2.
Telegrams : "Autopress, Birmingham." Telephone : 2971 Midland (5 lines).

MANCHESTER : 260, Deansgate, 3.
Telegrams : "Iliffe, Manchester." Telephone : Blackfriars 4412 (4 lines).

GLASGOW : 26B, Renfield Street, C.2.
Telegrams : "Iliffe, Glasgow." Telephone : Central 4857.

PUBLISHED WEEKLY. ENTERED AS SECOND CLASS MATTER AT NEW YORK, N.Y.

Subscription Rates :
Home and Canada, £1 10s. 4d. ; other countries, £1 12s. 6d. per annum.

*As many of the circuits and apparatus described in these pages are covered by patents, readers are advised, before making use of them, to satisfy themselves that they would not be infringing patents.*

## CONTENTS

| | Page |
|---|---|
| *Editorial Comment* | 431 |
| *Electric Gramophone* | 432 |
| *Proposed New Amateur Code* | 436 |
| *Tubular Condensers* | 437 |
| *Television Programmes* | 438 |
| *Problem Corner* | 438 |
| *Frequency Doublers* | 439 |
| *Something New in Car Aerials* | 440 |
| *Orchestral Pitch* | 441 |
| *The Montreux Plan* | 442 |
| *Frequency Modulation in America* | 443 |
| *News of the Week* | 447 |
| *New Tone-Control Circuit* | 449 |
| *Letters to the Editor* | 450 |
| *Paper Records* | 451 |
| *News from the Clubs* | 451 |
| *Unbiased* | 452 |
| *Random Radiations* | 453 |
| *Recent Inventions* | 454 |

# *EDITORIAL COMMENT*

## B.B.C. "Official"

### *Public Reaction to Broadcast News*

THE responsibility of British broadcasting towards the listener is, by virtue of peculiar circumstances, probably greater than that of any other agency through which news is conveyed to the public. The peculiar circumstances are that, however much the B.B.C. may try, it cannot remove from the public, and particularly listeners abroad, the deeply rooted idea that every statement in the nature of news made by the B.B.C. is either directly or indirectly expressing the opinion of our Government. The feeling exists almost universally that no matter what the news item may be, it has at least received the approval of some responsible Government official before it is transmitted.

We suspect that it is precisely with the object of trying to correct this impression and to emphasise the non-official nature of B.B.C. news that the Corporation so often includes irresponsible items ; but we think that some better means should be devised to achieve this object. The only effect of the present method is to cast a reflection in the minds of the public on the policy and capabilities of the Government.

### *Voice of the State*

It is by no means easy to imagine how the combined opinion of listeners that the voice of the B.B.C. is the voice of the State can be changed, unless it is by constantly referring in B.B.C. news to the source of statements made. The fact that the news almost invariably follows a number of purely official announcements tends to strengthen the opinion of the listeners that the news itself is officially approved.

If the B.B.C. confined its general news information to quotations from the morning and evening papers and indicated carefully with which paper the information originated, we believe that this would, to a very large extent, remove the present misconceptions. It would then be possible to add to the news so quoted other statements which if they were official in character could be expressly so described.

We believe that it is of the utmost importance that steps should be taken to remedy the present unsatisfactory position and to relieve the B.B.C. of the necessity of broadcasting transparently foolish items in a vain attempt to get rid of the official atmosphere now pervading its news broadcasts.

## The "A" Code

### *Proposed Amateur Abbreviations*

WE commend to the notice of all amateur transmitters the suggestion for a substitute for the "Q" code, put forward elsewhere in this issue. The "Q" code was originally devised for the marine service, and its compilers have quite rightly never made any attempt to provide abbreviated expressions for facilitating the exchange of experimental data between amateur transmitters.

If, as we hope, the present suggestion is received with favour the details of the code should be widely discussed, and, most important of all, the international aspect must not be forgotten. The temptation to provide abbreviations for every contingency must be resisted, as a code of this kind loses half its usefulness if it cannot be memorised in full.

# HIGH QUALITY REPRODUCTION AND NEW IDEAS IN OUTWARD FORM

# Electric

*ALL are agreed as to the extreme inconvenience of conventional apparatus for electrical gramophone reproduction, but few serious attempts have been made to evolve something better. Here at last is a "chair-side" amplifier that seems to provide a satisfactory solution to the problem.*

THE apparatus to be described is the result of a good deal of thought devoted to devising means for getting the best reproduction from gramophone records and therefore may appeal to readers of *The Wireless World*. Persons who have inspected it generally start off by considering it fantastic that eight valves should be devoted to gramophone purposes only,

but by discussing the design step by step it is hoped to show that there is method in this madness.

First of all, it may be necessary to explain why the prevailing practice is not followed of combining gramophone with radio. The writer is not greatly enamoured of automatic record-changers, partly because of their tendency to utter various scratching and clicking sounds during the changing-over process, and partly because of the necessity for thinking out in advance the whole programme to be played. The advantages of the auto-changer seem to be mainly in providing a continuous service of sound which is supplementary to something else (such as dancing or drinking beer) and therefore is not listened to critically. In view of the fact that the disc record suffers greater potential limitations of quality than radio transmissions, its chief justification is the ability to call at any time on works of music performed by selected executants, and which merit attentive listening. In these circumstances records can be treated more artistically by hand.

An essential requirement is that one must not be obliged to leap up every few minutes to change records or adjust the volume or tone. This means that the turntable and controls must be easily carried or wheeled to the chair side. The usual way of doing this is by means of a "playing desk" or its equivalent, consisting of a turntable, pick-up and volume control. Mains and pick-up leads are, of course, necessary links with the mainland. Having gone thus far, one might as well include the amplifier, for no extra leads are needed; in fact, one probable source of trouble is avoided by substituting loud-speaker leads for pick-up leads, the latter being very liable to introduce hum. Another point is that a satisfactory form of tone control is much more easily arranged when the amplifier is accessible. And if the apparatus is self-contained it is available for a number of purposes for which a good radio-gramophone or the equivalent might not be sufficiently portable.

As it is taken for granted that the reproduction is to be of the highest possible quality, and sufficient in quantity for domestic needs, and perhaps a little more, the equipment is bound to be fairly heavy, and easy movement to the most comfortable chair is best achieved by putting it on wheels or castors. Then, to ensure that it is not banished to some remote part of the house as a cumberer of the ground during times of disuse, the best policy is to make it in such a form as will be accepted as a useful piece of furniture. Its position near the easy chair is further assured by clothing it in fabric (to match, if possible) rather than in easily damageable polished wood. This idea was encouraged by the discovery that even oak finish was over 50 per cent. more expensive than padded tapestry on deal, as well as being far less sightly and serviceable. The design shown here takes the form of an occasional seat or table when shut up; when open, the pick-up and controls are conveniently accessible from a low chair, and there are spaces for selected and used records respectively each side of the main

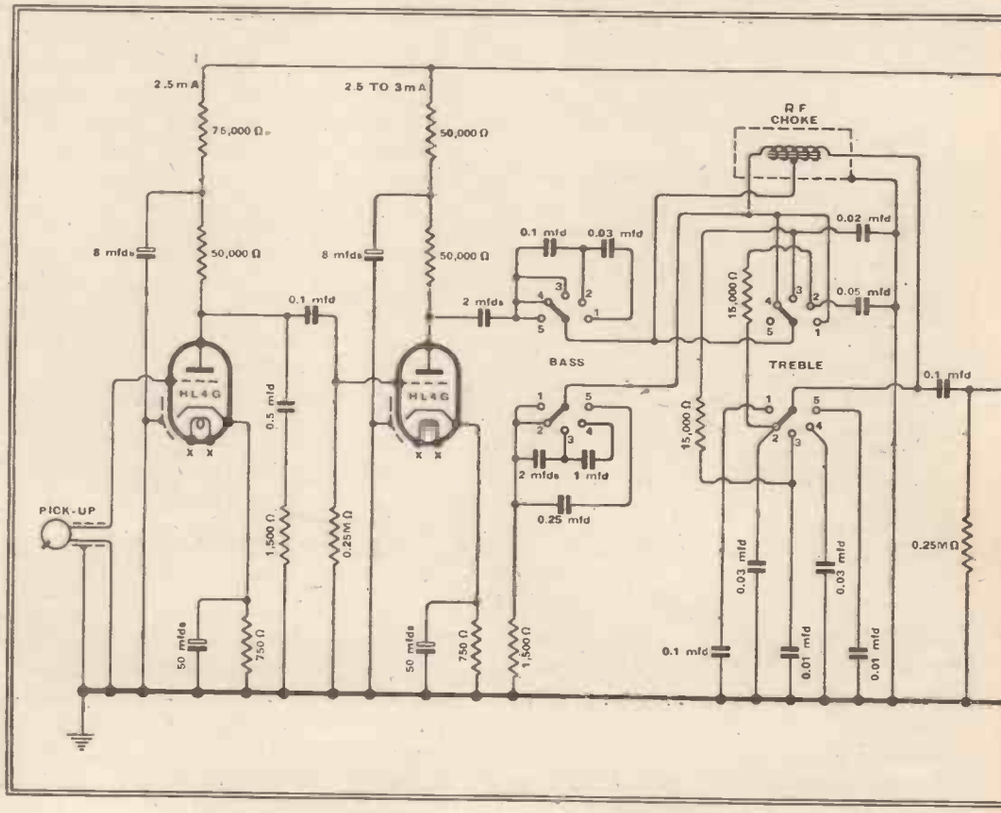


Fig. 1.—Complete circuit diagram of amplifier and tone control.

# Gramophone

By
M. G. SCROGGIE,
B.Sc., A.M.I.E.E.

compartment. When not in use for this purpose these spaces are handy for storing the rather lengthy flexes that have been fitted for taking care of all contingencies.

As it is intended that the doors should be open when in use as a gramophone, it was not considered that any special provision need be made for ventilation. In case any readers are attracted by this cabinet, it may be mentioned that a very satisfactory job was made up to the writer's design by H. G. Dunn & Sons, Ltd., of Bromley, Kent, upholstered in selected tapestry, padded, at an inclusive cost of just over £4, and the firm is in a position to produce duplicates to order.

### Choosing the Pick-up

There is nothing special about the turntable, which is a standard type driven by AC induction motor. The pick-up, however, called for more care in selection. The Telefunken T.O.1001 was finally chosen, because by adopting a sapphire point fixed in a diminutive armature it has been possible to avoid the usual needle resonance within the recorded range of frequencies, and hence not only to achieve a frequency characteristic that is substantially level throughout that range, but also extreme lightness and freedom. It is a vast convenience not to have to bother about needles, and a great comfort to know that record wear is negligible. A little trouble was experienced with the first sample, which tended to engender certain obscure rattling sounds, but the replacement has been free from this defect. It is worth while taking some trouble to mount the pick-up accurately as instructed, and this is facilitated by the lining washers supplied. The sapphire point, which is almost microscopic, is ingeniously protected by a spring roller device, but it is advisable to take care in letting it down on any records that are chipped at the edges.

Coming now to the amplifier itself, the objects have already been mentioned, as regards quality and quantity, but the tone control, perhaps, needs to be emphasised. In the Telefunken pick-up no attempt is made, probably wisely, to compensate for the restriction of bass in the recording, amounting to as much as 15 db. at 50 c/s. Also, the sustained output right up to and beyond the top limit of recorded frequency causes the amount of scratch reproduced from most records by means of an amplifier with a flat characteristic to be unbearable. There seems to be a tendency to record the upper frequencies with a slightly rising characteristic, which allows some reduction in scratch to be obtained while preserving the *overall* characteristic level; but generally it is necessary to sacrifice some "top" to obtain a reasonably silent background. Moreover, records differ very considerably in their balance of tone; so altogether a comprehensive tone control system is essential for getting the best out of them.

The bass compensation ought really to be regarded as over and above any adjustment available by means of the tone control, because it is only when the bass has been lifted 15 db. at 50 c/s that the overall characteristic (inclusive of the record itself) is flat. As this rise is as much as can be accomplished in any one

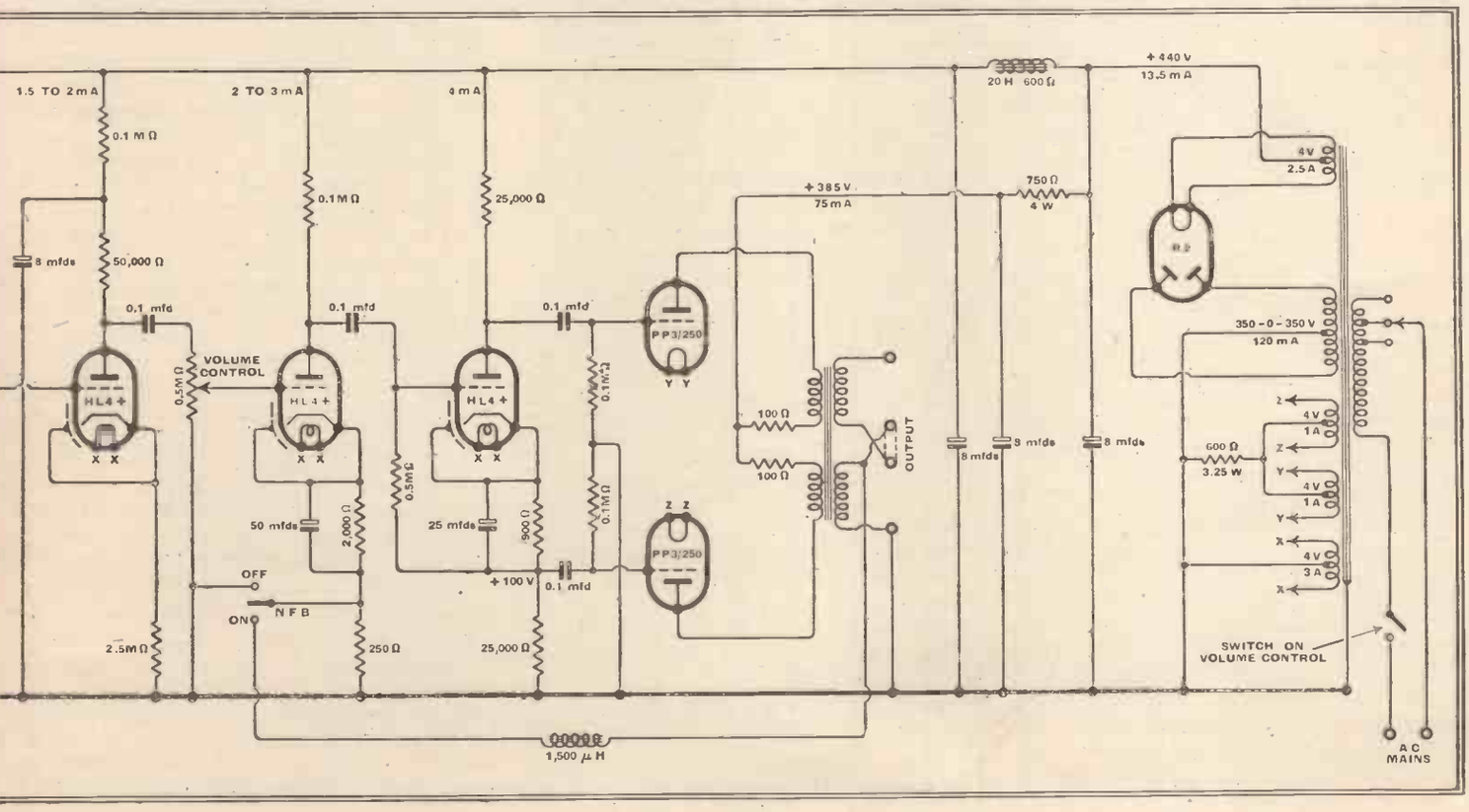

**Electric Gramophone—**

stage without the use of oscillatory circuits, it is best to do it separately from the tone control proper.

Leaving the subject of tone control for the moment and looking at the other end of the amplifier, there is the output stage. Modern tetrodes are attractive by reason of their power efficiency; but for the highest quality it is necessary to use negative feedback, which eliminates their other advantage of smaller drive voltage than triodes. Moreover, the efficiency and quality depend to a considerable extent on the load impedance being approximately right. Not only is it very convenient to be able to connect various loud speakers, singly or in combination, without having to think too hard about load matching, but the impedance of any one speaker varies largely with frequency. And although it is argued that tetrodes (properly used) distort no worse than triodes, nobody appears to have shown that they are any better. So, as the writer has been driven to the conclusion that the greater power output of multi-electrode output valves is largely illusory so far as the highest quality work is concerned, he conservatively stuck to triodes. As an output of about 7 watts was considered to be ample, a pair of PP3/250 valves are used. This is the actual measured output on the secondary side under the conditions of use; the theoretical output is slightly more.

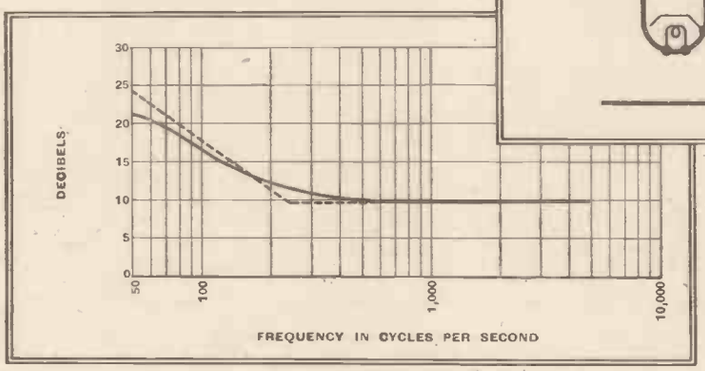


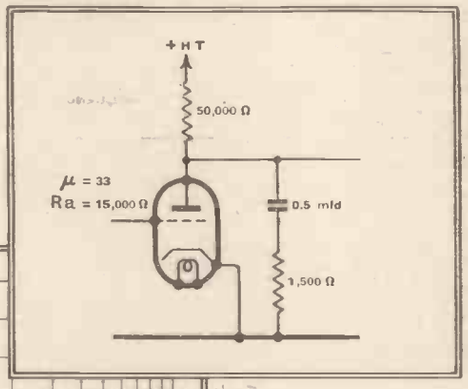


Fig. 2.—Frequency characteristic of the first stage, showing bass compensation. The dotted line indicates the theoretical requirement.

### Negative Feedback

Push-pull is justified on purely economic grounds, quite apart from its value in reducing the unpleasanter components of distortion and difficulties of decoupling. Without it a much more expensive output transformer and smoothing system would be required. The use of negative feedback with triodes may be more surprising, especially as it is not for tone control purposes. As can be seen from the circuit diagram, it is optional and without it there is a reserve of amplification. Normally it is used, however, and reduces residual hum, renders the output even less dependent on load impedance, and cleans up the performance generally. There would be no point in applying the feedback over the output stage only, as it would be likely to cause more trouble than it cured, by increasing the signal level in the previous stage. It has, therefore, been taken back to a point where the signal level is so small that even when increased it still comes well within the power of the preceding stage to handle without appreciable distortion. This also makes it possible to include the output transformer, too, as the low secondary voltage is enough for feedback. The amount of feedback actually used divides the amplification by slightly more than 4, equivalent to a loss of 12½ db.

To simplify the application of negative feedback over several stages, to minimise the opportunities for picking up hum, and to serve the interests of high fidelity and cheapness, resistance coupling throughout was adopted. This immediately raised the question of the phase-inverter. The method described by O. H. Schmitt (*Journal of Scientific Instruments*, March, 1938)[1] was given a trial, but the Cocking "concertina" circuit was finally preferred, because it remains balanced even if the valve ages, it is less tricky to design and adjust, its gain is about 50 per cent. higher for two valves, owing to its feedback it is extremely linear, and although the available output is less it was found possible by careful design and the use of choke decoupling (avoiding large voltage drop) to get rather more than enough to drive the output stage. The cathode is 100 volts more positive than the heater, and as the Tungsram HL4+ valve is exceptional in being rated up to 150 volts difference, as well as requiring only 2.4 watts for the heater, it was selected for this and all preceding stages.

The phase inverter stage requires 43 volts (peak) to drive it; a straightforward preceding stage gives a gain of × 27½, and, allowing for the negative feedback (which is conveniently introduced into its cathode circuit), calls for 7½ volts at its grid.

Coming back now to the subject of tone control: one possible method is to insert frequency-discriminating circuits in the negative feedback line so as to reduce feedback at those frequencies which it is desired to boost, and vice versa. This method was rejected because, although it is quite useful for moderate amounts of control, it does not lend itself to a steady rise of 6 db. per octave over as much as 2½ octaves, and greatly increases the risk of oscillation that is present when large amounts of negative feedback are attempted. So the method adopted is the well-known one of varying the coupling impedance in a stage of amplification. To obtain the required 6 db. per octave (which is the rate of bass loss in recording) it is necessary for the amplification of the stage to be directly proportional to the coupling impedance, and therefore the latter must at all frequencies be small compared with the valve anode impedance, which means that at some frequencies it must be *very* small. At such frequencies the valve amplifies only slightly, if at all; its amplification being reserved for those frequencies one desires to boost. Because of its very high anode impedance, a pentode is the best type of valve for large amounts of tone control; but in the present case two triodes were used, because one could be devoted to compensating for bass loss, leaving the other free for tone control proper.

### Coupling the Pick-up

Now, for absence of linearity distortion a triode really ought to be worked with a comparatively high external impedance, and as the coupling impedance for tone control is very low at some frequencies, the expedient is sometimes adopted of increasing the valve impedance by connecting a resistance in series. This method makes it difficult to maintain the rise in amplification uniform over a sufficient range of frequency, so cathode-ray tests were made to find the maximum signal that could be handled under low-load impedance conditions without appreciable distortion. As expected, this was fairly low (about 0.3 volt input). The output of the Telefunken pick-up, which has an impedance of 100 ohms, is about 0.1 volt peak on normal records. A 1 : 20 ratio transformer is recommended for use with it to increase the output; but a valve is cheaper, and has the advantage of not needing the careful screening that is necessary to prevent a transformer at this low-level stage from picking up hum. Although the signal level is low when the pick-up is applied straight to the valve, the low impedance makes it very easy to avoid hum. And the extra gain makes the amplifier suitable for alternative use with a needle-armature pick-up or a microphone.

Because tone control of the type chosen must be carried out at a low-signal level to avoid distortion, it is evident that it must be dealt with right at the start, and the first stage is devoted to compensating for bass loss in the record. At middle and high frequencies the coupling impedance is effectively the 1,500-ohm resistance, as the impedance of the 0.5-mfd. condenser in series is negligible, and the anode and grid resistances of 0.05 and 0.25 megohm respectively merely reduce

[1] Since writing this, it has been dealt with in *The Wireless World*, April 13th, 1939.

**Electric Gramophone—**

the effective coupling resistance to a negligible extent. At these frequencies the amplification is approximately ×3. But at low frequencies the major part of the coupling impedance is the reactance of the 0.5-mfd. condenser, which progressively increases as the frequency diminishes, and the amplification also increases in proportion until the anode resistance (effectively in parallel) exerts an appreciable shunting effect. Of course, the change-over, at 250 c/s, is not sharp, but, as can be seen from Fig. 2, the compensation is fairly close to the theoretical (and probably closer still to the inverse of the actual recording characteristic).

The second stage is similar, except that, instead of a fixed tone-compensating circuit, there is a variable tone-control system which will be described in detail presently. The normal gain of this stage (due to another 1,500-ohm coupling resistance) is again 3, so the normal maximum peak voltage given is about 0.9. To bring this up to the 7½ volts required by the pre-phase-inverter stage, and to allow a little in hand, another stage is obviously necessary. As the full gain of a stage is needlessly large, it is reduced by the omission of the biasing resistor by-pass condenser.

### Regulating Volume

Volume control has not yet been provided. To avoid overloading, the best place for volume control is as soon as possible—usually directly between pick-up and amplifier. On the other hand, for avoiding any noise, due to the volume control itself or to tone control switching, or any fault that might develop in the early stages, the later the better. As in the present case the maximum possible input is only slightly more than enough to overload the output stage with no reduction at all, it is quite safe to place the volume control in front of the fourth stage. It would, of course, be no use putting it anywhere beyond this, as the negative feedback would counteract it.

After putting in the power rectifier, the full tale of valves is thus made up; and as they are all of comparatively cheap kinds and of a minimum number of types, no further apology seems necessary. Although it would be quite satisfactory for all valves previous to the output stage to be of the HL4+ type, the first two (HL4g) are actually of the same characteristics but modified by bringing the grid to a top cap and the metal coating to an independent pin. This confers minor benefits in further reducing any tendency to hum, and in making it possible to cut out the first stage immediately by clipping the input lead to the second valve top. This is useful, among other things, for non-gramophone purposes, for which the bass compensation is in general not needed.

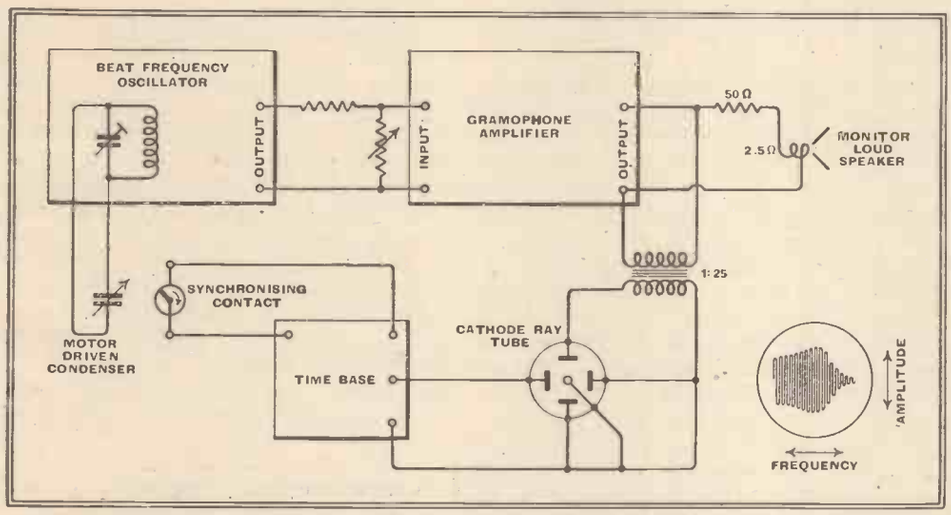


Fig. 3.—Diagram of apparatus used for studying the characteristics of the treble tone control. The inset shows the type of result obtained on the oscilloscope screen.

The tone control system gives independent bass and treble control with five alternatives for each. The bass control is marked "Flat" in the centre position and gives two degrees of boost on one side and two degrees of cut on the other. Actually "Flat" is arranged to give a slight boost, to supplement the efforts of the first stage. The treble control presented more difficulty, because it was desired to be able to introduce a sharp cut-off at certain frequencies in order to combat scratch. At the same time it is most essential to avoid any tendency to a preliminary resonant peak, which is shock-excited by scratch frequencies and degrades the performance to that of inferior types of pick-up with their armature resonances.

### Testing the Tone Control

As pure calculation of filters to a given performance is exceedingly tedious in all except idealised cases, the final adjustment was experimentally done with the help of cathode-ray apparatus improvised to show the frequency characteristic instantaneously on the screen. The effect of any adjustment could thereby be seen at once instead of only after a lengthy process of plotting separate points. As this apparatus was made up from what happened to be at hand, instead of being purchased ready-made for a mere few hundred pounds, it may be of interest, and the arrangement is shown diagrammatically in Fig. 3. A motor-driven variable condenser, made up from an old gramophone motor and other odd parts, happened to be left over from previous experiments with "ganging oscillators," and was, therefore, available, complete with synchronising contact, made once per revolution. The output of a beat-frequency oscillator was thus variable over a band of a few thousand cycles. The position of the band itself was, of course, variable by the normal frequency control. The motor and time base were adjusted to run in synchronism at as slow a speed as possible—something like 10 c/s.

The system finally arrived at, and shown in the complete circuit diagram (Fig. 1),

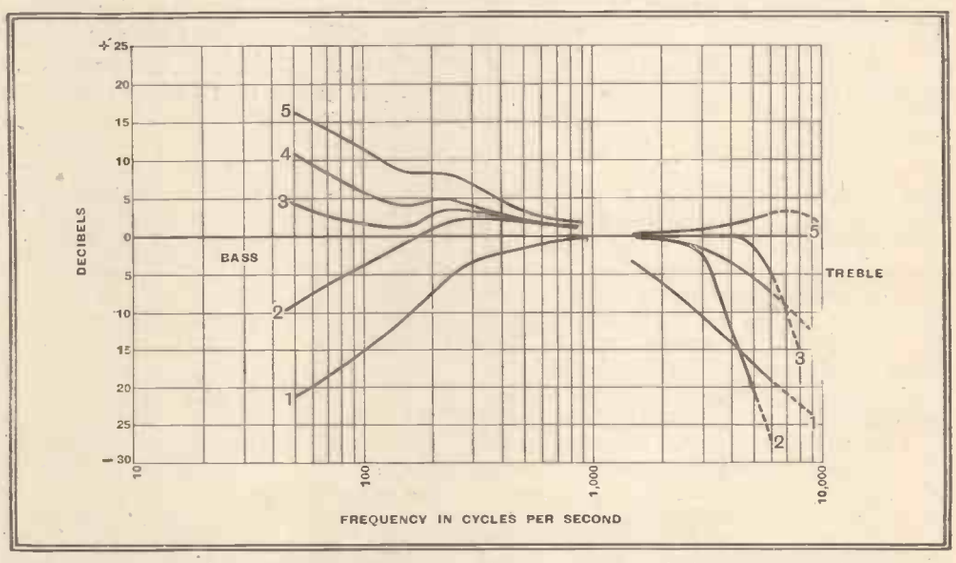


Fig. 4.—Measured frequency characteristics at different settings of the tone controls, inclusive of record, pick-up, amplifier, and output transformer. The characteristic of the record is level from 250 to 6,000 c/s, and falls 6 db per octave from 250 to 50. The sharp cut-off characteristics (2 and 3 on the treble side) are not so satisfactory aurally as 1 and 4.

**Electric Gramophone—**

consists of simple resistors and condensers except for a tapped choke made by centre-tapping a Varley screened iron-core RF choke (BP26). Some difficulty might be experienced in exactly duplicating this component, as the position of the tap is not very definite; but that matters little, because although the results (shown in Fig. 4) conform admirably to what was aimed at, they have served to demonstrate by the test of listening that for the best compromise between scratch and high quality, the sharp cut-off type of characteristic is less successful, even when free from appreciable resonances, than the steady droop. This is fortunate, because the latter is so much easier to calculate and construct, and *for gramophone purposes* the writer advises substituting the more conventional variations of treble tone for the two sharp cuts, 2 and 3. Rising characteristics—except perhaps for one very slight one—are not necessary or desirable if the system is to be used only with the Telefunken pick-up, but several degrees of fall, including a really drastic one, are helpful.

The frequency characteristics shown in Fig. 4 were taken with the help of the Decca EXP.55 standard frequency record, which is restricted uniformly below 250 c/s and therefore conforms to a theoretical rather than a practical characteristic; that is to say, one in which the level and falling parts meet in a sharp angle at 250 c/s rather than a smooth bend. This accounts for the irregularity in this region in Fig. 4. The dotted portions above 6,000 c/s have been filled in with the help of data from the cathode-ray apparatus. Apart from this, the curves are overall as far as the load—the record, pick-up, tone-control, amplifier, and output transformer characteristics being included. It should be noted that even with the most drastic treble reduction (No. 1) the note is brighter than when using some types of pick-ups with no tone control.

### The Smoothing System

Finally, referring to a few miscellaneous features of the design, the absence of choke smoothing for the output stage will be noted. This greatly simplifies the problem of avoiding hum pick-up with a sensitive amplifier on the same chassis as the power system. The rectified output, 440 volts, is too much for the PP3/250 valves, and the 750-ohm resistor serves the double purpose of smoother and voltage dropper.

The output transformer is wound with two identical secondaries, so, by connecting them in parallel or series, optimum load resistances of 2 ohms and 8 ohms are provided for. A number of loud speakers, each having several times these impedances, can be fed in parallel without any appreciable variation in the output from one speaker as the number in circuit is varied; and, unlike other types of output valve, triodes give even better quality when the load impedance is above normal.

The 100-ohm resistors in the primary side are for connecting a 0-5 voltmeter across for checking the static balance of the output valves. The dynamic balance is ensured by using a common biasing resistor, un-by-passed.

The 1,500-$\mu$H coil (actually a small iron-cored long-wave coil) in the feedback line was inserted because it was found that under certain dynamic conditions (such as a large amount of line capacity across the load) there was a tendency to momentary spurious oscillation.

The skirts of the tone and volume control knobs have grooves filed in them as markers and also to enable them to be operated by touch alone. The control panel is faced with matt white ivorine. The power transformer is a Partridge T350/120.

The Goodman "Infinite Baffle" loud speaker, although specifically not recommended by the makers for gramophone purposes owing to its extended and rising high frequency response, actually gives very satisfactory results in conjunction with this set when a falling treble characteristic is selected. This type of speaker has the advantage (apart from good general quality) of giving really low bass in a reasonably portable form—it is contained in an 18-inch cube. The whole equipment is, therefore, easily transportable in a small car for giving "sound" wherever wanted. The writer has used it very successfully in amateur dramatics, the audience being greatly impressed with the improvement over what is usually served up as music on such occasions.

Although the deficiencies of bad records can be "hushed up" by discreet use of the tone control, it is, of course, necessary to make a careful selection in order to demonstrate the capabilities of the apparatus. Lists of good quality recordings were published in *The Wireless World* some time ago, and the only one repeated here is a set of three which is attractive because it is of tuneful and varied music, brilliantly played and well recorded, inexpensive, covers a wide range of tone, and consists of short pieces necessitating no carry-over from one side to the next—the ballet suite "La Boutique Fantasque," recorded on H.M.V. 2846-8.

---

# Proposed New Amateur Code

## SAVING TIME AND REDUCING INTERFERENCE

A NEW and comprehensive code, expressly designed for the use of amateur transmitters, has just been submitted to the Radio Society of Great Britain.

This code comprises a series of over seventy 3-letter signals, planned to convey practically all the technical information, weather data, etc., that amateurs have occasion to exchange in the course of their transmissions.

The draft code has been drawn up by a Suffolk amateur, G3XT, of Stratford, near Saxmundham, who, though comparatively a newcomer to the ranks of transmitting amateurs, has had over fourteen years' experience of listening on the amateur bands, and is, therefore, conversant with amateur requirements as regards a signal code.

### Simplicity and Speed

It is claimed that the use of the new abbreviations, each of which begins with the letter A (a letter that is quick and easy to key in Morse), will effect an enormous saving of time, as it enables any typical amateur message to be sent, accurately and explicitly, with approximately one-half the amount of signalling incurred under the existing system. The originator suggests that, by eliminating superfluous signalling, the new "A" code, if adopted, should do much to reduce the present interference on the amateur bands.

An important advantage of the proposed abbreviations is that they are exceptionally easy to memorise, as the last letter of each signal (with a few unavoidable exceptions) is the initial letter of the subject covered. "ATR?" for example means "What is your receiver?" "ATW" means "Please wait," "ASA?" means "What type of aerial are you using for transmission?" and so on.

### Meteorological Data

A section of the code is devoted to weather data and conditions of reception. This affords a ready means of indicating, briefly but accurately, the prevailing weather and reception conditions on the band at the time of the QSO. The enquiry signal "AWX?" (meaning "What is the weather in your locality?") can be answered by abbreviations such as "AWR" meaning "The weather here is rainy," while more detailed information can be given if desired with the aid of the abbreviations AWB, AWT and AWV, referring to barometer readings, temperature and visibility respectively.

"AWA" meaning "Conditions of reception here are good," and "AWI," "Conditions improving," are among the signals intended to be used in reporting on the state of the band at any given time.

As the new code is sufficiently comprehensive to cover the whole field of amateur transmitting activities, it has been suggested that it could, if adopted internationally, supersede the present International Q Code as far as everyday amateur use is concerned.

# Tubular Condensers

## THEIR BEHAVIOUR AT RADIO FREQUENCIES

By F. R. W. STRAFFORD (Research Dept., Belling and Lee, Ltd.)

*EXAMINATION of a rolled paper-dielectric condenser would suggest that it might have appreciable inductance; an obviously undesirable property for a component to be used for by-passing RF currents. After considering the various forms of construction, the author of this article reaches the conclusion that condenser inductance is negligible compared with that of the connecting leads. Useful information on the choice of by-pass condensers is given.*

A TUBULAR paper-dielectric condenser is constructed by taking a long strip of special paper of appropriate thickness, to each side of which is attached a metal foil whose width is usually less than that of the paper. This assembly is wound into a tight roll and connections are taken out from each end of the roll. The whole assembly is usually impregnated with insulating compounds, waxes, etc., and enclosed in a cylindrical container of cardboard or similar material, the ends being sealed. Before the term "non-inductive" was applied to fixed condensers it was usual to connect to the foils at a single point only, somewhere on the length.

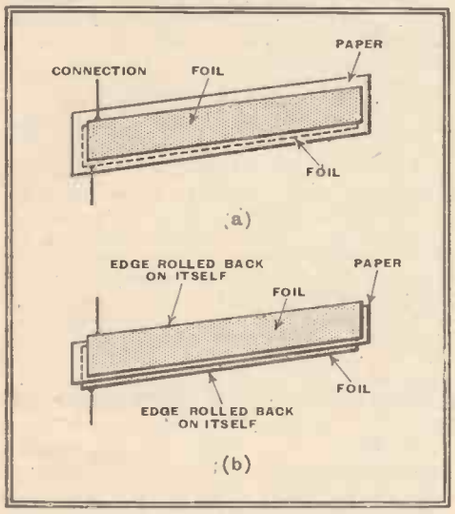


Fig. 1.—The two principal methods of condenser construction compared. Diagrams (a) and (b) show respectively the "inductive" and non-inductive types (both unrolled).

In a modern non-inductive tubular condenser this single-point connection is avoided by arranging the foils to overlap the edge of the paper so that during the winding process the edge of each foil is short-circuited back upon itself. Thus when the connection is made to the foil it may be regarded as connecting every point along the edge of the foil by a short route. Perhaps Fig. 1 will make this clear.

Now in considering radio receiver condensers of this type up to, say, 0.1 mfd. in capacity the reduction of inductance due to the connection method of Fig. 1 (b) may be considerable, but in practice the self-inductance of the condenser, whether connected by either method, is small compared with the inductance of the wires used for connection purposes, even when their length is reduced to, say, half an inch.

At first sight the reader might doubt this statement—an attitude excusable until certain somewhat obscure points are explained. It is a fact that we have a fairly long foil, perhaps six feet or more in length, rolled into a spiral, which makes us think of our textbook teaching on the enormous increase of inductance obtained by winding a conductor into a helix or spiral.

### A Fallacy Exposed

In the case of the tubular condenser it does appear at first sight that the same sort of thing will happen, but this can be disproved by the following argument.

Fig. 2 (a) depicts a conductor which may be in the form of a wire or a flat strip bent back upon itself with its inner faces nearly touching. Now if the ends A and B are the connections to the source of voltage the current flow as shown by the arrows is in opposition in each leg of the arrangement. Hence the magnetic flux is very nearly cancelled. For perfect cancellation the wires or foil would have to be infinitely thin and infinitely close to one another. If zero magnetic flux threads this circuit there must, by definition, be zero inductance in that circuit and when the flux is very small the inductance is small.

If the loop is wound into a spiral or helix, Fig. 2 (b), there is no reason to expect the inductance to increase to any appreciable extent, since there is very little increase in flux linkage.

Now let us open-circuit the end of the loop and imagine a large number of little parallel condensers to be connected between the two legs. This is shown in Fig. 3, and we now present the circuit of an unrolled paper condenser, in which each capacity may be referred to as the capacity per unit area of foil.

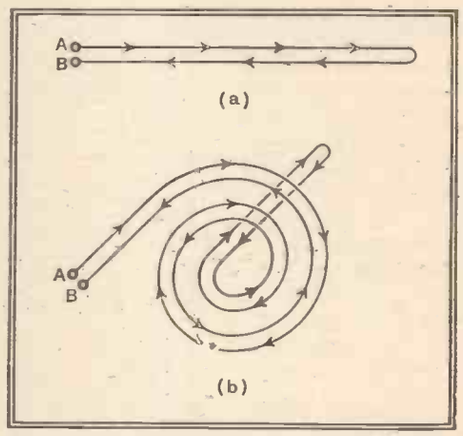


Fig. 2.—Diagram (a) shows a conductor bent back on itself; winding the same conductor into a helix, as in diagram (b), has a negligible effect in increasing inductance.

When an alternating potential is applied across A and B current will flow down each condenser circuit so that at any pair of opposite points along the foil, say at X and Y, the current will be equal and opposite. Hence the inductance will still be very small, in fact practically the same as when the loop was closed as in Fig. 2 (a). Similarly the same argument applies with regard to rolling the resultant circuit into a spiral—the inductance is inappreciably changed.

The foregoing should make it quite clear that there is no reason to expect large values of self-inductance in tubular condensers, particularly as the foils are usually separated by one- or two-thousandths of an inch, thereby providing an extremely closed form of loop and one through which very little magnetic flux can thread.

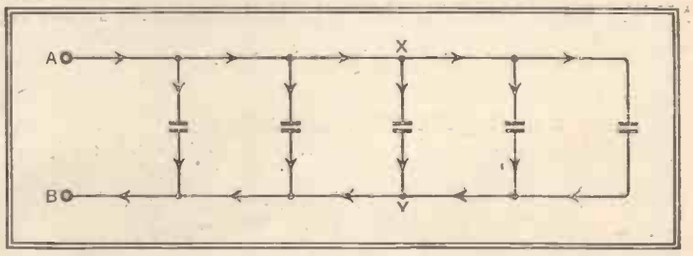


Fig. 3.—The equivalent circuit of an unrolled paper condenser.

Neglecting resistance effects in the condenser and its connecting leads, the equivalent circuit of a tubular fixed condenser (or any other fixed condenser for that matter) will be as shown in Fig. 4. C is the capacity of the condenser, L is the inductance of the foils on the condenser,

**Tubular Condensers**

and $L_1$ is the combined inductance of the two connecting leads, including the mutual inductance between them.

Careful measurements backed by calculations show that the inductance of the condenser itself is very small compared with the inductance of any connecting leads of useful length from the practical point of view. This statement holds even when the condenser is not wound in the so-called non-inductive manner, but is connected as shown in Fig. 1 (a).

It is obvious that there will be a frequency at which the inductance and capacity will resonate, and in these circumstances the impedance of the condenser between its two connecting extremities will be governed purely by the series resistance which is, of course, made up by the high-frequency resistance of the connecting leads, the resistance of the foils and the dielectric loss resistance referred in series with the condenser.

### Aid to Choosing Values

A family of curves of this resonant frequency for a range of condensers, and for lengths of leads up to 16 centimetres per head, has been prepared and is shown in Fig. 5. These curves should be very useful to designers of radio circuits and filters in that it gives the frequencies at which condensers of certain values and particular lengths of connecting leads commence behaving as inductances. In other words, a condenser should not be used at a higher frequency than the resonant frequency indicated for its particular capacity and lead length.

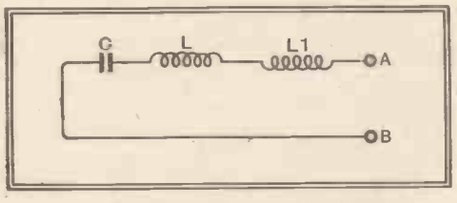


Fig. 4.—Equivalent circuit of a fixed condenser (neglecting resistance).

Instability in amplifiers employing several stages can often be traced to failure to take this fact into account, and as a general rule a condenser should not be employed at a frequency greater than half its resonant frequency as indicated from the curves.

On the other hand, if one is designing a circuit to handle one particular frequency it might be desirable to so adjust the value of capacities and lead lengths to form filter circuits of the rejector type to work at the resonant frequency of the circuit, for by this means the effective shunting value of the condenser is very much lower than would have been obtained by the calculated reactance, neglecting resistance and resonance effects.

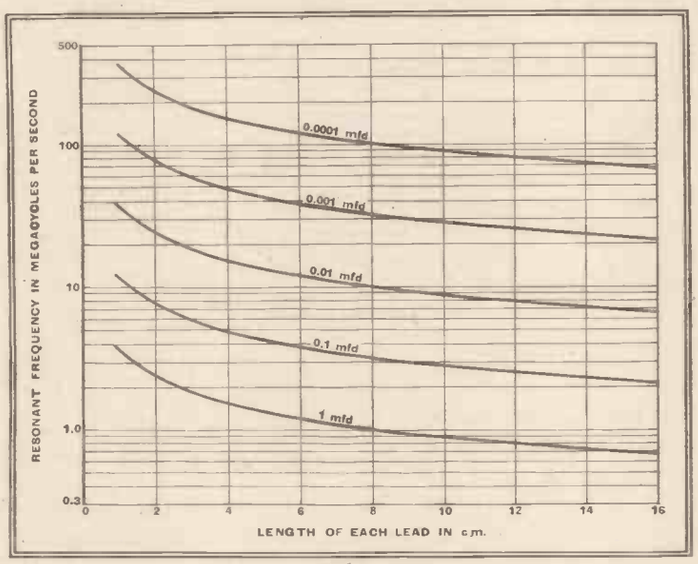


Fig. 5.—A useful guide to the choice of by-pass condensers: graph showing the resonant frequency of various capacities with 20-SWG leads of lengths up to 20 cm.

# Television Programmes

Sound 41.5 Mc/s Vision 45 Mc/s

**An hour's special film transmission intended for demonstration purposes will be given from 11 a.m. to 12 noon each weekday. The National or Regional programme will be radiated on 41.5 Mc/s from approximately 7.45 to 9 p.m. daily.**

THURSDAY, MAY 11th.

**3,** Joan Miller and Polly Ward in "Pest Pilot." **3.30,** Gaumont-British News. **3.40,** 241st edition of Picture Page.

**9,** Renée Houston and Donald Stewart in Cabaret. **9.40,** British Movietonews. **9.50-10.20,** 242nd edition of Picture Page.

FRIDAY, MAY 12th.

**3,** Charlie Kunz. **3.10,** "Foundations of Cookery," talk by Marcel Boulestin. **3.25,** British Movietonews. **3.35,** Wyndham Goldie in "Five At The George," a ghost play by Stuart Ready.

**9,** Trudi Binat—Starlight. **9.10,** "Derby Secrets," No. 4—Film. **9.20,** Marcel Boulestin. **9.35,** Gaumont-British News. **9.45,** "The Advantages of Paternity," a comedy by Horton Giddy. **10.15-10-25,** Olga Coelho in Brazilian folk music.

SATURDAY, MAY 13th.

**3,** The Jacquard Puppets. **3.15,** Gaumont-British News. **3.25,** Cartoon Film. **3.30,** "Spreading The News," a comedy by Lady Gregory.

**9-10.30,** Charles Heslop in "The Torchbearers," a satirical comedy by George Kelly.

SUNDAY, MAY 14th.

**3,** "The Conductor Speaks"—Sir Adrian Boult. **3.20,** "Derby Secrets," No. 5—Film. **3.30,** Yvette Guilbert—French diseuse. **3.40,** O.B. from the Chelsea Flower Show. The cameras will be accompanied on their tour of the exhibits by C. H. Middleton, F. H. Grisewood and Elizabeth Cowell.

**8.50,** News. **9.50-10.30,** Sybil Thorndike in "Sun Up," the play by Lula Vollmer. The scene takes place in a cabin in the mountains of North Carolina, June, 1917.

MONDAY, MAY 15th.

**2.40,** Chelsea Flower Show, O.B. **3,** "Hungarian Rhapsody"—the Hungarian State Ballet from the Adelphi Theatre. **3.30,** Gaumont-British News. **3.40,** Film. **3.50,** Eric's Wild Time. **3.55,** Cartoon Film.

**9,** Carson Robinson and his Pioneers in Cabaret. **9.35,** British Movietonews. **9.45,** "Our Rough Island Story." **10.5,** Charles Heslop—"In the Barber's Chair," No. 6. **10.15,** Cartoon Film. **10.20-10.30,** Basil Rodgers, the negro tenor with Henry Bronkhurst at the piano.

TUESDAY, MAY 16th.

**3,** Richard Hearne with Lily Palmer and George Nelson in "Take Two Eggs." **3.15,** British Movietonews. **3.25,** "In the Barber's Chair." **3.35,** "The Advantages of Paternity" (as on Friday at 9.45 p.m.).

**9,** "Take Two Eggs" (as at 3 p.m.). **9.15,** Peggy Wood—Starlight. **9.25,** Cartoon Film. **9.30,** Tennis O.B. from the Empire Pool, Wembley. Donald Budge, Ellsworth Vines, Bill Tilden and Nusslein in singles and doubles. **10-10.30,** "The Deacon and the Jewess," a play by H. F. Rubinstein.

WEDNESDAY, MAY 17th.

**3-4.30,** "The Torchbearers" (as on Saturday at 9 p.m.).

**9,** C. B. Cochran's "Night Lights" from the Trocadero. **9.40,** British Movietonews. **9.50,** Sunday in the Country. **10.10,** Cartoon Film. **10.15,** Isabelita Alonso in Spanish Songs and Dances. **10.25-10.35,** "Bridge without Sighs," in verse and cartoon by Reginald Arkell and Harry Rutherford.

# PROBLEM CORNER—19

**An extract from Henry Farrad's correspondence, published to give readers an opportunity of testing their own powers of deduction:—**

Dear Mr. Farrad,

I hope you will forgive me for writing, but I am rather worried about our wireless. I remember you helped my husband in some difficulty he had with it a few months ago. Now he is away for a few weeks on business, so I have been taking advantage of that to do the spring cleaning. Of course, we had to move the wireless into another room for a day, but I was very careful and did it myself. There is nothing very complicated to do, because we use a "mains aerial plug," and I made sure that it hadn't come out. But the reception is nothing like so good as it was, and I am afraid John—my husband—will want to know what is the matter. I got a man to examine it, but he said it was perfectly all right; so now I am writing to see if you can suggest something, for which I would be very grateful.

Yours very truly,
Mary Frickton.

*What did Henry Farrad suggest?* *See page 442.*

# Frequency Doublers

## WHY THEY ARE USED AND SOME TYPICAL CIRCUITS

By H. B. DENT (G2MC)

IT is now almost universal practice in amateur transmitting circles to employ a master oscillator with the frequency stabilised by a piezo electric crystal in order to ensure that the transmissions shall be kept within the allotted band of frequencies. The oscillations generated by this stage need not be on the working frequency of the transmitter, which may be either two, four or eight times, or a similar multiple, of that of the master oscillator.

*THE amateur wavebands are harmonically related, and so it is possible, by applying the principles of frequency doubling, to use a single quartz crystal to control transmissions on several frequencies.*

This is often a matter of convenience at working frequencies of 7 Mc/s or lower, and is only adopted if facilities are required for operation on two or more wavebands, but frequency multiplication becomes an almost essential part of the equipment when transmission is effected on 10 and 5 metres and crystal control is employed. Crystals can, of course, be obtained for direct control of a 10-metre oscillator, but they do not operate on the fundamental frequency of the crystal, but on a harmonic of it.

These crystals are very useful in portable ultra-high frequency transmitters, but for a fixed station it is often better to employ a more robust crystal. Seven megacycles is about the highest frequency for which a crystal can be ground and which is sufficiently robust for normal use, even if it is possible to obtain crystals for fundamental operation on 14 Mc/s.

It was explained in a recent series of articles on the design of an amateur transmitting station that an RF output at twice the crystal frequency can be obtained from the oscillator stage, and it was also mentioned that with only two valves in the transmitter sufficient RF power for short-distance communication could be effected on the fourth harmonic of the crystal frequency, i.e., in the 28 Mc/s amateur band.

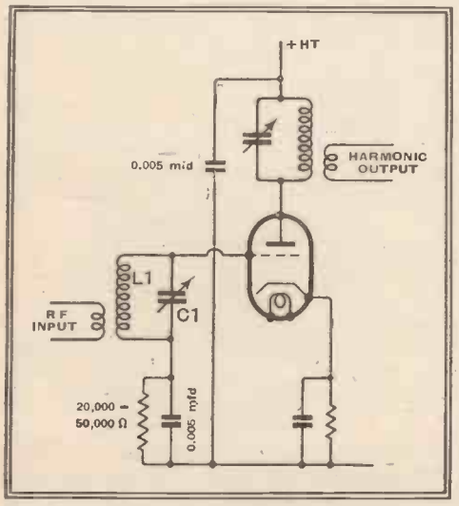


Fig. 1.—A simple frequency doubling circuit in which the anode circuit is tuned to twice the frequency of the grid circuit.

The efficiency of the output stage operated in the manner described was, however, not very high, being of the order of 30 per cent. only, as compared with 50 to 60 per cent. when it was used as a Class "C" amplifier. At 56-60 Mc/s the efficiency is even lower.

In a fixed station and where economy in valves does not have to be considered the best practice is to multiply the frequency of the master oscillator until the desired operating frequency is reached and the output can then be applied to a power amplifying stage of the Class "C" variety.

In the case of a five-metre transmitter in which a 7-Mc/s crystal is used the frequency must be multiplied eight times to reach the operating wavelength. It has been explained that with the tritet oscillator circuit an output at comparatively high power is available at the second harmonic, so that this leaves only a four-fold increase before the final amplifier.

It would be possible to quadruple the crystal frequency in the first stage, but the power in the fourth harmonic will be about one watt only; nevertheless, this might be sufficient to operate a doubling stage for a 10-watt final amplifier. This matter is actually being further investigated in view of the convenience it would afford in building a portable five-metre transmitter for field-day use.

The difficulty encountered in a five-metre transmitter is that owing to the comparatively low input impedance of most valves at these high frequencies quite a lot of driving power has to be provided to operate an RF amplifier under Class "C" conditions.

For a 50-watt output stage fitted with some neutralised triode valves the writer finds it necessary to provide about eight watts to drive the valve to full output, though considerably less will suffice if the frequency is changed from 57 to 28.5 Mc/s. It will thus be seen that the power has to be kept at a high level in the frequency doubling stages in order to avoid the need for a pre-amplifier before the final stage.

It is a good plan to increase progressively the size of the valves in the transmitter so that as the frequency is raised the power in the succeeding doubler stages also increases despite the fact that the efficiency may show a falling off at the higher frequencies.

Any circuit which in theoretical form looks like an RF amplifying stage, such as that shown in Fig. 1, can be used as a frequency doubler merely by tuning the anode circuit to twice the frequency of the grid circuit and by applying sufficient input to drive the valve into grid current.

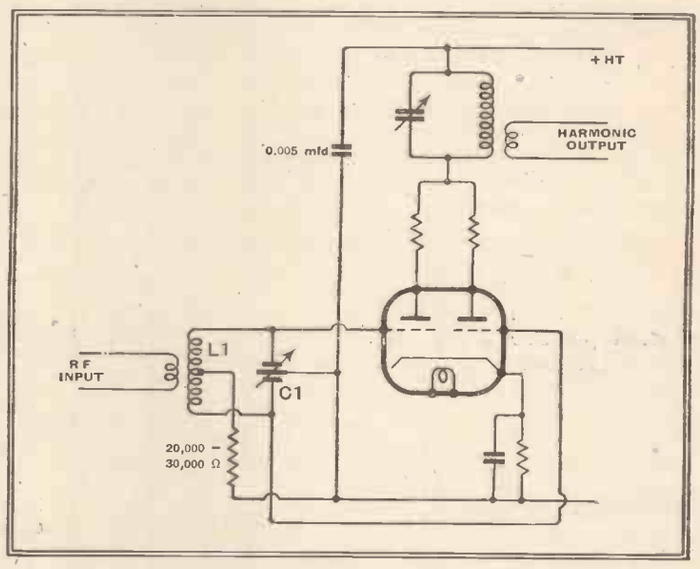


Fig. 2.—A push-pull doubler suitable for frequencies up to 28 Mc/s.

Alternatively, the grid circuit can be biased to twice or three times the "cut off" value. In either case the anode circuit should have a high L/C ratio, using only just sufficient capacity to tune to the required frequency.

Another arrangement that functions well as a frequency doubler is that shown in Fig. 2, for which either two valves, or a double triode such as the Mullard TV03-10, can be used. In the form shown it is quite satisfactory for doubling up to

**Frequency Doublers—**

28 Mc/s output. If, however, the anode circuit be modified and arranged as in Fig. 3, the RF output at the higher frequencies is improved, which is probably due to the fact that a better impedance match is effected between the valve, the circuit and the load.

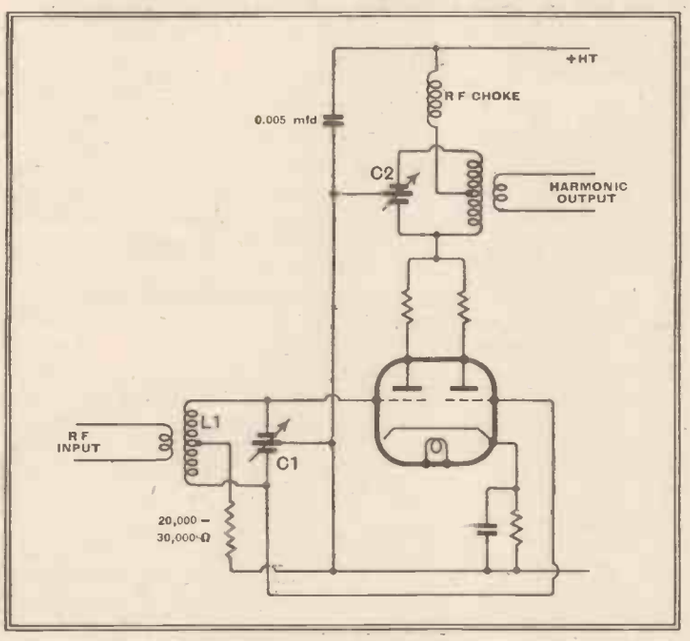


Fig. 3.—Method of modifying the circuit of Fig. 2 for operation up to the highest amateur frequencies.

The only difference is that a split stator condenser is used in the anode circuit and HT is applied through an RF choke to the centre of the coil.

In this circuit the grids are connected in push-pull, but the anodes are in parallel. It is essential to use a split stator condenser for C1 in circuits of Figs. 2 and 3, while the condenser must be mounted so that the shortest possible connections can be made between the two grids of the valve and the fixed vanes of the condenser. The earth lead should take the shortest possible path from the moving vanes of C1 to the cathode of the valve and it must be of large diameter.

Unless these precautions are taken the stage may go into self-oscillation, but such oscillations will not necessarily be at the input or output frequencies, but at a very high parasitic frequency, dependent on the length of the leads between condensers C1 and C2 and the valve and the earthing leads of C1 and C2 in Fig. 3.

Another precaution that should be taken is to connect anti-parasitic resistances of between 5 and 20 ohms close to each anode as shown in the circuits.

A vertical screen between the grid and anode circuits sometimes cures instability, but only when the self-oscillation is at either of the two operating frequencies; it will not cure parasitic oscillation.

A circuit which is proving very satisfactory as a frequency doubler from 28 to 56 M/cs and which provides sufficient output to load fully a 50-watt neutralised triode operated as a Class "C" amplifier is shown in Fig. 4.

The valve used is the Tungsram OS12/501 and its input which is at 28.48 Mc/s is provided by a push-push stage doubling from 14.24 Mc/s. The OS12/501 is connected as an RF pentode as this was found to give the best results in the writer's case; the valve has just under 200 volts on the screen grid. The screen current is about 15 mA and the anode current is 60 mA at 350 volts, with the anode circuit loaded, while the grid is biased to −120 volts. There is also a grid resistor, R1, of 10,000 ohms to provide a little extra grid bias from the rectified RF input. A very rough measurement shows that about 8 watts can be drawn from the anode circuit on 56.96 Mc/s though it may actually be more owing to the difficulty in obtaining reliable measurements at these high frequencies.

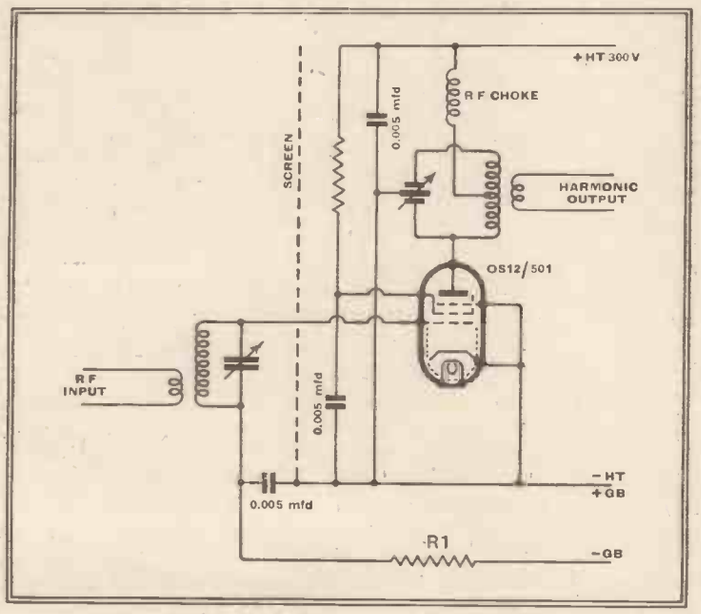


Fig. 4.—A recommended circuit for use on all the short and ultra-short amateur wavelengths.

This stage will drive a power amplifier with a comparatively low input impedance at the working frequency and give 20 mA of grid current. The grid bias for this valve is also −120 volts, while there is a grid resistor of 5,000 ohms in addition.

If this valve were used as a frequency doubler on lower frequencies, such as 7 to 14 or 14 to 28 Mc/s, lower screen and anode potentials could be used as the grid impedance of the amplifying valve would be higher and less driving power needed. This will, of course, result in a saving in HT current. No trace of instability has been encountered, though as a precautionary measure the grid and anode circuits were isolated by a vertical screen as shown in Fig. 4

Owing to the relatively small input power needed for the OS12/501 (the makers give this as 0.3 watt; the highest frequency is not stated, but it is apparently quite high as a ceramic base is fitted), it would appear to have great possibilities as an RF power amplifier on five metres. This matter is certainly well worth investigating.

## Something New in Car Aerials

THE problem of an efficient aerial for the car radio set is one that has engaged the attention of inventors ever since car radio itself first made its appearance. There can be little doubt that for efficiency, one of the best arrangements that could be employed would be a vertical rod rising from the roof, as not only would it be a better collector of signals, but it would be comparatively remote from the ignition system.

A vertical rod of the type mentioned is an obvious impracticability where cars have to pass under low archways or bridges, and, although many devices have been put forward, including rods which can be lowered manually, none has been entirely satisfactory. A new device developed in the laboratories of the Telefunken Company does, however, seem to fill the bill. It is, in effect, nothing more or less than a thick-walled rubber tube which is tapered and rather resembles a rolled umbrella, mounted vertically on the roof.

Inside this rubber tube is secured a flexible aerial wire. When any overhead obstruction is encountered, it pushes over the whole contraption to a position parallel with the roof. Immediately the obstruction is passed the rubber tube springs into its normal vertical position once more. Arrangements are made whereby the tube is fastened to the roof in an exceptionally simple manner. An insulating bush projects slightly from the roof, and the lower portion of the tube, which is completely hollowed out, is pulled over this bush in the same manner as the rubber covering on the handle of a cricket bat.

This arrangement has obviously still greater possibilities in the case of a vehicle fitted with a U.S.W. transmitter.

## NEW ADDRESS

IN connection with the review on page 429 of the last issue of the Model 60 signal generator made by Taylor Electrical Instruments, Ltd., it should be noted that the new address of the company is 45, Fouberts Place, London, W.1.

# Orchestral Pitch

## A CATHODE-RAY METHOD OF MEASUREMENT DURING A CONCERT

By BALTH. van der POL, D.Sc., and C. C. J. ADDINK

(Natuurkundig Laboratorium, N. V. Philips' Gloeilampenfabrieken Eindhoven, Holland).

*THE efforts which are being made to establish a new international standard of pitch should be materially assisted by these scientific measurements made during the course of recent broadcast performances.*

FROM September 27th to December 31st, 1938, a series of about 530 observations was made regarding the tuning of musical instruments and orchestras as observed in radio programmes. For this purpose a new, sturdy, entirely AC mains-operated measuring instrument was constructed containing a string kept in vibration by electrical means whose frequency was accurately adjustable between 400 and 470 c/s. By comparison with a chronometer and a synchronous motor the relative and the absolute calibration could be carried out to a precision of 0.2 c/s.

The method of observation was as follows: A frequency band of roughly 400-470 c/s was filtered out of the incoming music voltage. (For comparison, it may be noted that for $a = 440$ c/s we have $a$ flat $= 415$ c/s and $a$ sharp $= 466$ c/s.) The voltage allowed to pass in this frequency region was applied to the "grid" of a cathode-ray oscillograph, so that the spot was only visible when a note within this frequency band was present in the music. At the same time the alternating voltage developed by the vibrating string was applied to the deflection plates of the cathode-ray oscillograph in such a way—by a 90-degree phase shift between the two pairs—that a circle was described by the spot with an angular frequency equal to that of the measuring apparatus. A part of this circle was therefore only visible when approximately the same frequency was present in the music as that of the reference frequency.

When there was slight difference between these two frequencies the arc of the circle visible on the screen turned either to the left or the right at a frequency equal to the difference between the music frequency and the frequency of the measuring apparatus. The latter was then adjusted in such a way that when during the music the arc became visible it was also almost stationary. The frequency $a$ of the music could thus be read on the dial of the measuring apparatus. In this way the frequency of the note $a$, originating, for instance, from an organ stop, could be measured accurately to within $\pm 0.2$ c/s, whilst, owing to the continuous fluctuation in the tuning, an accuracy of $\pm 0.5$ c/s could be attained for orchestral instruments.

*Analysis of the Mengelberg Concert on October 27th, 1938.*—On this occasion Beethoven's first piano concerto was played. During the tuning of the orchestra the predominating tuning was 441 c/s, whereas the piano was at 440 c/s; the orchestra had a tendency in the *tutti* to take the $a$ 2 c/s higher, but it dropped 2 c/s again when the piano set in. After the interval a Brahms' symphony was played. During the tuning of the orchestra 443 c/s was noted, during the first part of the concert 444 c/s (horn) was found, whilst four minutes later 441.5 c/s was found as the mean value of all the instruments. During the second part of the symphony 442 c/s was found for the horn; afterwards a mean value of 442.5 c/s was found. The average for the string instruments in the third part of the symphony was 442.5 c/s, whilst at the climax towards the end the horns gave a predominating value of 443 c/s.

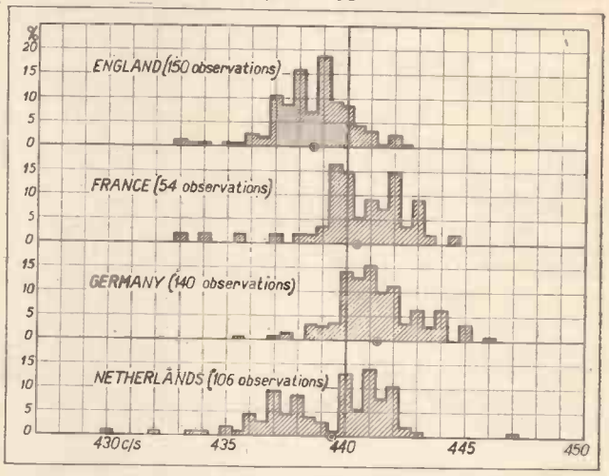


Graphs showing the "scattering" of pitch in the broadcast programmes of four countries from Sept. 27th to Dec. 31st, 1938. The vertical scale represents the percentage of occurrence of the various frequencies.

*Concert given by the Municipal Orchestra, Birmingham, October 27th, 1938 (oboe concerto with orchestra—and piano—of Bach).*—The tuning of the string instruments before commencement of the performance was 440 c/s; during the performance the value found for the piano was 435.5 c/s. During ensemble the orchestra dropped to the tuning of the piano. Later the orchestra, without the piano, rose to 438.5 c/s; at that moment the tuning of the oboe was 439 c/s. It was, furthermore, found that *generally* the wind instruments suddenly dropped about 2 c/s at the end of a long sustained note. Also, particularly, singers seem rather un-

**PERMANENTLY TUNED INSTRUMENTS** (pianos, organs, etc.).

| | Number of observations | Mean frequency (c/s) | Max. observed frequency (c/s) | Min. observed frequency (c/s) |
|---|---|---|---|---|
| England ... ... | 75 | 438.0 | 442 (piano, Nov. 9th) | 433 (concert-organ, Dec. 16th) |
| France ... ... | 40 | 439.9 | 443.5 (piano, Sept. 28th) | 430 (organ St. Eustache, Dec. 29th) |
| Germany ... ... | 58 | 440.8 | 445 (piano, Nov. 22nd) | 435.5 (harp, Dec. 7th) |
| Netherlands ... | 53 | 437.9 | 443 (V.A.R.A. organ, Dec. 5th) | 430 (organ St. Vitus' Church, Hilversum, Dec. 23rd) |
| **ORCHESTRAS** | | | | |
| England ... ... | 75 | 439.0 | 442.5 (string sextet, Dec. 27th) | 434 (harp trio, Dec. 28th) |
| France ... ... | 14 | 442.0 | 444.5 (orchestra, Dec. 15th) | 441 (orchestra, Dec. 28th) |
| Germany ... ... | 82 | 441.5 | 446 (string orchestra, Dec. 23rd) | 438.5 (orchestra (amusement), Oct. 24th) |
| Netherlands ... | 53 | 440.6 | 447 (V.A.R.A. "Kingler trio" Nov. 4th) | 436 (V.A.R.A. "Fantasia," Dec. 28th) |

**PERMANENTLY TUNED INSTRUMENTS AND ORCHESTRAS** (total for both together).

| | Number of observations | Mean frequency of all observations (c/s) | Max. observed frequency (c/s) | Min. observed frequency (c/s) |
|---|---|---|---|---|
| England ... ... | 150 | 438.5 | 442.5 | 433 |
| France ... ... | 54 | 440.4 | 444.5 | 430 |
| Germany ... ... | 140 | 441.2 | 446 | 435.5 |
| Netherlands ... | 106 | 439.3 | 447 | 430 |

**Orchestral Pitch—**

certain in the matter of accurate tuning.

The foregoing analyses show that the method of measurement employed has the advantage both of accuracy and rapidity of measurement; a constant tone of a duration of ½ second generally suffices to make the frequency measurable.

In the accompanying table we give the results of measurements as regards the extreme and the average tuning observed at performances in England, France, Germany and the Netherlands. Separate data are given for permanently tuned instruments and orchestras. The mean frequencies of all observations are: England, 438.5 c/s; France, 440.4 c/s; Germany, 441.2 c/s; and the Netherlands, 439.3 c/s.

Finally, in the series of graphs the ordinates present the percentage of occurrence of the frequencies given by the abscissæ, thus yielding a general impression of the scattering of the data.

# The Montreux Plan

## SOME ASPECTS OF THE NEW CONVENTION

ALTHOUGH the full text of the Wavelength Plan, which was evolved at the Convention Européene de Radiodiffusion, Montreux, which ended on April 15th after nearly seven weeks' duration, has not yet been published by the U.I.R., *The Wireless World* is now able to give some interesting facts gleaned from the Plan.

The European Zone which is embraced by the Plan has as its borders in the north and west the normal European boundaries. In the east it is marked by the 40th meridian of longitude, and in the south by the 30th parallel of north latitude. Thus it includes part of Asia Minor and all the Mediterranean coastal countries.

It is now learned that all the participating countries signed the Convention, but the following five signed with reservations:—Luxemburg, Iceland, Turkey, the U.S.S.R. and Greece. This means that Luxemburg, which has been allocated the 218.2-metre wavelength, which it is to share with two Estonian and a Greek station, will probably continue as a pirate on the long-wave band. Iceland is discontented over the fact that she has to share 1,453 metres (206.5 kc/s) with Turkey and the U.S.S.R., and may therefore use an alternative. Turkey, too, is disgruntled over the same matter.

Although the representatives of the telegraph administrations and broadcasting organisations of the various countries have signed the Convention, it still remains for the Governments concerned to ratify the undertakings through the usual diplomatic channels to the Swiss Government.

The Convention will continue to apply to all matters relative to broadcasting in Europe until such time as a new Plan is evolved, which can be effected by ten of the contracting Governments expressing to the Swiss Government their wish for a revision.

Although it is not yet known what attitude will be adopted regarding wavelengths by the five countries who signed with reservations, it is interesting to see who, according to the Plan, will be our neighbours. Droitwich (198.5 kc/s), whose power it is proposed to raise from 150 to 200 kW, will have on the one side Deutschlandsender (189.5 kc/s), whose power is to be raised from 60 to 200 kW, and on the other Ankara (120 kW), Reykjavik (100 kW) and Minsk (50 kW) sharing 206.5 kc/s.

As has already been pointed out the geographical position of Great Britain makes it possible for her to share wavelengths with other countries which would be impracticable for central European states. On the medium-wave band, therefore, we have only two exclusive frequencies, namely, London Regional (916 kc/s), the power of which is to be increased from 70 to 120 kW, and Midland Regional (1,087 kc/s). The channels on either side of London Regional are to be shared by Lwów (50 kW) and a projected 1-kW Spanish station and by two Germans, Graz (15 kW) and Klagenfurt (5 kW). Midland Regional has on one side Bratislava, the power of which may be raised to 120 kW, and on the other Heilsberg (120 kW), Lisbon (20 kW) and Alexandria I (5 kW). The main points about the nine non-exclusive channels allocated to Great Britain are that they are, without exception, shared with stations of lower power.

### Directional Aerials

For the first time in the allocation of shared wavelengths directional aerials have been taken into consideration. In all, some thirty stations have been allocated wavelengths with the stipulation that they use aerials directed in a certain quarter or alternatively use an aerial which reduces the indirect wave in a certain direction.

The only British stations affected by the directional aerial stipulation are Start Point and the projected relay transmitter at Norwich. Start Point, of course, already has an aerial which reduces radiations to the south, and Norwich must use an aerial reducing radiations to the N.E. and S.E.

Among the stations which are to use directional aerials the following are of interest:—Toulouse P.T.T., 825 kc/s (363.6 metres), must use an aerial reducing radiations to the N.E.; the 17 kW Saarbrucken transmitter (1,321 kc/s), the power of which it is proposed to raise to 120 kW, must reduce radiations to the S.S.W.; and Radio-Normandy, which has been allocated 1,420 kc/s (211.3 metres), the Yugoslavian common wave, must reduce radiations to the E.S.E.

Certain stations have been notified that if they are informed by a coastal station that their transmissions are affecting ship-to-shore traffic they must cease transmission at once. The frequencies so classified are 260 kc/s (1,154 metres), which is shared by four Norwegian stations (Bergen I, Hemnesberget, Oslo, and Tröndelag); 355 kc/s (845 metres) Bergen II; and 518 kc/s (579 metres) shared by three Germans (Innsbruck, Nürnberg, and Salzburg) and two Norwegians (Vest-Telemark and Hamar).

### Power Limitations

If the following stations wish to increase their projected day or alternatively night power they must use aerials reducing radiation in certain directions:—Madona (50 kW), Latvia; Smolensk (10 kW), U.S.S.R.; Odessa (10 kW), U.S.S.R.; Fredrikstad (1 kW), Norway, and Helsinki I (60 kW night power), Finland.

Power limitations have been imposed by the Convention. As was proposed long-wave stations will be permitted to use 500 kW by day and 200 kW at night. Medium-wave stations are divided into three categories: Between 192.3 and 200 metres, 10 kW; between 200 and 230.8 metres, 30 kW; and between 230.8 and 1,250 metres, 120 kW. Stations operating on a national common wave are limited to a power of 5 kW, whilst the aggregate power of stations working on such a wavelength must not exceed 10 kW. There are two types of international common wave, on one of these power is limited to 2 kW and on the other to 0.2 kW.

In the official Plan there are very, very many blanks in the columns showing the maximum day and night power, which apparently means that the stations will not recognise a definite maximum.

With such a gargantuan task before the Conference as that of accommodating a further 103 stations, bringing the total number to 373, in the already overcrowded medium- and long-wave bands, the general result is surprisingly satisfactory. Listeners must now "wait and see" what happens when the Plan becomes operative at one minute past midnight G.M.T. on the night of March 3rd-4th, 1940.

## HENRY FARRAD'S SOLUTION

(See page 438)

ASSUMING that "the man" was correct in pronouncing the set in order, the most probable cause of inferior results lies in the fact that reception by mains aerial often depends to a considerable extent on which way round the mains plug is inserted. Mrs. Frickton would not know anything about this, and would not have paid particular attention to the matter. Henry Farrad, therefore, suggested that she try reversing the plug.

# Frequency Modulation in America

## ANTI-NOISE BROADCASTING UNDER TEST

*OUR American correspondent has been given special facilities for investigating the working of frequency modulation by Major Edwin H. Armstrong. We are also indebted to Major Armstrong for having "vetted" the manuscript of this article.*

BY OUR NEW YORK CORRESPONDENT

NEARLY a dozen frequency modulated broadcasting transmitters with power ratings up to 50 kilowatts are at present under construction in the north-eastern states of the U.S.A. All of these employ the methods of Major Edwin H. Armstrong. The stations are owned by various organisations, but in each case the management is well experienced in broadcasting and has turned to frequency modulation only after studying the results of extensive field tests. This is accordingly not a mushroom growth. It may instead be a first step towards a reorganisation of American (and possibly European) broadcasting methods to attain advantages which justify the cost of new receivers—receivers which are deaf to most electrical noise and not susceptible to the commoner sorts of fading, but capable of reproducing with extreme fidelity all that which goes into the transmitting microphone. Your correspondent is painfully aware of a tradition that we Americans are given to bragging. Therefore, he has been at some pains in the following paragraphs to avoid any claims which have been contradicted by published matter or by statements of the various engineers interviewed, these men being chosen for the deliberate purpose of obtaining adverse views.

The Armstrong method of frequency modulation was announced about four years ago. It is based upon the concept that a radio receiver can be protected from most electrical noises if it can be made to ignore voltage changes at the grid of the first valve. Of course, the noises arrive at that grid as voltages. However, if the receiver is made deaf to voltage changes it also becomes deaf to ordinary broadcast signals, since these contain the desired sounds only in the form of changing voltages; that is, the radio-frequency energy stream (carrier), before it left the sending station, was moulded or modulated so that its voltage varies from instant to instant "in a sound-frequency manner." Since these variations are not apparent to a voltage-deaf receiver resort is had to a transmitter which sends forth *constant* carrier energy. The sounds are then imposed upon the carrier-stream in the form of variations in its *frequency;* that is, by "wobbling" instead of "moulding." The extent of the wobble represents the loudness of the sound to be conveyed, the rapidity of the wobble represents the sound pitch. Now, by giving the receiver the ability to perceive frequency changes it again becomes useful, though still deaf to voltage changes—among which reside the noises. The process is not perfect, of course, but in daily practice it approaches the ideal so closely that Armstrong receivers can operate virtually noiselessly when run "wide open" for the purpose of bringing up weak signals which, with ordinary transmission and reception, would be spoiled by noise. This statement will be made more specific in a later paragraph.

Objections were instantly raised to the original Armstrong system, whose history has indeed been one of critical re-examination by Major Armstrong himself and by other investigators. The matter is not simple and there are honest differences of opinion. However, much of the original doubt has been removed. The bogy of a transmitter "requiring a band width of 150 kilocycles" has turned out to be rather baseless for reasons to be explained later. Somewhat similar reasons exonerated the Armstrong receiver from the noise acceptance traditionally inherent in broad-band receivers. The so-called "prohibitive complexity" of the Armstrong receiver has been whittled down until there is a perfectly practical 6-valve type—though the 12- and 15-valve types are naturally better. However, the toughest of the traditions remained in the form of a sturdy conviction that Armstrong transmission was a short-range affair, not of

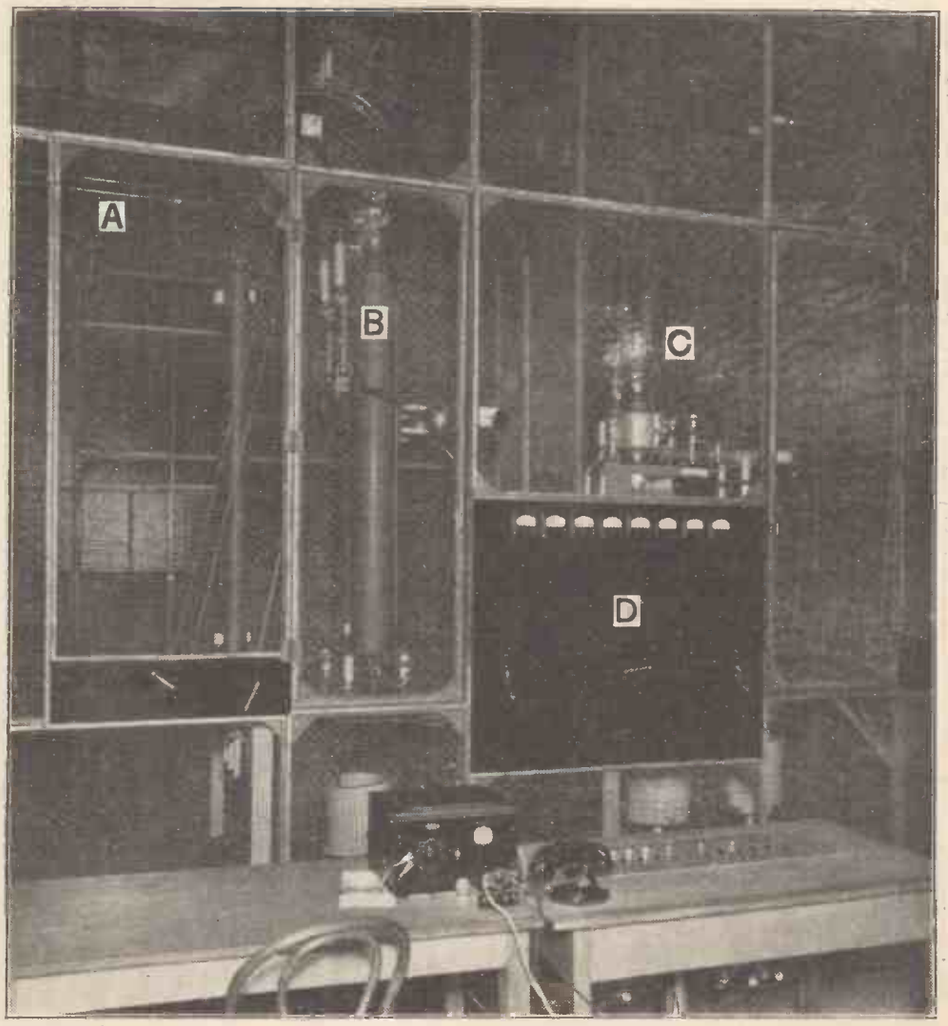


The last two stages of the W2XMN transmitter. A, input line from earlier stage. B, push-pull driver stage. C, push-pull output stage. D, meters for the two final stages; their needles remain quite stationary during operation.

# LAYOUT OF THE 40-kW FREQUENCY-MODULATED TRANSMITTER

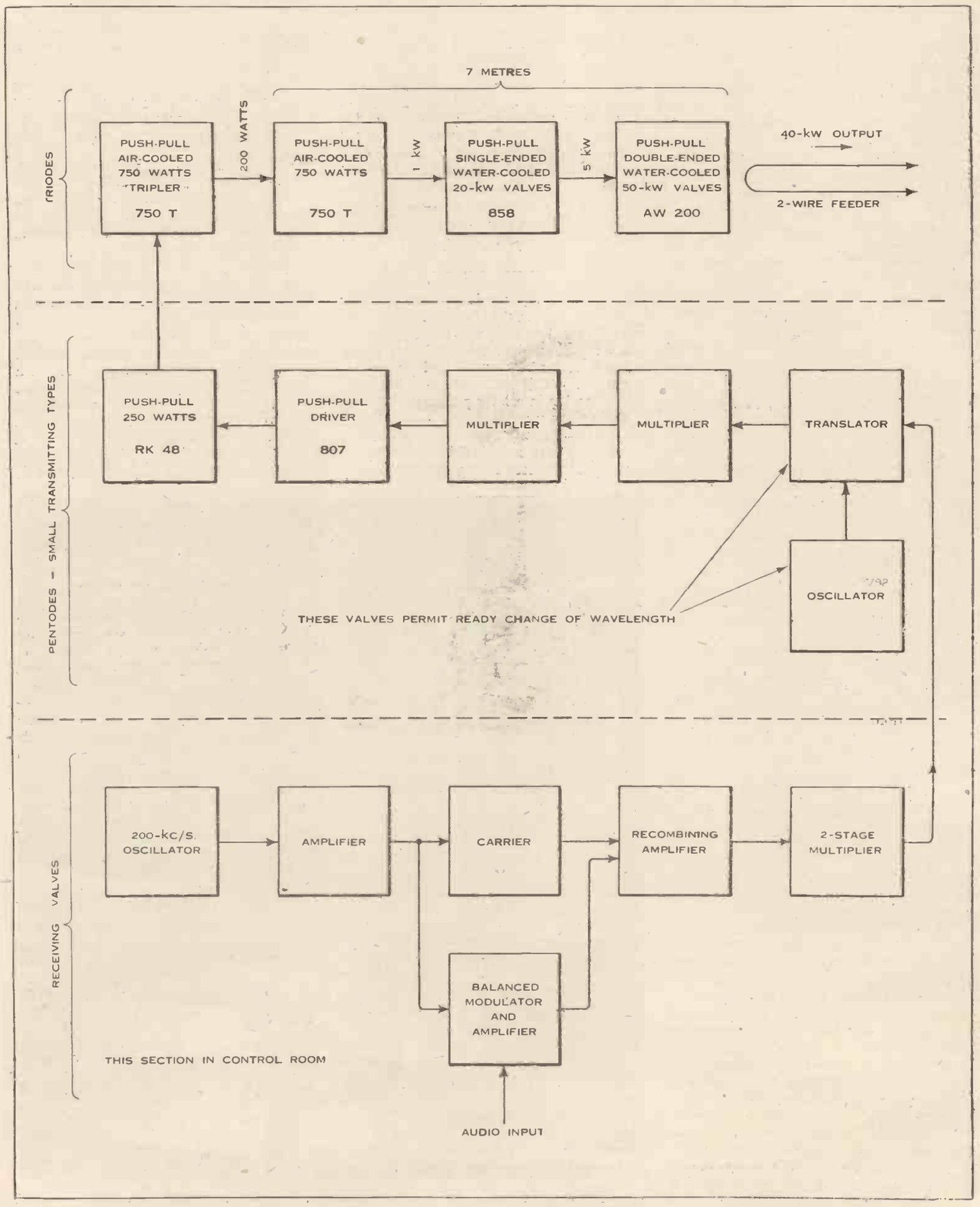


This block diagram shows the functions of the various stages of the experimental Armstrong station at Alpine, New Jersey

**Frequency Modulation in America—**

serious concern to a practical broadcaster—this despite the evidence in the original descriptive paper of 1935.

It became necessary to make a full-scale demonstration, and this is being done daily by the new 40-kilowatt Armstrong-modulated station W2XMN at Alpine, New Jersey, about fifteen miles from the centre (Columbus Circle) of New York City. This station, working at a wavelength of approximately 7 metres, and employing only half its rated power, is being compared with four different 50-kilowatt stations in the same area, each being the head station of a broadcasting chain. They are the rather elderly WEAF of the National Broadcasting Company Red network, working into a "T" antenna at 660 kc/s; WJZ (N.B.C. Blue network) operating with a modern vertical radiator at 760 kc/s; WABC of the Columbia Broadcasting System, at 860 kc/s; and WOR of the Mutual System, with a directional array aimed along the coast at 720 kc/s. Four of these five stations have very large radial earthing systems: W2XMN has none and needs none; also it has a further advantage conferred by 40-Mc/s operation—strong concentration of radiation into the horizontal plane is possible with a reasonably compact aerial array of "turnstile" type. The power gain at Alpine without resorting to a directional system is about five times. This is accomplished by fourteen dipoles, of which seven are in a vertical north-south plane, the other seven in a vertical east-west plane. The vertical mast forming the axis of the turnstile is supported between the top two cross-arms of a 400ft. tower standing at the top of the 500ft. cliff which forms the west bank of the Hudson River. The ability to utilise such a location is peculiar to frequency modulation. Were a conventional station to be located here no ground net could be provided. Even a 7-metre station working with 40 kilowatts might be impractical, if modulated in the usual manner, because of the overloading of nearby receivers. With the Armstrong system, however, receiver overload is hardly a problem. The transmitter of W2XMN is exceptionally simple in appearance. As shown by the block diagram most of the stages are quite small. The tuned circuits of the two watercooled stages are of the tubular variety, hence less formidable than the usual coil-and-condenser combinations.

### Technical Features

Most striking of all, every meter stands quite still; there are no amplitude variations. This permits running all the valves (except a few cheap receiving tubes) in pure Class "C" telegraph fashion, materially raising the efficiency, which approaches 50 per cent., even for the large final-stage tubes. Offhand, one is surprised that no broadening resisters appear on the tuned circuits—it is hard to escape the "great band width" idea—but after all the band width is well under half of 1 per cent. of the carrier. The station goes on the air with less than the normal hang-fire, and there is, of course, complete absence of the usual complaints from the power supply system since all the magnetic cores carry steady loads. The only disturbance is due to the air blasts cooling the glass seals of the final stage.

The line-of-sight range of the W2XMN

The small aerial can just be seen between the upper arms of the tower of the Armstrong station at Alpine.

antenna is about 35 miles, hence the main interest is in effects beyond that distance. At Bridgeport, Connecticut, 45 miles distant, the measured field-strength varies from 100 microvolts per metre upward. The 100-microvolt location is at the plant of the General Electric Company, where electrical shop noise is severe; moreover, a nearby steep hill is constantly being climbed by buses and trucks. Although the W2XMN signal here is 1/20th of the strength considered necessary in a quiet residential district for conventional modulation, virtually no noise has ever been heard on W2XMN except during two brief fades. No selective fading has been perceived. Several of the 50-kW stations cited before suffer from severe selective fading; all are subject to noise and interference, while ordinary fading is common.

Through the courtesy of Major Armstrong your correspondent spent an evening at Sayville, L.I., 50 miles from W2XMN and about the same distance from W2XCR, the 600-watt, 110-Mc/s Armstrong-system station of C. R. Runyon. The field of W2XCR has not been measured, but it is improbable that the signal at Sayville is ever as strong as 20 microvolts per metre—that is to say, 1/25th the value regarded as suitable for good reception with conventional modulation in quiet rural locations. On the evening of the test, conditions were such that a signal of 500 microvolts would have been utterly useless. Using an up-to-date high-fidelity receiver, it was possible to make very little use of the 50-kW signal of WABC at 55 miles, and then only by severe use of the tone control. Selective fading of WABC was bad. Even the 50-kW WEAF at 24 miles was frequently blotted out by crashes. Switching to the 42-Mc/s signal of W2XMN instantly and completely blotted out the atmospherics, though the signal field-strength was perhaps 90 per cent. less. Moreover, the fidelity of reproduction was very much better. Switching to the 110-Mc/s, 600-watt signal of W2XCR accentuated the contrast, for the atmospherics were still completely absent and there was no sign of fading. When the station was not modulating, it was possible to find a "background" at maximum receiver sensitivity, though this was not the usual uproar, but a light sound as of a very small steam leak. This is characteristic. Motor cars passing the house produced a mild patter, audible only if there were no speech, and then only for a few seconds.

### Long-range Reception

The potentialities of the transmitter at W2XMN is by no means exhausted at distances of 50 miles. At East River, Connecticut (85 miles), the carrier is strong, and very fair speech has been derived from it with makeshift receivers unsuited to the job. At points near Philadelphia (about 100 miles) the W2XMN signal has, by the testimony of numerous observers, been consistently fadeless and noiseless, although WOR and WABC (both nearer) are at times severely affected. At Schenectady, N.Y., roughly 120 miles from the station, much listening has been done by employees of the General Electric Company. Very good results are usually obtained despite the intervention of the numerous spurs of the Catskill Mountains.

**American Broadcasting Stations Using Armstrong Modulation Now in Operation or Under Construction**

| STATION | OWNER | AERIAL POWER |
|---|---|---|
| Alpine, N.J. | E. H. Armstrong | 20-40 kW. |
| Washington D.C. | Jansky and Bailey | 1 kW. |
| Mount Washington, N.H. | Yankee Network | 2 kW. |
| New York, N.Y. | J. V. L. Hogan | 1 kW. |
| Storrs, Conn. | D. A. Noble | 100 watts |
| Rochester, N.Y. | Stromberg-Carlson* | 2 kW. |
| Meriden, Conn. | Doolittle Radio Corp. | 1 kW. |
| Schenectady, N.Y. | General Electric | 10 kW. |
| Pittsburgh, Pa. | Westinghouse | 10 kW. |
| Springfield, Mass. | ,, | 1 kW. |
| Worcester, Mass. | Yankee Network | 50 kW. |
| Yonkers, N.Y. | C. R. Runyon | 600 watts |

* Licence applied for.

It thus appears that W2XMN has a service area which is at least comparable to the best of our present conventional stations, even when conditions are favourable.

**Frequency Modulation in America—**

Under adverse conditions W2XMN is superior.

It is difficult to comment on fidelity of transmission when the basis is simple listening and the same speaker is not used on both signals. However, it is fair enough to say that the Armstrong receiver and its speaker gave forth a product I have not heard equalled by any other radio receiver.

This is by no means due solely to the use of high-quality audio circuits, though it is quite true that these are "flat" to 16,000 cycles (sender, receiver, and loud speaker). Normally, such systems are useful only at very short ranges or under exceptionally favourable conditions. But here was quite another matter—a half-kilowatt station 50 miles away, an evening so noisy as to ruin conventional reception, yet in the living-room at Sayville there was undisturbed *silence* when the microphone at Yonkers was cut off. There were no valve noises, there was nothing at all but the patter of rain on the window. It was astonishing. Nor did listening with the ear to the loud-speaker grille disclose much more. It was by long odds the quietest radio circuit your correspondent has listened to, despite its broad response.

### Realistic Reproduction

The perennially difficult piano, the sound of pouring from a bottle into a glass, the tearing of paper, all were reproduced extremely well. The lighting of a safety match "came through" surprisingly well. Finally, the circuit was made two-way by telephoning to Yonkers—we speaking by wire, and Mr. Runyon by radio. The illusion that Mr. Runyon was in the room was very strong.

It may be argued that interference is eliminated principally by the use of 7 metres, not by the method of modulation. This is partially correct, but 7-metre interference is an actuality, and 7-metre motor car interference is extremely real. There is also fluctuation noise, which in some conventional 7-metre receivers is very bad, its source being principally the thermal agitation in the first coil of the set. (At shorter wavelengths the gain of the first valve is poor, and the shot noise in its anode circuit may rise above the input coil noise.) In any method of transmission a sufficiently strong carrier will swamp noise—any special merit must hinge on ability to do this with a weak carrier. In some measurements made by the General Electric Company, and reported to an informal gathering at Columbia University on March 22nd by G. W. Fyler and J. A. Worcester, it was found that for one particular receiver tested on a signal generator which could be modulated by either method the threshold of improvement of the signal/noise ratio (for fluctuation or receiver noise) was reached with a weaker carrier when frequency modulated. For any particular carrier strength the signal/noise ratio was more favourable by 20 to 25 db. when using Armstrong modulation. This is an inherent advantage, but its magnitude depends among other things upon the width of the frequency swing and also upon the type of noise encountered.

*(To be concluded.)*

## In Next Week's Issue

THE WIRELESS WORLD

# DC Mains Super

### A Three-band Receiver for DC Operation

DESIGNED especially for use with *The Wireless World* DC Quality Amplifier, this new receiver is a superheterodyne covering the important wavelengths in the bands of approximately 16-45 metres, 200-550 metres, and 1,000-2,000 metres. One RF and one IF amplifier are used with a triode-hexode frequency-changer, and a diode detector and AVC source. No AF amplifier is provided here, since the detector output is intended to feed into the DC Quality Amplifier.

There are two signal-frequency tuned circuits to afford good second-channel rejection, and the RF stage ensures a good signal-noise ratio. In the interests of quality of reproduction a simple form of variable selectivity is provided.

Tested with the amplifier the receiver gave outstandingly good quality of reproduction, and yet possessed adequate sensitivity and selectivity for all ordinary purposes. The hum level was so low as to be non-existent.

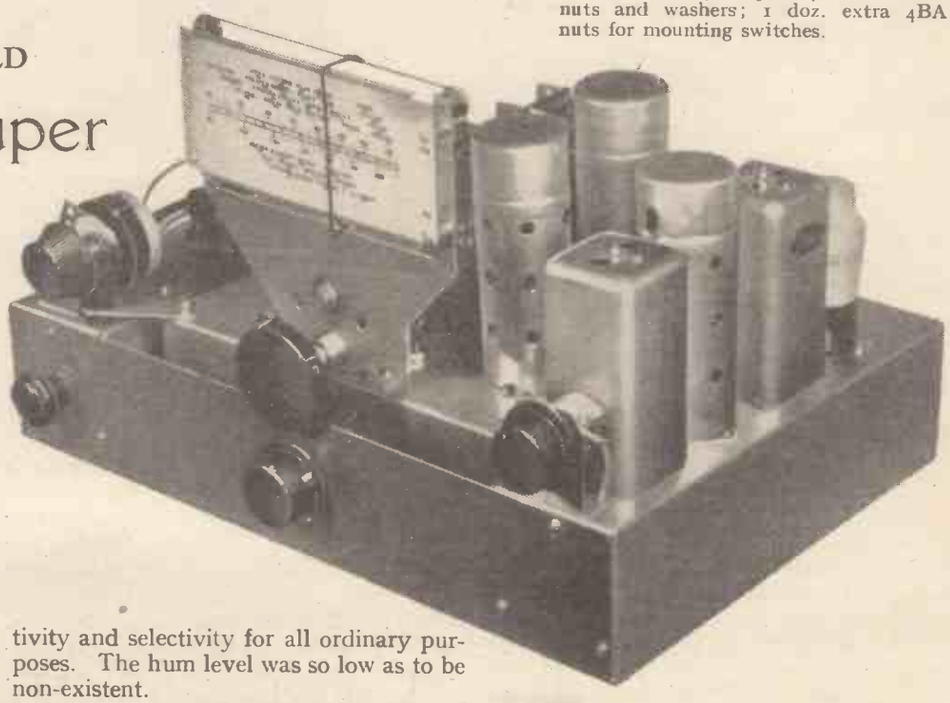

### LIST OF PARTS

| | |
|---|---|
| 1 Condenser, 3-gang, 0.0005 mfd. | Polar C1703 |
| 1 Dial, ratios 10:1 and 50:1 | Polar "Micro Horizontal Drive" |
| 9 Trimmers, 30-60 mmfds. | Bulgin SW122 |
| 1 Trimmer, 3,000 mmfds. | Bulgin CP7 |
| 1 Double Trimmer, 150-550 mmfds. | Polar 55 |
| 1 Set of Coils, PA1, PA2, PA3, PHF1, PHF2, PHF3, PO1, PO2, PO3 | Wearite |
| **Fixed Condensers:** | |
| 1 0.0001 mfd., mica | T.C.C. "M" |
| 1 0.0002 mfd., mica | T.C.C. "M" |
| 2 0.0003 mfd., mica | T.C.C. "M" |
| 1 0.0005 mfd., mica | T.C.C. "M" |
| 1 0.001 mfd., mica | T.C.C. "M" |
| 1 0.002 mfd., mica | T.C.C. "M" |
| 2 0.01 mfd., mica | T.C.C. "M" |
| 1 0.05 md., tubular | T.C.C. 341 |
| *18 0.1 mfd., tubular | T.C.C. 341 |
| **Resistances:** | |
| 3 300 ohms, ½ watt | Dubilier F½ |
| 6 500 ohms, ½ watt | Dubilier F½ |
| 1 10,000 ohms, ½ watt | Dubilier F½ |
| 2 50,000 ohms, ½ watt | Dubilier F½ |
| 1 75,000 ohms, ½ watt | Dubilier F½ |
| 1 100,000 ohms, ½ watt | Dubilier F½ |
| 2 1 megohm, ½ watt | Dubilier F½ |
| 1 9,000 ohms, 3 watts | Dubilier F3 |
| 1 10,000 ohms, 2 watts | Dubilier F2 |
| *1 Volume Control, 0.25 megohm, tapered | Reliance "SG" |
| 4 Valve holders, octal type | Clix X218 |
| 1 IF transformer, variable selectivity, 465 kc/s | Varley BP124 |
| 1 IF transformer, 465 kc/s | Varley BP122 |
| 6 Terminals, ebonite shrouded, A, E, PU (2) Output (2) | Belling-Lee "B" |
| 1 Connector, 4-way | Bryce 5C2 |
| 1 Cable, 4-way | Goltone R36/4MR |
| 1 Switch, rotary type, SPDT | Bulgin S92 |
| 1 Switch, rotary type, DPDT | Bulgin S114 |
| 1 Switch assembly comprising: 3 switches, 3-way, SP | Peto-Scott 632FE |
| 3 switches, 3-way, SP with earthing plates, locator and 8-inch rod | |
| 1 Length screened sleeving | Goltone |
| 3 Valve screens, octal type | Peto-Scott |
| 1 Shaft coupler, ¼-inch | Bulgin 2005 |
| 3 Grid clips, octal type | Bulgin P96 |
| Tuner Chassis | Peto-Scott |
| Receiver Chassis, with brackets | Peto-Scott |
| Miscellaneous: 8 lengths systoflex, 3 ozs. No. 20 tinned copper wire. Screws: 5 doz. 6BA ¼in. r/hd., 2 doz. 4BA ¾in. r/hd., all with nuts and washers; 1 doz. extra 4BA nuts for mounting switches. | Peto-Scott |
| **Valves:** 2 KTW63, 1 X65, 1 D63 | Osram |

*Two 0.1 mfd. condensers and the volume control can be transferred to the receiver from the DC Quality Amplifier.

# NEWS OF THE WEEK

## HOT-AIR GENERATORS

### Power Supply for Battery Sets

A RECENT German development is the introduction of three types of hot-air generators which provide sufficient power for operating battery receivers using two-volt valves. These generators run off a simple petrol or methylated spirit lamp using one litre of petrol for a period of ten hours' continuous working or one litre of methylated spirits for nine hours' working. A burner for charcoal or peat is also obtainable, so that the generator could be used where petrol or methylated spirit is unobtainable.

The smallest model provides just sufficient current for a Philips 338B battery superhet or similar receiver and is priced at approximately £17, although under German export arrangements the price would be considerably less. The medium-sized model supplies six watts, whilst the largest, priced at Rm.360 (approx. £30) gives 12 watts, which is sufficient for charging a six-volt accumulator such as that required to operate a receiver using a vibratory converter.

In the case of the two smaller models, two-volt accumulators are required for the filament supply of the receiver, and they are connected for trickle charging by the generator.

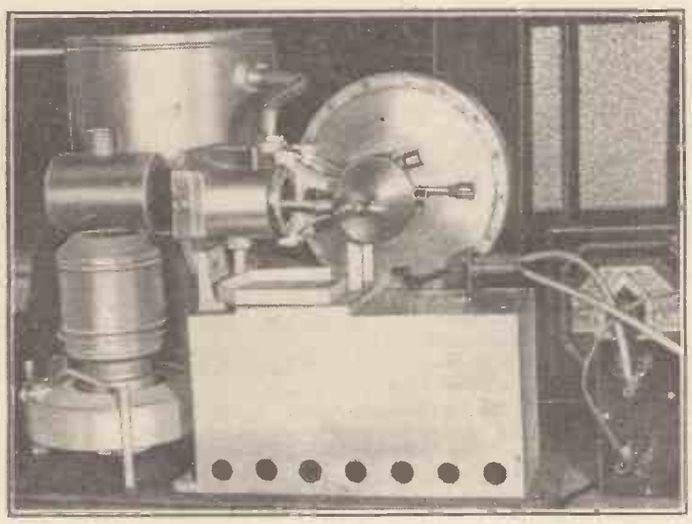

THE HOT-AIR MOTOR, showing the burner, which has been manufactured in Germany by P. Heinrici, for operating battery receivers.

## U.S. ARMY MANŒUVRES

### Directed Through Networks of the N.B.C.

THE General Staff of the United States Army, headed by General Malin Craig, conducted a remarkable broadcast from the National Broadcasting Company's Radio City studios during the early part of the month.

Through the use of more than a hundred thousand miles of wireless networks the manœuvres of army units in all parts of the U.S.A. were directed from the temporary headquarters in the New York studio. Replies to the broadcast orders were heard from 73 microphone positions, which included those in Hawaii, Alaska and Panama.

The Programme served to demonstrate the remarkable potentialities of wireless in war-time.

THE GENERAL STAFF of the American Army is seen conducting a public demonstration which was broadcast through 107 N.B.C. stations. General Malin Craig, Chief of Staff, is seen conversing with Mr. David Sarnoff, President of the R.C.A. and Colonel, U.S.A. Signal Corps Reserve.

## CONCERT PITCH

### Debate on International Standard

AS a result of extended deliberation under the sponsorship of the British Standards Institution, British interests have united in sending the following resolution to the Secretariat of the International Standards Association:

"That the International Standard of Musical Pitch shall be based on an absolute frequency of 440 c/s for the note A in the treble clef."

Other countries have also made their proposals, and a meeting of the I.S.A. Concert Pitch Committee with representatives of some ten different nations is being held at Broadcasting House, London, to-day and to-morrow. It is confidently expected that an International agreement of the figure to be adopted will be arrived at.

An article on the exact measurement of musical pitch appears elsewhere in this issue.

## TWENTY-FIFTH ANNIVERSARY

THE American Radio Relay League is celebrating its twenty-fifth anniversary this month. The League was formed in 1914, when communication by radio was carried on by means of roaring spark transmitters, which had a distance range by direct sound almost as great as the radio oscillations produced. Hiram Percy Maxim and Clarence D. Tuska inaugurated the movement as a means of keeping all amateurs in touch with one another, and by relaying communications from station to station to overcome the handicap of short range. From 237 members in September, 1914, the League has progressed to its present position, when it represents 51,000 amateurs in the United States and possessions.

## WHAT VIEWERS THINK

### Results of First Television Questionnaire

THE B.B.C. has made a preliminary analysis of the results of the television questionnaire, to which over 4,000 viewers sent in completed forms.

The results are encouraging, for they show that a large majority think that the programmes provided are satisfactory and improving and that the present balance of programme material is well in line with viewers' preference.

Plays and variety programmes direct from theatres, news reels, "Picture Page" and light entertainment are popular with at least 90 per cent. of viewers. Outside broadcasts come next, followed by full length plays, cartoon films and talks.

More than half the answers affirmed that the present length of the evening programme (1½ to 2 hours) was sufficient, although they would like it to begin earlier.

It was found that 91 per cent. of the forms had come from those who owned television sets for entertainment only and not for business, and it appears that the average number of people who watch television fairly regularly on each set is four.

## TRAIN TRANSMITTER

### Relays by Sixteen Stations En Route

A UNIQUE series of broadcasts is being carried out from the Union Pacific Exhibition train, as it makes its way from Los Angeles to Kansas City.

The train has been equipped by General Electric with a 50-watt transmitter which works on a wavelength of about 150 metres, using the call sign

**News of the Week—**

WOEG. Relays are being undertaken by sixteen medium-wave stations in cities through which the train is passing.

WOEG has a range of approximately twenty miles, and since the 80-year-old locomotive can pull the train at only 35 miles an hour, relays of nearly half an hour are possible as big cities are approached.

The 200-ft. transmitting aerial has been strung along three of the coaches, projecting 2ft. above their roofs.

## ANOTHER MOUNTAIN TELEVISION STATION

GERMANY'S second mountain-top television station, on the summit of the Feldberg, 2,720ft. above sea level, is now complete. It is situated roughly 20 miles north-west of Frankfurt, and will provide the large industrial populations of such towns as Frankfurt, Coblenz, Hanau and Offenbach with television.

The transmitter and also the aerial are housed in a wooden tower, as is the case at the Brocken, the reason for the latter being to prevent the formation of ice on the dipoles with the resultant impairing of efficiency. Three houses with four flats in each have been built in Konigstein, a small town at the foot of the mountain just ten miles from Frankfurt, to accommodate the staff for which there is no room in the tower.

When the cables connecting the station to the studios in Amerika House, Berlin, are completed, the station will begin operation. Public television booths will then be opened in towns within the service area, and eventually receivers will be put on the market.

RECEPTION AT 100 MILES. This illustration shows an untouched image of the Alexandra Palace television transmission received at the Isle of Wight.

## IN THE FAR EAST

**Broadcasting in Manchukuo**

DURING the past six years, broadcasting in Manchukuo, which is operated by the State Telephone and Telegraph Company, which also controls the entire news agency system, has undergone extensive developments. In 1933 there were only three small stations and barely 8,000 licensed listeners (0.04 per cent. of the population). There are now ten stations with a total power of 125 kW and approximately 100,000 listeners. Three of the stations are in Dairen, five in Hsinking, and one each in Mukden and Harbin. The station Hsinking II has a power of 100 kW.

The number of languages spoken makes broadcasting, as in India, extremely difficult, for the population consists of five main groups, Japanese, Koreans, Manchurians, Chinese, and Mongols, and fourteen announcers are now employed for the five-language service. The work of the broadcasting organisation is strenuous, for broadcasting fulfils the function of an elementary school for the largely illiterate population.

Close connection is maintained with the advanced broadcasting system of Japan, and sponsored programmes in favour of Japanese goods are permitted.

## OLYMPIC GAMES RELAYS

THE Olympic Broadcasts Committee of Finland is busy making preparations for a large number of running commentaries on the games to be held next year, and a special Radio Bureau has been formed. It has so far been decided to commence with the erection and wiring of fifty-two microphone booths for foreign commentators. Orders are being placed for new O.B. vans and sound-on-film recording equipment. The latter is especially important as the number of long-distance telephone lines for relaying purposes is limited.

## H.M.V.'s NEW LONDON SHOWROOMS

SHORTLY before midday on Monday, Sir Thomas Beecham pressed a switch in a portable control box and the new showrooms of His Master's Voice, at 363, Oxford Street, were formally declared open with a flood of music from loud speakers all over the building. It may be remembered that the previous showrooms on this site were destroyed by fire eighteen months ago, but the magnificence of the new building more than compensates for the memory of that unhappy incident.

More than 50,000 yards of cable were used in the equipment of the new premises, and 210 sound and television receivers in the numerous listening rooms, and in the first floor showroom, could be demonstrated simultaneously. Sixty television receivers can be fed from the tilted wire aerials which are about thirty feet long and composed of a number of short lengths of wire inclined to the roof at an angle of sixty degrees.

The personal recording studio, in charge of Mr. E. G. Huntley, enables the public to make their own records in identical surroundings to those in which commercial recordings are made. The cost of this service ranges from 10s. 6d. a session. The innovation should be useful to artistes, but the showrooms as a whole with their display of wireless receivers, television receivers and household appliances, as well as the large service department in the basement, should be of value not only to the public, but to the prestige of the wireless industry.

## CO-ORDINATING THE GERMAN INDUSTRY

AN order has been issued by Field Marshal Göring placing the entire German electrical and radio industries under the command of the Inspector for the Communications of the Armed Forces.

The work of the two industries and particularly that of the radio industry, is to be co-ordinated under the new head so that urgent requirements of the armed forces can be met. Furthermore, arrangements will be made whereby additional demands in an emergency arising out of sudden developments in the political or commercial situation will not overwhelm the industry.

As the whole field of electrotechnics is still in the stages of development, it is understood that the authorities intend to leave the industry a certain amount of freedom to maintain its progress, but the demands of rationalisation will have to be met.

## *FROM ALL QUARTERS*

**Remotely Controlled Television Cameras**

AN interesting refinement of the N.B.C.'s mobile television unit, which is closely similar to the two units employed by the B.B.C., is a remote-control circuit for focusing the cameras from the producer's panel in the mobile control room.

**Forest Fires**

IT is understood that an experimental transmitter is to be erected by the Forestry Commissioners on one of the highest points of the 2,850ft. Moel Siabod mountain, which overlooks Bettws-y-Coed, the Caernarvonshire beauty spot, in an endeavour to deal more speedily with forest fires. The watchman, who will be able to see about 100 miles on a clear day, will transmit a warning message which will be picked up at various centres equipped with fire-fighting appliances.

**Radio Tirana**

FOLLOWING the complete reconstruction of Radio Tirana, the station will take its place in the regular programme arrangements of other Italian stations.

**Foreign Listening in Germany**

REPORTING on market investigation, one of the German specialist papers states that the marked increase in the radio industry during recent months is due to the interest in listening to the news of home and *foreign* stations.

**Eskimo Operators**

RADIO-COMMUNICATION facilities in Greenland have expanded considerably during the past year. At the moment the country possesses twenty-three radio stations which handled 17,000 messages during 1938. The first batch of four native operators qualified for their licences recently and four other Eskimos are taking the radio course which was opened by the Danish Colonial Office at the beginning of the year.

**Ultra-Low Power**

A DANISH short-wave amateur, OZ-DR.479, has constructed a portable 1.2-watt, 112-Mc/s transmitter-receiver from which R6-S9 reports have been obtained over a distance of nearly 20 miles.

**R.S.G.B. Trophy**

To Mr. H. F. Wareing, W9NY, of Milwaukee, U.S.A., goes the R.S.G.B.'s International Five-metre Trophy for 1938. Mr. Wareing succeeded in making forty-two contacts with stations more than 200 miles away.

**Fifty Million Dollars for Nothing!**

THE advantages of licence-free reception is being stressed by the American broadcasting organisations in current publicity material. Newspapers are invited to "splash" the following: "Read the radio log in your newspaper—fifty million dollars' worth of radio entertainment—free. That's *American* radio!"

# New Tone-Control Circuit

## OBTAINING BASS AND TREBLE LIFT

By J. E. VARRALL

*A SIMPLE tone-control system, which enables both bass and treble response to be increased, is described in this article. Since coils are not used the possibility of hum pick-up is largely eliminated.*

THE most common tone-control circuits are the "top-cut" condenser filter and the "bass-cut" series condenser filter. These circuits are simple and effective, and today most sets are fitted with a resistance condenser shunt across some coupling circuit to give top-cut. Few sets, however, have the facility for top and bass boost, and in a high-fidelity receiver this is a very desirable feature. Top boost is useful to correct for sideband cutting in the RF amplifier, and bass boost to correct the deficiency in bass in gramophone records. It is also useful for correcting "scale distortion" when listening at a sound intensity below that experienced by a listener at the scene of the relay (for this, a tone-compensated volume control is a useful adjunct).

Boost circuits may be divided into resonant and non-resonant types. A resonant circuit, tuned to the frequency

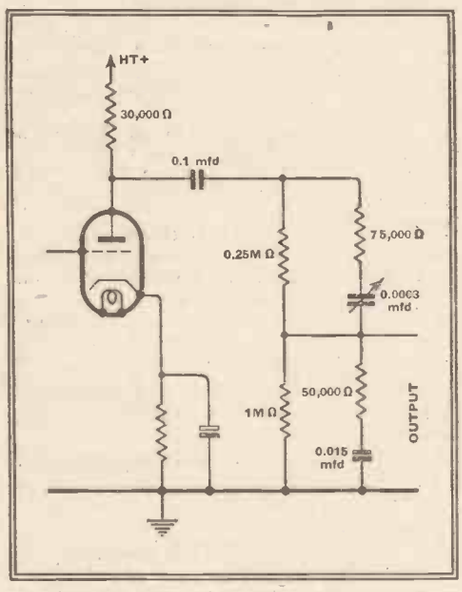


Fig. 1.—This diagram shows a normal tone-control circuit using condensers only.

at which maximum lift is required, may be made to increase the response considerably (20 db is a common figure) by virtue of its high impedance at resonance.

It suffers from the disadvantage of liability to shock excitation by transients, which may set up damped oscillations at the natural frequency of the circuit. Non-resonant circuits are less common, and suffer from the disadvantage of a very limited amount of gain. A gain of 10 db is obtainable with such a circuit in a range of about 4 octaves, i.e., the response at 50 c/s can be made about 10 db above that at 800 c/s. Such a circuit is shown in Fig. 1. Against the disadvantage of limited gain must be offset the advantages of its non-resonant nature, simplicity and absence of inductances, with their liability to pick-up hum. The limited gain of this circuit may be overcome by applying correction to two or more successive stages, but a simpler and more flexible arrangement has been used with success by the author.

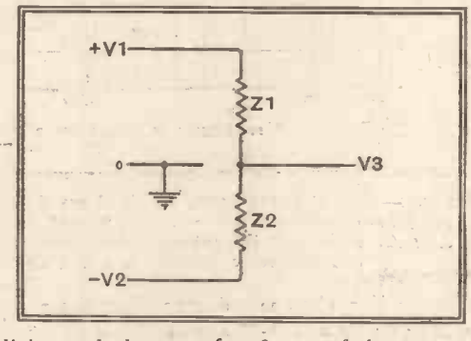


Fig. 2.—When two voltages in opposite phase are applied as shown here the output V3 depends on Z1 and Z2 and can be made zero.

Two impedances, Z1 and Z2, are placed across a source of supply, the two ends of which are in opposite phase (Fig. 2). If Z1 and Z2 are made of the same phase angle, and $\frac{Z1}{Z2}=\frac{V1}{V2}$, V3 will be zero, i.e., a nodal point will appear at the junction of Z1 and Z2. Further, if Z1 is made to decrease with increasing frequency, and Z2 to increase with decreasing frequency, the balance will be destroyed, and a finite value of V3 will be obtained for high and low frequencies. This condition is fulfilled by the simple filter of Fig. 3, the opposite phase supply being obtained from a wire-wound potentiometer in the cathode lead.

### The Practical Circuit

With the slider of the cathode potentiometer at the live end it may be possible to obtain a voltage node at the output lead, at the frequency at which $\frac{Z1}{Z2}$ is a maximum. The degree of suppression at this frequency will be governed by the accuracy of balance of impedances; since nearly perfect balance is obtainable, very large response variation over the frequency band is possible. The range over which suppression is effective will be dependent on the values of C1 and C2. If C1 is made small and C2 large, the entire mid-frequency band will be attenuated, and a lift obtained at each end. If C2 is made smaller, and C1 larger, the response begins to increase while still in the mid-frequency band due to the variation of Z1 and Z2 for medium frequencies.

If very large attenuations are required the circuit becomes critical in adjustment. Large attenuation is not usually needed in normal tone-control circuits, however, and response variations of over 20 db are obtainable without critical adjustment.

The response curve for a stage using a normal medium impedance triode with a nominal stage gain of 20 is given in Fig. 4. The triode should not be of more than 10,000 Ω AC resistance or the varying impedance of the tone-control circuit will alter the voltage fed to the network. Curves A1, A2, A3, A4 are for C=0.0003 mfd., C2=0.015 mfd., R1=75,000 Ω, and for different settings of the cathode potentiometer. Reference to these curves shows that if the cathode potentiometer is used as a volume control a decrease in middle band response of about 15 db results in a negligible decrease at 50 c/s and a decrease of about 5 db at 10,000 c/s. This

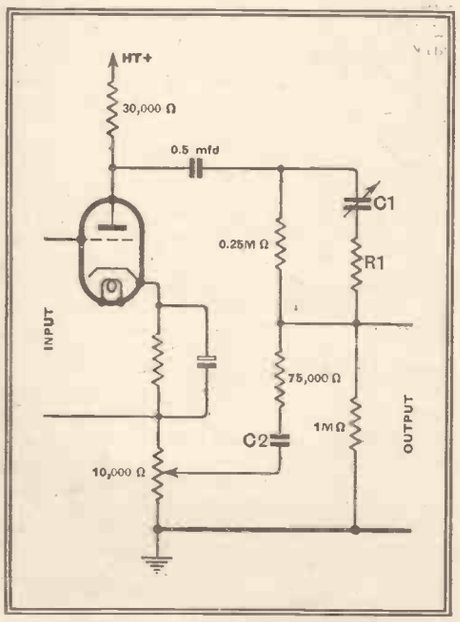


Fig. 3.—The new tone-control circuit; the response is varied by the cathode potentiometer.

compares favourably with the curves for ear sensitivity at different intensity levels. The cathode potentiometer can therefore be used as a tone-compensated control.

**New Tone Control Circuit—**

Curve B is obtained by short-circuiting R1 and curve C by changing C2 to 0.01 mfd. (the increased attenuation shows the importance of correct phase balance at the frequency of minimum gain).

This circuit, using as C1 a variable 0.0005 mfd. condenser, and as C2 condensers of 0.01, 0.015, 0.03, 0.05 and 0.5 mfd., selected by a switch, and as R1 75,000 Ω, has been found very satisfactory, and capable of giving a large number of different response curves.

It should be pointed out that as it is upon the gain over the middle register that the apparent volume depends, a simultaneous adjustment of the ordinary volume control and the cathode potentiometer of Fig. 3 is necessary if a change in response is needed without any alteration in volume. As it appears in Fig. 3, the cathode potentiometer varies apparent volume as well as changing the response.

It should not be overlooked, also, that neither of the input terminals is earthy. Consequently, the preceding coil must be a floating pick-up or diode detector, or a transformer coupling. The input can be applied between grid and earth, of course, but there is then a big drop in gain because of the negative feed-back on the cathode-resistance.

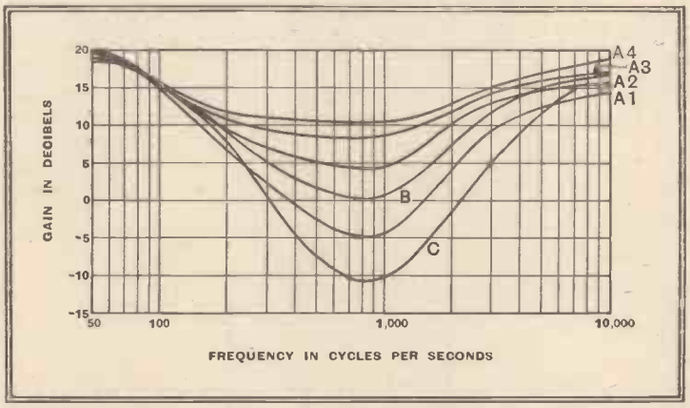


Fig. 4.—The response curves obtained are shown here. A1 to A4 are for C1 = 0.0003 μF, C2 = 0.015 μF and R1 = 75,000 ohms with different settings of the cathode potentiometer. Curves B and C are respectively with R1 = 0 and C2 = 0.01 μF.

# Letters to the Editor

The Editor does not necessarily endorse the opinions of his correspondents.

### *Secondary Emission*

AFTER reading the interesting article by "Cathode Ray" on secondary emission, it occurred to me that my fellow-readers would be interested to hear of another branch of electronics where the release of secondary electrons proves most interesting (and, incidentally, troublesome). I refer to the design of X-ray tubes to operate at pressures ranging from 60 to 100 kilovolts for diagnostic work, and up to much higher pressures for treatment work. It will be at once seen that these relatively high operating voltages produce correspondingly high electron velocities; so high, in fact, that the velocity of the secondary electrons released by primary bombardment of the anode is sufficient to produce X-radiation by their impact with whatever part of the tube they strike. The X-radiation produced by the secondary bombardment is, of course, of a much longer wavelength, having been produced by lower velocity electrons. This radiation is termed soft, being readily absorbed, and is usually filtered out from the main beam by metal filters, etc.

In diagnostic work a percentage of soft radiation is desirable to show up the tissue detail in the radiograph, hence the amount of filtration is somewhat limited, and as the X-radiation produced by the secondary emission electrons may be generated in various parts of the tube, depending on the general geometry of the electrodes, the main beam of the tube will suffer distortion due to interference from secondary radiation.

The second trouble experienced from the emission of secondary electrons is due to the fact that very high negative charges build up on the glass wall of the tube, due, of course, to the bombardment from secondary electrons, sometimes of the order of 30 to 40 kilovolts, leading to puncturing of the envelope. The high negative charge also produces considerable biasing action on the performance of the tube.

No attempt has been made to go into even the surface details of this piece of mechanism, though it is hoped that these few lines will prove interesting and constructive.

A. G. LONG,
Research Department, Newton and Wright, Ltd.
London, N.3.

### *Reproduction Level*

WITH reference to the article entitled "New American Quality Receiver" (March 23rd) and the letter from Mr. J. R. Hughes in your issue of April 13th, I should like to say that I heartily endorse the remarks of Mr. Hughes regarding natural volume for natural reproduction. The finest receiving equipment is not worth listening to at an unnatural output level.

It is quite easy to obtain the required volume for domestic listening from an amplifier with an undistorted output of 2-3 watts. I recently made some interesting tests at home with a first-class noise meter which registers sound in phons. It was found that when the output of the set on speech was regulated to equal the intensity of actual conversation, most lifelike reproduction was obtained. I was surprised at the low volume required from the set for these results, and I am convinced that on speech most people set the volume control far too high.

The correct setting of the volume control is rather critical, but is easier to find on speech than music. If all high-quality studio transmissions could be made at the required intensity, one could set the volume control for natural speech and leave it there for music, instead of having to fiddle about with the control repeatedly during an evening's listening.

G. A. BRIGGS,
Wharfedale Wireless Works.
Brighouse, Yorks.

### *Designing a School Receiver*

I AM planning a school wireless set which must satisfy the following requirements:—

1. It must be so arranged that the progress of the signal through the set can be readily followed, stage by stage.
2. It must be such that boys of the VI form can assemble it.
3. It must produce good signals and be something a non-scientific headmaster can show with pride to visitors as "made by our enthusiasts of the VI form."

I should appreciate the comments of your readers on the following proposed way of meeting the above requirements:—

(*a*) The set should be arranged on a board or set of boards, each unit being glass-covered to keep out the dust.

(*b*) The circuit should be Colebrook's RF, detector and tone correction stage (one board), followed by your resistance capacity amplifier (another board). This second part to be used for playing records.

(*c*) The inductances should be wound by the boys.

(*d*) All joints should be soldered.

(*e*) All valves should be 4-volt indirectly heated.

(*f*) Heater current to come from large-capacity accumulators. (No difficulty on this point here.)

(*g*) High-tension supply from accumulators also.

(*h*) Output to be about 12 watts.

Items (*f*) and (*g*) cut out all complications of rectifiers and their smoothing circuits. Later on a rectifier unit and smoothing circuit could be made as a separate unit and demonstrated on the set.

Your readers' comments on these suggestions would be appreciated by

"ASSISTANT MASTER."

### *Henry Hall in Germany*

REGARDING the letters that are appearing in *The Wireless World* on foreign relays and quality, I am afraid that I, for one, cannot totally agree with the views expressed by the writers of these letters.

It must not be forgotten that the performance of Henry Hall's Band for the German transmission was from a music hall and not from a studio, and it is evident that the acoustics of the building favoured the transmission very considerably. This transmission was not so well balanced as it might have been as it exhibited a preponderance of brilliancy with a lack of body, necessitating correction for this excessive brilliancy.

When "Quality Lover" turns to his explanation of the inferior quality of the B.B.C. transmissions, I am of the opinion that they are not guilty of using "carbon microphone technique" for musical transmissions. I find that the difference in the

quality of the B.B.C. transmissions from day to day is sometimes most marked and obvious to me when listening. As a matter of fact, some of the B.B.C. transmissions suffer from excessive "top" which also requires correction, while the opposite has also been found true.

These are the conclusions that have been arrived at after listening to as many varied musical transmissions as is possible, through the medium of a reproducer that clearly "shows up" the Effects Department of the B.B.C., whose treatment of transients leaves nothing to be desired.

Reverting to the correspondents, I am afraid that they cannot be such "lovers of quality" if their views are any criterion of their reproduction. R. C. HARRIS.

London, N.4.

### *Early Morning Reception : Shaver Interference*

I GET comparatively little trouble from vacuum cleaners, except on short waves, but the chief offender here is the proud owner of a new electric shaver; the interference this causes is terrific even at 50 yards with a road between. Luckily, I only get the trouble in the morning, but even then I am prevented from hearing any VK's or ZL's on 14 Mc/s. I am hoping the shaver develops a short or that the owner decides to grow a beard. No legislation seems to be forthcoming for the prevention of these abuses. W. H. PIERCE.

Beckenham, Kent.

### *Mr. P. K. Turner*

IN fairness to the new Hartley Turner Radio Co., to my friends in wireless circles, and to myself, I should like to explain that I gave up all my interests in the old company—Hartley Turner Radio, Ltd.—in the summer of 1938, and have no connection at all with the new firm.

Windsor, Berks. P. K. TURNER.

## Synthetic Reverberation

***Electro-optical Principle Utilised by C.B.S.***

A SYNTHETIC reverberation device recently demonstrated by Dr. P. C. Goldmark, chief television engineer of the Columbia Broadcasting System, will be widely used in creating a concert-hall effect from within any broadcasting studio.

Construction of the apparatus is based on the electro-optical principle. It is built into a single rack, and its most important feature is a disc, 20 inches in diameter, rotating at a speed of about 400 revolutions a minute. The outer rim of the disc is coated with phosphorescent material.

To use this disc for synthetic reverberation, the sound is converted into electrical energy which in turn is transformed into light. A special high-pressure mercury vapour quartz lamp is used as a source of light, and a quartz lens system projects a sharp image on the disc. This light image impressed on the revolving disc's phosphorescent surface produces on it bars of light of varying intensity. Intensity of light is synchronised with the intensity of sound signal fed into the apparatus.

This light image of the sound, temporarily "engraved" on the disc, is then picked off the disc by photo-electric cells placed around its circumference. The process is complete when the secondary sound image is picked up and superimposed on the original sound.

A great deal of optical research was carried out by Dr. Goldmark and his associates in order to evolve a method of transferring the maximum amount of light from the modulated light source on to the disc, and from the disc to the photo-cells. In order to ensure stable operation of the mercury vapour lamp serving as a light source, a cooling system was developed. It is automatically controlled by the lamp current and functions in such a way that when current in the lamp increases, and pressure in the lamp is built up, the cooling process commences. When the lamp current passes beyond a certain maximum point, the cooling automatically stops.

## Paper Records

***New Russian System***

A RUSSIAN inventor, Skvortsov, several years ago originated a method of sound recording on ordinary paper, but he died before completing the experimental work. Further work by Russian engineers has developed the system to the point where it is ready for commercial production. A recording has already been made of an actor, Abdulov, reading one of Mark Twain's stories.

Normal methods of sound-on-film recording and reproduction are employed, but the novelty is the printing and duplicating of the sound tracks on cheap paper. The perfected instrument consists of an automatic mechanism for unrolling the paper ribbon, with the usual lenses and photo-cell for reproduction, coupled to an amplifier and loud speaker. This instrument has been christened a paper phonogram. The actual ribbon is 35-mm. wide and 150 to 170 m. in length, but these figures can be modified. Under mass production it has been estimated that a paper-phonogram record providing one hour's play-back would cost about one-fifteenth of the price of an equivalent time on gramophone records.

Between 3,000 and 4,000 play-backs of a paper-phonogram reel are stated to be possible, and millions of positives can be printed from the negative. Within 24 hours of an original performance, paper-phonogram records can be supplied to the public. Another application is the insertion of these records in newspapers and periodicals to supplement the printed matter.

Needle loading from the top and automatic needle ejection are features of this RCA crystal pick-up. The needle is inserted in a hole at the top of the head and the point comes to rest against the bracket below, while the normal screw retainer is adjusted. To remove the needle, the screw is loosened and the pressing of a lever withdraws the retaining bracket to reveal a container into which the used needle drops.

## The Wireless Industry

WESTINGHOUSE have just issued a third edition of their descriptive pamphlet No. 11H (Westinghouse Rectifiers for Telecommunication). There are three sections dealing with power supply for telegraphy and telephony, other circuit applications in telegraphy and telephony and power supplies for radio communication.

◇ ◇ ◇ ◇

F. W. Lechner and Co., Ltd., 5, Fairfax Road, London, N.W.6, announce the introduction of 2-, 3- and 4-gang potentiometers and a wire-wound "Tropa" model for use under tropical conditions. Also a range of heavy duty rotary switches and switches with "Frequenta" insulation.

◇ ◇ ◇ ◇

"Drydex" HT and LT batteries are now available for the Philco Model P429 receiver. The 1½-volt LT battery costs 2s. 6d. and the 45-volt HT units 3s. 9d. each. A complete unit, Type H.1157, giving 90 volts HT and 1½ volts LT and fitted with a 4-way socket is available priced 10s.

◇ ◇ ◇ ◇

National Radio and Television Service Co., 126, Elthorne Road, Holloway, London, N.19, have developed a replacement cone assembly to be known as the "National Metacentre." It costs 27s. 6d. and can be adapted to fit most of the larger "hand made" moving-coil loud speakers.

## News from the Clubs

### *Radio, Physical and Television Society*

**Headquarters:** 72a, North End Road, West Kensington, London, W.14.
**Meetings:** Fridays at 8.15 p.m.
**Hon. Sec.:** Mr. C. W. Edmans, 15, Cambridge Road, North Harrow, Middlesex.

On April 21st a representative of Partridge, Wilson and Co., Ltd., lectured on "Rectifying Equipment." The lecturer brought a large quantity of apparatus with him.

On April 26th several members attended a meeting of the Golder's Green Society, at which Mr. Maurice Child described his 40-metre DF gear.

Recent lectures have been given on "Rectifier Equipment," "Thermo-electric Instruments" and "Television Time Bases." A transmitting evening was also held recently at which several DX stations were contacted. Several members now have full transmitting licences.

### *Slough and District Short-Wave Club*

**Headquarters:** 35, High Street, Slough, Bucks.
**Meetings:** Alternate Thursdays at 7.30 p.m.
**Hon. Sec.:** Mr. R. J. Sly, 16, Buckland Avenue, Slough, Bucks.

At the last meeting on April 27th a general discussion was held on the conditions on the amateur band.

At the next meeting, to be held this evening (May 11th), there will be a lecture entitled "High Voltage Electrical Phenomena."

### *Watford and District Radio and Television Society*

**Headquarters:** Carlton Tea Rooms, 77, Queen's Road, Watford, Herts.
**Hon. Sec.:** Mr. P. G. Spencer, 11, Nightingale Road, Bushey, Herts.

At the next meeting, which will be held at 8 p.m. on May 18th, there will be an auction sale of members' surplus apparatus.

### *Wirral Amateur Transmitting and Short-Wave Club*

**Headquarters:** Beechcroft Settlement, Whetstone Lane, Birkenhead, Cheshire.
**Meetings:** Last Wednesday evening in the month at 7.30 p.m.
**Hon. Sec.:** Mr. J. R. Williamson, 13, Harrow Grove, Bromborough, Cheshire.

At the annual general meeting held on March 29th it was stated that the total membership is now forty-five, an increase of eleven over last year.

### *Southend and District Radio and Scientific Society*

**Headquarters:** Strand Chambers, High Street, Southend-on-Sea, Essex.
**Meetings:** Alternate Fridays at 8.15 p.m.
**Hon. Sec.:** Mr. J. M. S. Watson, 23, Eastwood Boulevard, Westcliff-on-Sea, Essex.

It has been arranged that the Society shall co-operate with four other clubs in arranging field days during the summer. The Southend Society will arrange a field day on May 14th, and also a field night on September 16th-17th. On June 11th a field day will be arranged by the Romford Society, the Welwyn Club being responsible for the July 9th event and the Brentwood Society for that of August 20th. The final field day will be held on October 15th and will be arranged by the Ilford Society.

# UNBIASED

By FREE GRID

## *Piracy on the High C's*

I SEE that certain musicians of what may be termed the "so superior" class are on their hind legs once more denouncing people who listen to symphony concerts by wireless, instead of coming along to the actual concert hall and so increasing the gate money. Music reproduced by mechanical means is, we are told, at best but a poor travesty of the real thing. Mechanical means! Ye Gods! What on earth is a piano, or any other musical instrument but a device for reproducing music by mechanical means? I am not to be put off by people who would argue that a piano is not a reproducer of music, but a primary producer of it. It is, of course, nothing of the kind, but is merely a device to enable a man to reproduce certain combinations of sound written down by the composer.

It will be seen, therefore, when the question is thoroughly examined, that all music is reproduced by mechanical means, and so this fatuous argument against broadcasting which the so-called musical highbrows are once more putting forth, is without substance. It is true that there are plenty of very poor wireless sets about —far too many of them, in fact—but so also are there plenty of indifferent violins. A first-class wireless set, however, is entitled to rank equally with a first-class violin. Neither is perfect, although naturally the violin and other musical instruments, having had several centuries start are, as yet, still somewhat ahead of the wireless set.

This brings me to another question.

Not Paderewski.

What actually is the difference between a pianoforte recital as given by me and one given by Paderewski? That there *is* a difference I will certainly admit. But it has nothing to do with the fact that Paderewski possesses some "mystic" powers which I lack. There is nothing mystical or supernatural about it; it is simply due to the fact that, although we both press the correct piano keys, Paderewski does so with just the correct degree of pressure and the correct time intervals necessary to produce certain effects from the piano, and I do not. If properly analysed, Paderewski's playing could all be reduced to an exact degree of lb. per square inch and milliseconds of time. It is, in fact, all a question of elementary physics.

Let us, therefore, have done with all this palpable nonsense of the "so-superior" musicians I have mentioned, who are decrying home listening. Let the cold clear light of science shine on it, and all this pseudo-musical mysticism vanishes into thin air. Actually I very much doubt whether these anti-radio musicians themselves believe in all the diatribes they utter against broadcasting. I am coming more and more round to the opinion that in this commercialised age, the real cause of their worries is exactly the same as that which inspires football magnates to be so bitter in their views on television, namely, fear of a substantial falling-off in their gate money if they don't try to check this piracy of their profits.

## *Tellies or Talkies?*

SEVERAL readers have written to me criticising my attempt to reform the cinemas by inducing them to provide alternative programmes by means of a screen at each end of the building. The chief objection lodged against my proposal is that the slope of the cinema floor would, for obvious reasons, prevent it being possible to have a screen at either end. I must be credited with a little common sense and, if I had my way, I would march in with my army of occupation and sweep away sloping floors and other archaic ideas which the cinema has borrowed from the theatre.

To enable people in the back seats to see more clearly without a sloping floor, I would put the screen several feet higher than it is at present, and to prevent front-seat patrons having too oblique a view, I would tilt the screen slightly forward. Each seat would be built on the lines of a dentist's chair so that people could adjust it to the correct angle for avoiding a crick in the neck, all adjustments being carried out by built-in electric motors controlled from the arm of the chair.

You may well ask, as the Editor did, what has all this to do with wireless? My reply is that the cinema magnates have asked for it by their frightened plea that television, if unrestricted, will bankrupt them in two years. There will be no question of television bankrupting them if they will put their house in order and modernise their establishments, and I am, therefore, doing what is after all only my duty in endeavouring to get them to see what is really leading them to Carey Street, and to leave television alone.

To continue, therefore, with my proposals, I would have an arrangement whereby, on pressing the appropriate button, each patron's "dentist chair" would sink beneath the floor into a well-

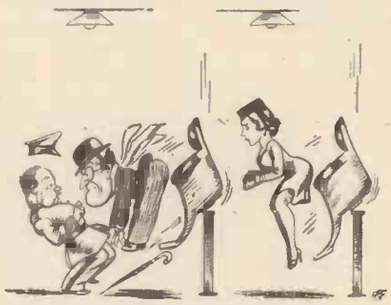

Automatic ejection.

lighted subterranean chamber, all loading and unloading being done in comfort down below. An attendant would load people into their seats under the floor, and at the same time would set a time switch which would automatically cause each seat to descend and eject its occupant when he had seen the pictures round once, and, in this way alone, cinema proprietors would soon recoup their capital expenditure on my proposed scheme, as they would more than double their present turnover of patrons.

Incidentally, I may point out that my idea would completely abolish the detestable practice of the person at the end of the gangway having to keep jumping up and down like a jack-in-the-box every time somebody in the row of seats wants to go in or out. It would also enable people to wear headphones without the annoyance of other people tripping over the leads. To prevent light shining into the auditorium from the subterranean chamber through the aperture in the floor when a seat was down below, a shutter would automatically slide over the hole, all subterranean-chamber lights being automatically switched off at the moment when a seat was actually passing through the floor.

If the cinema magnates refuse to accept my proposals then, of course, they can ruin themselves in their own way. No doubt, even if television did cause people to acquire a distaste for films they would still patronise the old cinema buildings as, even nowadays, some people seem to go there merely to eat and chatter, and, in fact, do anything but look at the pictures. It is doubtful whether many people would even notice that pictures were no longer being shown.

# Random Radiations

By "DIALLIST"

## An "Inert" Adventure

A WEEK or two ago I wrote of the inert dry cell, or the "cell, electric, inert," to give it its Army designation, wondering whether it still existed. It does, as a rather amusing little adventure that befell me the other evening proved. I was taking a class of signallers belonging to a Territorial unit that has not been in being for very long. After telling them how to get to work, I handed out a batch of brand new field telephone instruments and instructed the class to put in the dry cells—a pair in series—and connect them up. All the instruments with a single exception were found to be in working order. One was completely dead. It was brought to me to look over, and at first I couldn't find anything amiss. The connections seemed to be all right and there was no obvious reason why the thing shouldn't do its stuff. For some reason or other, I pulled out the cells and there was the explanation staring me in the cold printing on their cases; one was a dry cell; the other, an inert. As the latter hadn't been dosed with water, it wasn't pulling its weight. Somehow or other it had strayed in amongst a boxful of ordinary cells.

## Just the Thing

It was good to see Mr. Stanley G. Rattee's letter commenting on my remarks about inert cells. I haven't met him for a long time now, though he is one of the old stagers of wireless. I entirely agree with his suggestion that an HTB made up of inert cells would find a ready market amongst those who have acquired battery sets with an eye to A.R.P. So long as they are not filled with water, inert cells can be stored almost indefinitely; a battery of this kind would therefore be the very thing for the job. And I don't see why large inert cells should not be used for heating the filaments of the new 1.5-volt low-current valves. If the set intended for the dugout could be put away, batteries and all, with the certainty that it could be made to function as soon as it was wanted (let's hope it never will be!) by the simple process of running a little water into the filling holes, a lot of worry would be saved. Dry batteries unfortunately can't be relied on if they're kept in store for more than a few months on end.

## Saucer Records

WRITING from Frimley, a reader tells me of some queer experiences with gramophone records. Some time ago he ordered a set of a certain make containing a recording of a famous symphony. When they arrived he proceeded to play them over by means of a crystal pick-up and *The Wireless World* Quality Amplifier. All went well as far as the end of the second movement; but when the third began there came a sudden agonising drop in the pitch. On examination the record proved to be shaped rather like an upside-down saucer. Such was its convexity that it didn't get a proper grip of the spindle and so was driven much too slowly. He returned the faulty record, and, soon after, received another in its place. This turned out to be almost, if not quite, as bad as the first, and again a return was made. When they came to look over their stock, the manufacturers had to admit that all examples of this record were faulty. A new pressing had to be made, and it was seven weeks before a satisfactory record turned up.

## They Will Slip Through

What my reader can't understand is that a misshapen batch of records should have escaped the vigilance of all testers and have been passed into stock. It is rather surprising; but there is always the possibility that the records were flat enough when they passed from the factory into the stockroom *via* the test department. They may have warped through being badly stored. One would have thought, though, that such a serious deformation could hardly have escaped notice when they were passed out for sale. Still, it's astonishing what faults can slip through the best designed and most carefully run test department. To those who say that nothing defective should ever get through a good test room I always say: Pay a visit to the Mint; watch the vast number of tests to which every coin is subjected at each stage of its making. You'll feel convinced that no really misshapen coin, or any that was much below or above the standard weight could possibly pass into circulation. Then go to the Mint's museum and look at the displays of coins with the most glaring faults that have been returned by the banks.

## A Television Surprise

SOME of the answers given by viewers in reply to the B.B.C.'s questionnaire on television have come as a surprise to me, though I don't think that there's much doubt that the opinions expressed must represent the views of the majority of owners of television receivers. I quite expected that viewers would reverse the opinion expressed by listeners on the subject of women announcers. Listeners would not have them at any price; viewers prefer them. The reason isn't far to seek. Women's voices don't somehow fit in with the purely oral news bulletins; but they go very well with television's light fare. And the B.B.C. very wisely chose television announcers who are a delight to the eye as well as to the ear. What does surprise me is that O.B.'s take second place to variety and light entertainment in general in the the estimation of viewers. I'd have said that O.B.s would very easily head the poll.

## Changing Opinions?

That just shows how easily one can form an erroneous estimate, even though it is founded on the opinions expressed by a goodly number of televisor owners. Quite a few of my friends have vision receivers, and certainly I've found far more enthusiasm amongst them for races, boxing matches and other sporting and public events than for variety as television entertainment. It's not impossible that there has been a gradual change of opinion in recent months owing to the improved (and still improving) standard of televised light entertainment. At one time it was rather sorry stuff, and some who have owned receivers for a goodish time may have formed such a poor opinion of it that they ceased to turn it on. Now that it is of so much better quality they are discovering its merits and deciding that it deserves first place amongst the diversions offered by television.

## American CR Tubes

VARIOUS American manufacturers, I notice, are beginning to advertise cathode-ray tubes for constructors of vision receivers. Both they and the firms which specialise in "kits" are obviously expecting amateur experimenters and home constructors to begin in a small way, for most of the tubes announced are quite little fellows. The 3-inch screen seems to be the size that they expect to be most in demand, though several 5-inch tubes are available, those who announce them do so rather with bated breath; they are spoken of as just the thing for the man who intends to build something outstanding in the way of receivers. I wonder whether American manufacturers will eventually find as some of ours have done that their best sellers prove after all to be the vision receivers with the larger screens. You'd imagine that the midget set selling at a modest price would find a ready market; it goes pretty well, but in many cases the man in the street feels that it's better worth his while to pinch and scrape a bit in order to be able to buy a receiver with a screen measuring at least 7 inches by 5. It will be interesting to see what kind of prices the big American valve concerns ask for their cathode-ray tubes.

---

# Murphy B69

THIS is a battery superheterodyne which has been developed on the same lines as the "70" series of mains receivers described in our April 20th issue. It represents the maker's estimate of the minimum specification for the reception of broadcasting on short, medium and long waves, and employs a superheterodyne circuit with triode hexode frequency-changer, pentode IF amplifier, double-diode-triode detector, AVC rectifier and first AF amplifier and a single pentode output valve.

Improved quality of reproduction and efficiency have been achieved by the inclusion of a permanent magnet of unusual size in the loud speaker. The HT consumption is 10 mA on medium and long waves, 12 mA on short waves, and the total LT current is 0.45 amp.

The cabinet is similar in design to that of the A70, but there is no provision for optional tuning units. The price is £9. Space is provided for any standard 120-volt HT battery, and a moulded tray prevents acid creeping from the accumulator.

# Recent Inventions

***Brief descriptions of the more interesting radio devices and improvements issued as patents will be included in this section.***

### SCANNING SYSTEM

THE electron stream in a cathode-ray tube is usually controlled by the electrostatic field set up between two parallel deflecting plates, the direction of the control field being at right angles to the movement of the stream and therefore having no decelerating effect on the stream. By contrast, it is now proposed to control the stream by reflecting it from an equipotential surface set up inside the tube. The effect is first to slow up the stream as it approaches the equipotential field, and there to reverse it in direction.

As in the case of ordinary light, the angle of incidence of the electron stream is equal to the angle of reflection. Accordingly, as the contour or inclination of the equipotential surface is varied, the angle through which the stream is reflected will follow suit, and the stream can thus be made to travel over a fluorescent screen. In practice, a steady equipotential field is first created by applying suitable biasing potentials to a pair of parallel electrodes, and the stream is then deflected by varying the voltage on one of the electrodes at scanning frequency.

*O. Klemperer. Application date May 1st, 1937. No. 498511.*

o o o o

### FREQUENCY MULTIPLIERS

THE figure shows a two-valve circuit which is stated to be capable of delivering as much as 10 watts of energy at a frequency corresponding to the tenth harmonic of the input frequency. The first pentode generator V is stabilised by a piezo-electric crystal Q having the same frequency as a "tank" circuit L, C, and is coupled to the grid of a second valve V1 through a condenser. The output from the second valve is back-coupled through a circuit L2, C2 (tuned, say, to the tenth harmonic of the fundamental frequency of the crystal Q) to the pentode output circuit L1, C1.

The effect of this coupling is comparable with the action of two pendulums, one swinging ten times faster than the other, the slow one giving an impulse to the fast one each time the two come into phase. The circuit L2, C2 corresponds to the fast, and L1, C1 to the slow, pendulum, the transfer of energy being from the anode of V to the grid of V1. The multiplied frequency is drawn off at the output terminals T.

*Marconi's Wireless Telegraph Co., Ltd. (assignees of J. L. Reinartz). Convention date (U.S.A.), April 23rd, 1937. No. 499088.*

o o o o

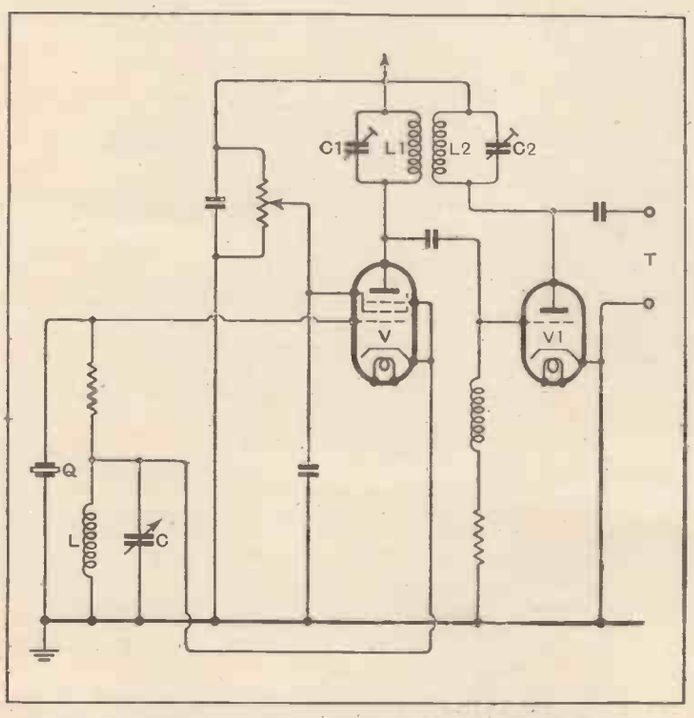


Frequency multiplying circuit for operation at the higher harmonics.

### DIRECTION-FINDERS

THE figure shows an aerial system designed to minimise the so-called "night effect" in direction-finding. The two main frame aerials A and A1 are spaced apart, with both windings set parallel to each other, and are mounted for rotation about a common shaft S. The two aerials are coupled in phase-opposition through coils L, L1 to a common receiver R, the output from which is applied to one pair of deflecting plates in a cathode-ray indicator tube T.

Mounted on the shaft S is a third or auxiliary frame aerial B, the pick-up from which is applied separately through a receiver R1 to the second pair of deflecting plates in the cathode-ray tube.

The arrangement gives a simplified indication both of the direction and "sense" of incoming signals. For instance, the trace on the fluorescent screen of the cathode-ray tube will be a straight line in the normal "maximum" position of the aerials, *i.e.*, when the pick-up on the frame B is greatest, and that from the two frames A and A1 cancels out. As the aerials are rotated into other settings, the trace formed on the fluorescent screen will vary from an ellipse to a circle. The "sense" of the signals is indicated by observing the movement of the trace as the shaft S is swung to right or left, the correct bearing being that on which the trace moves with the shaft and not against it.

*Telefunken Ges. für drahtlose Telegraphie m.b.h. Convention date (Germany), June 12th, 1937. No. 498995.*

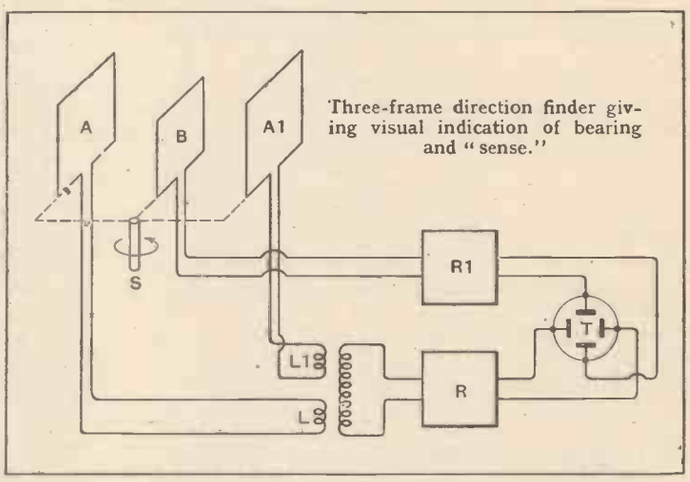


Three-frame direction finder giving visual indication of bearing and "sense."

o o o o

### TUNING INDICATORS

A MULTI-BAND receiver is fitted with a tuning indicator in the form of a series of transparent strips of glass, each marked with its appropriate station scale. The various strips are mounted one behind the other, lengthwise, in slots in the same pair of end-supports, so that they form a practically continuous surface, though each is separated from the other by a thin strip of opaque material.

The particular indicating strip selected is lit up by a pair of lamps which shine their light through the slots made in the end-supports. A single pair of lamps may be used, in which case they are moved into position by suitable gearing operated by the wave-change switch; or separate pairs of lamps may be fixed in position at the sides of each slip, and lit up as required.

The station-pointer is moved along a horizontal base, parallel to the strips, by a cord-and-pulley mechanism operated by the control knob. Or a "shadow" thrown by a light at the rear of the glass scales may serve as a pointer.

*Marconi's Wireless Telegraph Co., Ltd. Convention date (U.S.A.) June 30th, 1936. No. 497951.*

### "WATCH-DOG" SETS

RELATES to an installation of the kind used at sea to give automatic warning of the receipt of the S O S call or other emergency signal. According to the invention, the set is constantly and automatically supervised by a so-called "cycling" device, which serves to produce locally a weak signal similar to that for which the receiver is "watching."

So long as the installation is in proper order the arrangement is such that the "alarm" proper cannot be actuated by the local "test" signals. But should any part of the installation develop a defect, then the alarm is automatically rung by the test signals, as a warning to the wireless operator that the "watch" is no longer reliable. Between the testing periods, the receiving circuits are, of course, ready to respond to any genuine emergency call. In other words, the alarm can only be sounded (a) on the receipt of a genuine long-distance call, or (b) when the local "testing" signal shows that the receiver is out of repair and requires attention.

*Wallace and Tiernan Products, Inc. Convention date (U.S.A.) June 20th, 1936. No. 499028.*

**The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.**

GOODMANS 12" High-Fidelity Auditorium Loudspeaker (illustrated on the left). Power Rating 12 watts A.C. Peak.....£8.3.0

Chassis model (without stand) £7.13.0

*(Heavy Duty Transformer 15/- extra)*

# GOODMANS

*High-Fidelity* Auditorium

LOUDSPEAKERS

THESE vital factors sum up the performance of GOODMANS 12" High-Fidelity Auditorium Loudspeakers. The attainment of such efficient operating conditions is due mainly to the use of the patented dual exponential type diaphragms; an exclusive feature of GOODMANS High-Fidelity Loudspeakers. A specially constructed permanent magnet of Nickel Aluminium and Cobalt Alloy provides the high flux density of 15,000 lines per sq. cm. and together with the carefully designed, light but rigid speech coil and extremely flexible centring device, completes a perfect "team" of components. This provides a reproducer acknowledged as a standard amongst all quality loudspeakers.

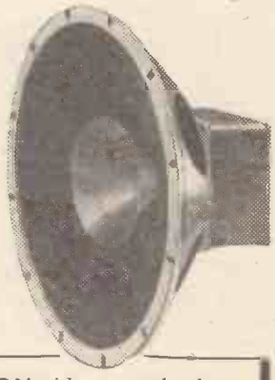

GOODMANS 10" High-Fidelity Auditorium Loudspeaker. Power Rating 6 watts. A.C. Peak. Complete with Standard Transformer £3.10.0

*(Heavy Duty Transformer 7/6 extra)*

## GOODMANS INDUSTRIES, LTD.

Lancelot Road, Wembley, Middx. 'Phone, WEMbley 4001.

**POST THIS COUPON** *with your card or letter heading for new* **TECHNICAL BROCHURE**, *entitled "The Attainment of an Ideal," giving interesting data on the fundamental principles of Loudspeaker construction. Please enclose 1½d. stamp.*

***—Third Edition of***

# WIRELESS DIRECTION FINDING

## BY R. KEEN, B.Eng.

**A BOOK OF INSTRUCTION AND REFERENCE FOR ENGINEERS, TECHNICIANS, TELEGRAPHISTS AND OTHERS ENGAGED OR INTERESTED IN THE USE OF DIRECTIVE WIRELESS TELEGRAPHY FOR THE NAVIGATION OF SHIPS AND AIRCRAFT**

The third edition of this well-known book deals with the principles of Wireless Direction Finding and gives an account of the circuits and apparatus used in its application to navigation. The Adcock Aerial has a separate chapter covering its principles together with much information on its installation and performance. Further chapters are included on Shore, Ship and Aircraft installations as well as a special section on the choice of a suitable site for the Aircraft Ground D.F., with Adcock Aerials.

Engineering students and research engineers will find useful references to a selected list of some 600 of the more important contributions to the literature of D.F.

**800 pages 550 illustrations**

**PRICE 25/- net By post 25/9**

*From leading Booksellers or direct from the Publishers:*

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

# CLASSIFIED ADVERTISEMENTS

## NOTICES

THE CHARGE FOR ADVERTISEMENTS in these columns is

12 words or less, 3/- and 3d. for every additional word.

Each paragraph is charged separately and name and address must be counted.

SERIES DISCOUNTS are allowed to Trade Advertisers as follows on orders for consecutive insertions, provided a contract is placed in advance, and in the absence of fresh instructions the entire "copy" is repeated from the previous issue: 13 consecutive insertions 5%, 26 consecutive, 10%; 52 consecutive, 15%.

ADVERTISEMENTS for these columns are accepted up to FIRST POST on MONDAY MORNING (previous to date of issue) at the Head Offices of "The Wireless World," Dorset House, Stamford Street, London, S.E.1, or on SATURDAY MORNING at the Branch Offices, 8-10, Corporation Street, Coventry; Guildhall Buildings, Navigation Street, Birmingham, 2; 260, Deansgate, Manchester, 3; 26B, Renfield Street, Glasgow, C.2.

Advertisements that arrive too late for a particular issue will automatically be inserted in the following issue unless accompanied by instructions to the contrary. All advertisements in this section must be strictly prepaid.

The proprietors retain the right to refuse or withdraw advertisements at their discretion.

Postal Orders and Cheques sent in payment for advertisements should be made payable to ILIFFE & SONS Ltd., and crossed & Co. Notes being untraceable if lost in transit should not be sent as remittances.

All letters relating to advertisements should quote the number which is printed at the end of each advertisement and the date of the issue in which it appeared.

The proprietors are not responsible for clerical or printers' errors, although every care is taken to avoid mistakes.

## NUMBERED ADDRESSES

For the convenience of private advertisers, letters may be addressed to numbers at "The Wireless World" Office. When this is desired, the sum of 6d. to defray the cost of registration and to cover postage on replies must be added to the advertisement charge, which must include the words Box 000, c/o "The Wireless World." All replies should be addressed to the Box number shown in the advertisement, c/o "The Wireless World," Dorset House, Stamford Street, London, S.E.1. *Readers who reply to Box No. advertisements are warned against sending remittances through the post except in registered envelopes: in all such cases the use of the Deposit System is recommended, and the envelope should be clearly marked "Deposit Department."*

## DEPOSIT SYSTEM

Readers who hesitate to send money to advertisers in these columns may deal in perfect safety by availing themselves of our Deposit System. If the money be deposited with "The Wireless World," both parties are advised of its receipt.

The time allowed for decision is three days, counting from receipt of goods, after which period, if buyer decides not to retain goods, they must be returned to sender. If a sale is effected, buyer instructs us to remit amount to seller, but if not, seller instructs us to return amount to depositor. Carriage is paid by the buyer, but in the event of no sale, and subject to there being no different arrangement between buyer and seller, each pays carriage one way. The seller takes the risk of loss or damage in transit, for which we take no responsibility. For all transactions up to £10, a deposit fee of 1/- is charged; on transactions over £10 and under £50, the fee is 2/6; over £50, 5/-. All deposit matters are dealt with at Dorset House, Stamford Street, London, S.E.1, and cheques and money orders should be made payable to Iliffe & Sons Limited.

SPECIAL NOTE.—Readers who reply to advertisements and receive no answer to their enquiries are requested to regard the silence as an indication that the goods advertised have already been disposed of. Advertisers often receive so many enquiries that it is quite impossible to reply to each one by post. When sending remittances direct to an advertiser, stamp for return should also be included for use in the event of the application proving unsuccessful.

## NEW RECEIVERS AND AMPLIFIERS

R.

C.

TELEPHONE: Holborn 4631.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1, by offering brand new receivers, maintain their reputation as the leading Mail Order House for surplus radios.

BRITISH Belmont 8-valve Plus Magic Eye All-wave A.C. Superhet Chassis, 4 wave bands, 2 short medium and long, fitted latest Mullard octal base American type valves. Brief specification: Short wave 6-18 metres (covers television sound), short wave 2, 18-50 metres, medium band 200-550 metres, long 900-2,000 metres; valve combination 6K7 Pre H.F., 6J7 oscillator, 6J7 mixer, 6K7 I.F., 6Q7 (DDT) detection, A.V.C. and first L.F., two 6F6s, parallel output, 5Y3 rectifier, plus 6G5 Magic Eye visual tuning, handsome dial, station names etched on glass, controls 2-speed tuning, volume and on-off, combined variable tone control and selectivity switch, wave change plus gramo. switch; size of chassis 13½in.×10in.×3in.; supplied complete with valves, escutcheon, knobs, but less speaker, £5/19/6 each; complete receiver in handsome walnut cabinet, details as above, complete with speaker, £7/7.

DECCA 6-valve 3-waveband Battery Chassis, fitted complete with Mazda and Osram valves, QPP output; these chassis give a sparkling performance on all wavebands, and are the product of a well known manufacturer, complete with valves, £3/3 each; complete receiver in handsome walnut cabinet, details as above, complete with speaker, £3/19/6 each.

ALL the Above Fitted Ring Valves Throughout.

SEE Our Advertisement under Components.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1. Telephone: Holborn 4631. [8380

*

*

DEGALLIER'S "Challenger Radio Corporation."

SEND 2d. stamp for Handsome Illustrated Catalogues Telling of our Superb Range of Receivers; direct public sales policy (saves you 40%), most exceptional value on the market, from a T.R.F. Midget at £3/5 to a 19-valve general purpose receiver, 6 bands, with two P.A. speakers, at 30 gns.; 6-page brochure of *Wireless World* report on this set is available; car radio; any known American valve, all 5/6 each; also American P.A. speakers, cabinets, and the Challenger 6-valve A.C. tuning unit, 5 bands 6-10, 12.8-50, 65-200, 190-550, 900-2,000 metres. Hours business 11 a.m. until 9.30 p.m.

DEGALLIER'S, 31, Craven Terrace, London, W.2. Paddington 6492. Nearest point Lancaster Gate Tube Station. [8443

# ARMSTRONG'S NEW HEADQUARTERS

After many years at our old premises in Camden Town we have moved our Offices, Show Rooms and Development Department to a modern building centrally situated in

**WARLTERS ROAD, HOLLOWAY, N.7**
(Adjoining Holloway Arcade).

We take this opportunity of sincerely thanking the vast number of "Wireless World" readers whose consistent custom it has been our pleasure to receive for so many years.

Incidentally, this is the seventh year we have advertised in the "Wireless World" *without a break.*

Send for Illustrated Catalogue of our full range, which includes the following outstanding chassis.

**MODEL AW125PP . Price £17.17.0**
**12-V. ALL-WAVE RADIOGRAM CHASSIS**
5 wavebands, 12-550 continuous, 1,000-2,000 m., R.F. Pre-Amplifier, 2 I.F. stages with Variable Selectivity, Manual R.F. gain control and 10 watts R.C. coupled Triode P.P. output.

**MODEL AW93PP . Price £10.10.0**
**9-V. ALL-WAVE RADIOGRAM CHASSIS**
3 wavebands, R.F. Pre-amplifier, 3 stages of A.V.C. and 8 watts R.C. coupled Triode P.P. Output.

*All communications to be addressed to*

**ARMSTRONG MANUFACTURING CO.,**
**WARLTERS ROAD, HOLLOWAY, LONDON, N.7**
(Adjoining Holloway Arcade).

*Telephone: NORth 3213.*

# EASY TERMS *by* L.R.S

ON ALL

**ARMSTRONG CHASSIS**

MODEL AW125PP - - - 12-VALVE ALL-WAVE RADIOGRAM CHASSIS
Cash 17 Gns. or £2 with order and 12 monthly payments of - - - - - - - - - - £1.8.0
MODEL AW93PP - - - 9V. ALL-WAVE RADIOGRAM CHASSIS - - Cash 10 Gns. or 21/- with order and 12 monthly payments of 17/-
(See Armstrong Advt. above)

Send for details of the 11 Armstrong Models and our CONVENIENT TERMS.

*Estd: — 1925* THE *'Phone NATional 6828*

**LONDON RADIO SUPPLY COMPANY**
11·OAT LANE·NOBLE ST·LONDON E.C.2

# Lockwood CABINETS

*ACOUSTICALLY DESIGNED*

A complete range for all *Wireless World* Receivers and Commercial Chassis

*Special Drawings free on request*

Send 1½d. stamp for details of Standard Models

**Lockwood & Co., 65, Lowlands Road, Harrow**
*Telephone: Byron 1818*

## NEW RECEIVERS AND AMPLIFIERS

FREE with each 1939 Sky Buddy 10-550 metres, a copy of Jones or A.R.R.L. handbook; this offer is open for one month only.—Send to Leeds Radio, 9, Grand Arcade, Briggate, Leeds, 1. [8421

1939 Belmont 570 5v., 3 wavebands, A.C., makers' sealed cartons, list 10½, few only, telephone dial, 6 gns.; push button, 6½ gns.; Midgets from 50/-; guaranteed American valves, cheapest prices; write requirements.—Johns, 63, Swains Lane, Highgate. [8442

## RECEIVERS AND AMPLIFIERS

### CLEARANCE, SURPLUS, ETC.

A

ANGLO-AMERICAN RADIO (and MOTORS), Ltd.,

ANOTHER Clearance of Demonstration Models.

£5/10.—10-valve A.C. superhet receiver chassis, with valves, push-pull output, 4 wave bands 12-30, 30-75, 200-550, 1,000-2,000 metres, with magic eye R.F. gain, tone, audio control selectivity, output approximately 6 watts; one only.

£10.—9-valve Crossley superhet, allwave, complete with valves, in splendid console cabinet, 12in. speaker, output approximately 10 watts; one only.

£8/10.—9-valve International chassis, allwave, with 12in Magnavox speaker.

£5/10.—8-valve Crossley receiver, in handsome table cabinet.

£5/10.—4-valve portable battery receiver, 2 wavebands, complete with battery, in green leatherette case.

ALL above are in good working order, but are being offered as a clearance line to make room for further stocks, and our usual guarantee does apply; cash with order or c.o.d.

ANGLO-AMERICAN RADIO (and MOTORS), Ltd.,

59, New Oxford St., London, W.C.1. 'Phone: Tem. 3231. [8444

1939 Midwest 15-valve A.C./D.C. Allwave, 6 wavebands, 5-1,500 metres, brand new, in handsome walnut console cabinet; listed £36/15. £20; two only.

1939 Midwest 9-valve A.C. Radiogram, 6 wavebands, 5-1,500 metres, brand new, in massive walnut cabinet; £18/10.

HENRY'S, 72, Wellington Ave., Stamford Hill, N.15. Stamford Hill 2907. [8438

## USED SETS FOR SALE

### HALLICRAFTERS

HALLICRAFTER 5.10 Receiver, as new, makers' carton, cost £20, for £15.—Lownds, The Cottage, Old Lenton, Nottingham [8431

*"Radio Data Charts," A Series of Abacs Post free 4/10*

## USED SETS FOR SALE

### McMURDO

McMURDO Silver 21-valve Masterpiece IV, 13 m.-2,000 m., 20 watts output, perfect order; cost £85, accept £18/10.—Box 9663, c/o *The Wireless World.* [8423

McMURDO Silver Masterpiece V, in special solid oak cabinet, 20 valves, 5 wavebands, 18in. speaker, a magnificent instrument, all as new, cost £95; accept £27/10.—Harris, Caterham 250. [8410

### SCOTT

SCOTT 15 De Luxe, 13-550 metres, 20 watts output; cost £95, 1937 model, £15/10.—Box 9664, c/o *The Wireless World.* [8424

### MISCELLANEOUS

A NUMBER of Reconditioned Sets in Good Order; from £5 upwards.—Halford Radio, 31, St. George St., W.1. [0617

## CAR RADIO

CROSLEY Push-button 1939 10 guinea Models, 5½ gns.; aerials, overheads, police type, etc., from 8/6; trade enquiries solicited.—Shippers, 18, Corporation St., Manchester. [0622

FINEST American Twin Running-board Aerials, completely rubber covered, maximum signal pick-up, minimum noise, easy mounting, now only 17/6 pair complete; handsome chromium roof aerials, to mount straight or "vee," complete, 15/-; immediate despatch, carriage paid; cash with order or c.o.d.

WIRELESS SUPPLIES UNLIMITED, Essex House, Stratford, E.15. Maryland 3191. [0577

## PUBLIC ADDRESS

V

VORTEXION P.A. Equipment.

IMITATED, but unequalled.

WE Invite You to a Demonstration.

A.C.-D.C. Dance Band Amplifier, 10 watts output, complete in case, with moving coil microphone, speaker and cables, weight 22lb.; 12 gns.

A.C.-20 15-20-watt Amplifier, 30-18,000 cycles, independent mike and gram., inputs and controls, 0.037 volts required to full load, output for 4, 7.5, and 15 ohms speakers or to specification, inaudible hum level; ready for use; 8½ gns., complete.

C.P. 20, 12-volt battery and A.C. mains model, as used by R.A.F., output as above; 12 gns.

A.C.20, in portable case, with Collaro motor, Piezo pick-up, etc., £14; C.P.20 ditto, £17/17.

50-WATT Output 6L6s, under 60-watt conditions, with negative feed back, separate rectifiers for anode screen and bias, with better than 4% regulation, level response, 20-25,000 cycles, excellent driver, driver transformer and output transformer matching 2-30 ohms impedance electronic mixing for mike and pick-up, with tone control, complete with valves and plugs; £15.

COMPLETE in Case, with turntable B.T.H. Piezo pick-up and shielded microphone transformer, £20.

80-WATT Model, with negative feed back; £25, complete.

120-WATT Model, with negative feed back; £40, complete

250-VOLT 250 m.a. Full Wave Speaker, field supply unit; 25/-, with valve.

ALL P.A. Accessories in Stock; trade supplied.

VORTEXION, Ltd., 182, The Broadway, Wimbledon, S.W.19. 'Phone: Lib. 2814. [8241

"PARTRIDGE P.A. Manual," standard handbook on electro-acoustics, amplifiers, and audio circuits; price 2/6 (free to trade).

"PARTRIDGE Amplifier Circuits," describes many modern constructional amplifiers, 2w. to 45w. output, battery, A.C.-D.C., etc.; price 2/- (no free copies).

PARTRIDGE, N., B.Sc., A.M.I.E.E., King's Buildings, Dean Stanley St., London, S.W.1. [0630

QUALITY Amplifiers and Microphone Equipments for Hire or Permanent Installation.—Harmony House, 116, Cambridge Rd., Southport. [8307

ALEXANDER BLACK, Ltd., pioneers of hiring microphone amplifying equipment since 1928. Booklet on request.—55, Ebury St., S.W.1. Sloane 6129. [0598

PUBLIC Address Contractors Can Hire P.A. Vans, loud-speakers, microphones and equipments of all types from Hire Dept., Grampian Reproducers, Ltd., Kew Gardens, Surrey. Tel.: Richmond 1175-6-7. [0618

## NEW MAINS EQUIPMENT

V.

ALL Transformers at Last Week's Prices.

VORTEXION, Ltd., 182, The Broadway, Wimbledon, S.W.19. 'Phone: Lib. 2814. [8440

## NEW LOUD-SPEAKERS

SINCLAIR Speakers for All Types.—Alma Grove, Copenhagen St., N.1. [0603

BAKERS' New Corner Horn Speakers, surplus bargains and triple cone conversions, from 29/6.—Leaflets free from Bakers Selhurst Radio, 75, Sussex Rd., South Croydon. [8434

## LOUD-SPEAKERS

### SECOND-HAND, CLEARANCE, SURPLUS, ETC.

ROLAS for 6/11; G12's, 47/6; ½d. stamp for lists.—Shippers, 18, Corporation St., Manchester. [0606

MAGNAVOX 66, 2,000 amps., wanted, quality feeder unit.—A. Chapman, 33, Dalyell Rd., Stockwell. [8430

VAUXHALL UTILITIES, 163a, Strand, W.C.2.—Rola P.M. speakers, 8in., 14/9; 10in., 19/6; Rola energised 10in., 17/6. [8436


# GRAMPIAN

## ANSWER EQUIPMENT QUERIES

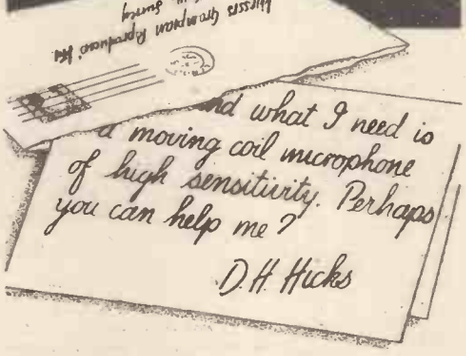


**Undoubtedly the finest moving coil microphone on the market is our type M.C.S. Quality is very good, the Response curve being sensibly linear throughout the Audio Spectrum, and Amplitude Distortion is negligible. Sensitivity and range of pick-up are very high, and increased by the fact that the input control can be opened up quite high before FEED-BACK occurs. High Output Voltage (0.1 v at normal speech) enables use with an amplifier of quite low gain. *No blasting or overloading possible.* No background noise such as carbon hiss, and no cavity resonance, owing to the specially designed square case with adequate venting. This microphone is weatherproof and entirely unaffected by damp.**

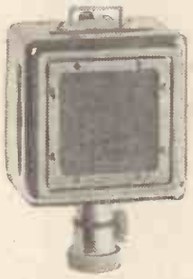

***Price .. .. 6 Gns.***
***Input Transformer 15/-***
***Spring Frame .. 15/-***

**Type M.C.R. This is a standard type Moving Coil Microphone utilising a paper diaphragm and speech coil of aluminium wire, and is attached by a special non-distortion suspension system to a high flux nickel aluminium magnet and cast metal case mounted in a spring suspension frame.**

***Price now reduced to 3 Gns.***

*We are also actual manufacturers of Loud Speakers of all kinds. Amplifiers, and all forms of P.A. Equipment—both portable and permanent.*

## STOP PRESS

**Latest Grampian Public Address Installations include:**

**OPENING OF WESTMINSTER HOSPITAL** *by Their Majesties the KING & QUEEN.*

**OPENING OF WEST HARTLEPOOL AIRPORT** *(Sir Kingsley Wood).*

**GRAMPIAN REPRODUCERS Ltd.**
Kew Gardens, Surrey. Tel.: Richmond 1175.


## LOUD SPEAKERS—SECOND-HAND, CLEARANCE, SURPLUS, ETC.

3,000 Speakers from 5/6 each, P.M. and energised, 4in. to 14in., including several Epoch 18in.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0591

EPOCH 18in., rebuilt, any field, £5; with A.C. equipment, £2 extra; Epoch 14in. mains energised, 70/-; fitted A.C., 30/- extra; several 10in., 12in., and 15in. energised and P.M.s, from 20/-.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0628

### Wanted

HARTLEY-TURNER Twin Diaphragm P.M. Speaker, excellent condition.—Burt, 65, Lyndhurst Grove, Peckham. [8439

## TRANSMITTING APPARATUS

A.C.S. RADIO, specialists in short-wave apparatus, communication receivers, including Hallicrafters, National and R.M.E. transmitting equipment, valves and components.—Send for free catalogue to A.C.S. Radio, 16, Gray's Inn Rd., W.C.1. Holborn 9894-5. G2NK. Technical Manager. [0550

G5NI—The oldest and largest distributors of amateur equipment, transmitting and receiving; short-wave catalogue, 1½d.; G5NI 70-page Manual, 7½d., post free; authorised direct distributors for Collins, National, R.M.E., Thordarson, Hammerlund, Bliley, Taylor, Eimac, etc., etc.—44, Holloway Head, Birmingham. [0531

## CABINETS

A CABINET for Every Radio Purpose.

CONVERT Your Set into a Radiogram at Minimum Cost; surplus cabinets from noted makers under cost of manufacture (undrilled); 30/- upwards; motors at wholesale prices.

"FIT-A-GRAM", Cabinet, 31×17×15; 21/-.

UNDRILLED Table Console and Loud-speaker Cabinets, from 3/6.

INSPECTION Invited; photos loaned to country customers.

H. L. SMITH and Co., Ltd., 289, Edgware Rd., W.2. Tel.: Pad. 5891. [0485

CLEARANCE Sale!! — Radiogram and television cabinets; prices slashed! 10 gns. worth for 50/-! 5 gns. worth for 20/-!—Write, wire, 'phone or call, Cameo Co., 23, Denmark St., W.C.2. (Tem. 5900.) [8353

## DYNAMOS, MOTORS, ETC.

D.C.—A.C. Convertors, motors, all voltages, for sale and wanted.—Easco, 18w, Brixton Rd., S.W.9. [0558

ALL Types of Rotary Converters, electric motors, battery chargers, petrol electric generator sets, etc., in stock, new and second-hand.

A.C.-D.C. Conversion Units for Operating D.C. Receivers from A.C. Mains, 100 watts output, £2/10; 150 watts output, £3/10.

WARD, 46, Farringdon St., London, E.C.4. Tel.: Holborn 9703. [0518

## RECORDING EQUIPMENT

ALL Recording Discs and Materials in Stock; tracker units, £4/7/6; recording motors, £3/17/6.—Write for further details, Will Day, Ltd., 19, Lisle St., W.C.2. [0595

FEIGH Recording Sets are Within Reach of All; ball bearing gear box, worm drive traverse; records on any disc, Morse, speech or music; diamond cutter-pickup on tone arm, the set 37/6; 6in. blanks, 3/3 doz.; 10in. discs, 7/- doz.—Electradix, 218, Upper Thames St., London, E.C.4. [0620

## VALVES

ALL Types of American Tubes in Stock of Impex and Arcturus makes at competitive prices.

WE Can Also Supply a Full Range of Guaranteed Replacement Valves for Any British non-ring, American or Continental type at an appreciably lower price.

SEND for Lists of These, and also electrolytic condensers, line cords, resistances, etc.

CHAS. F. WARD, 46, Farringdon St., London, E.C.4. Tel.: Holborn 9703. [0452

AMERICAN Valves, first grade, by leading makers, guaranteed, popular types; standard base 5/6, octal base 6/6; 6L6G, 7/6.—General Radio Distributors, 309, Falloden Way, N.W.11. [0626

2/9 R.C.A. American Valves, 50 popular types; also National Union, Hytron; also British non-ring valves, cheapest in Britain; ½d. stamp for revised lists.—Shippers, 18, Corporation St., Manchester. [0607

METROPOLITAN RADIO SERVICE.—Special offer: American valves, in makers' cartons, 3/- each; Octals, 3/6 each; American valves, first grade in all types; trade supplied.—1021, Finchley Rd., N.W.11. Speedwell 3000. [0436

## NEW COMPONENTS

RADIO Components, all makes in stock; complete range of Bulgin and Eddystone short wave parts; American valves specialists; all goods cash with order; post free; established 20 years.—O. Noyes, 163, Shepherd's Bush Market, London, W.12. [8346

# MAY the THIRTEENTH

**On APRIL the THIRTEENTH** the "Wireless World" substantiated our claims for the outstandingly good characteristics of our unequalled Output Transformer Type "036."

**On MAY the THIRTEENTH** we intend to establish our claim for the **WORLD'S BEST P.A. EQUIPMENT** when a Multi Unit Speaker driven by the latest Dual Channel 70-watt Amplifier will announce the opening of the new **KINGSBURY SWIMMING POOL.**

Like the Swimming Pool, the P.A. equipment is up to the minute, and the fact that the Opening is on the THIRTEENTH simply means that neither the design or production of the Pool or the P.A. equipment is a matter of luck.

We feel sure that every discriminating P.A. enthusiast will be interested in our new P.A. type Amplifiers, which we claim to be the embodiment of compact design, plus a generous undistorted output together with the added refinement of two independent input channels with Thermionic Mixing.

May we send YOU a copy of our latest catalogue and technical manual PRICE 6D.

*Specified by the Experts*

**SOUND SALES LIMITED.**

MARLBOROUGH RD., UPPER HOLLOWAY, LONDON, N.19.

*(Contractors to the G.P.O., etc.)*

*Tel.: Archway* 1661/2/3

Hours of Business—
Monday to Friday, 8.30 a.m. to 6 p.m.
SATURDAYS CLOSED

# For PROMPT DELIVERY of High Quality

LOUDSPEAKERS, LOUDSPEAKER CONES LOUDSPEAKER COMPONENTS, TRANSFORMER LAMINATIONS, TRANSFORMER HOUSINGS, TRANSFORMER WINDINGS, CHOKE WINDINGS, FIELD COIL WINDINGS, PERMANENT MAGNETS, PRESS TOOLS AND PRESSINGS, JIG BORING. AUTOMATIC SCREW MACHINE PARTS UP TO 2" DIAMETER.

Contractors to the Admiralty, War Office and Air Ministry.

## Call on BRITISH ROLA LTD.

MINERVA ROAD, PARK ROYAL, N.W.10.
'PHONE: WILLESDEN 4522-3-4-5-6

**BOOKS ON WIRELESS**

Write for complete list to
Iliffe & Sons Ltd., Dorset House, Stamford St., London, S.E.1
W.W.1

## COMPONENTS

### SECOND-HAND, CLEARANCE, SURPLUS, ETC.

PREMIER SUPPLY STORES.

PLEASE See Our Displayed Advertisement on page 5. [0488

LONDON'S CENTRAL RADIO STORES.

MORE Special Offers; see last week's issue; Decca chrom. speaker grill, 6d.; 7-pin Clix valve-holders, 3d.; K.B. tapped condenser tone controls, 6d.; Ex.-R.A.F. 3-wave buzzer wavemeters, 50 to 600 metres, 12/6; buzzer only, 2/6; R.A.F. mike buttons, latest type, 2/6; Muirhead 0.25 mfd., 7,500v. tested, 5/-; Wearite 500-0-500v. 150 m.a., 4v. 2a., 4v. 2½a., 4v. 2½a., 4v. 5a., 200-250 volts input, 17/6 each.

T.C.C. 2,000 mfd. 12v.w., 3/6; Weston 301 3in. 5 amps. M.C., D.C., 10/-; Turner 2½in. 75 m.a., M.C., 12/6; Ferranti M.C. 2½in. meters, 15 m.a., 15/-; 2 m.a., 17/6; 1 m.a., 25/-; 2½in. electrostatic, 450 volts, 27/6; 2in. 5 volts, 1,000 o.p.v., 17/6; 2.5 m.a., 50 m.a., 250 m.a., 16/- each; Ferranti Multi-range A.C., D.C. meter, 55/-; large super sensitive Weston 20,000 o.p.v., 48 ranges, £12; 2½in. 1 m.a. A.C., 35/-.

B.I. 4 mfd., 450v.w., oil filled, 2/- each; R.A.P. auto transformers, 100 watts, 8/6; T.C.C. 10 mfd., 400v.w., 4/-; Decca dual ceramic trimmers, 2×140, 2×250 mmfd., 6d. each; Paxolin, 30 mmfd., 3d.; 50ft. coils rubber connecting wire, ex-Philips, 9d.; T.C.C., 10 mfd., 250v.w., 2/-; bargains in 1939 radio sets; call and hear; many other bargains for callers; orders over 5/- post free; all goods in new condition and guaranteed.

LONDON'S CENTRAL RADIO STORES, London's Only Walk Round Radio Store, 23, Lisle St., Leicester Sq. (local Tube), London. 'Phone: Gerrard 2969. [8445

OLIVER'S Offer Aluminium Chassis, 18 s.w.g., 16in.×10in.×3in., new, undrilled, 6/6; any size made to order; quotations free.

RESISTANCES, electrolytics, etc.; send for lists.—Olivers, 676, Christchurch Rd., Boscombe, Hants. [8432

RYALLS RADIO, 280, High Holborn, London, W.C.1, offer new goods, post free.

ELLIPTICAL Speakers, Celestion, suitable Ekco replacements, 750 and 1,250 ohms, less transformers, speech 25 ohms, new, handle 8 watts, carry up to 120 m.a.; 5/6 each.

SPECIAL Offer of New Ferranti Transformers, AF5, OMP6, AF6c, OPM16c, 8/9; AF17c, B2 chokes, 6/9; OPM8 (15-1), AF10, B8 chokes, OPM1c, 4/9; all each.

GARRARD AC Induction Type AC7a Gramophone Motors, with pick-ups complete, 200-250v., 12in. turntable and unit plate, auto. stop, speed regulator, new; 32/6 each.

WEARITE 110 k.c. I.F.'s with Top Trimmers, 1/6 each; sets band pass air core superhet coils, ex Halycon, screened chassis type, 4/9 set five; 110 kc. with coil details.

B.I. Tubular 4mf. 200v., 6d. each or 4/- dozen; B.I. 0.05, 1/3 dozen. 7/9 gross; B.I. 0.25 mf. tubulars, 2/- dozen, 4/6 per three dozen.

SPEAKERS, pairs, brand new, elliptical cone speakers, made by first class firm, quality of reproduction outstanding, push-pull pentode transformer, fields 325 ohm for smoothing choke, 8,600 as bleeder, circuit available, handle 10-15w.; 14/- pair.—Ryalls Radio, see above. [8374

VAUXHALL UTILITIES, 163a, Strand, W.C.2.—Write for free list; Collaro A.C. gramophone motors, 28/-.

VAUXHALL.—Screened iron-cored 2-gang coils, switch, circuit, 11/3; I.F. transformers, 465 k/cs, 6/-.

VAUXHALL.—Hivac valves, all types; full range of pick-ups, from 11/-. [8437

COLLARO A.C./D.C. Record-changers, 200-250, plays eight 10in. or 12in. records, mixed, also incorporates repeater and rejector; limited quantity, £5/5, in sealed cartons.

HENRY'S, 72, Wellington Ave., Stamford Hill, N.15. Stamford Hill 2907. [8216

SOUTHERN RADIOS Bargains.—Sale now proceeding of hundreds of bargain lines, goods previously advertised still available.—Southern Radio, 46, Lisle St., London, W.C.1. Gerrard 6653. [8236

MAINS RADIO DEVELOPMENT Co. Can Now Offer Immediate Delivery of Transatlantic All-wave Tuning Packs. Stamp for details. Carriage paid by return, immediate delivery, telephone Tudor 4046, call mornings. Stamp for list 226.

AMAZING Opportunity.—Fifty N.S.F. marked and coloured coded resistors, ½, 1 and 2 watt, wire ends, 20 good sizes in every parcel of 50 resistors; 2/6 per 50 only.

TUBULAR Condensers.—400 volt working, wire ends, best make. 0.0001-0.05 mfd., 4d.; 0.1 mfd., 4d.; 0.25, 0.5 mfd., 6d.

CLIX Unused Chassis Valve-holders, 5-pin, 7-pin, 3d. each. All American sizes, 6d. each. Best sleeving, 1½d. yard.

CENTRALAB Latest Potentiometers, long spindle, unused. All sizes, 5,000 ohms. to 2 megohm, 2/-; with mains switch, 2/3.

FIRST-GRADE Boxed American Tubes, guaranteed, 4/- each; octals, 4/6; T.C.C. dry metal 8 mfd., 600 volt, 2/3.

POLAR MIDGET Latest Three-gang Condensers, screened, trimmers, ¼in. spindle, 0.0005 mfd., 100 k/c tracker (perfect straight two-gang), 2/6.

DUBILIER Mica Tag Condensers, 0.00005, 0.0001, 0.0002, 0.0003, 0.0005 mfd., 3d.; 2/6 dozen.

ERIE One Watt, colour coded, unused resistors, any size, 50 ohms to 5 megohm, your selection, 3d.; 2/6 dozen. Two watt, 6d.

MAINS RADIO DEVELOPMENT Co., 4-6 Muswell Hill Road, London, N.6. Tudor 4046. [8394

FOR Disposal Below Cost, quantity of new receivers, amplifiers, feeder units, chokes, condenser banks, Ferranti and other transformers, etc.; state requirements; write, 'phone or call.—W. T. Rickards, 17, Heathfield Rd., King's Heath, Birmingham. Highbury 1804. [8390

*The LITTLE METER that does the* BIG JOBS

BRITISH MADE

THE UNIVERSAL

# AVOMINOR

*Regd. Trade Mark*

**ELECTRICAL MEASURING INSTRUMENT**

| D.C. VOLTAGE | |
|---|---|
| 0-75 mv. | 0-100 v. |
| 0- 5 v. | 0-250 v. |
| 0-25 v. | 0-500 v. |
| **A.C. VOLTAGE** | |
| 0- 5 v. | 0-100 v. |
| 0-25 v. | 0-250 v. |
| | 0-500 v. |
| **D.C. CURRENT** | |
| 0-2.5 ma. | 0- 25 ma. |
| 0-5 ,, | 0-100 ,, |
| | 0-500 ,, |
| **RESISTANCE** | |
| 0- 20,000 ohms | |
| 0-100,000 ,, | |
| 0-500,000 ,, | |
| 0- 2 megohms | |
| 0- 5 ,, | |
| 0-10 ,, | |

Weighing only 18oz. and measuring but 4¾"×3¾"×1¾", this is a really portable meter of high accuracy for measuring A.C. & D.C. volts, D.C. milliamps and ohms. An accurate moving-coil movement gives a 3" full scale deflection. Total resistance is 200,000 ohms. Complete with leads, interchangeable testing prods and crocodile clips; and instruction booklet.

**£5.10.** *(leather case 10/-)*

DEFERRED TERMS IF DESIRED

***Write for descriptive pamphlet***

*Sole Proprietors & Manufacturers:—*
**The Automatic Coil Winder & Electrical Equipment Co., Ltd.,**
Winder House, Douglas Street.
London, S.W.1. *'Phone: Victoria* 3404/7

# RADIOMART

G5NI (BHAM) LTD.

**THE SHORT-WAVE SPECIALISTS**

**SPECIAL OFFER!!!**
Fully shrouded Transformers by America's largest manufacturer. While they last.

| | |
|---|---|
| All 230 v. primary and fully impregnated. | |
| T28708—375 375 v. 150 m/A., 6.3V5A. 2.5V3A. 5V3A. | 15/- |
| T19610—350 350 v. 150 m/A., 2.5V6A. 2.5V2A. 5V3A. | 12/6 |
| T7236—375/375 v. 120 m/A., 6.3VCT. 4A. 5V3A | 10/6 |
| T7326—350/350 v. 100 m/A., 6.3VCT. 3A. 5V3A | 8/6 |
| T7307—350/350 v. 80 m/A., 6.3VCT. 3A. 5V3A | 7/6 |
| T7000—320/320 v. 80 m/A., 6.3V4A. 5V3A | 7/6 |
| T6025—320/320 v. 80 m/A., 2.5V6A. 5V3A | 7/6 |
| T464919—10V4A Primary Tapped 110—250 v. | 5/6 |
| T1113AB—110/230 v. 500 watt Auto Transformer | 29/6 |
| The following chokes are interleaved and impregnated. | |
| T7007—250 m/A., 135 ohms, 20-8 Hy., cadmium shrouded | 12/6 |
| T7007A—150 m/A., 250 ohms, 30-12 Hy., cadmium shrouded | 12/6 |
| 100 m/A., 20 Hy., 500 ohms, unshrouded | 4 11 |
| 60 m/A., 15 Hy., 250 ohms | 1 11 |

**HEAVY DUTY TRANSFORMER** for models, bells, etc., 6 v. 3 a., 2/3. 4 mf., 1,500 v. test 500 v. wkg. oil filled condensers. 2/-.

**HEAVY DUTY** Mains Transformer, worth 45/-. 350-350, 150 m/A. 4 v. 2.5 a. CT, 4 v. 6 a., CT, 12/6; 300-300 v., 80 m A., 4 v. 3 a., CT. 4 v. 2 a., CT. 8/6. Moving Coil Speech Transformers, 1/11.

**GANG CONDENSERS** with Airplane Dial, 8 and 80-1. Cost 35/-. Few only. 4/11. Utility, 7/6. Microdials, 3/9.

**W.B. 8in. PERMANENT MAGNET SPEAKERS AT ONE-THIRD COST** Extension Type (no Transformer), 8/11. Standard Type (with Transformer), 10/6. Energised 8", 1,200 ohms with Transformer, 6/11.

**PUSHBACK** Wire, 6 yds., 6d., heavy, 9d. Resin-cored Solder, 6ft., 6d.; Screened Flex, single, 6d. yd.; twin 9d. yd. Assorted Solder Tags, 6d. packet. Humdimmers, 6d. each.

Centralab pots, all sizes, 1/6; switched, 2/-; tubular glass fuses, 2d. Milliammeters, 0.25 m.a., upwards, 5/9; Super, 6/9.

**OUR NEW 66-PAGE MANUAL,** packed full of valuable information. Post Free, 7½d.

**THE NEW RAYMART CATALOGUE** shows dozens of New Short-wave Components and is yours for 1½d. post free.

**VALVES.**—A complete range of replacements, showing a saving of over 50 per cent. Quotations on receipt of types required. Quantity Discounts to Service Engineers. TRADE enquiries for communication equipment solicited.

**RADIOMART** *Telephone: MIDland 324*
G5NI (Birmingham) Ltd.
**44, HOLLOWAY HEAD, BIRMINGHAM**

We do quite a lot of business making up transformers to customers own specifications; but we *have* a standard list. May we send you a copy?

**W. BRYAN SAVAGE LTD**

*Westmoreland Rd., London, N.W.9. 'Phone: Colindale 7131*

*"Radio Laboratory Handbook." Price 8s. 6d. net. Post free 9s.*

## COMPONENTS—SECOND-HAND, CLEARANCE, SURPLUS, ETC.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1. Holborn 4631.

PRESS Button Assembly (complete with circuit), comprising compact unit size 6in.×6in.×2in., complete with six press buttons and manual trimmer for balancing circuits, complete with ten silver mica capacitators; ideal for adapting existing receiver for press button tuning; 9/11 each.

SET of 4 Skeleton Type All-wave Coils (manufacturers type unshielded), comprising oscillator coil, wave trap, broadcaster aerial coil and short wave coil with circuit; 2/6 set of 4.

EARPHONES by Standard Telephones, 2,000 ohms resistance; 5/11 per pair.

AMERICAN Press Button Car Radios, 6- and 12-volt models, manual tuning plus 6 press buttons, medium wave only, 6 gns.; medium and long, £6/15.

CAR Aerials, running board type, 8/6; chromium roof type, 11/6.

***

T.C.C. New Range of Compact Electrolytic Condensers, as follows:—

T.C.C. 8 Mfd. Tubular Electrolytic, wire ends, 500 volt working, 600 volt surge; 1/6 each.

T.C.C. 8 Mfd. Midget, wire ends, size 2½in.×1½in., 500 volt working, 600 volt surge; 1/6 each.

T.C.C. 8 plus 8 4-lead Midget Electrolytics, 500 volt working, 600 volt surge; 2/9 each.

T.C.C. 1 Mfd. Tubular, wire ends; 1/- each.

T.C.C. Bias Condensers:—50 mfd. 12 volt, 1/-; 25 mfd. 25 volt, 1/-; 25 mfd. 50 volt, 1/3; 50 mfd. 25 volt, 1/3; 50 mfd. 50 volt, 1/6.

***

WEARITE Mains Transformers, standard for the season and exclusive to us, made to strict electrical standards, wire end type, all windings centre tapped, screened primaries, tapped inputs, 200-250 volts, screw adjustment.

TYPE R.C.1, 250-0-250, 80 m.a. 4 volts 2.5 amp., 4 volts 4.5 amp.; 9/6 each.

TYPE R.C.2, 350-0-350, 120 m.a. 4 volts 2.5 amp., 4 volts 5 amp.; 11/- each.

TYPE R.C.3, 350-0-350, 150 m.a. 4 volts 2.5 amp. 4 volts 2 amp. 4 volts 5 amp.; 12/6 each.

R.C.4 500-0-500, 150 m.a., 4 volts 2 amp., 4 volts 2 amp., 4 volts 2.5 amp., 4 volts 5-6 amp.; 19/6 each.

TYPES R.C.1. and R.C.2 Drop Through Type, capped.

TYPES R.C.3 and R.C.4 Upright Mounting Type, fully shrouded.

WEARITE Auto Transformers, type R.C.5, fully shrouded, input 100-110 volts, output 200-250 volts, 100 watts; 12/- each.

***

PLESSEY Slow-motion Drives.

TYPE 1841-1125, size of dial 5in. square; 2/- each.

TYPE 1393, size of dial 4×5; 1/10 each.

TYPE 1510, size of dial 4×5; 1/10 each.

TYPE 2077, clock face dial, separate indications, size of dial 5×5 (R. and minute-hand type), geared; 4/6 each.

TYPE 2806, size of dial 8×3, overall height 8in.; 1/3 each.

TYPE 1825, size of dial 5½×1¾; 1/3 each.

ALL Above With Plain Unprinted Scales Only.

***

CRYSTAL Pick-up, high grade American, bronze finish complete with arm; £1/5 each.

STANDARD Octal Base Valve Holders; 4d. each.

AMERICAN Valve Holders, best quality, 4-, 5-, 6-, and 7-pin; 3d. each.

CLIX 5-pin Chassis, 3d. each; Clix 7-pin chassis, 4d. each; Bulgin S.P.S.T. twist switch, 9d. each; Bulgin D.P.D.T. twist switch, 1/- each.

T.C.C. Paper Tubular Condensers, all sizes up to 0.1, 5d. each, 4/6 doz.; 0.25 ditto, 7d. each; 0.5, 10d. each.

POLAR N.S.F. 1 Watt Resistances; 3½d. each, 3/- doz.; all sizes up to 2 meg.

MAINS Smoothing Chokes, Wearite unshrouded, fitted wire ends:—30 henry 80 m.a., 500 ohms, 7/6 each; 40 henry 150 m.a., 500 ohms, 10/6 each.

AMERICAN Valves.—Complete range of Raytheon 1st Grade stocked; competitive prices consistent with quality; write for lists.

***

LISSEN Valves, brand new, boxed, as follows:—H2, L2, 2/- each; BB.220A, 3/11 each; SGV, SG 215, 3/11 each.

***

CENTRALAB Volume Controls Available as Follows, with switch, long spindle:—1,000, 5,000, 10,000, 25,000, 50,000, 100,000, 250,000, 2/- each.

G.E.C. Relays, make and break type, 3,300 ohms; 4/- each.

100 Watt Auto Transformers, 100-250 volts reversible, wire end type; 5/11 each.

RADIO CLEARANCE Bargains Continued in Third Column.

# PREMIER ★ RADIO ★

### THE NEW PREMIER 10-15 WATT ALL-BAND TRANSMITTER

Designed to meet the demand for a really compact self-contained T.X., for 'Phone or C.W. on all bands. A 6L6 is used as a modulated oscillator in a Tritet circuit, allowing a fundamental and second harmonic operation, without coil changing, from any one Xtal. A 6C5 speech amplifier is R.C. coupled to a 6L6 modulator, giving approx. 9-10 watts audio. A 400-v. power supply with generous smoothing gives hum-free output. In steel cabinet, in black crackle, 12"×9"×8". Complete with Xtal and coils for 7 and 14 mc. operation ... ... ... **£10-10-0**

**PREMIER 10 watt C.W. TRANSMITTER** for A.C./D.C. mains, 7 mc. Xtal Controlled. Complete with Xtal valves and meter, **£4-4-0**

### PREMIER SHORT-WAVE KITS

Complete to the last detail including all Valves and coils, as well as theoretical and wiring diagrams and lucid instructions for building and working. Each kit is supplied with a steel Chassis and Panel and uses plug-in coils to tune from 13 to 170 metres.

1 Valve Short-Wave Receiver or Adapter Kit ... 17/6
1 Valve Short-Wave Superhet Converter Kit ... 20/-
1 Valve Short-Wave A.C. Superhet Converter Kit 22/6
2 Valve Short-Wave Receiver Kit ... ... ... 25/-
3 Valve Short-Wave Screen Grid and Pentode Kit 58/6

**PREMIER U.S.A. QUARTZ TRANSMITTING CRYSTALS.** 7 mc. Band, 10/- each, with Calibration Certificate. Enclosed holder and Base, 3/-.

**DUMMY ANTENNA**, a necessity for the A.A licensee, 15/- each.

**TRANSMISSION LINE**, Low Impedence 72 Ω 3d. yd. Super quality 80 Ω 6d. yd.

**PREMIER SHORT-WAVE COILS**, 4- and 6-pin types, 13-26, 22-47, 41-94, 78-170 metres, 1/9 each, with circuit. Special set of S.W. Coils, 14-150 metres, 4/- set, with circuit. Premier 3-band S.W. coil, 11-25, 19-43, 38-86 metres. Suitable any type circuit, 2/6.

**ULTRA S.W. COILS**, 4-10 metres Wound silver plated Wire. Mounted on Trolitul base. Inside diam. coils ¾", 3, 4, 5, 6 or 7 turns, complete with base, 1/- each.

**UTILITY** Micro Cursor Dials, Direct and 100.1 Ratios, 3/9.

**PREMIER** Short-Wave Condensers, all-brass construction, with **Trolitul** insulation. 15 mmf., 1/6; 25 mmf., 1/7; 40 mmf., 1/9; 100 mmf., 2/-; 160 mmf., 2/3; 250 mmf., 2/6.

**TROLITUL DOUBLE SPACED TRANSMITTING CONDENSERS.** 15 mmf., 2/9; 40 mmf., 3/6; 100 mmf., 4/-; 160 mmf., 4/6.

**NEW TROLITUL SPLIT STATOR CONDENSERS**, 50×50 mmf., 10/6.

**COIL FORMERS**, 4- or 6-pin low-loss, 1/- each.

**AMERICAN VALVES.** We hold the largest stocks of U.S.A. tubes in this country and are sole British Distributors for **TRIAD** High-grade American Valves. All types in stock. Standard types, 5/6 each. All the new Octal Base tubes at 6/6 each, 210 and 250, 8/6 each.

**EUROPA MAINS VALVES**, 4 v. A.C. Types, A.C./H.L., A.C./L., A.C./S.G., A.C./V.M.S.G., A.C./H.P., A.C./V.H.P., A.C./P., and 1 watt D.H. Pentodes, all 4/6 each. A.C./Pens., I.H., 5/6; A.C./P.X.4, 6/6; Oct. Freq. Changers, 8/6; Double Diode Triodes, 7/6; Triode H. ex. Freq. Ch., 8/6; Tri. Grid Pen., 10/6; 3½-watt D.H. Triode, 7/6. 350 v. and 500 v. F.W. Rect., 5/6. 13 v. 2 amps. Gen. Purpose Triodes, 5/6; H.F. Pens. and Var.-Mu. H.F. Pens., Double Diode Triodes, Oct. Freq. Changers, 7/6 each, Full-wave and Half-wave Rectifiers. 5/9 each.

### MATCHMAKER UNIVERSAL MODULATION TRANSFORMERS

Will match any modulator to any R.F. load. 50 watts, 17/6; 150 watts, 29/6; 300 watts, 49/6.

**MATCHMAKER UNIVERSAL OUTPUT TRANSFORMERS.** Will match any output valves to any speaker impedance. 11 ratios from 13 : 1 to 80 : 1. 5-7 watts, 13/6; 10-15 watts, 17/6; 20-30 watts, 29/6. Send for full details.

**PREMIER AC/DC MOVING IRON METERS.** 2½ in diam. Flush Mounting. All ranges. 10 m.a., 30 m.a. 50 m.a., 100 m.a., 250 m.a., 500 m.a., 5/9 each.

**AMMETERS.** 1, 3, 5, 10 or 30 amps., 5/9 each.

### PREMIER 1939 HIGH FIDELITY AMPLIFIERS

**A New Complete Range of 7 High Fidelity P.A. Amplifiers for A.C. or A.C./D.C. Mains operation.**

| | Kit of Parts with Valves. | Completely Wired and Tested. |
|---|---|---|
| 3-watt A.C. Amplifier ... | £2 0 0 | £2 15 0 |
| 3-watt A.C./D.C. „ ... | £2 0 0 | £2 15 0 |
| 6-watt A.C. „ ... | £5 5 0 | £6 0 0 |
| 8–10-watt A.C./D.C. „ ... | £4 10 0 | £5 5 0 |
| 15-watt A.C. „ ... | £5 15 0 | £7 0 0 |

Black Crackle Steel Cabinet 15/- extra.

**NEW PREMIER SELF-POWERED RF TUNING UNIT**, incorporating a Var.-Mu pentode amplifier followed by a power grid detector. Designed for high-fidelity reception. Wave range 200-560 and 800-2,000 metres. **£4 - 9 - 6** complete with valves.

**IGRANIC** insulated midget jacks 1/6 each. Plugs 1/3.

*Send for full details.*

Orders 5/- and over sent Post Free. Under 5/- please add 6d. Postage.

**Have you had our 1939 Catalogue, Handbook and Valve Manual? 90 pages of Radio Bargains and Interesting Data. Price 6d.**

**ALL POST ORDERS TO: Jubilee Works, 167, Lower Clapton Road, London, E.5.** *Amherst* 4723.
**CALLERS TO: Jubilee Works, or our NEW PREMISES, 169, FLEET STREET, E.C.4.** *Central* 2833
**or 50, High Street, Clapham, S.W.4.** *Macaulay* 2381.

## COMPONENTS—SECOND-HAND, CLEARANCE, SURPLUS, ETC.

RADIO CLEARANCE, Ltd., continuing bargains in components, etc.

***

STANDARD Telephone Mains Transformer, Type 1, input 200-250 volt, output 250v. 40 m.a., 4 volt 2.5 amp.; 2/6 each.

TYPE 2, input 200-250 volt, output 250 volt 200 m.a., 4 volt 2.5 amp.; 3/- each.

TYPE 3, input 200-250 volt, output 200 volt 500 m.a., 4 volt 4 amp.; 5/6 each.

HELLSEN 8 mfd. Cardboard Electrolytics. 450 volt working, wire end; 1/- each.

CONDENSER Block, four, 0.05 mfd., metal cased, 500 volt working; 1/9 each.

TYPE 4 Smoothing Choke, 500 m.a. 100 ohms 12 henrys; 8/6 each.

CONDENSER Block, two, 6 mfd., 2.1 mfd., metal cased, 500v. wkg.; 2/3 each.

METAL Safety Case with Base and 2 Valve Holders, size 7½×6in.×5¼in.; 2/6 each; finished brown crackle.

METAL Safety Case with Base and 2 Valve Holders, size 12½in.×8¾in.×5¾in.; 3/6 each; finished brown crackle.

32 M.f.d. 400 volt working, can type wet electrolytic; 1/6 each.

16 M.f.d., 450 volt working; 1/- each.

ALL Orders to the Value of 5/- Post Free; postage must be enclosed with orders for less than 5/-; enquiries 1½d. stamp if reply expected. Hours of business: Week-days, 9 a.m. to 7 p.m.; Saturdays, 9 a.m. to 1 p.m. Postal rates apply to the United Kingdom only, orders for Ireland and abroad must include sufficient postage to cover whatever the value of same.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1. Telephone: Holborn 4631. [8413

### Wanted

URGENTLY Required, first grade test gear and all-wave radios; remember, we pay more; full market value paid; offers per return.

LONDON'S CENTRAL RADIO STORES, 23, Lisle St., Leicester Sq., London, W.C. [8447

WE Buy for Cash All Types of Modern Second-hand Radio Sets and Accessories, test meters, parts, etc. We pay more than any other dealer. Part exchanges. Bring, send or will call.—University Radio, Ltd., 238, Euston Rd., London, N.W.1. 'Phone: Euston 3810. [8366

## REPAIRS AND SERVICE

"SERVICE With a Smile."

AMERICAN Valves, spares, linecords, rewinds; repairers of all types of American and British receivers.—F.R.I., Ltd., 22, Howland St., W.1. Museum 5675. [0434

LONDON'S CENTRAL RADIO SERVICE.

RADIO Repair Service; all makes and models; crystal sets to Autotropes; quotations by return; collected and delivered; dealers represented.—'Phone: Gerrard 2969. Ex 2 L.C.R.S., 23, Lisle St., Leicester Sq., W.1. [8446

BAKERS.—Send your next speaker repair, any make, to the pioneer manufacturers, Bakers Selhurst Radio, South Croydon. [8435

LOUD-SPEAKER Repairs, British, American, any make, 24 hours service; moderate prices.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0590

GUARANTEED Repairs Any Transformers, choke, motor: armature, converter, dynamo, etc.; keenest prices, immediate quotation, prompt dependable service.—See below.

L.T.P. (LONDON TRANSFORMER PRODUCTS, Ltd.), Willesden, N.W.10. Willesden 6486 (3 lines). [6892

MAINS Transformer Service. Repairs, rewinds, or construction to specification of any type, competitive prices and prompt service.—Sturdy Electric Co., Dipton, Newcastle-on-Tyne. [0516

EPOCH Speaker Replacements, cone assemblies supplied from 4/-; field coil and transformer rewinds; trade radio service.—National Radio Epoch Reproducers, 126, Elthorne Rd., N.19. Arc. 1319. [8433

METROPOLITAN RADIO SERVICE.—Guaranteed repairs to American and British receivers; American valves, service parts and rewinds; trade supplied.—1021, Finchley Rd., N.W.1. Speedwell 3000. [0435

SCOTT-SESSIONS REPAIR SERVICE.—All types of receivers overhauled, rebuilt, repaired, including American communication sets, W.W. Monodials, All-wave Super-Seven. Variable Selectivity IV., etc.

SCOTT-SESSIONS REPAIR SERVICE, popular for 15 years from Land's End to John-o-Groats; van collection London area; immediate, courteous and skilled attention to every instruction.

SCOTT-SESSIONS REPAIR SERVICE. Exchange Works, Muswell Hill, N.10. Tudor 4101-2. [7497

REPAIRS to Moving Coil Speakers a Speciality: cones and coils fitted, fields altered; prices, including eliminators, quoted; loud speakers, 4/-; L.F. and output transformers, 4/-, post free; guaranteed satisfaction; trade invited, estimates free; prompt service.—Loud-Speaker Repair Works, 5, Balham Grove, London. Battersea 1321. [0394

## SITUATIONS VACANT

WANTED, assistant for dispatch dept. radio, mail order house, male or female; radio knowledge essential.—Box 9682, c/o *The Wireless World*. [8427

TRANSFORMER Manufacturer, Westminster district, requires lad, 17-18, to learn all processes in production of special transformers.—Box 9711, c/o *The Wireless World*. [8448

LONDON Firm, commencing production radio meters, requires technical expert to undertake design and oversee production; only person who has had similar position considered.—Box 9681, c/o *The Wireless World*. [8426

ROYAL Air Force.—Men of good education required for enlistment and training as wireless operators and armourers, age limits 17¼-35. Write or call.—R.A.F. Recruiting Depot, Victory House, Kingsway, London, W.C.2, or any R.A.F. Recruiting Depot. [8419

# ELECTRADIX

## BARGAINS IN METERS.

We have a liquidated stock of 2½" panel Meters by Weston, Turner, Elliott, etc. Milliammeters for Transmitters 100 m/a with shunt switch, Volt and Ammeters of practically every range. R.F. Thermo Ammeters for small transmitter aerials, etc. Transmitting and S/W Condensers, by Cyldon, Eddystone, J.B., etc. Enclosed Keys, Rotary and Delay Automatic Switches, Cambridge distant Thermometers.

**HIGH-GRADE** Unipivot Instruments for Lab. work. Model K, 60-0-60, alum. case with thermo attachment. Two Type K ditto, mahogany case. Cambridge Induction Micrometer Unipivot, Model L, mirror scale 0-120, two shunts and vibrator, £7/10/-.

Portable Sub-Standard Moving Coil Meters, mirror scale. C.Z. ammeters G.E.C. 5-0-5 a., reads to 1/10 amp., in screened case, 7in. × 7in. × 3½in., unused. 20/-.

**MIRROR GALVOS**, Reflecting Beam, by Paul Gambrell, Sullivan and Tinsley, £3. Standard Res. Boxes and Univer. Shunts, from 15/-. 2½in. panel Electrostatic meters to 2,000 volts, £2. 3in. dial, 6,000 volts, £4/10/-. 12,000 volts Ev. Edg. Lab. type, £5/10/-, or pair for 2 phases, £10. X-Ray type, 60,000 volts, £4/10/-. Two Laboratory Table "Kelvin" Electrostatic Voltmeters, 100 to 600 volts, large scale, 70/-.

**MICRO-AMMETERS** for Valve Voltmeters, etc., 0 to 50 microamps full scale, 50 mV. moving coil, flush panel, 2½in. dial. Reads direct signal strength on crystal, 1,000 ohms. 40/-.

Weston Model 354. Central zero 1 to 15 amps., polar mag. dead beat. Flush panel, 2½in. dial. Sale price, 5/-. Weston, 0 to 30 m/a., mov. coil milliammeters, 17/6; 0-5 m.a., 17/6. Hoyt CZ mov. coil milliammeters, 25-0-25 m/a., 10/-.

**E665 WESTON SERVICE TESTER**, D.C./A.C. for any circuit, any valves, moving coil meter selector circuit switch. A 20-guinea set for £8/17/6. Guaranteed. Several Signal Generators and Oscillators.

**ELLIOTT & E.E.** No. 108, with moving-coil meter and graded Rheo., 37/6. Silvertown astatic horizontal Galvos, jewel pivots, 7/-. Ammeters, all ranges to 20 amps., 7/-.

If you have Resistances to measure you will find a Standard **RESISTANCE BOX** of great use. Tested and guaranteed to G.P.O. standard. We have a few left. 1,000 ohms, 4,300 ohms, 8,000 ohms, 12,400 ohms. Cheap.

**MEGGERS AND OHMMETERS.** Evershed Bridge with decade res. box 10,000 ohms. Meggers. 100 volts, 250 volts, and 500 volts, and small MEG. for D.C. mains. N.C.S. Ohmer, 500 volts to 20 megs. Ev. Edg. Metrohm, 250 volts .01 to 20 megs. Silvertown Portable Test Set, Bridge. Cheap.

**FOCOMETER.** Lens Calibrator for testing focal length of Lens, with microscope stand, fine adjustment. Cost £30. £3/15/-.

**MILLIAMMETERS.**—8 m/a back of panel illuminated milliammeters. Skeleton type, 970 ohms D.C. with plain scale and 1in. needle with mica panel, back lamp and bracket. Great bargain at 3/9 post free. Bulgin Midgets, 8 m/a, 6/-. Sifam, 1½in., 10 m/a, 8/6. 2,000 meters to select from.

**HIGH FREQUENCY AERIAL RADIATION METERS.**—Flat panel, 2½in. dial, Hot wire, 0-500 m/a, 7/6; 0 to 1 amp., 10/-; 0 to 2 amps., 12/6; 0 to 2½ amps., 12/6. 3in. dial ditto, 0-4 amps., 21/-. Panel 4in. dial, 3 amps., £1/10/-; 7in. dial, 2 to 15 amps., £1/15/-.

**D.C. CURRENT RECORDERS**, Nalder Chart Recording Ammeters, wall type, 0 to 5 amps., moving coil. Shunts to other ranges. 12-hour drum clock, £5/10/-. Time Switches, 1 amp. to 500 amps., 48 hours, £1 to £4.

TWO CLEAR SCALES WITH MIRROR ARE ON THE

THE DIX-ONEMETER. 55/-.

**DIX-ONEMETER**

The Dix-Onemeter with only 6 Terminals, but 50 Ranges, is a valuable instrument for laboratory work. It is of portable size to go in the pocket, but big enough to cover the whole range of D.C. electrical measurements, 50 microamps. to 20 amps. and 20 millivolts to 2,000 volts.

**55/- ONLY**

Multipliers from 6/6 each.

**THE DIX-MIPANTA.** A wonderfully versatile moving-iron multirange meter for service on A.C. jobs. No projecting terminals. THREE ranges of volts: 0-7.5, 0-150, 0-300. Used for MILLIAMPS, reads: 0-12½ m/a and 0-75 m/a. In black bakelite case. Measures only 2½in. by 2½in. The Dix-Mipanta, 19/6.

Send for our Latest Bargain List "W" Free.

**ELECTRADIX RADIOS**

218, UPPER THAMES STREET, LONDON, E.C.4

'Phone: Central 4611



*Second Edition—Completely Revised*

# RADIO DATA CHARTS

## A SERIES OF ABACS

**providing most of the essential Data required in Receiver Design.**

**By R. T. BEATTY, M.A., B.E., D.Sc.**

"Radio Data Charts" provide designers of wireless apparatus with a ready and convenient means of solving problems without having recourse to complicated formulæ and mathematics.

By the use of the new "Radio Data Charts" such abstruse problems as the design of tuning coils are solved almost as easily as the simple application of Ohm's Law.

**4/6 net** **By post 4/10**

*From leading booksellers or direct from the publishers.*

**ILIFFE & SONS LTD.,**

**Dorset House, Stamford St., London, S.E.1.**

W.W.93


## SITUATIONS VACANT

AIR MINISTRY.

DIRECTORATE of Signals (Civil Aviation).

APPLICATIONS are invited for appointments as Civilian Wireless Operators at Air Ministry Civil Aviation Wireless Stations.

APPLICANTS, who should not have reached their 40th birthday on June 1st, 1939, should preferably possess the First Class Postmaster-General's Certificate or the Air Operator's Certificate in Wireless Telegraphy and have had experience of radiotelephony, direction-finding and maintenance work. Operators will be required to serve at any Air Ministry Civil Aviation station at home or abroad. At present there is only one station situated outside the United Kingdom manned temporarily by Air Ministry staff.

SALARY is at the rate of 67/- a week, rising by annual increments for approved service to 112/- a week inclusive. Should candidates be required to serve abroad, appropriate additional allowances would be paid.

THE first two years of service will constitute a probationary period and confirmation of appointment will be contingent on an operator passing an examination in all phases of his work.

POSTS will be Unestablished, i.e., non-pensionable in the first instance. A proportion of the total staff is pensionable, however, and subject to the existence of vacancies in the permanent staff operators may be considered for establishment according to their seniority, conduct and ability, provided that the probationary period has been satisfactorily completed.

REQUESTS by Postcard for Forms of Application should be addressed so as to reach the Under-Secretary of State, Air Ministry (S.1.e.), Kingsway, London, W.C.2, not later than May 24th, 1939.

SELECTED Applicants will be required to attend at the Air Ministry for interview on June 12th and 13th, 1939.

NO application will be considered unless the applicant states that he will be able to attend on either of these dates.

NO other arrangement regarding interview can be entertained. [8425

WAR DEPARTMENT.

STAFF for Scientific Research.

APPLICATIONS Invited for the Undermentioned Appointments to the Staff for Scientific Research for service in the first instance as follows:—

(A)—(D), (F), (G), and (I), at the Research Department, Royal Arsenal, Woolwich, S.E.18.

(E) and (H), at the Chemical Defence Experimental Station, Porton, Wiltshire.

JUNIOR Scientific Officers and Assistants III should preferably be under the age of 30; others preferably under 40.

THE Qualifications Required are:—

(A) Scientific Officer (Male). First- or Second-class Honours Degree in Physics with at least 4 years' experience in research and experimental work in design of oscillographs, valve amplifiers, etc., or in measurement of short-time transients.

(B) Scientific Officer (Male). First- or Second-class Honours Degree or equivalent in Chemistry with at least 4 years' research experience in physical chemistry; experience with explosive reactions desirable.

(C) Junior Scientific Officer (Male). As for (A) or (B) but with less research experience.

(D) Assistant I (Male). Degree or equivalent qualification in Physics with considerable experience in a research or industrial electrical and/or physical laboratory. Experience in the measurement of short-time transients desirable.

(E) Assistant I (Male). Degree in Physics or equivalent qualification and several years' laboratory and/or industrial experience in physical research or experimental work. Knowledge of the applications of photo-electric cells and general workshop practice desirable.

(F) Assistant II (Male). Degree or equivalent qualification in chemistry with experience in a chemical research laboratory.

(G) Assistant II (Female). Degree or equivalent qualification in Physics or Chemistry with a sound knowledge of languages (German essential) and experience of abstracting and indexing technical literature.

(H) Assistant II (Male). Degree or equivalent qualification in Physics with several years' practical experience in research or experimental work.

(I) Assistant III. Have passed an Intermediate Science examination or possess some equivalent qualification in Chemistry and Physics. Practical experience in a chemical laboratory or a wireless equipment laboratory essential.

SALARY Scales, etc.:—

SCIENTIFIC Officer. £400 by £18 to £454, and thence by £25 to £680 a year (efficiency bar at £580). Exceptionally a commencing salary up to £454 a year will be given to candidates with special qualifications and experience in research or experimental work. The Federated Superannuation System for Universities applies to these appointments.

JUNIOR Scientific Officer. £275 by £18 to £347 a year. After two years' probationary service (if reached) the Federated Superannuation System for Universities would apply.

ASSISTANT I (not pensionable). £400 by £18 to £515, with extension in certain cases to £580.

ASSISTANT II (not pensionable). £315 by £12 to £385 a year.

ASSISTANT III (not pensionable). Male: £150 by £12 to £310. Female: £130 by £12 to £260. (Efficiency bar at £214.) Higher commencing salaries up to £214 may be approved according to qualifications and experience, and in this connection the possession of a University degree will be taken into consideration.

THE Increments are Annual and Subject to Approved Service.

PROMOTION to Higher Grades, and/or (in the case of Assistant grades) appointment to pensionable posts, are governed by suitability and merit as and when vacancies arise. Ex-members of H.M. Forces given preference, other things being equal.

APPLICATION Forms Obtainable by Postcard from the Under-Secretary of State (C.5), War Office, London, S.W.1, and to be lodged by 20th May, 1939. Candidates should state clearly the index letter of the appointment for which they are applying. Quote Appts. 137 (D). [8428


*FOURTH EDITION—*
*Revised and Enlarged with 50 Additional Pages*

# WIRELESS SERVICING MANUAL

**By W. T. COCKING**

*(of "The Wireless World")*

**The most complete book of reference of its kind. A reliable practical guide or amateur and professional.**

The present Edition of the "Wireless Servicing Manual" brings the material of the book right up to date and includes an additional chapter on television receivers which is practically the only source of servicing information available on this subject

Testing apparatus is fully dealt with and the methods of locating and curing faults in receiving equipment are explained in detail.

Ganging, Automatic Volume Control, Instability, Distortion, Mains Hum, Whistles, Local Interference and Aerials are all separately treated.

The reference material, including base-connections for British, Continental and American valves and the various colour codes for components, has been extended and revised.

***BOUND IN CLOTH BOARDS***
***SIZE 7½ ins. × 5 ins.***
***288 Pages***

**PRICE 5/- net**
**By post 5/5**

**Issued in conjunction with "THE WIRELESS WORLD" and Published by the Proprietors:—**

**ILIFFE & SONS LTD.,**
**Dorset House, Stamford Street, London, S.E.1**

W.W.20

THE SIGN of PSEI PRECISION

ELECTRICAL INSTRUMENTS

- Geared slow-motion dials.
- Metal Chassis.
- Racks and Panels.
- Turned and Machined Parts.
- Short-Wave.
- Ultra S/Wave.
- Dia-thermy.
- Electro-Medical.

For MANUFACTURERS only—

We specialise in the production of equipment and parts to individual needs and gladly offer our long experience in the design of special requirements.

. . . and all allied equipment.

Please write for details to—

P.S.E.I (Holdings) Limited, Pilot House, Stoke Newington, Church Street, London, N.16. 'Phone: Clissold 9875.

CONTRACTORS TO H.M. GOVERNMENT

WELBURN 12 WATT AMPLIFIER

Designed and built for consistent hard work. Reliability and first class performance on both speech and music were our first consideration.

NOTE THESE POINTS:
No distortion; No hum: Cool running; Small Input (only 0.008v); Output 12 watts; Overall Gain 116dBs; No pre-amplifier required. Linear Amplification combined with Level Response; Mike-Gramo. Mixer; Mazda Valves; Self-contained in dust-proof steel case.

A SOUND JOB FOR ALL *SOUND* PURPOSES

*Write for 12 pp. descriptive brochure*

RETAIL PRICE £14

WELBURN RADIO LTD.
QUEENSWAY TEAM VALLEY
GATESHEAD-ON-TYNE

THE INSTITUTE OF WIRELESS TECHNOLOGY
(Founded in 1925. Incorporated).

PROFESSIONAL MEMBERSHIP

The advantages of professional membership are open to all qualified wireless engineers.

*Full information, with syllabus, may be obtained from the Secretary, Institute of Wireless Technology, 4, Vernon Place, Southampton Row, London, W.C.1. 'Phone: Holborn 4879.*

Pamphonic
AMPLIFIERS

Pamphonic Reproducers Ltd. (*Associated with PYE Ltd.*)
45, St. Pancras Way London, N.W.1.

'Phone: EUSton 1727.

ENGINEERS!
ARE YOU EARNING LESS THAN £10 PER WEEK?

If so, you cannot afford to carry on without reading our 268-page Handbook. The book explains clearly and definitely many ways of carving out a successful career. Among other things it explains the Services of our unique Appointments Department; outlines Home-Study Courses in all branches of Civil, Mechanical, Electrical, Motor, Aero, Wireless, "Talkie" Engineering, Building, Govt. Employment, etc., and gives details of B.Sc., A.M.I.C.E., A.M.I.E.E., A.M.I.Mech.E., A.M.I.A.E. A.M.I.W.T., A.M.I.R.E., G.P.O., MATRIC., and all Exams. We Guarantee —"NO PASS—NO FEE." Whether you be an old hand or a budding apprentice get this book to-day. FREE and POST FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY.
337, Shakespeare House, 17/19, Stratford Place, London, W.1.

NO A.R.P. SHELTER is COMPLETE WITHOUT a
UNIVERSAL 3 VALVE BATTERY SET

with British Ring Valves Detector, L.F. and Power, and W.B. Permanent Magnet Moving Coil Speaker. In Walnut Cabinet, as illus. A real station getter and fully guaranteed.

22/6 CARRIAGE PAID.

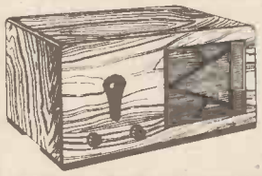

.0005 2 Gang Condensers..... 2/- each
.0005 3 Gang Condensers..... 3/6 each
Magnum Multi Contact Switches..... 1/3 each
American Valve Screens ..... 4d. each
POST FREE.

UNIVERSAL, 8 & 10, Brown Street, MANCHESTER, 2
'Phone: Deansgate 5009.

## SITUATIONS VACANT

AIR MINISTRY.

DIRECTORATE of Technical Development.

APPLICATIONS are Invited for an Appointment as Chief Designer at the Royal Aircraft Establishment, South Farnborough, Hants, to superintend a design and drawing office engaged in the design of aircraft and ground communication systems. Candidates should have had sound electrical and mechanical engineering training up to Degree standard and recent experience in a large production organisation and in the design of radio-communication and tele-communication equipment. A knowledge of the procedure and methods involved in the preparation of information for production and contract purposes is also necessary.

SALARY Scale: £650 a year, rising by annual increments of £25 to £800 a year.

THE Appointment Will be Non-Pensionable in the first instance.

REQUESTS for the Necessary Application Form Should Be Made (quoting Ref. No. 321 I) to the Chief Superintendent, Royal Aircraft Establishment, South Farnborough, Hants, enclosing stamped addressed envelope. The closing date for the receipt of forms is 19th May, 1939. [8429

SHORTHAND-TYPIST, familiar wireless technical terms, wanted in London; quick and accurate.—Apply Box 9712, c/o *The Wireless World.* [8449

## ELECTRIC DRY SHAVERS

ELECTRIC Dry Shavers, A.C./D.C., 200/50 volts, "Minute Man," list price £2/10, our price £1/10, complete with leatherette case, one year's guarantee; send for details; trade supplied.

HENRY'S, 72 Wellington Ave., Stamford Hill, N.15. 'Phone: Stamford Hill 2907. [8441

## MISCELLANEOUS

CHEAP Printing.—1,000 billheads, 3/6; sample free.—Creteway Press, 18, Buxted, Sussex. [8180

PHOTO-ELECTRIC Cells, brand new; 15/- each.—Universal, 221, City Rd., London, E.C.1. [8370

G.P.O. Engineering Dept (no experience required); commencing £3/13 per week; age 18-23; excellent prospects; free details of Entrance Exam. from B.I.E.T. (Dept. 574), 17-19, Stratford Place, London, W.1. [8396

EVERY Radio Dealer Who is Not a Regular Reader of "The Wireless and Electrical Trader" should send his trade card at once for a specimen copy and full details of the "Trader" Services. "The Wireless and Electrical Trader" has the widest influence, the largest weekly circulation, and is read by all the leading manufacturers and traders Trade only, 15/- per annum, post free.—Published at Dorset House, Stamford St., London, S.E.1. [0615

"ENGINEER'S Guide to Success" Shows How to Qualify in Television Radio Engineering and Servicing, sound recording, wireless communication, etc., by studying at home with the T.I.G.B. Write to-day for this Great Guide—free—which gives full particulars, contains the world's widest choice of engineering courses—over 200—and alone gives the regulations for qualifications such as A.M.I.E.E., A.M.I.R.E., A.M.I.T.E., A.M.I.W.T., C. and G., etc. Training until successful guaranteed.—The Technological Institute of Great Britain, 82, Temple Bar House, London, E.C.4. (Founded 1917. 20,000 successes.) [8409

## PATENT AND TRADE MARK AGENTS

GEE and Co. (H. T. P. Gee, Mem. R.S.G.B., etc.), 51-52, Chancery Lane, London, W.C.2. Holborn 4547-8. Handbook free. [0001

## PATENTS

THE Proprietor of the Patents Nos. 461128, for "Scanning Device for Television," and 461417, for "Improvements in or relating to a system for facsimile transmission and reception," is desirous of entering into arrangements by way of licence and otherwise on reasonable terms for the purpose of exploiting the same and ensuring their full development and practical working in this country.—All communications should be addressed in the first instance to Haseltine Lake and Co., 28, Southampton Buildings, Chancery Lane, London, W.C.2. [8420

## TUITION

RADIO Training.—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0611

WIRELESS.—Complete training. Marine, Broadcast and Television. Posts waiting. Mod. fees. Boarders taken. Approved college, prosp.—Dept. W., London Radio College, Grove Park Rd., London, W.4. (Chi. 3244.) [0580

## BUSINESSES AND PROPERTY FOR SALE, TO BE LET, OR WANTED

NEED for Radio and Cycle Dealer on Large New Estate. Main road position. Success assured. No premium. —Apply Fairway Homes, Mutton Lane, Potters Bar. Tel.: 931. [8371

"THE Wireless and Electrical Trader" is an essential part of the equipment of every Wireless Trader; its pages reflect the very latest turn of trade events, and it is read by all the leading dealers and manufacturers, for particulars of businesses offered or wanted. By subscription to the trade only, 15/- per annum, post free.—Send your trade card for specimen copy to Dorset House, Stamford St., London, S.E.1. [0614

## BOOKS, INSTRUCTION, ETC.

"WIRELESS World," Vols. 21-40; "Popular Wireless," start 1927, unbound; offers.—Davidson, 30, Whitefield Rd., Stockton Heath. [8422

AMERICAN Valve Data.—The new 200-page Raytheon Valve Data Book gives full characteristics and applications of all types of American valves; invaluable to all servicemen; post free, 2/3; abroad, 3/-.—Leonard Heys, 36, Henry St., Blackpool. [0594

GALPINS

*ELECTRICAL STORES*

75, LEE HIGH RD., LEWISHAM, LONDON, S.E.13

Telephone: LEE GREEN 5240

Terms: Cash with Order or C.O.D. Charges Extra.

NEON TRANSFORMERS, input 200/250 volts 50 cycles 1-phase output, 10,000 volts 10 m/A., 12/6 each, post 1/-. Ditto, 7,000 volts 8 m/A., 10/-, post 1/-. Ditto, 5,000 volts 5 m/A., 7/6, post 1/-. (All brand new.)

THE 'RACON' MOVING COIL HORN SPEAKER UNITS. 15 ohm Speech Coil 6 volt field handle, 15 watts, 15/- each, post 1/6.

'MAGNAVOX' P.A. MOVING COIL SPEAKERS, 700 and 2,000 field, 15 ohm speech coil. Handle 30/35 watts with horn 42 in., 22in. flare (new in packing case), 67/6 each, C/f.

A.C. INDUCTION MOTORS, Approx. ¼ h.p., 1,420 r.p.m. 200/250 volts 50 cy. 1 ph. As new, 21/- each.

EX-NAVAL 1-VALVE BUZZER WAVEMETERS, 200/24,000 metres. Complete in solid teak case. Size: 15×10×8 (less valve). Turner unit enclosed in copper tank (Sullivan high note buzzer). Price, 7/6 each, C/forward. Not sent C.O.D.

EVERSHED EX-R.A.F. HAND DRIVEN GENERATORS, with 2 outputs 800 volts 30 m/A. and 6 volts 2 amps., 25/-, post 1/6.

VOLTAGE CHANGER AUTO TRANSFORMERS, 100/120 volts to 200/240 volts or vice versa, 250 watts, 17/6, 500 watts 25/-, 1,000 watts 37/6, 1,500 watts 42/6 each. C/forward. All fully guaranteed.

MOVING COIL METER MOVEMENTS for recalibrating into multitrange meters. Low m/A. deflection. 2½in. dial, 5/- each; 4in. and 6in. dial, 6/- each. Post 1/-. (Note: All these meters are by good makers—Elliott, E. Edgcumbe, etc.)

ELECTRIC LIGHT CHECK METERS, 200/250 volts, 50 cy., 1 phase, 5 and 10 amps., 6/- each. P.F.

ERNEST TURNER 1st GRADE MOVING COIL MILLIAMP METERS, 2in. scale, 0 to 5 m/A., 12/6. 0 to 50 m/A., 12/6. 0 to 250 m/A., 12/6 each.

X-RAY TRANSFORMERS, by well-known makers, all fully guaranteed. 50 cycle mains, 40,000 volts, 10 m/A., £5. 68,000 volts, 20 m/A., £7/10/-. 100,000 volts, 30 m/A., £10/10/-. All carriage forward

A.C. MAINS RELAYS, 230 volts, trip at ½ amp. A few also at 400 volts, 7/6 each. Post 9d.

EX-R.A.F. ROTARY CONVERTORS. D.C. to D.C. 12 volts input, 500 volts 75/100 m/A. output, brand new 25/-, post 1/-; S.H. condition, 20/-, post 1/-. Also a few with damaged brush, gear windings O.K., 10/- each, post 1/-.

SPOT WELDING TRANSFORMERS, 220/240 volts, 50 cy., 1 phase input ½ to 5 volts at 1½ kilowatts. Makers, Foster. 45/-. C/F.

EX-G.P.O. GLASS TOP RELAYS, Type B. Useful as Keying Relays, 5/- each, post 6d. Also a few only that need points which are easily fitted, 2/6 each, P/F.

MAINS SMOOTHING CONDENSERS. Philips 1 mf., 3,000 volt working, 5/- each, post free. Siemens, 4 mf., 1,500 v. test, 2/6 each. T.C.C. 4 mf., 300 v. A.C. wkg., 2/- each. Standard Telephone 1 mf., 400 v., wkg., 3 for 1/-, post 4d., or in lots of 100, 12/6, post 1/6. T.C.C. 2,000 mf., 12 v., wkg., 3/- each.

EX-R.A.F. DOUBLE WOUND GENERATORS, giving two outputs, 1,200 volts 100 m/A., and 10 volts 4 amps., 15/- each, post 1/6.

"EPOCH" SUPER CINEMA MOVING COIL SPEAKERS, 6 volt field (less cone), 15/-, C/F.

"STANDARD" TELEPHONE COPPER SCREENED 23 S.W.G. TELEPHONE WIRE, 100 yd. coils, 4/-. All new.

ZENITH WIRE WOUND RESISTANCES (Vitreous) 5,000 ohm. carry 170 m/A., 10,000 ohm 50 m/A., 2,500 ohm 170 m/A., 750 ohm 300 m/A., 255 ohm 500 m/A. 1/- each. Post 4d.

SILVERTOWN GALVANOMETERS, jewelled movement, very sensitive, 5/- each.

ZENITH VARIABLE RESISTANCES, 30 ohms carry 2½ amps., 8/6 each.

DYNAMOS, all shunt wound and fully guaranteed, 220 volts 15 amps. £6/10/-, 220 volt 10 A. £3, 100 volt 20 A. £6/10/-, 80/90 volt 10 amps. £2/15/-, 25 volt 8 amps., 32/6.

SWITCHBOARD VOLTMETERS, Everett Edgcumbe, etc., 6in. dial, moving coil, 0 to 300 volts 15/-, 0 to 500 volts 17/6, A.C. 0 to 250 volts, 15/-.

STANDARD TELEPHONE MAINS TRANSFORMERS 200/240 volts input, 50 volt 8 amp., also 500 volts 150 m/A., output, 12/6 each.

"SULLIVAN" TRANSMITTING CONDENSERS, variable, in glass tank, 0005 mf., and 001 mf., 7/6 each, post 1/-.

STEEL CABINETS. Useful as Transmitting Racks. Size 40×17½×24in., 12/6 each. C/F.

3,000 WATT AUTO TRANSFORMERS, 0 to 220 volts in steps of 10 volts. Useful as small arc welders. Fully guaranteed, 65/- each. C/F.

PHILIPS 10-WATT PRE-STAGE AMPLIFIERS, less valves (in good condition), 10/6 each. Post 1/6.

EX-G.P.O. PEDESTAL TELEPHONES WITH AUTOMATIC DIALS, 5/6 each. Post 9d. Telephone wall boxes, consisting of A.C. bell 2 m/f. microphone transformer, 2/- each.

# FOUNDATIONS of WIRELESS

—SECOND EDITION

*A Book of First Principles for the Wireless Enthusiast*

PRICE 4/6 NET

By Post 4/11

Issued in conjunction with "THE WIRELESS WORLD" and published by the proprietors—

By A. L. M. SOWERBY, M.Sc.

**An Elementary Text Book on Wireless Receivers**

"Foundations of Wireless," based on a series of articles which appeared in "The Wireless World," covers the whole field of wireless from the simplest electrical phenomena to the construction of a modern set, and all the vital points in receiver design are treated in full detail. Chapters are devoted to direct and alternating currents; typical circuits; the properties of inductance and capacity; the nature of high frequency currents; the tuned circuit; and amplification by the valve.

Eleven of the eighteen chapters of the book deal with the discussion of receivers, in which the whole process of design is reviewed stage by stage to the finished article. Special attention is paid to the important subject of tuned circuits and band-pass filters, on the correct design of which the performance of every type of set ultimately depends. Moreover, the process of detection, so often imperfectly understood, is clearly explained.

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

Third Edition Revised by O. F. BROWN, B.Sc.

# *The* ELEMENTARY PRINCIPLES *of* WIRELESS TELEGRAPHY *and* TELEPHONY

*by* R. D. BANGAY

PRICE 7/6 net by post 8/-

*From all leading Booksellers or direct from the Publishers*

**The standard book of instruction for wireless beginners and students. The style is clear and simple and attention is given to the theoretical elements of electricity and magnetism to the dynamo: and to the properties of waves. A leaflet which gives full particulars of the volume, including a synopsis of the chapters, will be sent on request.**

ILIFFE & SONS LIMITED, DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1 W.W.2.

CHASSIS • RECEIVERS • RADIOGRAMS • SPEAKERS

AMPLIFIERS • MICROPHONES • RECORDING EQUIPMENT

3-Band Tuning Unit

**TYPES ACT5 & UT5**

5-waveband Tuning Units of quality, covering the following ranges: 12-35 m.; 30-80 m.; 75-200 m.; 200-550 m.; 660-2,000 m. Tuned RF stage on all bands; triode hexode frequency changer. Full vision scale with spreader drive. Hand built and calibrated. For use with I.F.s of 465 Kcs. Complete with 4 v. AC valves or 6.3 v., .2 amp. E type valves.

PRICE .. .. £5 . 10 . 0

3 BANDS from 16 to 2,000 m... .. .. .. £4.10.0
4 BANDS from 12 to 2,000 m... .. .. .. £5. 0.0
6 BANDS without gaps from 4½ to 2,000 m. £8. 0.0
*Full details on request.*

**JOHN McCLURE LTD.** (G6JM) ERSKINE ROAD, LONDON, N.W.3. *PRImrose 5435*


## INDEX TO ADVERTISEMENTS


| | PAGE |
|---|---|
| A.C.S. Radio | |
| Air Ministry | |
| Air Service Training, Ltd. | |
| Ambassador Radio Works | |
| Anglo-American Radio (& Motors), Ltd. | |
| Armstrong Manufacturing Co. | 2 |
| Automatic Coil Winder Co., Ltd. | 4 |
| Belling & Lee, Ltd. | |
| Birmingham Radiomart G5NI | 4 |
| British Institute of Engineering Technology | 7 |
| British Insulated Cables, Ltd. | |
| British McMurdo Silver Co., Ltd., The | |
| British Mechanical Productions, Ltd. | |
| British Rola, Ltd. | 4 |
| British Thomson-Houston Co., Ltd., The | |
| Capstan Cigarettes | |
| Degalliers | |
| Edison Swan Electric Co., Ltd. | |
| Electradix Radio | 6 |
| Evrizone Radio & Television Co., Ltd. | |
| Fluxite, Ltd. | |
| Galpin's Electrical Stores | 7 |
| Goodmans Industries, Ltd. | 1 |
| Grampian Reproducers | 3 |
| Hartley Turner Radio, Ltd. | |
| Henley, W. T., Telegraph Works Co., Ltd. | |
| Institute of Wireless Technology | 7 |
| International Correspondence Schools | |
| Jackson Bros. (London), Ltd. | |
| Lockwood & Co. | 2 |
| London Radio Supply Co. | 2 |
| Marconi-Ekco Instruments, Ltd. | |
| McClure, John, Ltd. | 8 |
| Pamphonic Reproducers, Ltd. | 7 |
| Peto-Scott Electrical Instruments (Holdings), Ltd. | 7 |
| Premier Supply Stores | 5 |
| Quartz Crystal Co. | |
| Salford Electrical Instruments, Ltd. | Inside Front Cover |
| Savage, W. Bryan, Ltd. | 4 |
| Sound Sales, Ltd. | 4 |
| Taylor Electrical Instruments, Ltd. | |
| Universal Electric | 7 |
| Varley, Ltd. | |
| Welburn Radio, Ltd. | 7 |


Printed in England for the Publishers, ILIFFE AND SONS LTD., Dorset House, Stamford Street, London, S.E.1, by The Cornwall Press, Ltd., Paris Garden, Stamford Street, London, S.E.1. "The Wireless World" can be obtained abroad from the following: FRANCE: W. H. Smith & Son, 248, Rue Rivoli, Paris; Hachette et Cie, Rue Réaumur, Paris, and branches; Messageries Dawson, 4, Rue de Faubourg Poissoniere, Paris. BELGIUM: W. H. Smith & Son, 71-75, Boulevard Adolphe Max, Brussels. AUSTRALIA: Gordon & Gotch, Ltd., Melbourne (Victoria), Sydney (N.S.W.), Brisbane (Queensland), Adelaide (S.A.), Perth (W.A.), and Launceston (Tasmania). NEW ZEALAND: Gordon & Gotch, Ltd., Wellington, Auckland, Christchurch and Dunedin. INDIA: A. H. Wheeler & Co., Bombay, Allahabad and Calcutta. CANADA: Imperial News Co., Toronto, Winnipeg and Vancouver; Benjamin News Co., Montreal; Gordon & Gotch, Ltd., Toronto. SOUTH AFRICA: Central News Agency, Ltd.; Wm. Dawson & Sons (S.A.), Ltd., Cape Town. UNITED STATES: The International News Co., New York.

*Sixth Edition* *Revised and Enlarged*

# HANDBOOK of TECHNICAL INSTRUCTION for WIRELESS TELEGRAPHISTS

by H. M. DOWSETT
(M.I.E.E., F.Inst.P., M.Inst.R.E.)

**This standard handbook is planned primarily for the use of wireless operators, whether prospective or actual. It is virtually a complete theoretical course for students wishing to qualify for the Postmaster-General's Certificate of Proficiency.**

CONTENTS INCLUDE:

The Electric Charge and the Condenser—The Condenser in Practice—Direct Current and Ohm's Law—Scalar and Vector Quantities and Curve Plotting—Primary Batteries—Accumulators—Magnetism—Electro Magnetism—Self-Induction—Dynamo Electric Machines—Measuring Instruments—Switchboards and Switchgear—Alternating Current Effects, and Vector Diagrams—Alternating Current Fundamental Formulae—Alternating Current Generators, Alternating Current Motors and Transformers—Damped Oscillations—Commercial Types of Spark Transmitter—Aerials and Radiation—Simple Receiver Circuit and Crystal Detector—Thermionics and the Various Applications of the Valve—Depth Sounding—Valve Transmitters—Wavemeter and Transmitter Adjustment—Theory of Valve Receiver Circuits—Valve Receivers—Short Wave Aerials and Apparatus—Marine Direction Finders—Marine Audio Relay Service—Distress Call Apparatus—Lifeboat and Emergency Outfits—Trawler Apparatus—Maintenance of Marine Radio Installations and Possible Faults.

NOW ON SALE PRICE 21/- By post 21/9
Foreign Postage 22/-.

*Obtainable from leading booksellers or direct from the Publishers.*

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

*THE*

# WIRELESS ENGINEER

The Journal for Professional Engineers and Advanced Wireless Experimenters

Monthly 2/6 net. Annual Subscription 32/- post free.

ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1

W.W.2

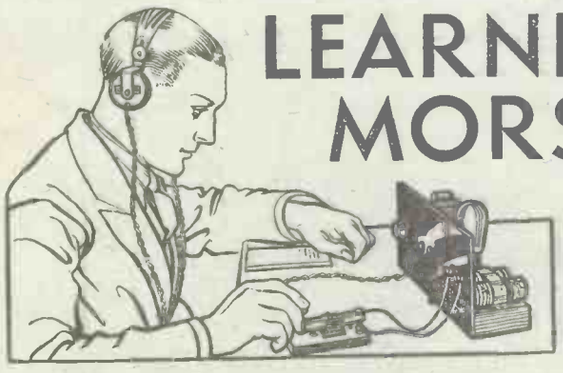

# LEARNING MORSE

AN EASY METHOD OF MASTERING THE INTERNATIONAL SIGNAL CODE

*Published from the Offices of* The Wireless World ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1

6D NET BY POST 7d.

# The ELECTRICAL REVIEW

*The Complete Technical Journal*

Practical articles on all aspects of electricity supply and utilisation — industrial, commercial and domestic. Latest news of the electrical industry and developments. Advertisement pages form a comprehensive buyers' guide.

*Contents of May 12th Issue :—*

COST OF CONTINUITY.
The economics of stand-by plant and bulk supply.

POWER STATION ENGINEERS.
Activities of the Electrical Power Engineers' Association.

DUAL PROPAGANDA.
National Service publicity draws public to electricity showrooms.

WOMEN IN CONFERENCE.
Report of the annual meeting at Cardiff of the Electrical Association for Women.

ALL THE WEEK'S NEWS.

EVERY FRIDAY 6d. Subscriptions : United Kingdom £1 14 8 Canada £1 12 6 Other Countries £2 1 6 per annum, post free.

ELECTRICAL REVIEW LTD.
Dorset House, Stamford Street, London, S.E.1

# YOU WILL ENJOY "POP"

## POP - - - - Silence is Copper

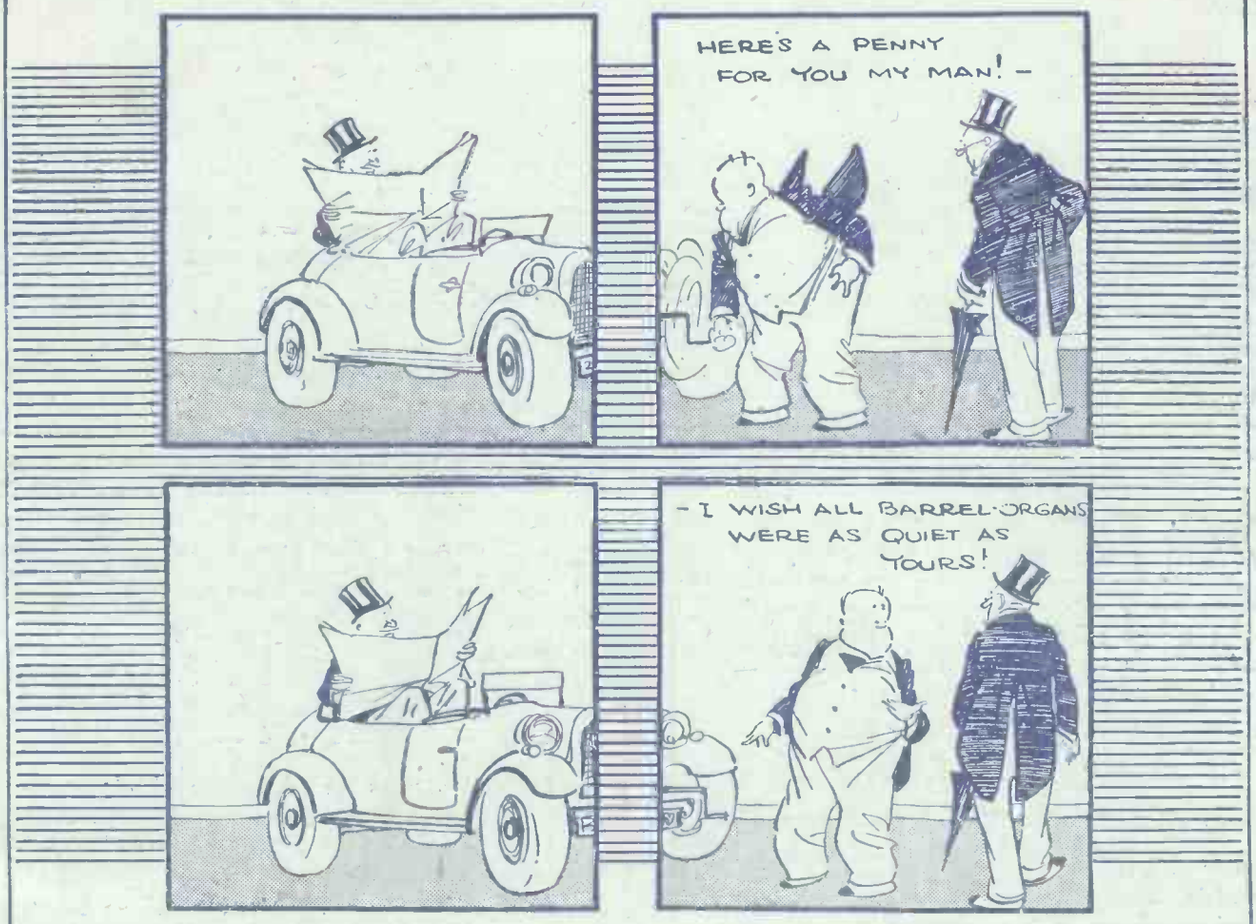


**There is no doubt whatsoever that "Pop" of the DAILY SKETCH is consistently the funniest and most entertaining cartoon character in daily journalism. Have a laugh every morning.**

*Read him in the*

# DAILY SKETCH

***All the News and Pictures Fit to Print***

DOUBLE-REGENERATION SUPERHET

# The Wireless World

6D

## THE PRACTICAL RADIO & TELEVISION JOURNAL

Thursday, May 18th, 1939.

No. 1,029. Vol. XLIV. No. 20.

Copyright. Registered as a Newspaper for transmission in the United Kingdom. Entered as Second Class at the New York, U.S.A., Post Office

# 'AVO' Precision ELECTRICAL TESTING INSTRUMENTS

Regd. Trade Mark

BRITISH MADE

## The Universal AVO MINOR

Electrical Measuring Instrument.

This compact precision moving-coil instrument covers all A.C. and D.C. testing. It has 22 ranges for measuring A.C. voltage, D.C. voltage, current and resistance. All readings are direct. No calculations. The high total resistance of the instrument—200,000 ohms—ensures accurate readings. Complete with leads, interchangeable testing prods and crocodile clips, and instruction booklet ..... **£5. 10s.**

*Leather Carrying Case, 10/-*

**16 Gns.**

*Model 7 Resistance Range Extension Unit (for measurements down to 1/100th. ohm)* **12/6**

*Also, the 36-range Universal AvoMeter* 13 Gns.

*The 22-range D.C. AvoMeter* 9 Gns.

*Leather Carrying Case - - 25/-*

SIX RANGES

| | |
|---|---|
| 0-.0005 Mfds. | .003-.005 Mfds. |
| .0005-.0015 Mfds. | .005-.01 Mfds. |
| .0015-.003 Mfds. | .01-0.1 Mfds. |

## The "AVO" CAPACITY METER

A simple and accurate capacity meter, reading capacities directly from a calibrated dial. Six ranges; measurements can be made from a few mmfd. to 0.1 mfd. (100,000 mmfd.) correct to within an error of less than 1%. Measurements carried out by a resonance method, the unknown condenser being introduced into a tuned circuit coupled to a radio frequency oscillator. A meter gives visual indication of resonance; length of meter deflection gives a comparative measure of losses of condenser under test. **£23**

## The MODEL 7 46 Range Universal AVO METER

Electrical Measuring Instrument.

A compact multi-range A.C./D.C. meter, it has 46 ranges covering A.C. and D.C. current and voltage, also resistance, capacity, audio-frequency power output, and decibels. No external shunts or series resistances required. The meter conforms with B.S. first grade accuracy requirements; has a 5in. mirror scale; is provided with automatic compensation for errors arising from variations in temperature; and is protected by an automatic cut-out against damage through overload.

*All "AVO" Instruments are available on Deferred Terms.*

● *Write for fully descriptive Leaflets*

*Sole Proprietors and Manufacturers:—*

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.

Winder House, Douglas Street, London, S.W.1. *Phone: Victoria 3404-7.*

# 20 —— 20,000

# CLASSIC QUALITY AT A REASONABLE PRICE!

The 346 type Amplifier is "engineering built" to the same high standard as our famous 4/12 watt model, and in spite of its reasonable price is, as the curve shows, capable of giving an equally good performance. Like the 4/12 watt model, the smaller Amplifier has become a **classic** among Amplifier connoisseurs. The specification includes: 036 type special output transformer, balanced bias with vernier adjustment, self-contained smoothing and volume control. We feel sure that you will agree as a result of a demonstration that the 346 type Amplifier priced at £10 represents a definite Challenge to anything on the market, and upholds SOUND SALES Quality Claims in every respect.

*May we send YOU a copy of our latest catalogue and Technical manual? PRICE ... ...* **6d.**

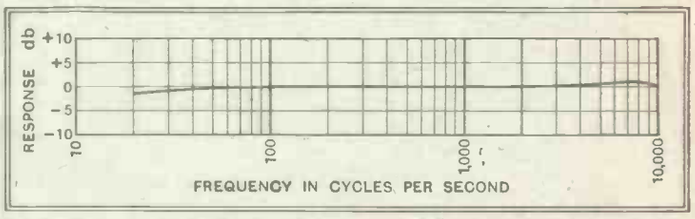


# SOUND SALES LIMITED

**MARLBOROUGH ROAD, UPPER HOLLOWAY, LONDON, N.19**

Telephone: ARChway 1661-2-3.

*Contractors to the G.P.O., Air Ministry, War Office, etc.*

The Wireless World
THE PRACTICAL RADIO JOURNAL
29th Year of Publication

No. 1029 THURSDAY, MAY 18TH, 1939. VOL. XLIV. No. 20.

Proprietors : ILIFFE & SONS LTD.

Editor :
HUGH S. POCOCK.

Editorial,
Advertising and Publishing Offices :
DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1.

Telephone : Waterloo 3333 (50 lines).
Telegrams : "Ethaworld, Sedist, London."

COVENTRY : 8-10, Corporation Street.
Telegrams : "Autocar, Coventry." Telephone : 5210 Coventry.

BIRMINGHAM :
Guildhall Buildings, Navigation Street, 2.
Telegrams : "Autopress, Birmingham." Telephone : 2971 Midland (5 lines).

MANCHESTER : 260, Deansgate, 3.
Telegrams : "Iliffe, Manchester." Telephone : Blackfriars 4412 (4 lines).

GLASGOW : 26B, Renfield Street, C.2.
Telegrams : "Iliffe, Glasgow." Telephone : Central 4857.

PUBLISHED WEEKLY. ENTERED AS SECOND CLASS MATTER AT NEW YORK, N.Y.

Subscription Rates :
Home and Canada, £1 10s. 4d. ; other countries, £1 12s. 6d. per annum.

*As many of the circuits and apparatus described in these pages are covered by patents, readers are advised, before making use of them, to satisfy themselves that they would not be infringing patents.*

## CONTENTS

| | Page |
|---|---|
| *Editorial Comment* | 455 |
| *New Communication Receiver* | 456 |
| *Dry-cell LT in U.S.A.* | 459 |
| *"The Wireless World" DC Mains Super : Circuit Arrangement* | 460 |
| *Problem Corner* | 462 |
| *Television Programmes* | 462 |
| *Cathode-Ray Amplifier Tester* | 463 |
| *Letters to the Editor* | 466 |
| *News of the Week* | 467 |
| *Frequency Modulation in America (concluded)* | 469 |
| *Invicta New Junior Portable : Test Report* | 471 |
| *Television Topics : Saw-tooth Current Waves* | 473 |
| *New Apparatus* | 474 |
| *Random Radiations* | 476 |
| *Direct Recording Blanks* | 477 |
| *Recent Inventions* | 478 |

# EDITORIAL COMMENT

## The Post Office Relays

### *Is the Position Satisfactory ?*

WHEN the Post Office some considerable time ago proposed the development of a relay service in Southampton as a starting-off point before extending such a system on a national scale, the project met with so much opposition that the Post Office abandoned the idea of carrying it out in that location. More recently the Post Office has announced the intention of developing their own relay system on a national scale as a service in addition to, or in competition with, the privately owned relay systems whose licences the Post Office has now renewed for a further term of ten years.

The question has recently been asked : Why should the radio industry, which contributed so actively to opposing the Post Office scheme for Southampton, now apparently acquiesce in the present Post Office proposals? In our view the suggestions made in connection with Southampton and those now put forward are so fundamentally different that the whole outlook on the proposition has changed.

In the case of Southampton the proposal was to supply the broadcast programmes at audio frequency, which in all probability would have necessitated the use of a particular type of loud speaker and terminal apparatus at the listener's end, and would have made a wireless receiver unnecessary to anyone satisfied with a choice of the two or three alternative programmes which the service could provide. Under the new scheme, with programmes supplied at radio frequency, a normal type of wireless receiver becomes a necessity, and in consequence the radio industry not only has nothing to fear in the way of a falling-off in demand for sets, but the Post Office has given firm assurances that there will be no attempt made to market apparatus for the purpose, but the listener will purchase his equipment through the usual channels.

If the Post Office had developed relays on an audio-frequency basis there would have been every justification for fearing that broadcast listening would have had a most serious set-back and it would ultimately have interfered with the freedom of the individual to receive programmes at will. The cost of wireless receivers would also have increased as a result of a reduction in demand ; so that receivers might again have become a luxury commodity as they were in the early days of broadcasting.

Now the position has, we think, been satisfactorily cleared up, and the only question which it seems necessary to ask is whether, except for the purpose of meeting special emergency, the expenditure of the Post Office on a relay distribution is justified. It will only give three or four of the same stations which are already available under normal conditions of reception, and the only advantage which the Post Office scheme can claim, as far as the listener is concerned, will be greater freedom from electrical interference and perhaps a higher standard of quality. This latter advantage would, of course, justify the scheme in the opinion of a great many listeners, but only time will show how far the standard of quality will be improved.

## Gas and Electricity

### *The Influence of Wireless*

IN a recent annual report of a gas corporation a very frank admission was made that the demand for a mains supply of electricity for a wireless set has frequently been a factor in the ousting of domestic gas lighting, and a reference was made to the future possibility of obtaining wireless reception by means of gas-operated appliances.

However effective gas equipment of this kind might prove to be in time to come, we think that electricity has so long a start that any gas appliance, whether for operating the receiver directly or used for generating electricity for the receiver—which latter we presume to be the arrangement in question—would have a very uphill struggle to retard the ousting of gas where electricity is sought for operating the modern broadcast receiver.

# Nev

*IN this article there appears a description of an American communication receiver which is especially interesting in view of the use which is made of regeneration. It is obtained at signal-frequency and also at intermediate frequency, and as a result very high sensitivity and selectivity are obtained with a simple circuit*

By McMURDO SILVER (*Edwin I. Guthman and Co., Inc., Chicago*)

THE use of regeneration to obtain high sensitivity and selectivity is one method of approaching the engineering goal of high efficiency combined with minimum cost and complexity. In a carefully designed receiver it permits the elimination of several undesirable characteristics and enables the attainment of results directly comparable to those given by more complex methods. Ever since the high-performance possibilities of the double-regenerative superheterodyne known as the Jones "Super-Gainer" were revealed to amateurs in 1935 the writer has been amazed that no factory-built communication receivers have utilised this idea. The reason probably is that such receivers have closely followed broadcast receiver design technique, to which regeneration, in the U.S. at least, is anathema, since Mrs. John W. Public can't be taught how to use it.

Knowing what can be had from an easily operated double-regenerative receiver, the writer recently designed a communication receiver along these lines. The performance came up to his fondest expectations, and even exceeded them in regard to the signal-noise ratio.

By using a regenerative frequency-changer, regenerative IF amplifier, diode second detector, pentode AF and tetrode output stages, very high sensitivity and selectivity can be obtained with a very good signal-noise ratio. In the "Silver-Super" here described the signal-noise ratio actually measures from 25 : 1 and 50 : 1; specifically, at an input of one microvolt absolute the signal output is 50 milliwatts, of which the noise component is between only 1 and 2 milliwatts!

This same technique also provides continuously variable selectivity, which, at the turn of a knob, can be adjusted to anything between the extremes of 12 kc/s and less than 1 kc.—necessary for single-signal CW telegraph reception. Another advantage lies in the fact that through this

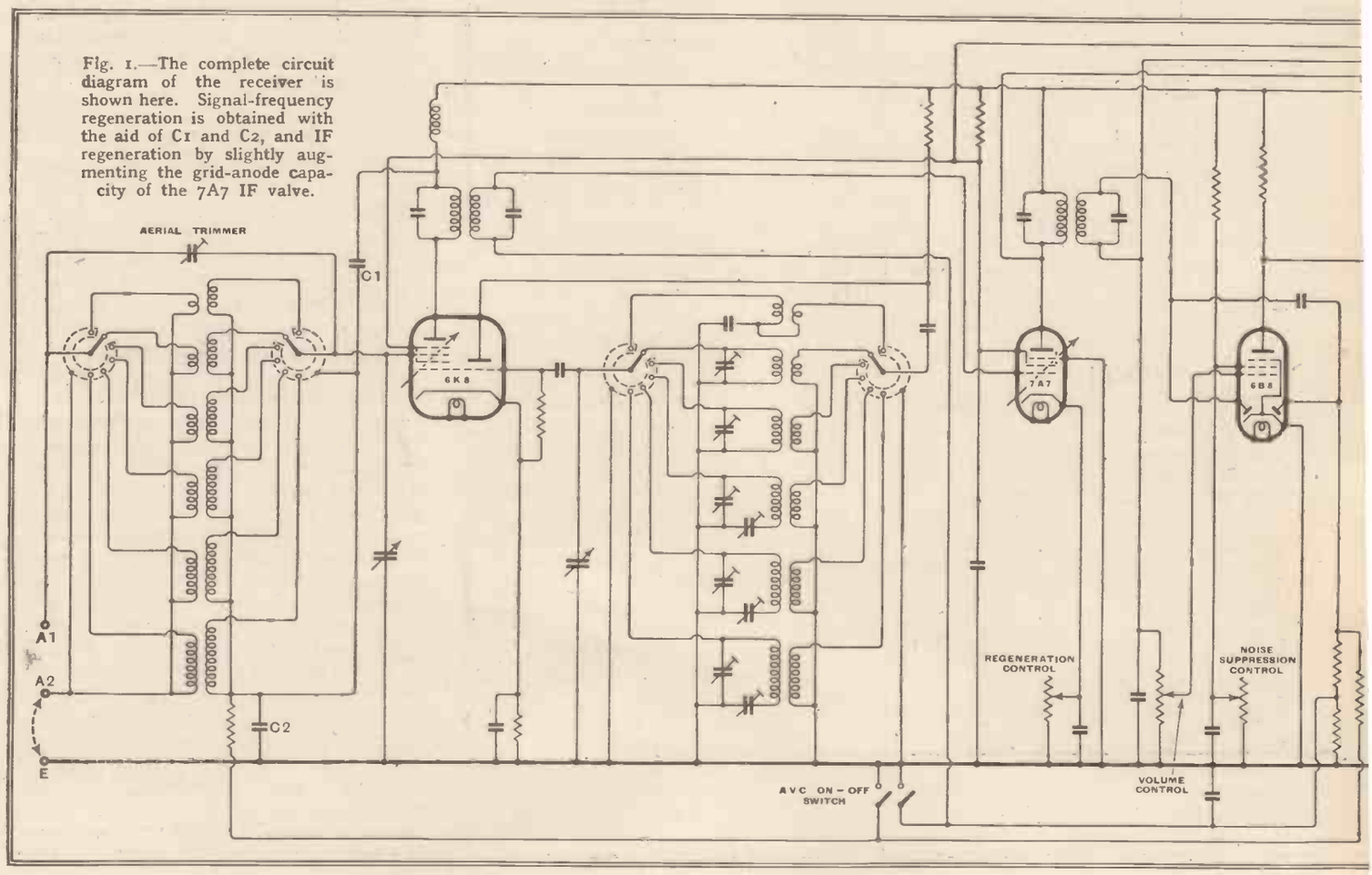


Fig. 1.—The complete circuit diagram of the receiver is shown here. Signal-frequency regeneration is obtained with the aid of C1 and C2, and IF regeneration by slightly augmenting the grid-anode capacity of the 7A7 IF valve.

# Communication Receiver

## A SUPERHETERODYNE WITH DOUBLE REGENERATION

technique practically all of the difficulties encountered in the home construction of a modern communication receiver are eliminated, and it becomes a simple matter to "align" such a receiver at home without any test oscillators or test gear whatsoever; received signals alone are sufficient when one or more IF transformers are factory pre-aligned.

Another advantage of double-regenerative superheterodynes, or of any receiver using regeneration, is one which is very important where service check-up is at a premium, as in the case of expeditions. In any receiver depending upon "repeater" gain through a multiplicity of valves and components, progressive slow deterioration of the parts seriously impairs results. In a regenerative receiver such slow deterioration merely means that the regeneration control must be advanced a little farther. This may seem to be a pointless argument if high-quality parts are used, but it is not, for, no matter how good any part may be, the possibility of deterioration, if not actual failure, is always present. So important has this factor been to a significant expedition of scientific investigation shortly sailing for far-distant points that the "Silver-Super" won selection almost "hands down," particularly after its performance had been checked against conventional receivers.

The receiver here described has a 6K8 regenerative frequency-changer, regenerative 7A7 "loctal" all-glass IF amplifier, 6B8 diode detector, AVC, first AF stage and noise limiter, and 7C5 beam power valve. As accessories, beside the fundamental purpose of signal amplification, a 7A7 is used as a beat oscillator to give single-signal CW reception, a 6SF5 single-ended triode for S-meter operation, a VR150 automatic HT voltage regulator, and, of course, a power supply rectifier—in this case an 80.

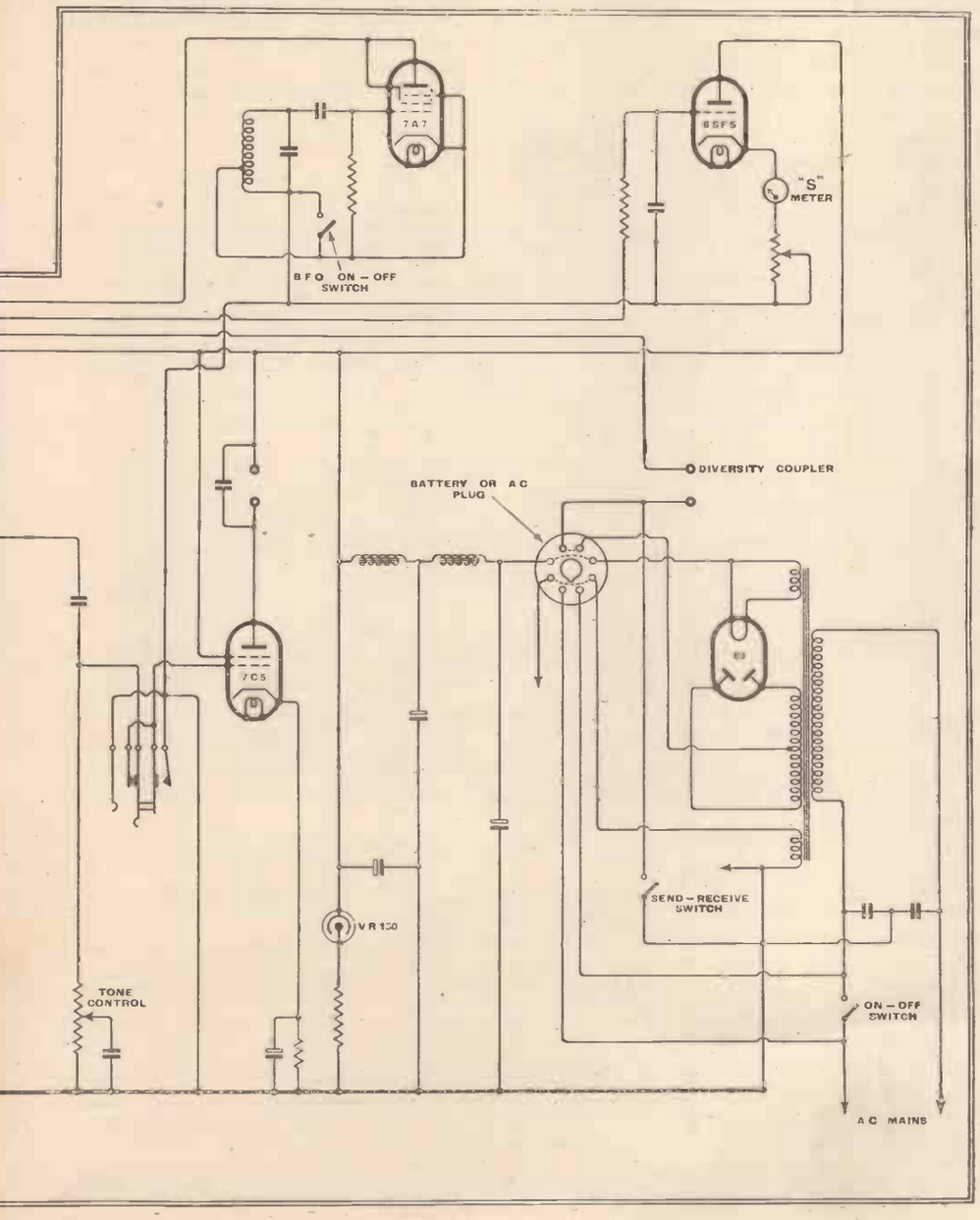


The wavelength range selected as essential to present-day amateur operation was 5 to 625 metres—specifically 480 kc/s to 61 Mc/s. Such a range in a single receiver covers every amateur band at present amenable to conventional engineering treatment, the broadcast band, and the 600-metre commercial band. Such a range automatically demanded a high LC ratio, and with the sensible tuning condenser value of 140 $\mu\mu$F automatically broke up into six bands each of about 2.2 : 1 frequency ratio. Each band uses individual coils, with all unused coils shorted out of circuit and with every coil mounted directly on wave-change lugs for short leads. Ceramic switch insulation was discarded because of mechanical difficulties, and the new "X2B" insulation was selected instead.

### RF Regeneration

No RF amplifier was even considered, since gain and image rejectivity at the higher frequencies could not be obtained to any worth-while degree with any simple single stage. Instead, regeneration was employed in the frequency-changer. The circuit diagram of Fig. 1 shows how this was obtained, not as a variable function, but as a fixed gain contribution.

With a 6K8, having the cathode connection common to the mixer and oscillator sections, cathode regeneration could not be employed, since it would involve highly undesirable mixer-oscillator coupling. The use of a reaction coil would involve extra switching operations and would also reduce the high-frequency range of each wave band. So a new method was devised. An RF choke in the anode circuit of the mixer provided an RF impedance, some of the voltage across which could be coupled back to the grid circuit. This idea is really very simple and works out very nicely. The choke itself had to be designed to present the needed RF impedance over the entire range of 480 kc/s to 61 Mc/s, and in designing it several interesting facts were discovered. In appearance it is just an ordinary 10 mH RF choke, except that it is wound on a ceramic dowel and the

**New Communication Receiver—**

coil is very narrow. The fact that it works at 5 metres as well as at 500 is due to the careful choice of the physical size and shape, the wire size and insulation, as well as the winding pitch. The RF voltage across this choke is tapped off in the desired amount through the condenser C1 and fed back to the low potential end of the grid circuit—to the AVC return. The ratio of feed-back capacity C1 to C2 determines the degree of regenerative feed-back. Since high-impedance aerial primaries are employed, which prevent different aerial characteristics from reacting upon the first tuned circuit, no question of "dead spots" occurs, and this regenerative feed-back may be made fixed. Thus mixer regeneration introduces no extra control, critical or otherwise, yet gives more gain and selectivity at the higher frequencies than could a non-regenerative RF stage. Because it sharpens up tuning, a manual aerial trimmer condenser is provided. It is not critical in setting, but is a simple way of getting the very maximum out of the mixer as well as a means of eliminating five or six internal trimmer adjustments. The full experience gained in the design of a precision frequency meter of extraordinarily high-frequency stability was brought to bear on the oscillator circuit, with the result that it is very stable indeed. Two further assurances of such stability were incorporated. One is a VR150 automatic voltage regulator tube, and the second is a send-receive switch which cuts voltage to all valves—even HT voltage to the filter itself. This arrangement allows valve heaters to be run continuously at low power cost—less than 30 watts is consumed by all heaters—so that the usual "warm-up" drift is entirely absent. Even the penuriously minded operator will be willing to turn on heaters an hour or two before the start of operation if by so doing warm-up drift is eliminated, as it is in the "Silver-Super."

### IF Regeneration

The IF amplifier uses one of the new all-glass 7A7 "Loctal" RF pentodes. This tube has no base, socket pins being set right into its glass "stem"; has low inter-electrode capacity; practically no lead inductance; is fully self-shielded, and has higher gain than the older 6K7 or even the new single-ended 6SK7 tubes. It is fed by a high-Q permeability tuned 455 kc/s IF transformer, which, using silver-plated-on-mica tuning condensers, has all the stability of air-tuned transformers with smaller size and higher gain. A second similar transformer couples this 7A7 to the diode second detector. Regeneration is obtained by slightly augmented grid-anode capacity at the 7A7 socket and by very high IF transformer coil Q. It is controlled by cathode bias variation, with normal operation just below critical regeneration, which occurs at optimum bias.

Any attempt to regenerate ordinary 455 kc/s IF transformers results in a frequency shift of something like 2-10 kc/s, enough to lose a signal entirely as regeneration is varied. The remedy lies, among other tricks of the transformer engineer, in using very loose primary to secondary coupling in the regenerated transformers. This also desirably increases selectivity, but reduces gain. This last is of no practical consequence, however, since regeneration gives all the gain that can be used. If the receiver builder will remember this point the next time he builds a regenerative IF amplifier, and uses transformers specifically designed for such use, he can escape the usual frequency shift with regeneration variation. Actually, the IF amplifier is never operated in an oscillating condition for CW reception. Regeneration is used only to get gain and crystal selectivity, and the separate beat-frequency oscillator tube is used for CW. This allows the IF selectivity to be made so sharp that when the beat oscillator is offset 1,000 c/s, so that the loudest beat of 1,000 c/s is at IF resonance, the second audio beat (audio image) 2,000 c/s away is practically inaudible. Single-signal CW reception is thus obtained, while a bit less regeneration gives phone selectivity which is a joy and a delight in cutting through QRM.

The diode second detector and AVC circuits are essentially conventional, except for choice of optimum circuit constants and splitting of the AVC voltage to the mixer and IF valves in the best proportions for AVC. An AVC on-off switch is, of course, provided. To be really useful the S-meter should not be in an amplifier anode circuit or it will not register on signals which are below the AVC delay bias. So a 6SF5 single-ended triode is used as a valve-voltmeter to read signal voltage appearing across the diode load resistor upon the scale of the calibrated S-meter in its anode circuit. A variable cathode resistor allows initial "setting up" of the meter scale for correct readings.

By using a diode-pentode for the detector and AF stage instead of the usual diode-triode, a noise limiter, which is as effective as it is simple, becomes possible. The pentode of the 6B8 is used as an AF amplifier, its grid being fed from the arm of the potentiometer forming the diode load. This pentode has the characteristic that its "saturation" is controlled by its screen voltage; that is, the strength of the signal it can pass is

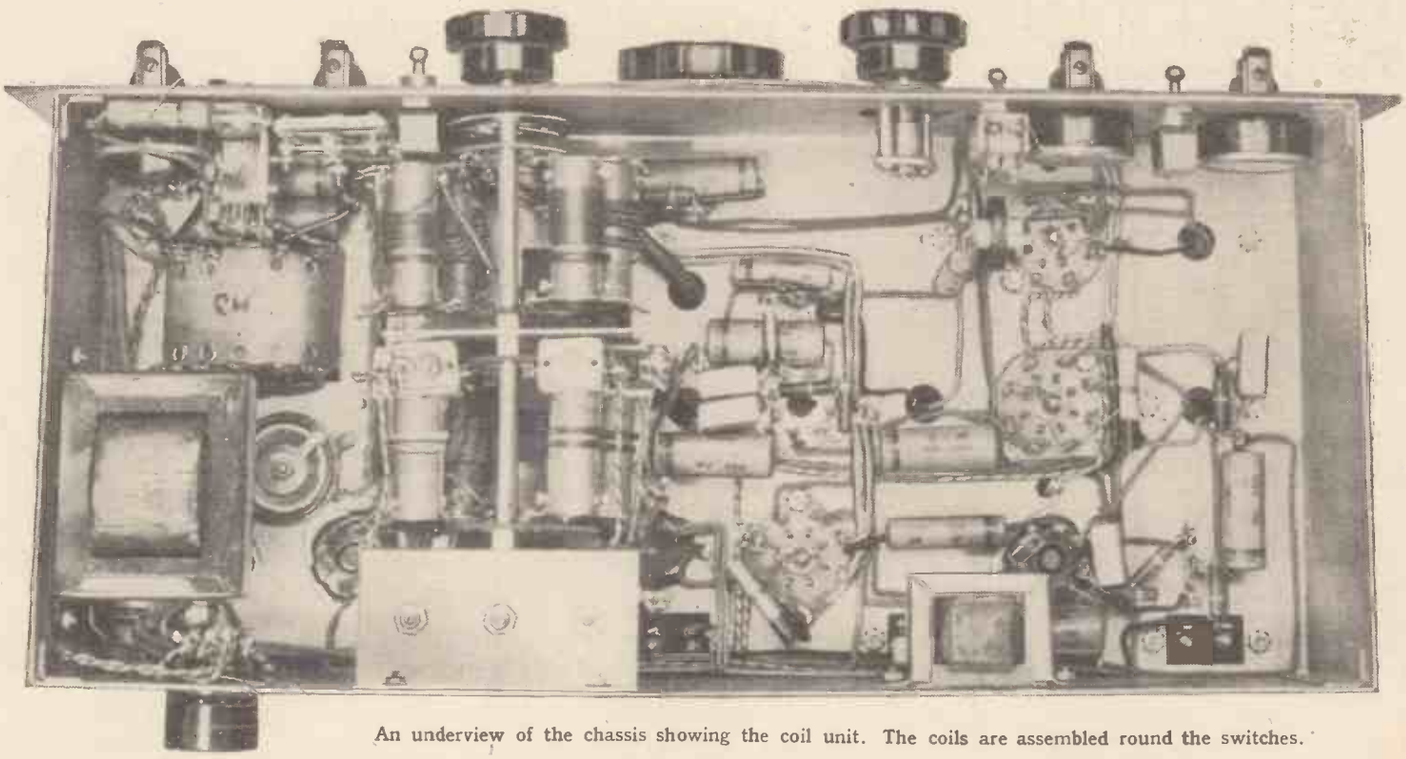

An underview of the chassis showing the coil unit. The coils are assembled round the switches.

**New Communication Receiver—**

governed by its screen voltage. Nothing is easier than to provide a screen voltage rheostat, with the result that screen voltage can be set so that the pentode will just pass as loud a signal as may be tuned in, but no more. Thus it cannot pass noise crashes louder than the signal. The net result of this limiting action is to allow noise to be held down to the signal level—and in operation this sounds as if the noise had been completely eliminated. This whole operation could have been made automatic, but this is undesirable because then the system becomes such a perfect "hole-puncher" that a local noise will completely shut off reception until it ceases. This is the true measure of the effectiveness of any of the so-called "hole-punching" noise-eliminating systems.

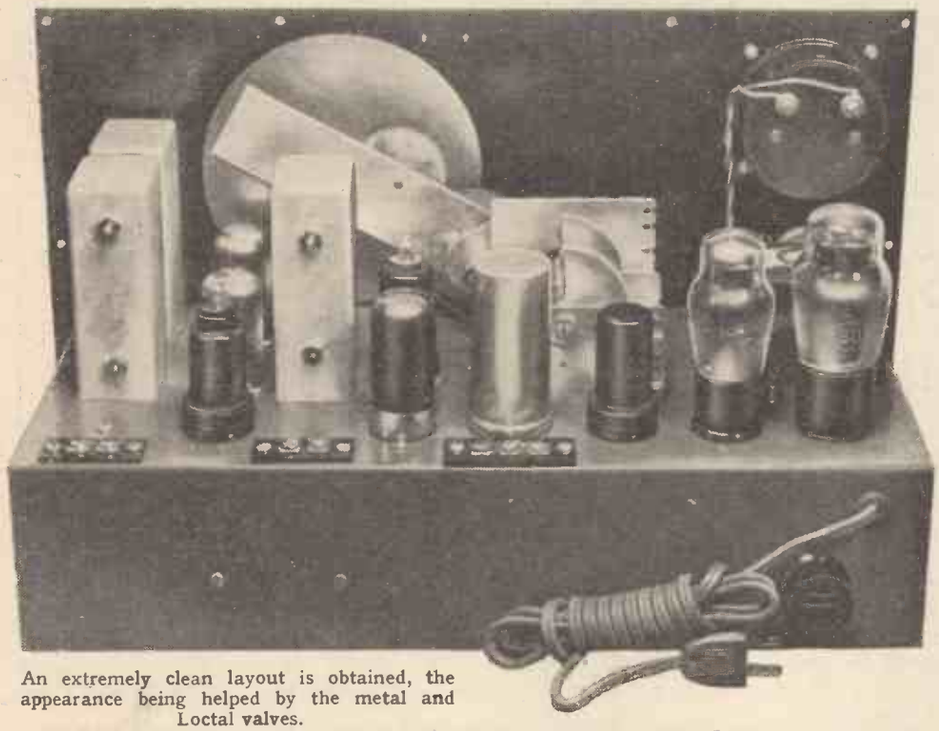

An extremely clean layout is obtained, the appearance being helped by the metal and Loctal valves.

A headphone jack is included in the 6B8 anode circuit after the tone and volume controls. This provides a nice audio discrimination against heavy low-frequency noise, for the high pentode anode resistance in effect "tunes" the phones so that they do not respond to the low tones, which are useless for either CW or intelligible phone reception. They are there on the speaker, however, which is where they belong for the reception of music. The 7C5 audio stage is so conventional as not to deserve special comment.

The power supply is worthy of notice, not because it uses a power transformer, large high-inductance filter choke and plenty of 450-volt can-sealed dry electrolytic filter capacity, but because it allows either battery or AC operation of the same receiver. An 8-pin socket with dummy plug strapped across for AC operation allows the power circuits to be broken by pulling out the dummy plug. This opens the rectifier +HT lead and the heater circuit, to which batteries, or a 6-volt battery and vibrator, or generator HT supply, can be connected by another plug. It also brings out to this plug the send-receive switch and the on-off switch, so that both function on either AC or battery operation. Plenty of space is left in the back of the set cabinet for a vibrator or generator HT supply—even for a complete dry battery supply—not to mention one of the writer's recently invented "Diversity Couplers," the addition of which turns the "Silver-Super" into a full-fledged anti-fading dual diversity receiver.

Upon the premise that no communication receiver is any better than the controllability of its operating functions, front panel control has been made quite complete. The large satin-chromium tuning dial is 7¾in. in diameter, with six accurately calibrated wavebands occupying 324 degrees of its circumference, with the high-frequency bands at the outside where the effective dial scale length is greatest—21⅞in., to be exact. Around this outer dial edge is a 500 division scale which is directly readable to one part in 5,000 against the 0-10 decimal indicator scale. This, plus the great effective dial scale length, provides what might be called "spread band" tuning in that each frequency range is unusually widely spread out for a main dial. For those desiring it an 0-200 division, 4in. diameter band-spread dial is available which is driven from the main dial shaft through a 12:1 positive, no-backlash, gear train. Easily mounted and with its band-spread dial "peeking out" at the upper right of the main dial, it gives over eleven feet of dial scale for each 2.2:1 frequency band with, through its own 0-10 decimal indicator, a direct readability to 1 part in 21,600. Dial drive is direct through its centre knob for fast band-skipping, or 15:1 vernier through the large knob at its lower right, properly placed for long hours of fatigue-free tuning. Other controls are noise limiter, tone, headphone jack, antenna trimmer, send-receive, wave-change, vernier tuning, AVC on-off, audio gain, BFO on-off, IF gain, selectivity, and BFO pitch control. The panel is finished in silver on etched-black, and in its grey enamel steel cabinet with hinged cover the set presents an appearance which is unusual among communication receivers; in fact, the stark and strictly utilitarian appearance that has come to be associated with this type of set has been entirely avoided.

# Dry-Cell LT in U.S.A.

FROM OUR NEW YORK CORRESPONDENT

THE dry-cell valve has had a hectic life in America. Originally there was a contest between a Westinghouse triode and a General Electric triode. The former had a coated filament which ran at 0.25 ampere, 1.1 volts; the latter used a thoriated filament at 0.06 ampere, 3.3 volts. Westinghouse believed in connecting dry cells in parallel, General Electric preferred them in series—in either case the filaments gave up the ghost when the rheostat was turned up too far. The 3.3-volt tube begat a fragile RF tetrode; the 1.1-volt tube had no offspring.

We went next to "air" cells and 2-volt tubes, mostly of the 0.06-ampere sort, including a pentagrid converter whose oscillator section rebelled at the notion of working on 0.12 watt of filament power. This tube was accordingly made to go by adding another triode externally, causing one engineer to refer to it as the "tube with the outboard mutual conductance." This and similar incidents caused the 2-volt series to diverge until there are 0.06, 0.12 and 0.24-ampere filaments. If always turned on by rheostat instead of switch, and that under the supervision of a dependable voltmeter, these tubes do very well indeed. In honour of long service they were recently renamed. The little "30" triode is now the "1H4-G" and so on down the line. This line, incidentally, includes a general purpose triode, an RF tetrode, sharp and remote cut-off RF pentodes, several pentagrid converters, a diode-triode, a diode-pentode, several loud speaker pentodes, single and double Class "B" loud speaker triodes and even a low-mu loud speaker triode. We had thought the matter settled.

Now we have a 1.4-volt series of dry-cell tubes to be fed from a single cell without the use of a regulating rheostat of any sort.

These valves are in tubular glass bulbs with octal bases, and comprise RF and AF pentodes, a pentagrid frequency-changer and a diode-triode. Filament current is 0.05 or 0.1 amp.

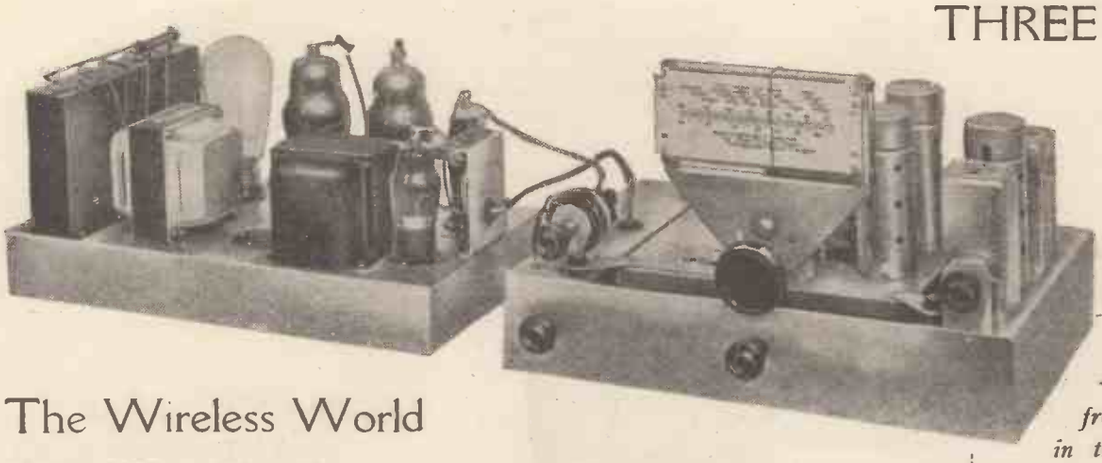

# THREE-BAND RECEIVER FOR THE DC QUALITY AMPLIFIER

*APPARATUS for DC mains operation differs from AC equipment chiefly in the output stage, and the early circuits are always substantially the same. There are, however, minor points of difference which are well brought out in this receiver. It is a superheterodyne designed for use with the DC Quality amplifier.*

## The Wireless World

# DC Mains Super

AMONG the series of articles on receiver design which appeared last year in *The Wireless World* considerable space was devoted to the design and construction of a high-quality amplifier for DC mains operation.[1] This amplifier has two KT31 valves in push-pull in the output stage; they operate with negative feed-back and deliver an output of 5 watts. The penultimate stage is a triode-connected KTZ63 (or 6J7) operating as a phase-splitter, and the first stage is an H63 (or 6F5) amplifier.

The design of DC mains apparatus differs from AC chiefly in the output stage, since the main limitation of the DC supply is its low voltage. The early stages of a receiver differ from AC practice only in that the valve heaters are connected in series instead of in parallel and that a few extra by-pass condensers are necessary. It is, therefore, usually a very simple matter to modify the design of the early part of an AC set for DC operation.

In response to numerous requests, however, the details of a receiver designed especially for use with the DC Quality Amplifier is given in this article, and it will be instructive to see how closely it follows normal AC practice. A general-purpose receiver has been selected as the example and it covers the usual medium and long wavebands in addition to covering the

[1] *The Wireless World*, February 24th, 1938.

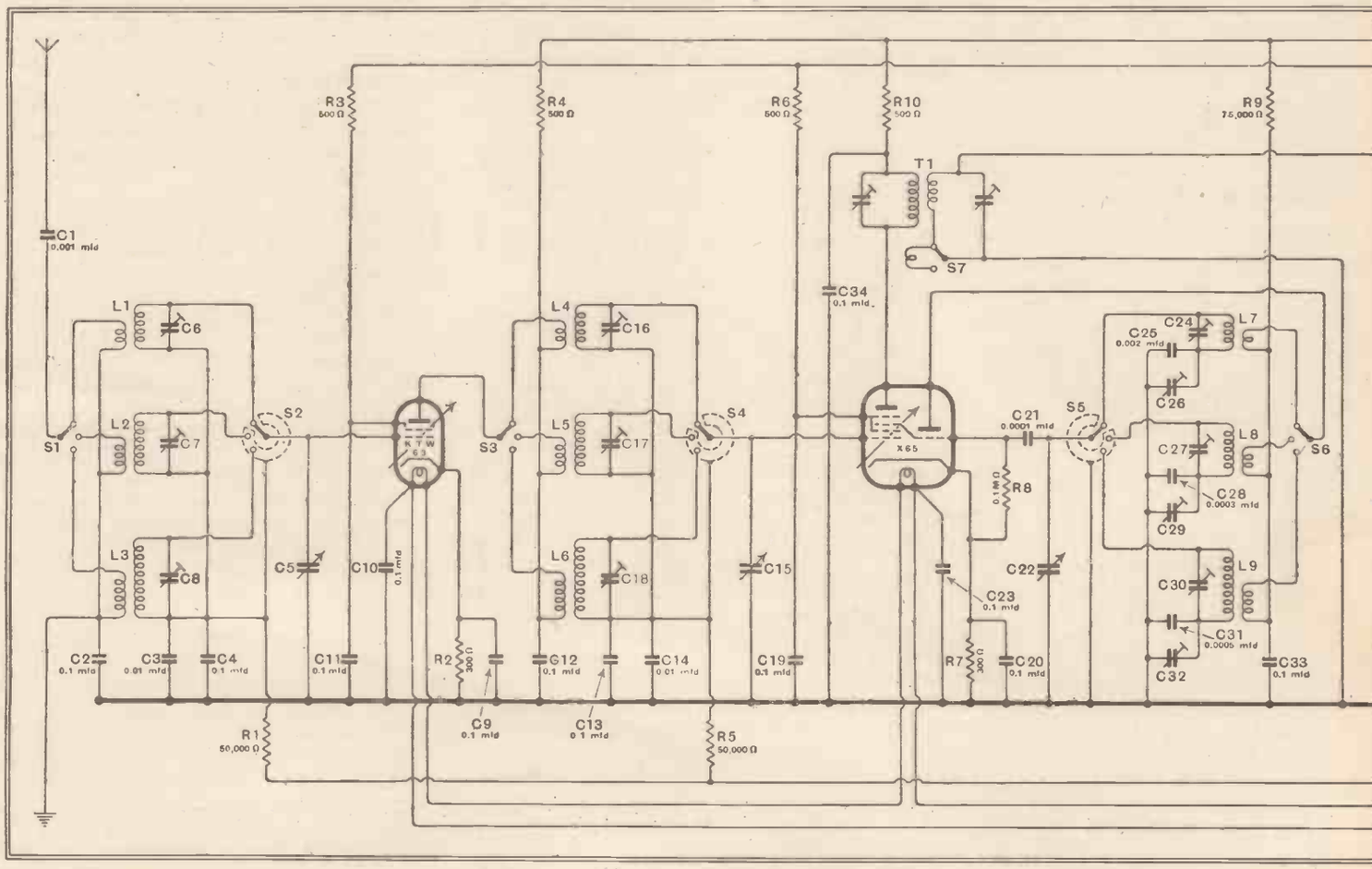

most useful portion of the short waves in one band.

The circuit diagram is shown in Fig. 1, and it will be seen that there is one RF stage, frequency-changer, one IF stage, and a diode detector and AVC source. The output of the detector is taken to the DC Quality Amplifier, from which the power supply is also derived.

The valves used have their heaters connected in series with those of the amplifier, consequently they must consume the same current—0.3 ampere. The heater voltage rating does not matter much, but the lower the voltage chosen the less will be the voltage between heater and cathode of the valves towards the positive end of the chain. This is some slight advantage and we accordingly adopt 6.3-volt valves.

Referring to Fig. 1, the general arrangement of the circuit will be seen to be quite straightforward and conventional. The RF valve is a KTW63 (or 6K7) which is self-biased by the 300-ohm resistance R2 shunted by the 0.1 $\mu$F condenser C9. The screen is fed from the 100-volt line and decoupled by R3 and C11.

The switch S2 selects the appropriate coil—L1, L2, or L3—for the band desired, while S1 changes the aerial connection. Parallel trimmers C6, C7 and C8 are provided and tuning is carried out by the section C5 of the gang condenser. AVC is applied to the valve through the tuning coils, the filter R1 C3 being provided. C3 is given a value of 0.01 $\mu$F for short waves, but is shunted by the 0.1$\mu$F condenser C4 to provide a more effective by-pass on the longer wavelengths.

Similar circuits are used for the coupling between the RF and frequency-changer valves, the coils being L4, L5 and L6, with the trimmers C16, C17, C18 and the tuning condenser C15. Decoupling of the anode circuit of the RF stage is obtained with R4 and C12.

The frequency-changer is a triode-hexode—the X65—and AVC is applied to it through the filter R5 C14; as in the case of the RF stage, the 0.01$\mu$F condenser C14 is shunted by C13 of 0.1 $\mu$F. The screen of the triode-hexode is fed from the 100-volt line and decoupling is provided by R6 and C19. Grid bias is obtained in the usual way from the cathode resistance R7, which is shunted by C20.

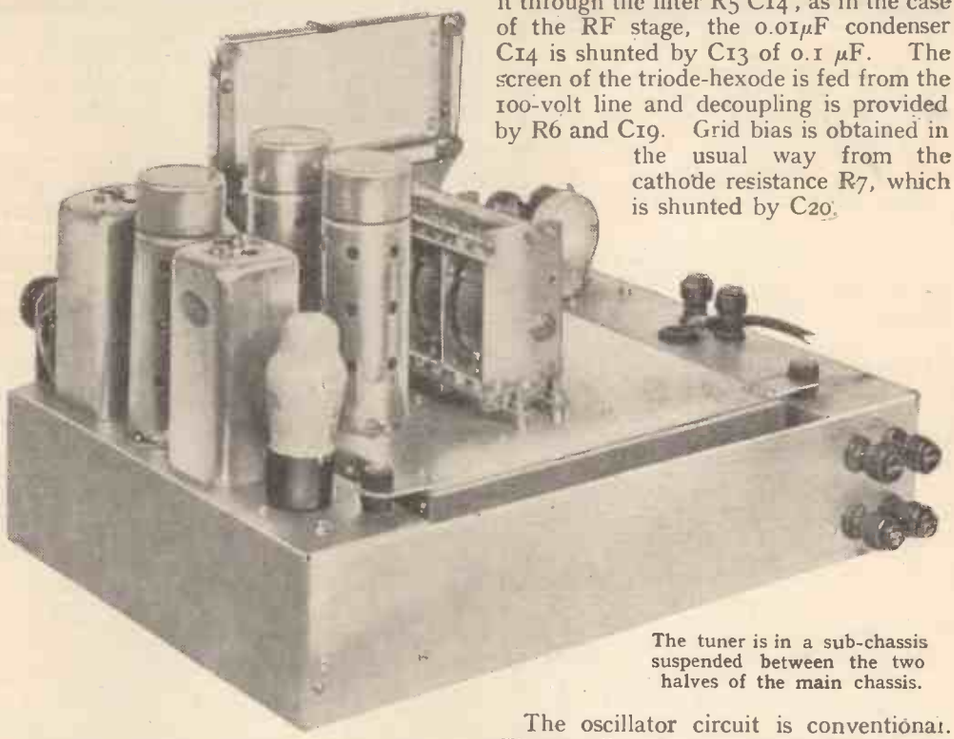

The tuner is in a sub-chassis suspended between the two halves of the main chassis.

The oscillator circuit is conventional. The parallel trimmers C24, C27 and C30 are provided, as well as adjustable padding condensers on each band. On short waves the padding capacity comprises C25 and C26 in parallel, while for the medium waveband C28 and C29 are effective. On long waves, C31 and C32 are the relevant condensers.

The intermediate frequency is 465 kc/s and the first IF transformer, which couples the FC and IF valves, is of the variable selectivity type. The coil coupling is fixed mechanically. The two main windings provide the normal coupling for high selectivity, but a third winding which is tightly coupled to the primary can be thrown into circuit by S7 to increase the total coupling for low selectivity. This system is very simple and in practice works very well.

The IF stage is another KTW63 (or 6K7), but is not controlled from the AVC system. This is to reduce the possibility of distortion through overloading the IF valve when receiving strong signals.

Following the IF valve comes the detector, for which the D63 (or 6H6) diode is used. The two anodes and cathodes in this are strapped so that the valve operates as a single diode. IF filtering is provided by R14 and C39 and the load resistance is the volume control R18.

The alternating potentials across this resistance constitute the AF output and any desired fraction of them can be taken off through the coupling C43 R19 to the first AF valve in the amplifier. The steady voltage across R18 is used for

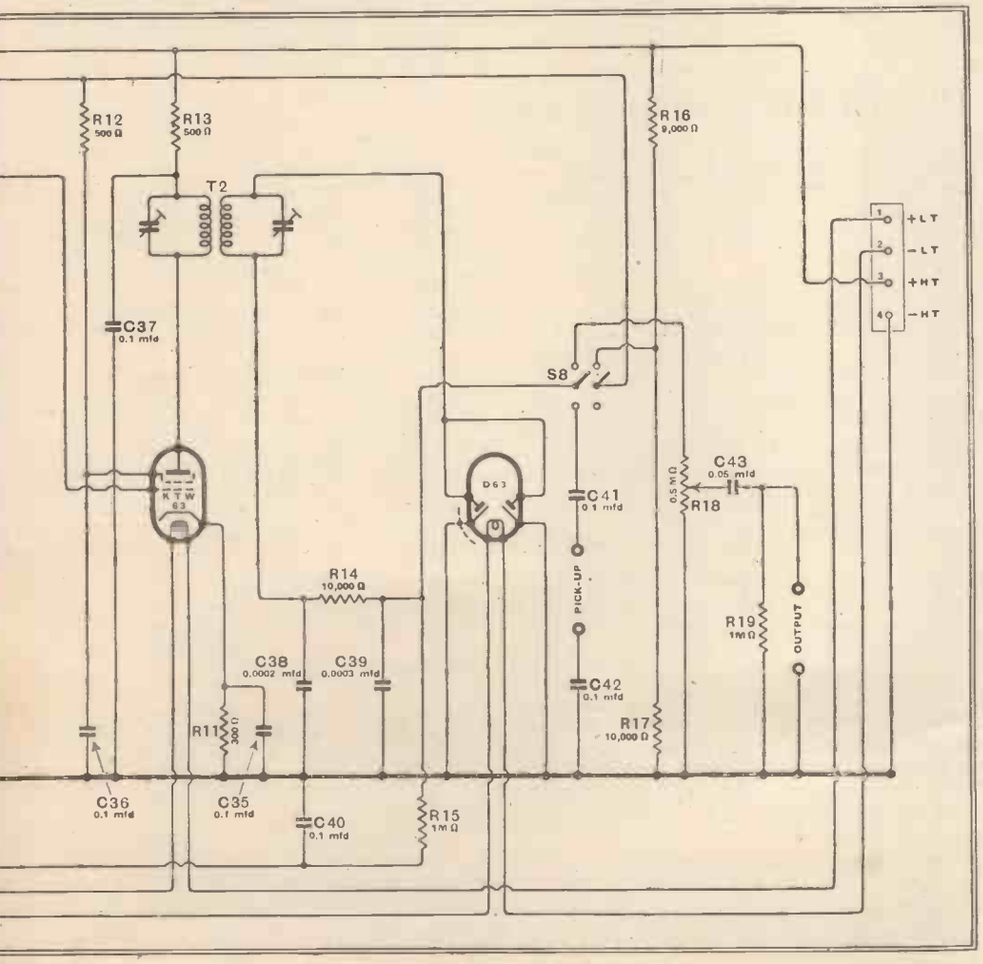


Fig. 1. This diagram shows the complete circuit of the receiver portion. Isolating condensers C1, C2, C41 and C42 are connected in the aerial, earth and pick-up leads.

**DC Mains Super—**

AVC purposes and is taken off through the filter R15 C40, the purpose of which is to remove the AF signal from the AVC line.

The switch S8 is for the change over from radio to gramophone and on the latter breaks the screen supply to the first three valves. The screen supply is taken from the voltage divider R16, R17.

The differences from AC practice, apart from the heater supply, are merely those brought about by the fact that the circuits are not insulated from the mains. It must never be forgotten that with a DC mains set the circuits are inevitably in direct connection with the supply mains.

It is, therefore, necessary to insert the condensers C1 and C2 in the aerial and earth leads to prevent short-circuiting the mains. It is also advisable similarly to insulate the pick-up, and this is done by C41 and C42.

The heaters are connected in series, the detector being at the negative end of the chain, and by-pass condensers C10 and C23 are joined to chassis from the heaters of the RF and FC valves in order to prevent any RF voltages from being developed on these heaters. Such voltages would be likely to cause modulation hum.

Certain minor changes are necessary in the amplifier in order that the receiver may be used with it. Actually, C1, C2 and R1 in the amplifier are removed and transferred to the receiver, where they become C41, C42, and R18. This is done as it is more convenient to have the volume control on the receiver chassis than on the amplifier.

The grid of the H63 is taken straight to one input terminal and the other is joined to chassis. A 4-way connection block is fitted and two of its terminals taken to −and +HT, while the other two are used for the heater supply. The heater lead between the H63 and the KTZ63 is cut and the two ends taken to the terminal block. No other change is needed, for the barretter is still capable of controlling the additional valves.

*(To be concluded.)*

### LIST OF PARTS

1 **Condenser**, 3-gang, 0.0005 mfd., **C5, C15, C22** — **Polar C1703**
1 **Dial**, ratios 10:1 and 50:1 — **Polar "Micro Horizontal Drive"**
9 **Trimmers**, 30-60 mmfds., **C6, C7, C8, C16, C17, C18, C24, C27, C30** — **Bulgin SW122**
1 **Trimmer**, 3,000 mmfds., **C26** — **Bulgin CP7**
1 **Double Trimmer**, 150-550 mmfds., **C29, C32** — **Polar 55**
1 **Set of Coils**, PA1, PA2, PA3, PHF1, PHF2, PHF3, PO1, PO2, PO3 — **Wearite**

**Fixed Condensers:**
1 0.0001 mfd., mica, **C21** — **T.C.C. "M"**
1 0.0002 mfd., mica, **C38** — **T.C.C. "M"**
2 0.0003 mfd., mica, **C28, C39** — **T.C.C. "M"**
1 0.0005 mfd., mica, **C31** — **T.C.C. "M"**
1 0.001 mfd., mica., **C1** — **T.C.C. "M"**
1 0.002 mfd., mica, **C25** — **T.C.C. "M"**
2 0.01 mfd., mica, **C3, C14** — **T.C.C. "M"**
1 0.05 mfd., tubular, **C43** — **T.C.C. 341**
*18 0.1 mfd., tubular, **C2, C4, C9, C10, C11, C12, C13, C19, C20, C23, C33, C34, C35, C36, C37, C40, C41, C42** — **T.C.C. 341**

**Resistances:**
3 300 ohms, ½ watt, **R2, R7, R11** — **Dubilier F½**
6 500 ohms, ½ watt, **R3, R4, R6, R10, R12, R13** — **Dubilier F½**
1 10,000 ohms, ½ watt, **R14** — **Dubilier F½**
2 50,000 ohms, ½ watt, **R1, R5** — **Dubilier F½**
1 75,000 ohms, ½ watt, **R9** — **Dubilier F½**
1 100,000 ohms, ½ watt, **R8** — **Dubilier F½**
2 1 megohm, ½ watt, **R15, R19** — **Dubilier F½**
1 9,000 ohms, 3 watts, **R16** — **Dubilier F3**
1 10,000 ohms, 2 watts, **R17** — **Dubilier F2**

*1 **Volume control**, 0.25 megohm, tapered, **R 18** — **Reliance "SG"**
4 **Valve holders**, octal type — **Clix X218**
1 **IF transformer**, variable selectivity, 465 kc/s **T1** — **Varley BP124**
1 **IF transformer**, 465 kc/s, **T2** — **Varley BP122**
6 **Terminals**, ebonite shrouded, A, E, PU (2), Output (2) — **Belling-Lee "B"**
1 **Connector**, 4-way — **Bryce 5C2**
1 **Cable**, 4-way — **Goltone R36/4MR**
1 **Switch**, rotary type, SPDT, **S7** — **Bulgin S92**
1 **Switch**, rotary type, DPDT, **S8** — **Bulgin S114**
1 **Switch**, assembly — **Peto-Scott 632FE**
comprising: 3 switches, 3-way, SP, 3 switches, 3-way, SP with earthing plates, locator and 8-inch rod, **S1, S2, S3, S4, S5, S6.**
1 **Length screened sleeving** — **Goltone**
3 **Valve screens**, octal type — **Peto-Scott**
1 **Shaft coupler**, ¼-inch — **Bulgin 2005**
3 **Grid clips**, octal type — **Bulgin P96**
**Tuner Chassis** — **Peto-Scott**
**Receiver Chassis**, with brackets — **Peto-Scott**
**Miscellaneous:** — **Peto-Scott**
8 lengths systoflex, 3 ozs. No. 20 tinned copper wire. Screws: 5 doz. 6BA ¼in. r/hd., 2 doz. 4BA ¾in. r/hd., all with nuts and washers; 1 doz. extra 4BA nuts for mounting switches.

**Valves:**
2 **KTW63, 1 X65, 1 D63** — **Osram**

*Two 0.1 mfd. condensers and the volume control can be transferred to the receiver from the DC Quality Amplifier.

## PROBLEM CORNER–20

**An extract from Henry Farrad's correspondence, published to give readers an opportunity of testing their own powers of deduction:—**

All Hallows School,
Berkhamsted.

Dear Henry,

I have been making up a gramophone turntable and control panel for a show we are doing here, and thought I would paint stroboscope stripes round the turntable, like the B.B.C., for keeping the speed right. But I don't seem to be able to get the thing to work at all as it should. Can *you* see what's wrong (you always can!). I've been over it heaps of times. The proper speed is 78 r.p.m. and as the mains frequency is 50 a second, and therefore 3,000 a minute, there ought to be 3,000/78, or 38½, white stripes around the turntable. Actually, I've put on 38, which ought to be near enough, because it corresponds to 79 r.p.m. But it just doesn't do!

No, our lamps are *not* run off DC! I have good reason to remember that, because old Crabbie gave me one of his sarcastic impots for waving a knife about at table years ago to make sure. He couldn't be made to see that it was in the interests of science. And it *is* a genuine 50 cycles, because we are on the Grid now.

Yours ever,
Tony.

*Why didn't the stroboscope work? Solution on p. 472.*

# Television Programmes

Sound 41.5 Mc/s — Vision 45 Mc/s

**An hour's special film transmission intended for demonstration purposes will be given from 11 a.m. to 12 noon each weekday. The National or Regional programme will be radiated on 41.5 Mc/s from approximately 7.45 to 9 p.m. daily.**

THURSDAY, MAY 18th.

**3,** "The Chance of a Lifetime," a sporting romance by John Pudney. **3.35,** British Movietonews. **3.45,** 243rd edition of Picture Page, introducing scenes from the "Dorchester Floor Show."

**8.30,** Tennis O.B. from the Empire Pool, Wembley. Donald Budge, Ellsworth Vines, Bill Tilden and Hans Nusslein in singles and doubles. **9,** Flotsam and Jetsam in Cabaret. **9.35,** Gaumont-British News. **9.45-10.15,** 244th edition of Picture Page.

FRIDAY, MAY 19th.

**3,** O.B. from the Crystal Palace of Veteran Motor Cars. **3.20,** Gaumont-British News. **3.30,** Cartoon Film. **3.35,** "A Game of Cut-Throat," with Leon M. Lion and Waldo Wright.

**9,** "For those in Peril," a drama of the sea by Edward Poor Montgomery. **9.25,** British Movietonews. **9.35,** "Smiling at Grief," a play by Walter Hudd. **10,** Cartoon Film. **10.5,** "Birds"—Film. **10.15-10.40,** "The Lover," a play by C. Martinez Sierra.

SATURDAY, MAY 20th.

**2.50,** Motor Racing O.B. from Crystal Palace. **3.5,** Scenes from the Grosvenor House Cabaret. **3.25-4.35,** Motor Racing O.B. continued.

**9,** Adelaide Hall in "Dark Sophistication," a Coloured Cabaret from the Old Florida Club. **9.30,** Tennis O.B. from Wembley (as on Thursday at 8.30 p.m.). **10-10.35,** "The Chance of a Lifetime" (as on Thursday at 3 p.m.).

SUNDAY, MAY 21st.

**3,** Music Makers. **3.10,** "London Wakes Up"—Film. **3.30,** "The Deacon and the Jewess," a play by H. F. Rubinstein.

**8.50,** News. **9.5,** Mendlessohn's Violin Concerto in E Minor played by Szigeti with the B.B.C. Television Orchestra. **9.30,** "The Plough that Broke the Plain"—Film. **10-10.40,** "Blind Man's Buffet," a Food Bee conducted by Marcel Boulestin. The blind-folded victims will endeavour to name the edibles which are placed in their mouths.

MONDAY, MAY 22nd.

**3-4.25,** Sybil Thorndike in "Sun Up," the play by Lula Vollmer.

**9,** John Carr's Jacquard Puppets. **9.10,** "Derby Secrets"—Film. **9.20,** "Lonesome Like," a play by Harold Brighouse. **9.50,** Gaumont-British News. **10-10.30,** The Vic-Wells Ballet in Act III of the "Sleeping Princess."

TUESDAY, MAY 23rd.

**3,** "For Those in Peril" (as on Friday at 9 p.m.). **3.25,** Gaumont-British News. **3.30,** Derby Pre-View; O.B. from Epsom Downs. **3.35-4.10,** "The Lover" (as on Friday at 10.15 p.m.).

**9,** "Intimate Cabaret." **9.15-10.30,** Boxing O.B. in which it is hoped to televise the Harvey-Farr fight.

WEDNESDAY, MAY 24th.

**2.30,** The Derby. O.B. from Epsom of the 156th renewal of the Derby Stakes. **3.10,** Naunton Wayne in Cabaret, with Billy Costello (Popeye the Sailor). **3.40,** Cartoon Film. **3.45,** Vanity Fair—modern dress design.

**9-10.30,** D. A. Clarke-Smith in "The Great Adventure" by Arnold Bennett.

# Cathode-Ray Amplifier Tester

## A COMPACT PORTABLE INSTRUMENT FOR DIAGNOSING AMPLITUDE DISTORTION

By C. B. GUEST

*DEVELOPED primarily for testing cinema amplifiers, this instrument provides the means of tracing faults by inspection of a pattern and with the minimum of preliminary adjustment.*

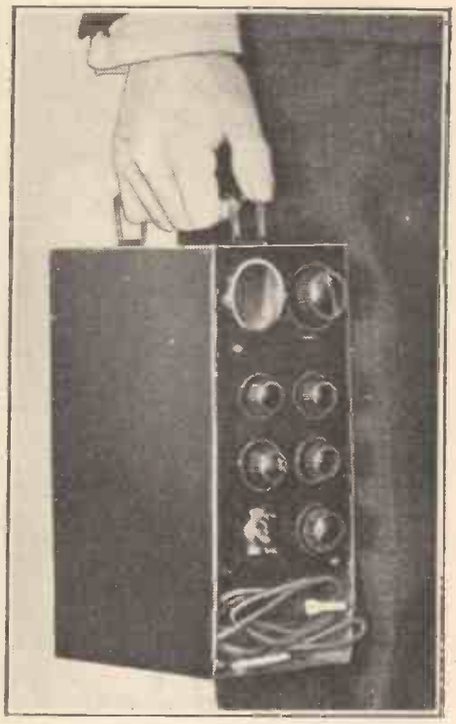

THE testing of a faulty amplifier, the fault being, say, in the nature of slight distortion, has always been troublesome by meter methods. A meter in the anode circuit of the power stage is useful in indicating overloading, but is of very doubtful value in locating the source of the distortion which is causing the change of current.

For instance, supposing our amplifier has a valve which runs into grid current long before it is entitled to do so. How are we to prove it? Then again, there is parasitic oscillation which may occur for only a fraction of the cycle of operations. The list of possible unknowns is endless, and they often require a considerable amount of mental juggling to track to their lair.

### Need for Simplicity

Without a doubt the most useful tool available both for research and the servicing of amplifiers is the cathode-ray tube, but conventional circuit arrangements, excellent as they are for use in the laboratory or on the service bench, do not always meet the requirements of portability demanded for outdoor work. Now most cathode-ray tubes need a minimum input of about 30 volts to give even a small image, and it is not easy to build a really light portable test equipment of straight-line characteristics. Then there is usually a time base to adjust before a waveform passing through the amplifier can be examined. Needless to say, slight departures from the proper waveform cannot be determined without a reference wave superimposed on the tested wave, an obviously difficult thing to do. The impracticability of determining small amounts of distortion in the waveform of music and speech will need no explanation to those who have listened to a note while comparing its trace on the CR tube.

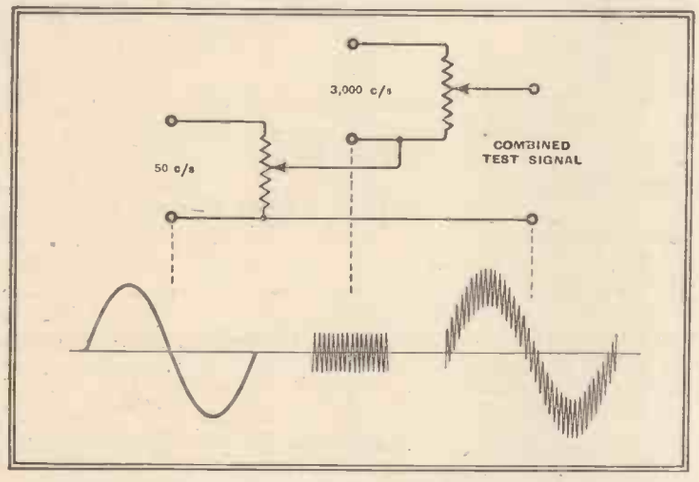


Fig. 1.—The test signal consists of a 3,000-cycle note impressed on a 50-cycle wave.

The equipment to be described has the advantage of being independent of waveform and giving a direct indication of the linearity or otherwise of the input-output characteristic throughout the whole of a cycle. The principle on which this works is dependent upon two frequencies, differing by a ratio of at least 60 to 1, applied to the amplifier under test. The low frequency, say 50 c/s, is of comparatively large amplitude, the high frequency, say 3,000 c/s, being small relative to the low frequency. The high frequency is superimposed on the low frequency as in Fig. 1.

In carrying out a test on an amplifier the amplitude of the test signal is increased until the full working range of the valves is covered. Since amplitude distortion, with which we are most concerned, is merely a departure from a straight line, or change in slope of a line, then at the point of maximum positive sweep on a valve or amplifier with a curved characteristic the amplification of the superimposed high frequency will be greater than that at the point of maximum negative sweep, giving an output waveform resembling Fig. 2 (*a*). The next step is to filter out the low frequency, leaving only the high-frequency component, Fig. 2 (*b*), to be passed on to the horizontal sweep of the cathode-ray tube, the vertical sweep of which is obtained from the same source as the low-frequency sweep to the amplifier, in our case the 50 c/s mains supply.

It will be noted that the success of this system is dependent upon the smallness of the amplitude of the high-frequency sweep

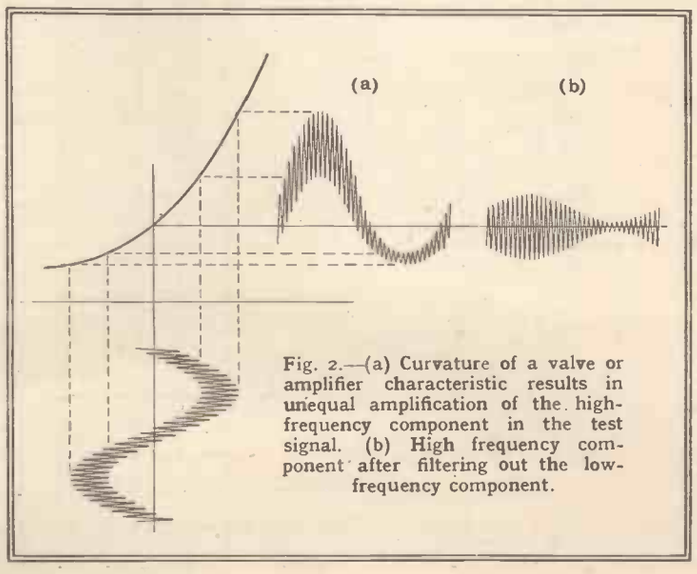


Fig. 2.—(a) Curvature of a valve or amplifier characteristic results in unequal amplification of the high-frequency component in the test signal. (b) High frequency component after filtering out the low-frequency component.

**Cathode-Ray Amplifier Tester—**

to the amplifier under test. The reason for the 60 : 1 frequency ratio will also be apparent, for this has the effect of dividing the cathode-ray vertical sweep into 60 different parts, each giving a measure of the slope at its own point.

A study of the few examples given in Fig. 3 will give a working idea of the effects produced by different curves. Weird and wonderful are some of the patterns produced by gross overloading, and a lot may be learnt about effects which may never have been expected. One point worth noting is that if one both listens to the sound and looks at the picture, then in every case it will be found that the picture indicates distortion long before it can be detected by ear.

The cathode-ray tube used in this equipment is the RCA A13 which, although small, has been entirely satisfactory. The image is magnified by a lens mounted on the front of the panel, and not the slightest difficulty has been experienced in viewing the image. It has the further advantage of a built-in metal shield, which is of importance in portable equipment, and is modest in its voltage requirements.

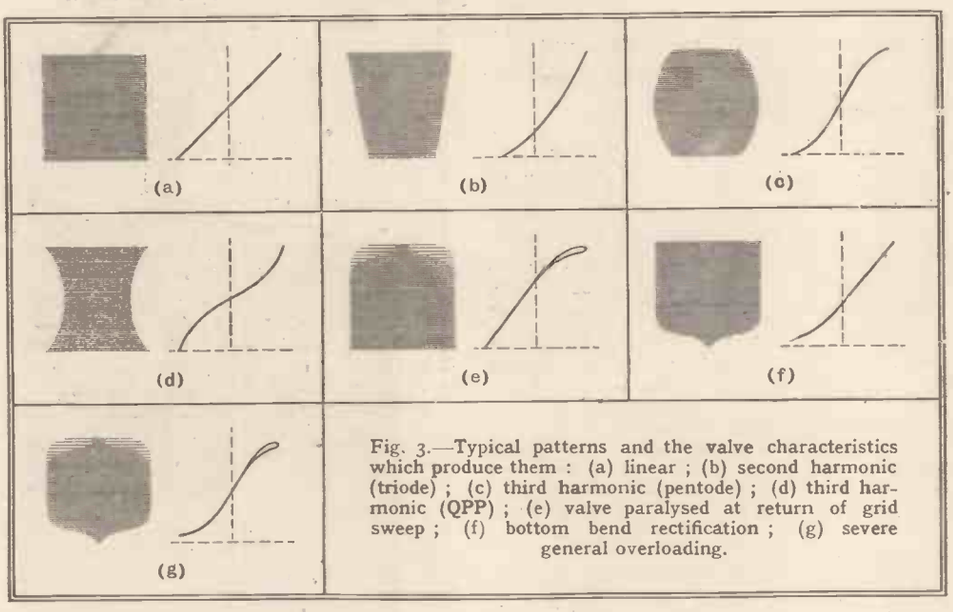


Fig. 3.—Typical patterns and the valve characteristics which produce them : (a) linear ; (b) second harmonic (triode) ; (c) third harmonic (pentode) ; (d) third harmonic (QPP) ; (e) valve paralysed at return of grid sweep ; (f) bottom bend rectification ; (g) severe general overloading.

The high-frequency oscillator is of the usual type with the coils in a metal case. The secondary of the oscillator is stepped down in a ratio of 10:1, and is in series with an 0.05-mfd. condenser and 5,000-ohm potentiometer. The condenser is to prevent the low frequency from circulating in the oscillator coils and modulating it. Likewise a 0.05-mfd. condenser is fixed across the low-frequency potentiometer to by-pass the high frequency component.

The oscillator valve is one half of a 6A6, the other half being used for the horizontal sweep amplifier. It should be noted that small amplitude distortion of the sweep amplifier is not of great importance, since we are utilising only the outline drawn by the sum of the peaks of the high-frequency sweep.

The mains transformer is wound with No. 42 SWG enamelled wire, which makes a very compact transformer, but it is advisable to use a somewhat heavier gauge of wire. The rectifying valve is a 1-V half-wave, and with the tiny 15-henry choke and 8 + 8-mfd. dry electrolytic smoothing condensers produces about 280 volts HT. No tapping is provided on the mains side of the transformer, and the equipment appears to function happily on anything between 220/260 volts.

### Hints on Operation

A point of considerable importance centres around the high-pass filter input to the sweep-amplifying valve. This is series tuned, and the input load is therefore approximately that of the resistance of the coil, which is but a few hundred ohms. If the test is applied to a high-impedance circuit then due regard must be paid to this load. However, in most cases it will only be necessary to insert a resistance in series with the input to the filter of 5,000 ohms or so. In the case of individual valve tests, the high-frequency amplitude is so small that the low load is no disadvantage. A switch is provided which opens the filter circuit when this is not required.

In conclusion, it may be pointed out that, although the primary duty of the equipment is the locating of audio amplifier troubles, its usefulness does not terminate here. Numerous other appli-

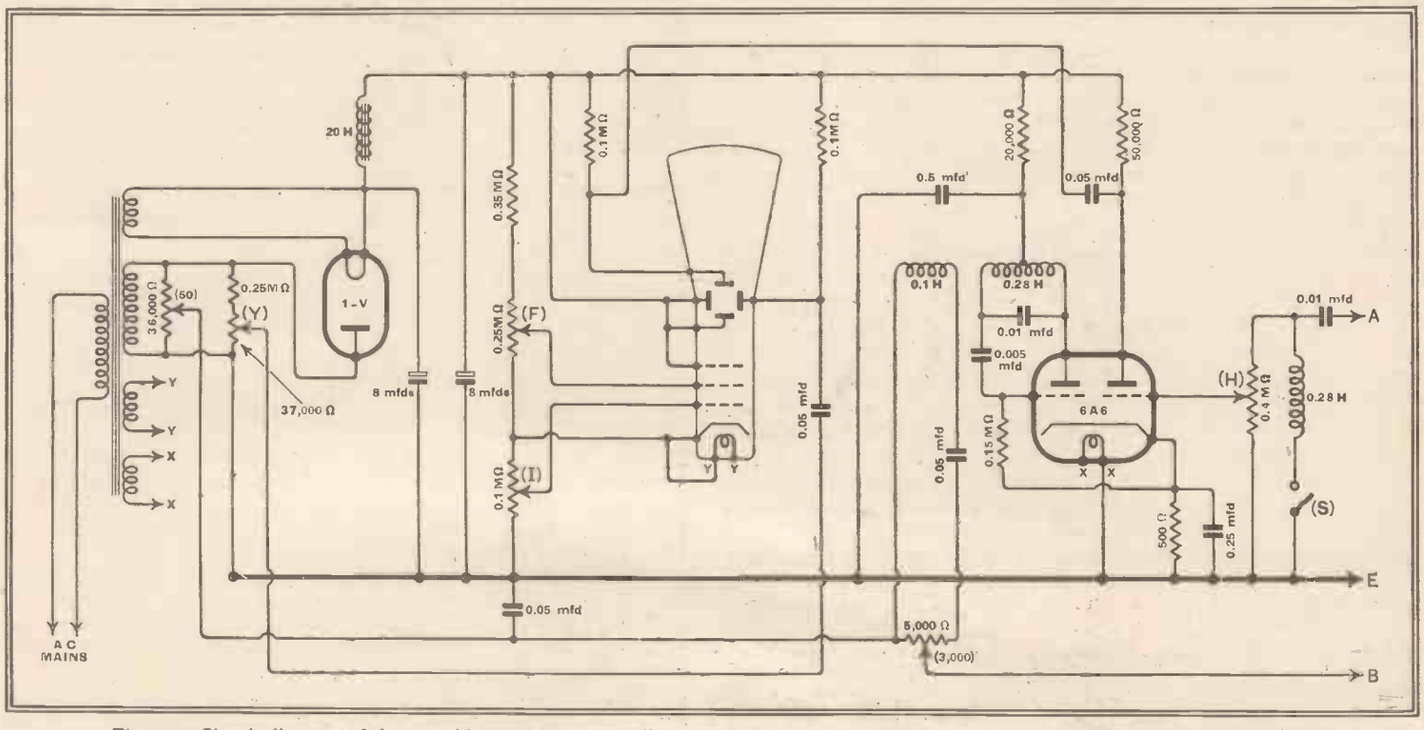


Fig. 4.—Circuit diagram of the portable cathode-ray amplifier tester. Lettering in brackets refers to the controls shown in Fig. 5.

**Cathode-Ray Amplifier Tester—**

cations are possible, for instance, inter-valve and output transformers may be examined provided that due consideration be given to the value of the primary current and voltage required to load the transformer under test, which may easily exceed the rating of the midget mains transformer fitted to the equipment. However, if tests of this kind are contemplated, then a much larger or a separate 50-cycle sweep transformer is desirable. Under normal working conditions output transformers are, of course, tested in conjunction with the valve or valves to which they are connected, preferably on a resistance output load which is, unlike the loud speaker, constant at all audio frequencies. Under laboratory conditions of test some weird and wonderful patterns often appear which challenge analysis and offer ample opportunity for the experimenter to "wonder why." One interesting experiment on a valve amplifier is to filter out not only the 50 c/s but the 3,000 c/s as well, by fitting a condenser of about 0.001-mfd. capacity in series with the input to the cathode-ray internal amplifier filter, which now mainly passes on the third and higher harmonics of the 3,000-c/s frequency. It is reasonable to expect that the picture drawn will resemble the parent 3,000-c/s picture, but often it is much different and in some cases may indicate, at various points, a failure to amplify the harmonics at all.

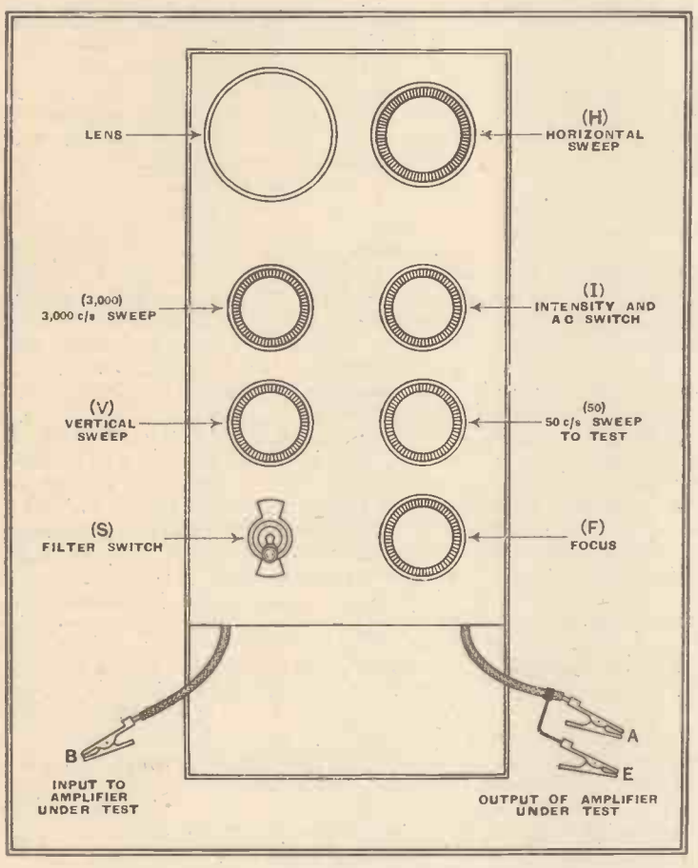


Fig. 5.—The arrangement of the controls on the front panel.

Accessibility has been sacrificed in the interests of compactness. Fortunately the instrument has proved to be completely reliable.

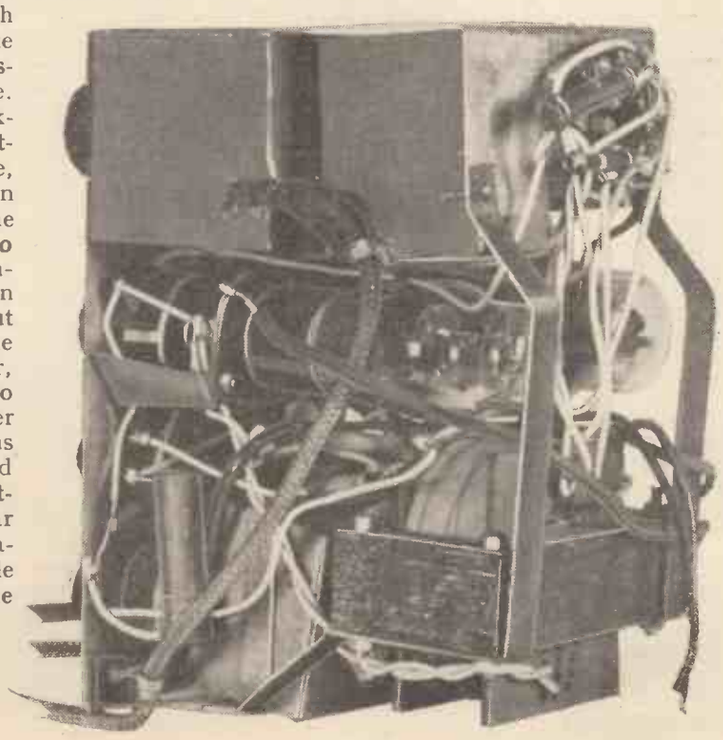

Rear view of chassis. The mains transformer is unusually small and is wound with 42SWG wire.

Much may be learnt about individual valves which can be both enlightening and instructive.

Finally, to the writer, a cinema engineer, speed in locating trouble is often a vital factor, and the test equipment described was originally designed for this purpose; it has proved its value where other methods would have been unsatisfactory.

# News from the Clubs

### *Golders Green and Hendon Radio Scientific Society*

**Headquarters:** Regal Cinema, Finchley Road, Hampstead, London, N.W.2.
**Hon. Sec.:** Lt.-Col. H. Ashley Scarlett, 60, Pattison Road, Hampstead, London, N.W.2.

Mr. D. N. Corfield recently lectured on "The Application of the Cathode-Ray Tube to Measurement." Waveform comparison and analysis were demonstrated. The lecturer also demonstrated an electronic switch which enabled the input and output waveforms to be superimposed.

The 80-metre DF competition organised by the Society will take place near St. Albans on May 21st. All interested are invited to write to the Hon. Secretary.

### *Tufnell Park Radio Club*

**Headquarters:** 33, Pemberton Terrace, Tufnell Park, London, N.19.
**Meetings:** Tuesdays and Fridays at 8 p.m.
**Hon. Sec.:** Mr. J. G. Wright, 78, Gladsmuir Road, Highgate, London, N.19.

On May 5th Mr. King gave a lecture and demonstration of a well-known make of commercial superhet. On May 9th another member demonstrated an ultra-short wave converter.

The following programme of Friday-evening talks by members has been arranged. In each case the talk will last from 9.30 to 10.15 p.m.

May 19th.—"Propagation of Wireless Waves."
May 26th.—"Reception of Wireless Waves."
June 2nd.—"Short-Wave and Anti-Interference Aerials."
June 9th.—"The Amateur Bands."
June 16th.—"Valves for Short-Wave Working."
June 23rd.—"The Interpretation of Meter Readings."
June 30th.—"Hints and Tips on Learning Morse."

### *Sale and District Radio Society*

**Headquarters:** St. Mary's School, Barker's Lane, Sale, Lancs.
**Meetings:** Thursday evenings.
**Hon. Sec.:** Mr. S. C. O. Allen, 31, Ennerdale Drive, Ashton-on-Mersey, Lancs.

A series of lectures has been arranged on the fundamental principles of electricity and magnetism with reference to radio communication. Two members of the Society hold full transmitting licences and three have artificial aerial licences.

This club is additional to those given in the "Directory of Wireless Societies," published in *The Wireless World* of April 6th.

# Letters to the Editor

The Editor does not necessarily endorse the opinions of his correspondents

### *Talkie Quality*

I AM afraid I do not agree with "Dialist's" Swindon correspondent on what he calls, in your issue of April 27th, the "villainous quality" of the sound reproduction in cinemas.

As an ex-sound and maintenance talkie engineer, I doubt very much whether the control of sound in an auditorium is left to the already overworked projectionist (here I agree with him)—particularly in large cinemas.

Surely there still remains the automatic volume control system whereby the manager, assistant manager, or someone responsible can control the volume from the auditorium.

In my experience, most cinemas found time to run through the feature films and noted the bad spots. Scratches on a film cannot be avoided, but oil is another matter, and this shows the projectionist does not attend to his apparatus properly.

I agree that the projectionist cannot judge the correct amount of volume needed for the auditorium by the sound in the "box," but a cinema properly run should have someone in the auditorium to check the volume.

In conclusion, I maintain that the average quality of sound reproduction today in at least first-class cinemas is of a high standard, and "villainous quality" is an unheard-of thing.

M. L. DIXON.

London, W.C.

### *Reproduction Level and "Scale Distortion": A Reply from America*

WE read the letter of Mr. J. R. Hughes relative to the article on our receiver, printed in *The Wireless World* of April 13, 1939, with a great deal of satisfaction. It is not too often that a correspondent grasps the fundamentals behind a design as thoroughly as Mr. Hughes has. I think that we see eye to eye with one another technically, and I will even go so far with him, from a practical point of view, as to agree that reproduction at the original level, all other things being as near perfection as is possible, represents higher fidelity than reproduction at any other level. Beyond this, however, we differ, and our absolute conviction of the impracticality of his stand is the basis for our satisfaction in his letter, for if he is wrong here he has only proved our point.

Our contention is that the average music-lover in this country would be promptly dispossessed by his landlord or hailed into court by his neighbours if he persisted in operating his reproducer at concert volume. This situation is created by a combination of circumstances such as crowded living conditions, poor building construction in so far as sound-proofing goes, a lack of musical appreciation on the part of the average man, or at least a determination on his part to select his own music and the time when he will hear it. This situation, although perhaps regrettable in part, is actual and must be faced, we think, not only by the average American, but also by a great many Englishmen.

We have solved this problem to the extent of making it possible for the listener to hear the deep bass and high overtones of music in the proper proportions to the middle register at no matter what loudness he must or wishes to listen. As this indicates, our set, having more power output than the average, is capable of reproducing concert volume in the average living-room if the user wants it. Further, by adjustment of the controls he may secure compensation not only for the average ear characteristics at the volume level which he selects, but also for individual ear defects, room acoustics, recording or transmission limitations, etc., as well, and arrive at a result which gives him his music the way he wants to hear it, whether that requires a flat curve or any other possible curve lying between the limits shown by the two curves printed in the article.

Relative to how a person will want to hear his or her reproduced music sound, it might be well to point out that the reduction in volume, in a well-designed concert hall, will depend not only on where the person sits, but also on the acoustical time constant of the hall. In any event, it will be small when compared with the reduction usually necessary for reproduction in the home.

For further information we suggest reading an article in the *Atlantic Monthly* for January, 1935, by the well-known composer and director, Leopold Stokowski, entitled "New Vistas in Radio."

In conclusion, let us say that we feel we have designed a radio and gramophone which gives tone balance and high-fidelity reproduction at concert volume as well as the most faithful reproduction at reduced or home level, which is not possible with any other commercial instrument. We believe it represents a great advance in the art.

L. G. PACENT,
H. C. LIKEL,
Pacent Engineering Corporation.
New York, U.S.A.

### *Single-wire Feeders*

I AGREE with Mr. Redfearn's remarks in your issue of April 27th; a twin-wire current-fed aerial is more suitable for the novice. However, my article was not intended to be a discussion on aerials.

I should like to point out at the same time that, although a voltage-fed aerial was shown in Fig. 1, the inscription underneath stated that the aerial could be either an end-fed (voltage-fed) or a Windom, but even when a Windom is used and matched it will radiate harmonics, due to the fact that it acts as a long-wire radiator to these unwanted harmonics.

A. G. CHAMBERS (G5NO).

Coventry.

### *Condenser Impedance*

HAVING carried out experiments on the impedance of condensers at high frequencies, and published some data[1] on the capacity for minimum impedance at any frequency, I was very interested in Mr. F. R. W. Strafford's article on this subject, and welcome his more comprehensive data taking into account leads of various lengths.

[1] *The Wireless World*, September 29th, 1933, and November 20th, 1936, *Radio Laboratory Handbook*, p. 321.

To make this information suitable for the purpose intended (i.e., for design) it is necessary, however, to specify the disposition of the leads. It would seem to be the natural thing to run them as straight as possible, joining the points between which the approximation to zero impedance is desired. Calculating the inductance at 100 Mc/s of straight lengths of 20 SWG wire of double the lengths given in Mr. Strafford's Fig. 5 (which refers to *each* lead), the capacity required for resonance is far less (e.g., for 8 cm. leads at 100 Mc/s, 14$\mu\mu$F instead of 100$\mu\mu$F), and I can only conclude that the inductance was calculated for parallel leads in Mr. Strafford's data, but as the distance apart is not specified I cannot confirm this.

My own data excluded external leads, and referred only to the inductance of the condenser itself, which I had found by experiment to be approximately equal to that of a straight piece of wire joining its terminals. Assuming these to be 1in. apart, the optimum capacity at 100 Mc/s is 100$\mu\mu$F, whereas the equivalent in Mr. Strafford's data (a pair of leads each 1.25 cm. long) is 1,000$\mu\mu$F.

Although it is impossible to cover all possible wiring conditions exactly by simple data sheets, I feel that if supplemented by more definite information on the conditions assumed, Mr. Stafford's graph would provide a higher order of approximation.

Bromley, Kent. M. G. SCROGGIE.

### *Proposed New Amateur Code*

WITH reference to the announcement on page 436 of your last issue, we feel it desirable to point out in fairness to your readers who may be members of the Radio Society of Great Britain that the proposed new Code was first submitted to the Society as recently as May 4th last. On receipt, the author was informed that the Code would be placed before the Council for consideration at its meeting on May 9th.

The Council agreed, in view of its interest, to study it individually prior to the next meeting, which will be held early in June.

J. CLARRICOATS,
Secretary-Editor,
The Radio Society of Great Britain.

London, S.W.1.

### *Inert Cells*

MY observations with respect to inert cells, published in your issue of April 27th, have resulted in my receiving a "purely friendly protest" from Mr. R. A. Gascoine, who suggests that my memory is at fault concerning the 1916 experiments. He claims that the apparatus was his and the results obtained should be credited to him.

In lodging his claim he refers to the matter as a "trivial affair," but, all the same, the last thing I desire to do is to assume as my own something to which others believe me to be not entitled.

From long association with Mr. Gascoine I have no doubt of his sincerity in the matter and crave his indulgence, as well as that of your readers, for what appears to have been a misstatement of fact.

STANLEY G. RATTEE.

London, E.C.4.

# NEWS OF THE WEEK

## MARCONI RESEARCH

**Features of the Company's Annual Report**

IN the course of his report at the annual meeting of the Marconi Wireless Telegraph Company, Mr. H. A. White, the chairman, stressed the importance of research, which has been the life-blood of the Company whose future, he said, depended primarily on the continuation and expansion of the work.

The erection of a new main building for research laboratories, and the enlargement of the Marconi College at Chelmsford, where students of nineteen nationalities were at present working, were the joint cause for a major part of the increase in the value of the Company's fixed assets, which had risen from £297,589 at the end of 1935 to £549,420 at the present time.

***Opportunities for Research***

"As a general rule," said Mr. White, "the student coming to us without actual research experience does not become a productive member of the staff until he has completed at least two years of service after the six months' probation period at the Marconi College."

"There is no foundation," he continued, "for the assertion frequently heard in these days that there is nothing more to discover in the field of high-frequency engineering for wireless purposes. There are, on the contrary, immense opportunities for research, including, for instance, the investigation of the lowest band of ultra-short waves from 1 to 3 metres, and of micro waves measured in centimetres and perhaps ultimately in millimetres."

Certain observations of Mr. White's with regard to exports are of particular interest. He stated that during the last twelve years more than eighty per cent. of the Company's sales have been to foreign countries. This proportion has decreased considerably during the last year or two, but the home market does not in normal times offer sufficient scope, so that it is of vital importance to the company to maintain its export business.

***Recent Marconi Inventions***

During the year under review, 274 British patent applications and 874 applications in oversea countries were filed in addition to a large number of applications in other countries by subsidiary and associated concerns. The total number of Marconi patents now in force at home and abroad approximates to 6,500.

***Television Mass Production***

"The Marconi-E.M.I. Television Company was formed in 1934 by Electric and Musical Industries, Limited, and ourselves," said Mr. White, "on a fifty-fifty basis for the production and sale of television transmitters and of apparatus accessory to them and, as was to be expected, it has not yet earned any profits in this pioneering activity."

He wound up this part of his report by stating that the sale of television receivers was rising in the London area with such rapidity that radio manufacturers are preparing for mass production in the very near future.

## NAVIGATION MADE TOO EASY

**Limiting Use of Wireless in Ocean Racing Yachts**

IN order not to place an undue handicap upon racing-yacht owners who are unable for financial reasons to install the expensive transmitting equipment which gives their more wealthy opponents an advantage over them, the Royal Ocean Racing Club has issued a special regulation. It prohibits the use of wireless for the transmission of signals or messages in order to obtain assistance in determining position or obtaining weather reports or forecasts.

It would seem that the rule also tends to maintain the standard of skill required in navigation. Although yachts engaged in ocean racing will no longer be allowed to ascertain their position by calling two coast stations and obtaining cross bearings, the use of wireless for the *reception* of direction finding and meteorological signals is unaffected by this new rule.

## BRITISH TELEVISION IN U.S.A.

ENGINEERS are installing Baird big-screen television apparatus in several famous Broadway cinemas in New York. The entire equipment has been shipped from England and will be placed in operation as soon as the installation is completed. The National Broadcasting Company will seize any opportunities to televise the King and Queen during their visit to New York, and hundreds of people will appropriately be able to see Their Majesties by means of British receivers if present plans materialise.

## AMERICAN TELEVISION

**Transmitting Frequencies**

ALTHOUGH nineteen bands for American television stations are provided in the new assignments by the Federal Communications Commission few of them are at present in use or, for that matter, likely to be in the near future.

None of the receivers at present on the American market provides for more than the first five television bands in the accompanying table of allocations; they are those from 44-90 Mc/s. The present position, therefore, regarding the bands between 96 and 108 Mc/s is somewhat indefinite, and there is apprehension as to their possible usefulness for transmitting for home reception. The bands from 156 Mc/s have been chosen as the most suitable for relaying transmissions. One of them, for example, will shortly be used for transmission between New York City and Schenectady, about 120 miles away.

**American Transmitting Frequencies**

| Mc/s | |
|---|---|
| 44-50 | Television |
| 50-56 | Television |
| 56-60 | Amateur |
| 60-66 | Government |
| 66-72 | Television |
| 72-78 | Government |
| 78-84 | Television |
| 84-90 | Television |
| 90-96 | Government |
| 96-102 | Television |
| 102-108 | Television |
| 156-168 | Television Relay |
| 168-180 | Government |
| 180-192 | Television Relay |
| 192-204 | Government |
| 204-216 | Television Relay |
| 216-224 | Government |
| 224-230 | Amateur |
| 230-234 | Government |
| 234-246 | Television Relay |
| 246-258 | Government |
| 258-270 | Television Relay |
| 270-282 | Government |
| 282-294 | Television Relay |

Government assignments are actually slightly narrower to provide guard bands. All television bands accommodate a sound and vision channel.

Some of the receivers provide for reception on two bands only; they are those used by the N.B.C. transmitter, W2XBS, in the Empire State Building, New York City, and the C.B.S. transmitter, W2XAX, a few hundred yards away in the Chrysler Building. The frequencies used by W2XBS are: vision 45.25 Mc/s and sound 49.75 Mc/s. The C.B.S. transmitter, W2XAX, uses 51.25 Mc/s for vision and 55.75 Mc/s for sound.

After a long controversy as to the best method of using the 6-Mc/s bands it has been decided in favour of the normal transmission of sound and the use of a type of semi-single-side-band vision signal. For reasons mainly to do with filtering losses the side-band towards the low-frequency edge of the channel is not attenuated at once, but a relatively sharp cut-off is provided near the edge of the channel, starting about 0.75 Mc/s from the vision carrier.

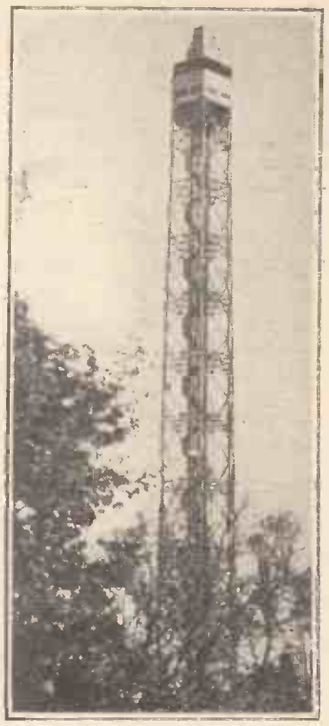

UP ALOFT. The transmitter of the Milan ultra-short-wave station is installed at the top of the Littoria Tower.

## ULTRA-SHORT WAVES IN ITALY

ITALY'S second ultra-short-wave transmitter has recently been installed by the E.I.A.R. in Milan, where use has been made of an existing tower, known as the Littoria Tower, in the North Park. The most interesting feature of the station is that the transmitter has been installed in a building erected at the top of the tower. This, of course, avoids the losses encountered when using a long transmission line from the transmitter to the aerial.

The aerial, which consists of six vertical aluminium tubular di-poles of a quarter wave-length, surmounts the transmitter building. The station, which is at present transmitting the second Italian programme from 4 to 6.30 p.m. G.M.T. on 43.79 Mc/s (6.85 metres) with a power of 400 watts, will ultimately be used for television. It is with this in view that the present experimental transmissions are directed.

## REAL SERVICE

FOLLOWING the offer of the Rola Company (Aust.) Pty. to repair free of charge loud speakers damaged in the bush fires, the Australian journal *Radio and Electrical Retailer* states that many applications for this service have been received. Although some of the speakers received were but tangled wrecks, in every case Rola was able to effect a repair.

Examination showed that the

News of the Week—

heat in some cases was so great that the brass screws were melted into a shapeless mass. To bring this about, approximately 1,500 degrees Fahrenheit would be necessary, and although steel is supposed to lose its magnetism at 1,000 degrees F. all the permanent magnets still retained their properties.

## ARGENTINE'S RADIO PLANS

ELONGATED countries like Norway, Sweden, the Argentine and Chile have tended to build a great number of low-power broadcasting stations in order to cover the country, and to-day the Argentine possesses no fewer than fifty broadcasting stations, about 75 per cent. of which are of purely local importance, half of them being under 10 kW, while 25 per cent. are scarcely 1 kW. Most of them belong to private societies.

Like Sweden, the Argentine, too, is now changing to higher-powered stations. Instead of fifty stations there will probably be thirty-one, six of them being in the capital, Buenos Aires. Four of those in the capital are to have a power of 50 kW and the remaining two 10 kW each. The power of the regional stations will be determined by local conditions and requirements.

Short-wave stations for overseas broadcasting are also envisaged. Revenue would still be sought by sponsored programmes, but all the undertakings would, as far as possible, be united in one national corporation.

## THE SCIENCE MUSEUM

IN the annual report of the Advisory Council of the Science Museum, which has just been issued, mention is made of the interesting acquisition of one of the original manuscripts, dated 1888, of Henrich Hertz, whose work laid the practical foundations of radio communication. This important document, which describes his work on the propagation of electro-magnetic waves, was presented by his widow, Frau Elizabeth Hertz, now resident in England.

The successful television exhibition held in the Museum last year has provided the nucleus of a permanent collection which has been set out in a small gallery adjoining the radio communications section, although it is pointed out that the space is inadequate for this important branch of wireless.

It is recorded that the number of visitors to the Museum in 1938, exclusive of readers in the Science Library, was 1,137,635, which is over 130,000 less than the previous year.

## FLYING DOCTOR RADIO SERVICE

THE excellent work that is being carried on by the Flying Doctor Radio Service under the auspices of the Australian Aerial Medical Services, formerly the Australian Inland Mission, is reported by Mr. E. J. T. Moore, who is the official nominee of the I.R.E. (Australia) on the Board of the A.A.M.S.

The main station of the service, situated at Broken Hill, is linked by wireless to eighteen outposts, at each of which the sets are operated by pedal generators. During a recent period of four weeks the Flying Doctor was actually in the air for fifty hours.

## SET METERS FOR LISTENER RESEARCH

RADIO set meters are being used to gauge "listener reaction" in America, according to Mr. R. J. E. Silvey, head of the B.B.C. Listener Research Section, who has just completed a tour of the United States.

A meter has been devised which, when fixed to a set, registers the hours during which it has been switched on and the frequencies upon which it has operated.

## I.W.T. OFFICERS

THE continued progress of the Institute of Wireless Technology, as manifested by the increase in applications for admission to membership, was stressed at the thirteenth annual general meeting of the Institute held on April 28th, when the following officers were elected for the year 1939-40:

President, Sydney A. Hurren; Hon. Treas., George Lea; Council, Frank Boyce, Horace A. Brooks, B. Tunbridge Hogben, William E. Miller, H. A. G. Howse, Leslie H. Paddle, Gerald P. Sayers and Timothy F. Williams.

It is interesting to note that it will be Mr. Hurren's third year of office as president.

## RADIO-CONTROLLED CARS

TWO cars controlled by wireless crashed head-on at the Cowley Works of Morris Motors last week. The collision was staged before the directors and research engineers to test two methods of construction. The cars were started 150 yards apart, and on the first run missed each other. At the second attempt the desired result was achieved. The cars met at 30 miles an hour. One of them was wrecked, but the other, a new model, sustained only superficial damage.

## *FROM ALL QUARTERS*

### Civil Defence Research

DR. E. V. APPLETON, the well-known physicist, who is secretary of the Department of Scientific and Industrial Research, has been appointed chairman of a committee of eminent scientists appointed by the British Government to supervise researches into civil defence measures.

### New T.C.C. Director

MR. E. W. DOREY, A.M.I.E.E., who has been associated with the Telegraph Condenser Company for eighteen years, has been appointed a director of the firm. He will be in charge of the general sales organisation.

### Television Lectures

A COURSE of four lectures on television is to be given by Mr. H. J. Barton-Chapple at the Polytechnic, 309, Regent Street, London, W.1, on Thursdays from 7.30-9 p.m., commencing on June 8th. The fee for the course is 6s.

### The Four R's

"CLEVELAND, Ohio, has a director of education who pins his faith to the 'Four Rs' as the foundation of learning, which he bases on Readin', Ritin', 'Rithmetic and Radio."—*The Journal of Education.*

### Floating Signal School

H.M.S. *Chrysanthemum*, the convoy sloop which is now permanently berthed off the Victoria Embankment, London, ahead of H.M.S. *President*, will house the signal school of the R.N.V.R.

### Radio's Part in Jutland Battle

How radio helped both sides in the battle of Jutland will be brought out in a new naval play, "Jutland," by Captain Taprell Dorling, D.S.O., R.N. ("Taffrail"), to be broadcast on the National wavelengths on June 2nd. Although the radio equipments of both fleets were remarkably efficient, "Jutland" will show how slender was the amount of wireless information received from patrolling aircraft. On the other hand, intercommunication between ships reached a high standard.

### Sir Louis Sterling

THE directors of Electric and Musical Industries announce that they have with regret accepted Sir Louis Sterling's resignation from the position of Managing Director which he has held for the past seven and a half years. The Company was formed in 1931 to amalgamate the Gramophone Company (H.M.V.) and the Columbia Graphophone Company.

### Interference-free Electrical Apparatus

BELLING AND LEE have been accepted by the British Standards Institution as an approved testing authority under the Radio Interference-Free marking scheme which was outlined in *The Wireless World* of April 13th.

### Licences Fall

A DECREASE of 5,259 in the number of wireless licence holders during last month is indicated by the total number in force at the end of April which was approximately 8,962,850. This is believed to be the first case of a decrease in a month's figures since 1927. The past year's increase was 358,450.

### "Camera caddies" at Golf Match

PLANS are nearing completion for the B.B.C. to televise a golf match from Combe Hill on June 1st. One mobile unit will be used, and the three cameras will be strategically placed to cover at least eight or nine holes. Between shots an army of "camera caddies" will heave the co-axial cable to different parts of the course. The Emitron cameras can now operate at distances up to a thousand feet from the scanning van.

### Portable Transmitter

LISTENERS with a critical ear may be able to gauge the changes in signal strength as Henry Longhurst, broadcasting his description of the Amateur Golf Championship at Hoylake, Liverpool, on May 26th, traverses the greens and bunkers with the new B.B.C. knapsack transmitter.

### News in Afrikaans

A TRANSLATION in Afrikaans of the weekly B.B.C. news for Empire listeners is now broadcast on Sundays in the short-wave programme at 7.30 p.m., B.S.T. The bulletin in English directed to South Africa is normally radiated at 7 p.m., B.S.T.

### B.B.C. Audiometer Tests

THE B.B.C. is now using an audiometer in St. George's Hall to gauge the strength of applause for individual items. The first application of this almost infallible device is in connection with the "I Want to be an Actor" series. The audiometer is operated for fifteen seconds at the conclusion of each turn and the total volume of sound recorded affords a fair basis of comparison.

### Italy After Montreux

THE E.I.A.R. seems quite satisfied with the Italian wavelengths allocated at Montreux. At present she operates in the medium band twenty-four stations on fourteen frequencies, four of which are exclusive. Next spring, when the plan becomes effective, she will be operating thirty-six stations on fifteen medium wavelengths, six being exclusive. The additional stations are all low-powered relay transmitters.

### Touring Guide

A PROFUSELY illustrated 48-page touring guide is included free with each issue of the special touring number of our sister journal, *The Motor Cycle*, on sale to-day, May 18th. No fewer than thirty-three specially designed maps printed in two colours are contained in this guide, which has been specially prepared to introduce tourists to the most beautiful parts of Great Britain.

### Learners

FOR those of our readers who are contemplating learning to drive a car we would recommend the third edition of "*The Autocar* Guide for the 'L' Driver," which explains in simple language what the beginner must be able to do in order to pass the driving test. The booklet is obtainable from booksellers price 1s., or from the publishers, Dorset House, Stamford Street, London, S.E.1, price 1s. 2d. post free.

# Frequency Modulation in America

## ANTI-NOISE BROADCASTING UNDER TEST

**(Concluded from last week's issue)**

*IN last week's issue the results of receiving tests made on the experimental American frequency-modulated broadcast transmissions were described. This article deals with the special type of receiver necessary, and also discusses such matters as transmitter efficiency and details of modulation.*

**BY OUR NEW YORK CORRESPONDENT**

THOUGH greatly decreased in size and number of adjustments, the set at present used for receiving frequency-modulated transmissions is fundamentally like its 16-foot ancestor. It remains a superheterodyne. A high-gain tuned radio-frequency stage is followed by the usual frequency-changer, an IF system of very high gain, a second detector and an audio system. However, one of the later IF stages is a "limiter" stage, prevented from responding beyond a certain amplitude, and the detector is preceded by a circuit designed to convert frequency swings into amplitude swings. In its simplest form the limiter IF stage is merely a pentode with reduced DC voltages, so chosen that its maximum performance is reached with 3 to 10 microvolts of carrier applied to the input circuit of the set. A signal increase of 10,000/1 then produces little increase of voltage at the succeeding valves, though there still remains the possibility of cross-modulating the incoming signal for extreme overload. The 3- to 4-stage IF systems thus made possible accounts for the ability of the receiver to utilise weak signals.

The detector is usually a balanced pair of diodes fed in such a way that the carrier affects them equally, but changes in frequency disturb the balance by an amount proportional to the extent of the frequency swing. In the original Armstrong receiver this was done by feeding each diode from a series-resonant tuned circuit in series with a resistor which preserved linearity. The two circuits were resonant on opposite sides of the carrier frequency and spaced widely enough to bracket the maximum swing. In the General Electric M-125 receiver there is used instead a circuit resembling the "discriminator" circuit used by the same firm in automatic frequency control systems. Here the two diodes are fed from the ends of the secondary of a 3-megacycle IF transformer, this secondary being coupled to its primary both magnetically (balanced) and by capacity (connected to the centre-tap of the secondary). At resonance the system is balanced and the two diodes receive the same voltage, though in opposite phase. Any departure from resonance produces phase shifts which upset the balance and feed unequal voltages to the diodes, whose rectified output feeds the audio system. The merit claimed for this system is greater sensitivity.

The audio system, loud speaker and cabinet demand the treatment normal to any true high-fidelity receiver. In the case of the Armstrong receiver there is used an audio system almost perfectly flat to 16,000 cycles. Degenerative feed-back and ballasting are used to remove various undesirable effects. The output tubes can deliver an undistorted output of 25 watts to a pair of speakers in a columnar baffle designed to load the "woofer" or low-pitch speaker. In the G.E. receiver audio degeneration (overall) is used with R. & C. ballasting at suitable points in the amplifier, which eventually feeds a maximum undistorted output of 15 watts to a 10-in. parabolic-diaphragm speaker with an exceptionally massive baffle-cabinet well braced and vented. The system is down only 5 db. at 15,000 cycles and has negligible harmonic distortion.

### AVC and "Limitation"

Since the detector works at essentially constant level it cannot become a source of AVC voltage. A good limiter may compress amplitudes by as much as 100 db. Accordingly, AVC is derived from the limiter tube, but it is not certain that this feature will be retained.

According to the General Electric Company: "The cost of a frequency modulation receiver as compared to an amplitude receiver of equal quality is probably about

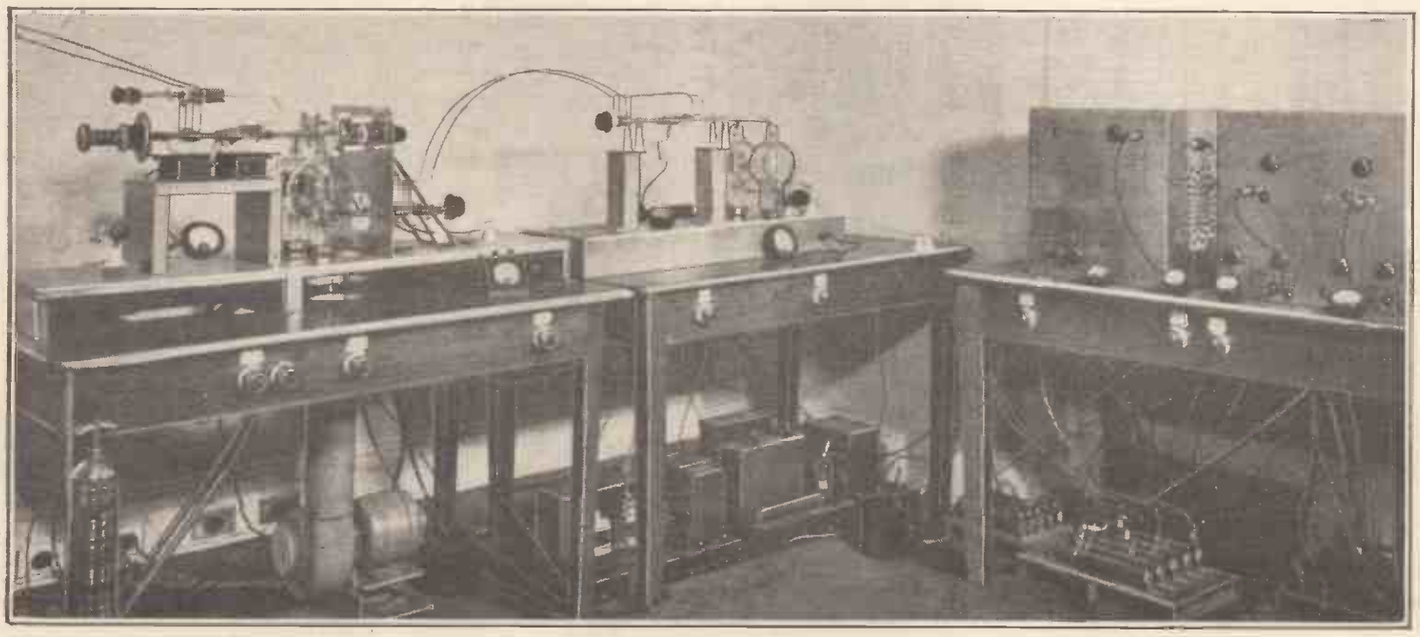

The power amplifying stages of the Yonkers station. On the right are the earlier amplifying stages, in the centre the push-pull driver and, on the extreme left, the push-pull output stage, which delivers 600 watts at 110Mc/s. The output valves are air-cooled by a blower under the bench.

**Frequency Modulation in America—**

the same. In general, however, the cost of the frequency-modulation receiver will be higher since the fidelity will ordinarily greatly exceed that of the amplitude-modulation receiver, requiring additional expense in the audio and reproducing system."

For equal power and frequency the cost of the frequency-modulated transmitter may not differ greatly from that of an amplitude-modulated transmitter. The ability to operate at steady load effects savings sufficient to pay for the added low-power stages.

It has already been stated that the valves operate more efficiently *for the same frequency*. Thus the W2XMN transmitter, still working on 7 metres, might be modified, as in the following table, using the same final valves as at present.

| Modulation method | Valve capacity | 40-Mc/s carrier output | Carrier possible at low frequency |
|---|---|---|---|
| | (kW.) | (kW.) | (kW.) |
| Low level freq. mod. | 2 × 50 | 40 | 100 |
| Low level amp. mod. and Class B final ... | 2 × 50 | 10 | 25 |
| High level amp. mod. | 2 × 50 plus 2 × 50 for modulators. | 40 | 100 |

Note.—This theoretical tabulation is not altogether fair to the Armstrong system in practice. Whereas W2XMN has met with no service failures during 5-hour runs at an output of 40 kilowatts, other transmitters using output valves of the same type have encountered difficulty in maintaining very much smaller carrier powers at about the same frequency with amplitude modulation.

Both the second and third systems are less efficient in the use of power, and produce unsteady loads on the power line. The second system produces less output. The third system requires more large valves.

Simply as a matter of review, the Armstrong method of frequency modulation is that of splitting a low-frequency carrier (say 200 kc/s) into two streams so that one may continue as an unmodified carrier while the other stream is passed through a balanced modulator and inductive amplifier before the two channels are recombined in a resistive load. The balanced modulator as usual delivers only side-frequencies, having balanced out the original carrier. The inductive amplifier produces phase shifts in the side-frequencies, proportional to the amplitude of modulation, and these phase shifts are subsequently much increased by passing the modulated carrier through many frequency multiplications. Various devices for preserving linearity need not here be mentioned. Some intentional unlinearity is allowed to remain for the purpose of securing exaggerated high-pitch modulation and thereby better over-riding of residual noise. This is compensated at the receiver.

### Maximum Permissible Swings

Over-modulation does not have as definite a meaning as in amplitude modulation, but for optimum performance the deviation or swing used should be that for which both sender and receiver were designed. In any case, the swing should be materially wider than the audio channel, i.e., a 15,000-cycle audio channel requires a swing of 4 to 10 times 15,000 cycles on either side of the carrier frequency.

Various investigators agree that for fluctuation or "ground" noise the improvement in signal-noise ratio is

$$1.7\frac{\text{frequency deviation}}{\text{audio band width}},$$

and also that for "impulse" noises, such as ignition, most static and many power-line noises, the improvement is

$$2\frac{\text{frequency deviation}}{\text{audio band width}}.$$

However, there is less perfect agreement as to the range in which these effects take place, that is, the ratio of carrier-to-noise required before the action begins. From what has previously been said it is apparent that the threshold, if any, is low. There is at least agreement that noise reduction has definitely set in when the limiter valve has "taken hold," and this takes place in various of the present receivers with carrier input (to the receiver) of from 2 to 10 microvolts. Any given value of field strength is more easily attained with frequency modulation, since peak power is used constantly.

The Armstrong receiver derives an advantage from another effect. The accompanying oscillogram (a) is that of an atmospheric crash in the form it had assumed upon reaching the loud speaker or output transformer of a conventional General Electric K-80 receiver. The oscillogram (b) is produced in the same receiver by discharging a condenser into one of the tuned circuits.

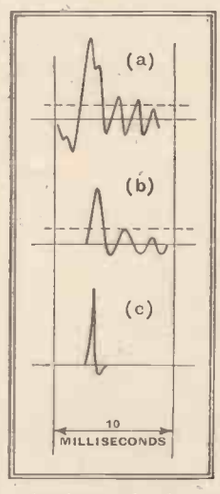


Oscillograms of impulse interference: (a) and (b) are to the same scale.

The resemblance clearly shows that in both cases the original disturbance shocked the receiver-tuned circuits into oscillation. Oscillogram (c) shows the waveform of an atmospheric crash about two minutes later with the oscilloscope connected across an approximately critical series resistor in the aerial, the receiver being removed. All three oscillograms are typical for this particular thunderstorm.

The dotted lines represent the approximate level of the amplitude-modulation peaks due to voice modulation on a carrier which, prior to modulation, delivered about 1,600 microvolts to the receiver input. The waveform (c) can be eliminated more completely if attacked by an amplitude limiter before its form factor becomes altered by conversion into an oscillation such as (b) or (a). In the normal amplitude-modulation receiver this is a difficult condition because of the "fly-wheel" effect of the high-Q circuits essential to normal selectivity with good gain. In a broad-band system this difficulty is materially lessened and (for any sort of modulation) the limiter becomes more effective. However, it is especially so for amplitude modulation, since there is no possibility of peak-cutting distortion, and therefore the gain ahead of the limiter is normally kept high enough to ensure limiter action.

If station W2XMN is taken as typical, the off-hand impression is that the channel width required for Armstrong modulation is some 20 times that occupied by an amplitude-modulated station.

### Possibilities of Sharing Channels

This is a great mistake. It is to be remembered that W2XMN and W2XCR both transmit high-fidelity signals. The comparable amplitude-modulated transmitter would require a channel 40 kilocycles wide, in which it would place two side-bands about 16 kc/s wide, leaving a 4-kc/s guard-band at either edge. Thus for the same fidelity (noise not considered) the amplitude-modulated station requires 1/5th the band width, not 1/20th. Nor could amplitude-modulated stations be spaced more closely without sacrifice of fidelity—one need only listen to the nearest good receiver to discover that. On the other hand, for frequency modulation not only is closer spacing permissible, but two stations can operate on the same frequency with *much less* "hash area" than is found for amplitude modulation.

These somewhat surprising statements have both theoretical and experimental proof. First as to the requisite spacing of two FM stations *not* working on the same frequency. Referring back to the early public discussions by Major Armstrong, it will be recalled that he pointed out an advantage of wide-band or large-deviation frequency-modulation due to the fact that the beat-frequencies generated in conjunction with noise-frequencies remote from the carrier position were either self-cancelling in the detector or inherently inaudible, hence that a wide swing permitted most of the operation to take place in regions incapable of contributing noise (other than high level impulses which can still contribute to some extent by cross-modulation), thus doubling the band width quadruples signal-over-noise in terms of power. Now if two FM stations delivering comparable signal strength are centred with a supersonic separation between their carrier positions, many of the resultant beat-frequencies are eliminated by approximately the process above referred to, while others are eliminated by the effect mentioned in the next paragraph.

Where two FM stations are operated on the *same* channel there ensues an effect which comes as a pleasant surprise. It is this: if one signal is of more than double the field strength of the other—that is, 6 db. superior to it—*that signal takes possession and the other disappears*. Messrs. W. E. Fyler and J. A. Worcester reported an experiment done with a 50-watt trans-

**Frequency Modulation in America—**

mitter at the General Electric plant in Schenectady, New York, and a 150-watt transmitter at Albany, 15 miles away over

The "turnstile" aerial at W2XCR, formerly W2AG, at Yonkers, N.Y. It comprises 14 sections and is supported by a 100ft. tower.

open country. Both transmitters operated on 41-Mc/s and could be modulated by either method.

Tests were then made with a portable receiver at various points along the road between the two stations. With amplitude modulation there appeared the familiar effect that the station spoils far more territory than it uses. Of the 15 miles of road 13 were occupied by a dismal garble. With Armstrong modulation the effect was altogether different; for nearly 13 of the 15 miles there was no interference at all. The remaining 2 miles showed a mixture of the two stations, but not in the usual way. As the receiving car proceeded the stations popped in by turns as one or other attained the requisite 6 db. superiority due to the standing wave pattern inevitable at 40 Mc/s. By stopping the car it was possible to find a cross-over point so sharp that one station or the other could be selected by pushing the aerial over an inch.

The difference lies in the fact that for conventional amplitude modulation one station must attain a superiority of 30 to 40 db. (say 250 times) before it can swamp the other. In the large area where garbling exists it is difficult for a listener to escape the effect, since an aerial capable of providing so large a directional discrimination is too complex for household use—and at wavelengths of more than 10 metres becomes very costly. On the other hand, the smaller area of interference of the FM system is due to level differences easily counteracted by an aerial with one director or reflector. If one were content simply to listen to one of the two stations no directionality at all would be needed even in this area except for the fact that the standing-wave pattern moved from time to time, giving an effect like that of the aerial movement above described. For a considerable distance on either side of this area the dipole plus director or reflector (or at the most both) suffices to select either station at will. At points nearer to one station or the other one is merely in the normal state of the present-day listener, but with fading reduced in an exceptionally good degree.

At the April 10th meeting of the Washington Section of the Institute of Radio Engineers, Mr. I. R. Weir, of the General Electric Company, reported on a further test of the same kind, made by observers in two cars driving from an experimental 200-watt Armstrong transmitter at Albany, N.Y., towards the 40-kilowatt W2XMN transmitter 120 miles away. The transmitters were on the same frequency. From Albany to Hudson, N.Y. (30 miles), the Albany 200-watt sender blocked off W2XMN, which remained unheard up to that point. At Hudson, which is well into the hills, W2XMN began to break through, being heard on the south side of each hill, while the north side still produced the G.E. 200-watt transmitter. The effect was similar to that in the Schenectady-Albany test previously cited, that is, the stations alternately took possession of the receiver. A few miles farther south W2XMN "took over" permanently and Albany's signal was heard no more. It is to be noticed that the cross-over region seems to be too close to W2XMN, but this is accounted for by massive highlands to the south towards W2XMN.

---

**Test Report**

# INVICTA NEW JUNIOR PORTABLE

## Four-valve Superheterodyne Battery Receiver

## Price £7 15s. (including batteries)

ALTHOUGH taking up no more space than the early type of battery portable with a straight circuit, this receiver has a full superheterodyne circuit which gives considerably greater range and selectivity for an expenditure of only a few more milliamps of HT current.

The provision of a superheterodyne circuit carries with it the advantage of being able to employ automatic volume control, which is of great value in a portable where the directional properties of the frame aerials may produce considerable variations of the input voltage. With automatic volume control one need not be so careful over the placing of the set, but at the same time the advantages of a frame aerial from the point of view of cutting out interference are not lost. If anything, the "minimum" is sharpened by the action of AVC.

***Circuit.***—The input from the frame aerials is taken to the grid of an octode frequency changer. The next stage is a variable mu pentode operating at 465 kc/s. The coupling transformers have silvered mica fixed condensers and are adjusted at the works by moving the position of the iron dust core. The double-

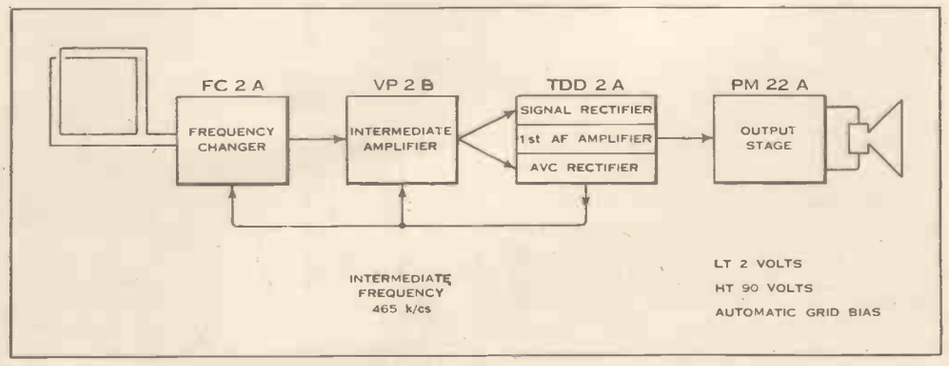


Schematic circuit diagram of the Invicta New Junior portable.

**Invicta New Junior Portable—**

diode-triode valve which follows is connected in the usual way with one diode for signal rectification and the other for AVC. The bias derived from the latter diode is applied to both the IF and frequency-changer valves. The volume control takes the form of a potentiometer input to the triode amplifying portion of the second-detector stage, which is transformer coupled to the pentode output valve. A resistance in the negative HT lead provides bias for the output stage, and the delay voltage for AVC.

***Performance.***—The measured LT current was 0.5 amp., and the total HT current 14 mA from the 90-volt battery.

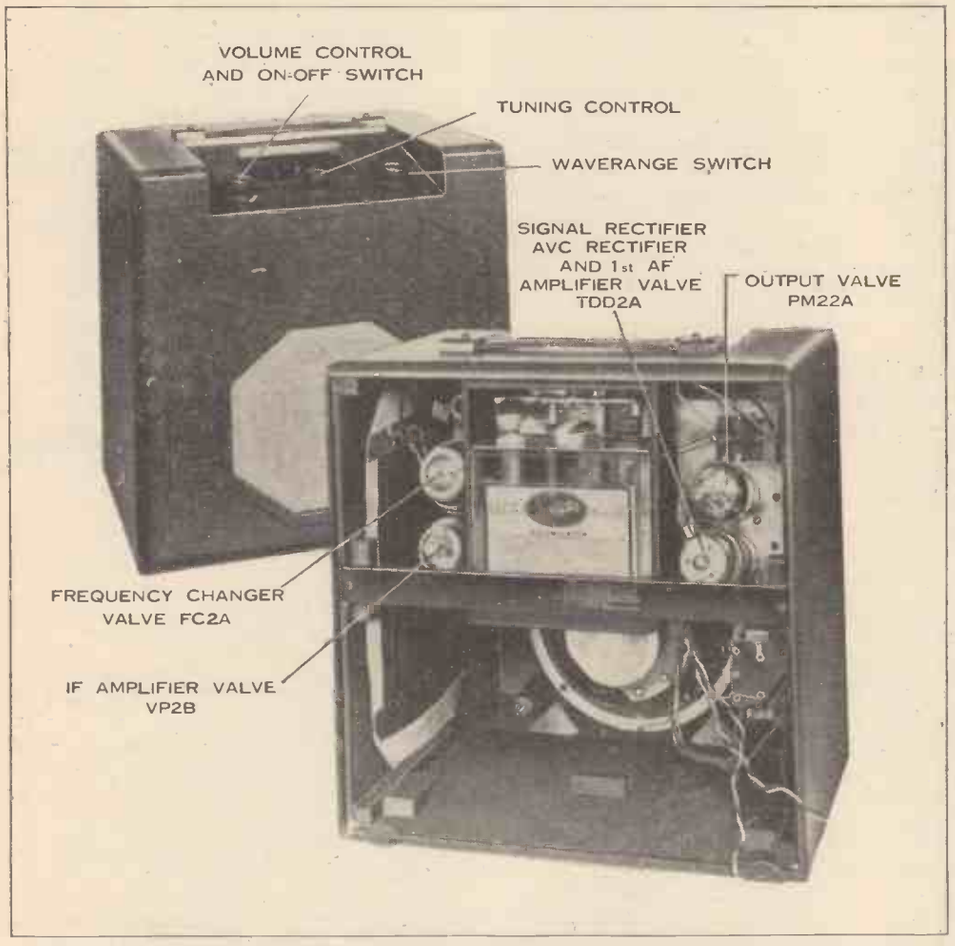


Although the chassis houses a superheterodyne circuit, it is remarkably compact and leaves plenty of room for batteries.

Although this is appreciably greater than the average HT consumption for a simple straight set, there can be no doubt as to the additional return in the matter of performance.

The number of stations received on both the medium- and long-wave bands is comparable with that to which most people are accustomed with their four-valve superheterodyne table models, and the selectivity is also practically the same. In other words, the London Regional transmitter at a distance of fifteen miles does not spread more than 1½ channels on either side of its normal setting, and the Deutschlandsender could, under favourable conditions, be received clear of Droitwich and Radio-Paris by making use of the directional properties of the frame.

The most notable feature is the ease with which these results are obtained. Whereas with a straight receiver a very good performance can be obtained by skilful use of the reaction control, in this set the work is all done by the circuit, and the volume control is the tap which turns on the finished results.

The Celestion loud speaker, which, incidentally, has a really sensible output transformer as far as size is concerned, gives efficient conversion of the output available from the last valve. Provided the volume control is not turned up too far on the local station, the quality is perfectly clear and is not marred by any attempt to produce an artificial bass resonance. On all stations other than the local the volume control may be disregarded, as the range of AVC is sufficient to prevent overloading.

***Constructional Features.***—Separate frame aerials are mounted on opposite sides of the cabinet. They are of interesting design, and the turns are self-supporting. It would appear that the coils are first of all wound as a short cylindrical single layer, and then folded over at the corners to produce a flat edgewise coil.

By careful disposition of the components it has been found possible to dispense with screening for the IF transformers, the economy in space thus effected being one of the reasons for the compactness of the chassis. As a result there is ample space for batteries, and the LT battery is of 18 ampere hours capacity. This is of the unspillable type, but it should be examined after coming back from charging to see that there is no acid on the outside, as it is rather near to the tuning condenser vanes and the oscillator coil can.

The collapsible carrying handle is well placed from the point of view of balance of weight, and the cabinet is fitted with a turntable. The total weight is 21¼ lbs.

***Summary.***—The makers have achieved a very efficient performance with simplicity, and hence potential reliability in the design and layout of the chassis. In conclusion, we would commend the circuit diagram and list of component values which are pasted on the inside of the back panel of the set for the use of servicemen.

| *WAVERANGES* | |
|---|---|
| *Medium* - - | *200—550 metres* |
| *Long* - - | *800—2,000 metres* |

## HENRY FARRAD'S SOLUTION

(See page 462)

TONY has overlooked the fact that a lamp run on a 50 c/s supply flickers every *half-cycle*, that is to say, 100 times per second. Therefore, he should have put on 77 stripes. The time taken by the turntable to rotate through a distance equal to that from one stripe to the next would then be a hundredth of a second when running at the correct speed, and the stripes would all have shifted exactly one place round when next most brightly illuminated and hence would apparently stand still, according to the principle of stroboscope action.

## The Wireless Industry

SOLUTIONS for silvering mica and ceramic dielectrics are the subject of a booklet entitled "Liquid Silver" issued by Melton Metallurgical Laboratories, Seymour Road, Slough, Bucks.

A new edition of the leaflet dealing with rotary converters for radio, television and PA equipment has been issued by the Electro Dynamic Construction Co., Ltd., St. Mary Cray, Kent. It includes a three-page list of prices of complete power supply units for all the leading makes of receivers.

Mack Radio Stores, Elphinstone Street, Camp, Karachi, India, would like to receive catalogues and price lists from manufacturers of wireless components.

The suppression of interference from DC and other commutating machines at the source is dealt with in Rado Interference Bulletin No. 60 issued by Belling and Lee, Ltd., Cambridge Arterial Road, Enfield, Middlesex.

Mr. W. E. Wilkins, B.Sc., A.M.I.E.E., the Northern representative for Westinghouse metal rectifiers, has changed his address to Agden Lane Farm, Agden, Lymm, Warrington.

# Television Topics

## SAW-TOOTH CURRENT WAVES

MAGNETIC deflection of the electron beam necessitates a saw-tooth current through the deflecting coil. Such current may be generated by connecting the coil to a source of constant potential. The resulting current rises slowly for the scanning stroke. If the potential supply is disconnected so that the current may cease for the flyback, the coil begins to oscillate freely (with the circuit capacity or the self-capacity of the coil). If this operation is interrupted after the completion of one half-oscillation and the coil is connected again to the potential supply, the current rises again in a linear way. The free half-oscillation, therefore, represents the short saw-tooth stroke.

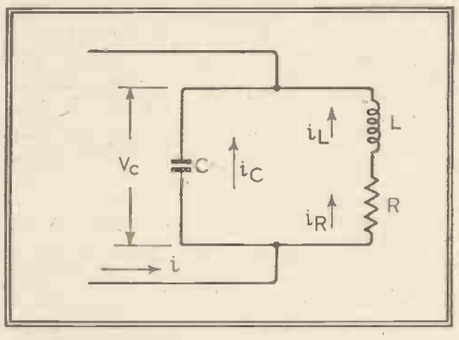


Fig. 1.—This diagram shows the basic circuit of the deflecting coil; R represents the coil resistance and C the circuit capacity.

With such a generator of saw-tooth currents it is important that at the moment when the half-oscillation is released by the linear rise, the exact conditions of connection are present (equal absolute value of the current and equal first-time differential quotient). If this is not the case, balancing oscillations occur. These must be avoided because they cause interference on the picture.

In deflection circuits for television purposes the winding capacity of the coils is so small that for the frequencies in question the damping given by the ratio L/C of the coil practically suppresses the balancing operations. If a coil of this kind has to be fed through a cable with the saw-tooth current, it is possible that the additional output capacity of the cable may alter the ratio L/C in such a way that the coil is only damped comparatively slightly and that the desired current curve is falsified by balancing operations. Additional damping of the coil is not always possible in view of the current stroke to be applied, and, on the other hand, an extension of the short backward oscillations is also rarely permissible.

In Fig. 1 is shown the coil L in series with its ohmic resistance R, and parallel to both is the distributed winding and lead capacity C. Through the coil L a saw-tooth-shaped current ($i_L$) has to flow, and the question is what current $i$ has to be supplied to the arrangement so that no balancing oscillations are possible.

Fig. 2(a) shows the curve of the required coil current. The linear current rise passes the value zero at the moment of time $t_0$. At the moment of time $t_1$ the linear curve is released by the sine half-oscillation. (Both operations follow each other with equal $di/dt$.) The maximum value is not reached at $t_1$, but a little later at $t_2$. In accordance with the fact that the coil oscillations are damped, the negative maximum amplitude is drawn smaller than the positive amplitude. The negative maximum value is reached at $t_4$, and at $t_5$ the linear rise starts again, which passes again the zero axis at $t_6$.

The potential existing at the coil L may be easily constructed from this current curve; it is the differentiated curve (Fig. 2(b)). The potential Vc of the condenser C is the sum of the potentials at the coil L and at the resistance R. The latter is proportional to the curve (a), and for the sum of the coil potential and resistance potential shown in Fig. 2(c) the proportionality factor R is taken as 1. From the curve of the potential present at the condenser the current causing this potential curve can be obtained by another differentiation (Fig. 2(d)). It is to be observed that in (c) the negative maximum value of the condenser potential is not reached at $t_3$, but only a little later. Accordingly, in (d) the current value zero is passed after $t_3$. The curve of the condenser current $i_c$ is exactly equal, but in a reflected sense, to the first postulated coil current, which is

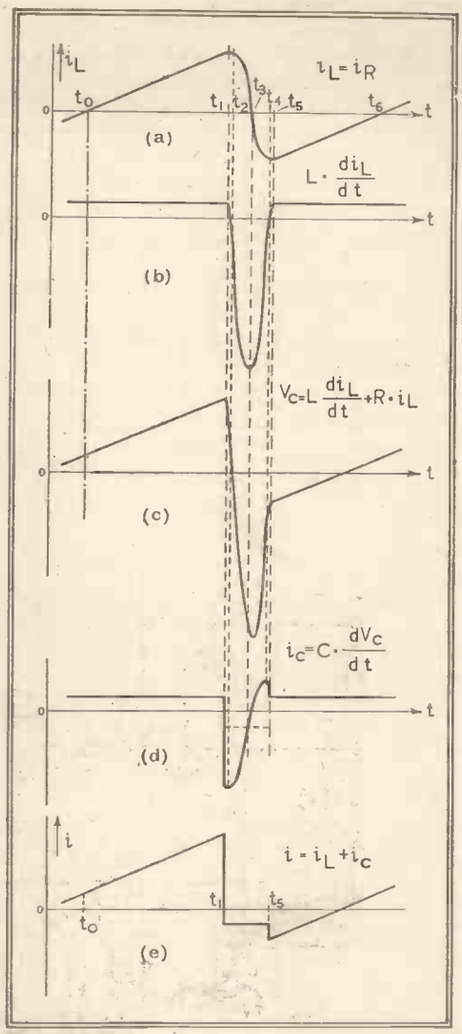


Fig. 2.—The method of determining the relation between the coil and input currents is shown here. (a) represents the desired coil current, (b) the voltage across the coil, and (c) the voltage across the condenser; (d) shows the condenser current and (e) the line current.

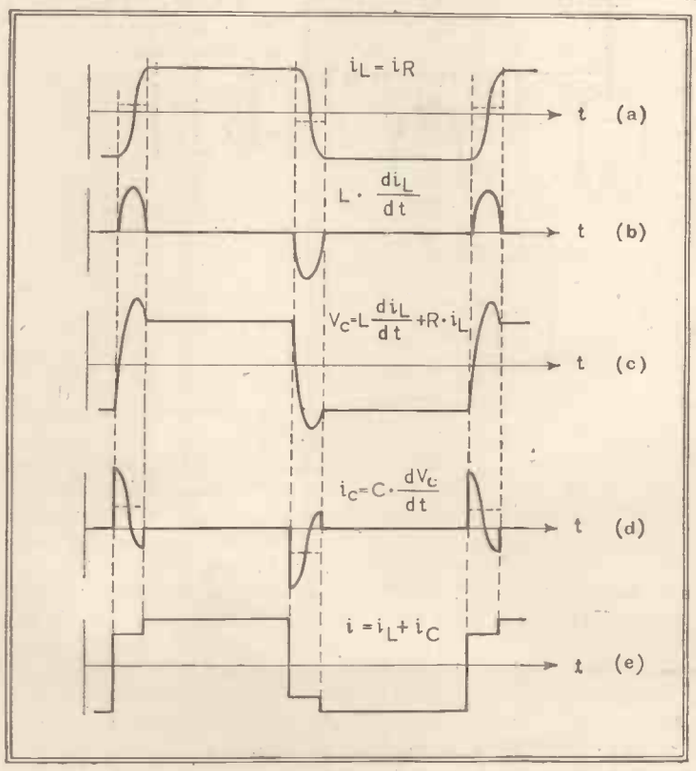


Fig. 3.—These diagrams are similar to those of Fig. 2, but for the case where a rectangular coil current is desired.

**Television Topics—**

obvious because the current always swings backwards and forwards between L and C. This equality does not, however, hold good for the zero axis shown in Fig. 2(d), but for the dash-dot axis for which the current value zero is passed at $t_3$. The dash-dot axis follows from the necessity for the areas enclosed by the current curve to have the same proportions, determined by the damping, as in the curve of Fig. 2(a). If the currents of Figs. 2(a) and (d) are added together, we get the current $i$ which is required by the whole arrangement. This current is shown in Fig. 2(e) and is of step shape.

This method of determining the current is not limited to saw-tooth currents. As a further example may be considered the case where a rectangular current has to flow through the coil L as in Fig. 3(a). This leads in a similar way to the curves of Fig. 3(a-e). Here, again, a step-shaped current $i$ is produced which causes the coil to oscillate in the desired way without balancing operations. As the coil oscillations are damped they take place in Fig. 3(a), not around the zero axis of the current, but around the parts of the axis which are shown in dashed lines. In accordance with the damping, the curve in Fig. 3(b) is somewhat asymmetrical. In spite of this, the condenser current (Fig. 3(d)) has a half-oscillation which is the same but in a reflected sense as the coil current.

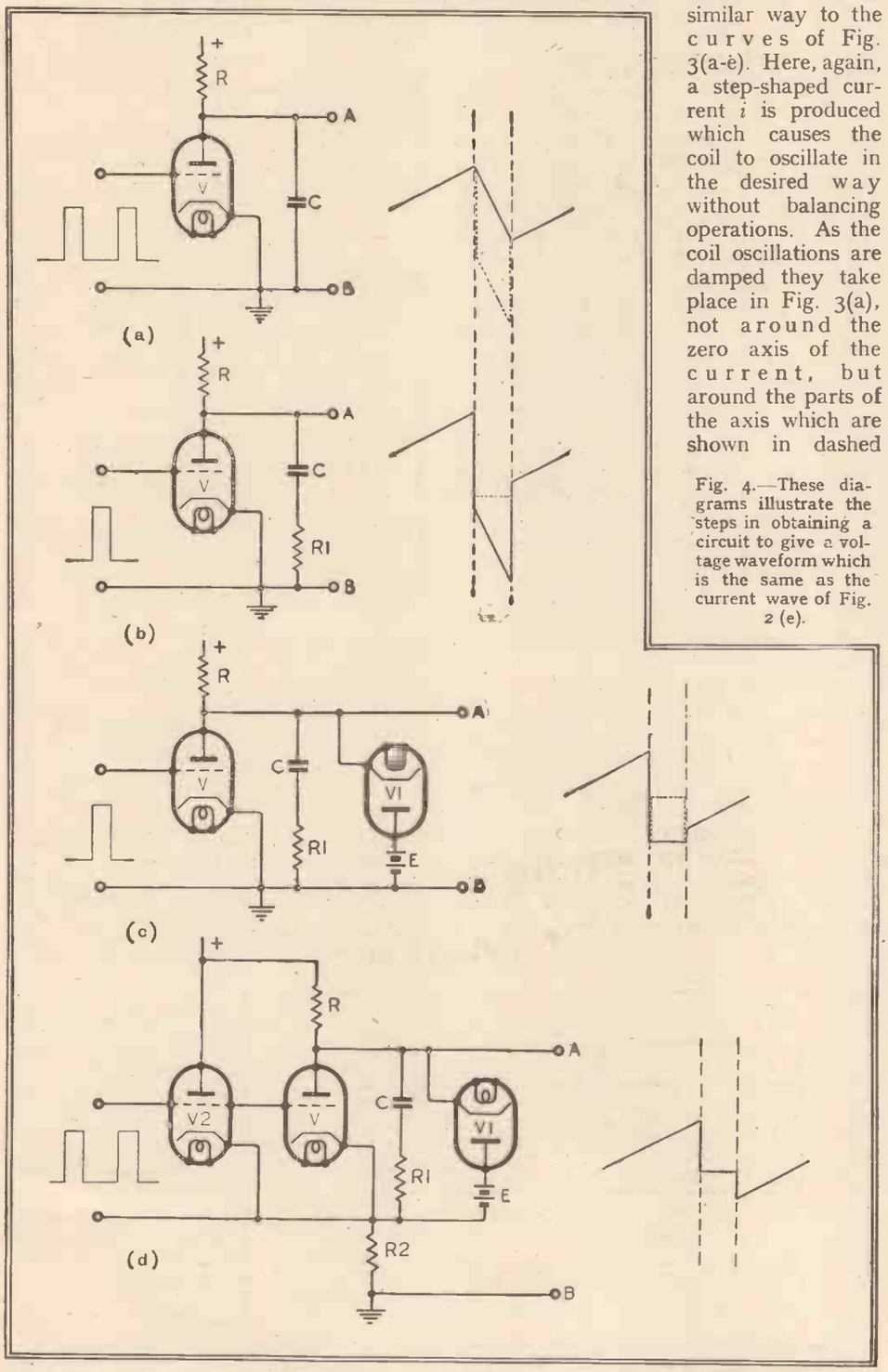


Fig. 4.—These diagrams illustrate the steps in obtaining a circuit to give a voltage waveform which is the same as the current wave of Fig. 2 (e).

The generation of the necessary current curves may readily be carried out, and the necessary steps are shown in Fig. 4 for the case of a saw-tooth coil current. At (a) a condenser C is charged from the HT supply of the discharge valve V through a resistance R, and is discharged through the valve V, which is controlled by positive impulses on the grid. A saw-tooth potential is developed across C.

If a resistance R1 (b) is connected in series with the condenser a potential is present at the terminals A and B, which consists of a saw-tooth and a superimposed impulse as shown on the right. If a rectifier V1 with a potential supply E is connected in parallel with the condenser C and the resistance R1(c), the result is that the impulse is cut off horizontally parallel to the $t$ axis. If, during the impulse, a positive impulse is added to the existing impulse we obtain the required step-shaped potential curve which, if used as a control potential for a pentode, produces the desired step-shaped current curve. In Fig. 4(d) the circuit of Fig. 4(c) is raised by the potential drop across a resistance R2 connected in the cathode lead of a discharge valve V2, which is controlled by positive impulses in a similar way to the valve V. In Fig. 4(a-d) (right-hand side) the potential curve existing between the terminals A and B is shown, and the potential which is obtained at the next stage is indicated by dotted lines. This method of determining the circuit characteristics necessary has been developed by the Telefunken Co.

## In Next Week's Issue

**CATHODE - RAY OSCILLOSCOPE.** How to make a simple general-purpose oscilloscope for operation with a 2½-in. tube.

**AERIAL MASTS.** Problems of mechanical design; choice of types; strength and other properties of materials.

**DC MAINS SUPER.** Constructional details.

# New Apparatus

### "OMCO" DUMMY ANTENNA

THE adjustment of amateur transmitters is generally carried out on an artificial load resistance consisting of a standard tungsten- or carbon-filament lamp. The resistance is usually doubtful and the impedance at RF unknown. Such a simple device is therefore unsuitable where measure-

"Omco" type D.100 dummy antenna resistance for powers up to 100 watts.

ments of output power and efficiency are required.

To meet this difficulty the "Omco" dummy antenna has been developed. The resistance element is an opposed two-layer coil of fine wire widely spaced on a mica former and enclosed in a gas-filled bulb mounted on a 4-prong base which fits the standard American-type valve holder.

By a careful choice of material for the wire and adjustment of the residual inductance in relation to the distributed capacity it has been found possible to render the resistance independent of both frequency and load up to 15 Mc/s and 100 watts. In practice it may be used without appreciable error up to at least 22 Mc/s. Two types are available, with resistances of 73 and 600 ohms. The former has an inductance of 0.33$\mu$H and the latter of 1.1$\mu$H. The distributed capacity is the same in both types, namely, 5 micro-mfd.

The price is £1 and retail supplies are obtainable from Webb's Radio and G5NI (Birmingham), Ltd. Trade enquiries should go to Electronic Engineering Services, Ltd., Swakeleys Road, Uxbridge, Middx.

Varley mains transformer and choke for the Three Band AC Super.

## RECENT VARLEY RRODUCTS

THREE components of interest to readers of this journal have recently been submitted by Varley. The first is a new beat-frequency coil assembly designed for receivers of the communication type. It is made in two values to beat with IF stages working at 465 kc/s or 1,600 kc/s, and is intended for use in an electron-coupled oscillator with a screen-grid or RF pentode valve.

Coarse adjustment of frequency is effected by a bottom-capacity trimmer screw, and fine adjustment by an inductance trimmer passing through the top of the can. A range of 10 kc/s is given for 180-degree rotation of the latter control, and a shaft adaptor and mounting bracket for front of panel control is available, price 6d. The 465 kc/s coil costs 6s. 6d., and the 1,600 kc/s coil 5s. 6d.

The other two components have been produced for the power supply circuit of *The Wireless World* Three Band AC Super (December 22nd and 29th, 1938). The mains transformer (EP45), which is in

The new Varley beat-frequency oscillator coil is fitted with a fine adjustment which is adaptable for front-panel control.

skeleton form with leads for direct connection in the circuit, has an electrostatic shield between primary and secondary and gives 90 mA at 300-0-300 volts, 2 amps. at 4 volts, and 3 amps. at 6.3 volts. The primary is tapped 200, 220, and 240+10 volts.

The smoothing choke (DP56) is also fitted with loose connecting leads, and gives an inductance of 30 henrys at 90 mA with a DC resistance of 800 ohms. The price of the choke is 12s., and of the mains transformer 22s. 6d.

## Marconi and Osram KT44

A NEW valve intended primarily for use in magnetic time-base circuits has been released. It is the Marconi and Osram KT44, and has characteristics similar to the well-known KT66. Its heater rating, however, is 4 volts 2 amperes, and it has a 7-pin base with a top-anode connection. It is priced at 15s.

# Film Industries 6/15/PP Amplifier

THIS compact and low-priced 15-watt amplifier is supplied in kit form with blue prints and full instructions for wiring. The chassis is of channel section, and is constructed of 16 SWG steel with all holes drilled ready for assembling the components.

There are two input circuits with a centre-tapped fader, and the output transformer has tappings giving output impedances of 4, 8 and 16 ohms. The first stage is a resistance-capacity coupled triode with a shunt resistance-capacity tone control across

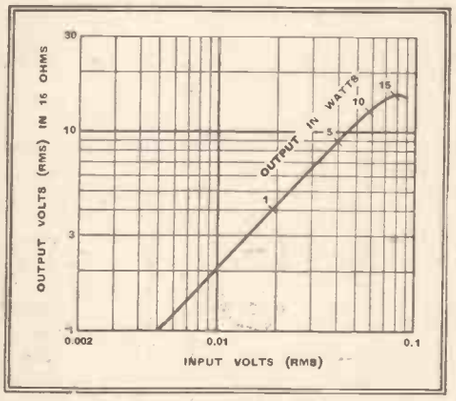


Input-output curve of the Film Industries amplifier at 400 c/s. Output resistance 16 ohms.

15-watt amplifier built from a kit of parts.

its anode circuit. The second stage, also a triode, is transformer-coupled to two 6N6G double-triode output valves operated in Class B push-pull. High-tension current is derived from an MU14 rectifier with one stage of smoothing. A fuse is included in the HT circuit as well as in the mains leads. The mains transformer is adjustable for AC mains between 200 and 250 volts.

The group of three frequency characteristics taken with the tone control in the minimum, maximum and midway positions indicate that the flattest response will be found somewhere in the first half of the range of tone control. The rising characteristic at maximum high-note response is useful, and will no doubt be appreciated for PA work where clarity of diction is important.

An output of 15 watts is reached with some overloading apparent on the cathode-ray tube. Departure from pure sine wave is discernible when the level passes 5 watts. Full output was reached for an input of 0.08 volt.

The amplifier should prove useful, among other things, for modulating amateur telephone transmitters, and has, in fact, already demonstrated the good quality of reproduction it is capable of giving under these conditions.

The makers are Film Industries, Ltd., 60, Paddington Street, London, W.1, and the price is £9 9s.

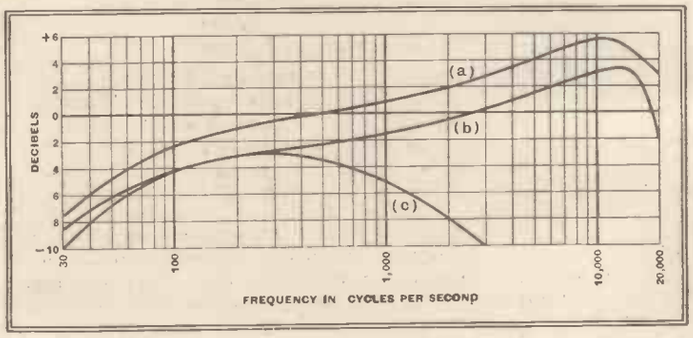


Frequency response of the Film Industries 6/15/PP amplifier with the tone control (a) in the maximum, (b) midway and (c) minimum high-note positions.

# Random Radiations

By "DIALLIST"

## Not So Easy

AT a friend's house the other evening my eye was caught by a new "all-wave" receiver standing in the place previously occupied by something that, to say the least of it, wasn't exactly up to date. "Hullo," I said, "you've gone in for a new set, I see." He told me that he'd had to, as the reproduction of the old one had become so awful that he couldn't stand it any longer. I had been wondering for many months how he could stand it at all! "Do you make much use of the short-wave range?" I asked. His reply was that he'd tried it once or twice, but hadn't found much except for the Empire transmissions and one or two Europeans, and had decided that the tuning was a bit too difficult for him. He thought that the set must be capable of bringing in short-wave stations in countries farther away, he'd like to be able to bring some of them in at times; but he didn't feel up to doing the niggling and fiddling with the tuning knob that appeared to be called for.

## Worth Thinking Over

At his suggestion I tried the receiver. It wasn't one of the small, cheap "all-wave" sets. By to-day's standards the price paid for it wasn't a low one, and it was obviously good value for money. On the medium and the long waves it was a distinctly good performer and quite easy to handle. But when I turned to the short-wave range I found myself in deep waters. To a sketchily calibrated scale, some six inches in length and covering about 12.5 megacycles, add a thick pointer and a not-so-slow-motion drive not entirely free from backlash, and the process of tuning in a distant station becomes almost as exasperating as doing one of those horrible puzzles which call on you to separate inseparable keys or to shake steel balls into inadequate holes. I did manage to get hold of a number of distant stations, but it wasn't easy. I asked my friend if he wouldn't gladly have paid an extra pound for simpler tuning arrangements on the short waves. He most certainly would, and as there must be many like him, I pass on the hint to set manufacturers.

## The Rustlers

ARE you annoyed by the paper rustling in which some announcers and some speakers indulge when they are before the microphone? I must say that I am. Lately we seem to have had a good deal more of it than for some time past. Possibly announcers have been agitated by seeing larger crops of fearsome foreign names than usual on the typewritten sheets before them. Possibly we have had more than the normal quota of speakers new to the microphone and suffering from fright thereof. I don't know; but I'm sure that paper rustling has increased for some reason or other. Years ago I made the suggestion that the news bulletins, at any rate, should be typed on some fine washable fabric such as cotton or linen instead of paper. I still think it would be a good idea; but if it's not practicable, the paper manufacturers, if asked, would doubtless put their heads together to produce a rustle-poof paper intended specially for broadcasting purposes. With so many stations in the world to-day, all giving such quantities of news items and talks, the demand should be considerable.

## The Real Enemy

I'VE always believed firmly that television's greatest enemy in the London area is not the cost of the apparatus necessary for receiving it, or the shortness of the programme hours, or the comparative smallness of the domestic screen. The real foe is interference, particularly that produced by car ignition systems. Go into the average dealer's shop and witness a demonstration of television. At intervals, depending on the density of the traffic stream in the neighbourhood, the images on the screen are all but blotted out by a snowstorm, whilst noises that are anything but pleasant are torn from the loud speaker. The demonstrator explains that that's merely a passing car, which he can't help; the would-be purchaser reflects that motor cars are not unknown in the neighbourhood of his house. He is told, possibly, that it will be "quite easy" to get rid of the interference at his home. If it's so easy, he cannot help wondering why the dealer hasn't rendered his demonstration room immune!

## A Big Problem

From articles and letters that have appeared from time to time in *The Wireless World*, one surmises that, though *some* cars may not have their performance seriously affected by *some* interference-suppression systems, there is as yet no system that will adequately (and satisfactorily) cope with *all* cars. It's a very unsatisfactory position, and it's high time that the car manufacturers and the radio industry went into a huddle to tackle this serious problem by co-operative effort. Here we are, on the one hand, spending immense sums to develop the broadcasting of entertainment on the ultra-short waves, and, on the other hand, producing vast quantities of motor-driven vehicles so designed that each one that takes the road is doing its bit towards making the use of these waves more difficult. Given a fair chance, the ultra-short waves might play an even more important part in human affairs than the medium and long. But if they're not given that chance they may become in time all but useless.

## Creeping

PERHAPS I'm wrong, but I don't notice much improvement in the matter of oscillator creeping in the moderately priced class of receiver. I was using one recently which wouldn't hold even the local stations! If, for example, I adjusted it carefully to resonance with the London National at the beginning of the nine o'clock news bulletin, the announcer's S's sounded like the release of soda-water from a syphon before he was half-way through his reading. This wasn't a press-button set, though I'd had sets of that kind that were almost as bad. Another set would creep from one station to another on the short waves, if left to itself; in fact, to hold a transmission you had to be constantly juggling with the tuning knob. One would have thought in these days of button-tuning the problem of oscillator creep would be receiving plenty of attention. Creep is preventable, of course; but to do so puts up costs, and that, I suppose, is the reason why it is found in so many of to-day's sets.

## W6XBE in S.A.

FROM Johannesburg comes a letter telling me of R8 reception of W6XBE, the new General Electric short-wave station. Its writer is surprised at his success. As the station's beam for the transmission that he heard was directed on Asia, he suggests that some lateral refraction must have been taking place for it to be heard so strongly in South Africa. I don't think so. W6XBE is on Treasure Island, San Francisco. I haven't had time to work out the Great Circle course, but, so far as I can see by looking at a terrestrial globe, a continuation of the path between San Francisco and Southern Asia would pass not a long way from Johannesburg. In the ordinary way, I learn, American broadcasting stations on the short waves are not well received in that city. I predict, though, that my correspondent will be able to receive this beamed transmission from W6XBE on most days when conditions are not unfavourable. By the way, the time at which he heard the broadcast that he reports was a little before 15.00 GMT. The frequency was 9.53 Mc/s.

## Water Wears Away a Stone

YOU can't help feeling sorry for the fellows who come round trying to sell vacuum cleaners; theirs is a hard job, and I'm afraid that one is apt to be a bit short with them. I always try to be as gentle with them as I can when they manage somehow or other to penetrate the outer defences to my den. The other day, though, I couldn't help asking one of them whether the one that he was demonstrating was guaranteed not to interfere with wireless. He professed to think that it was innocuous, so I got him to turn it on and then switched on the set, with the usual results. "My wife does want a new one," I said, "but I've sworn an oath not to buy anything that causes interference. Tell your people that you've lost a possible sale because yours does." If readers would take the same line the makers of these appliances would soon begin to do a bit of useful thinking. Similar reports from representative after representative would eventually have their effect.

## Non-interfering!

Just as I'd written that last paragraph a card was brought in to me with the information that its owner was very anxious to see me, as he had something special to display. A vacuum cleaner man! As he pencilled on the card "Does not affect wireless sets," I saw him. He was most anxious that I should make a practical test, so I switched on a set, bidding him put his cleaner together. He finished assembling the bits and pieces, plugged in and switched on. A

noise like that made by a squadron of aeroplanes all but drowned the London Regional programme! "There you are," said he. "W-w-where?" I gasped. "You see," he explained, "it does not stop the set working." He had apparently the idea that interference meant something that put the set right out of action! As kindly as possible I disillusioned him. Then I led him to a distant room, switched on a set there and let him hear what his infernal machine could do at long range—the second set is 80ft. from No. 1 and connected to another aerial. At that moment my next-door neighbour came in to ask if I could render first aid to his receiver, which had gone mad and was emitting horrible noises. The vacuum cleaner merchant left, a sadder and (I hope) a wiser man.

## Not the Food of Love

THE other evening, when I was endeavouring to do some work, my ears were assailed by appalling strains of mangled music. The noise sounded rather like that which used years ago to be produced at times when some enthusiast was proudly demonstrating to a friend the marvellous volume of which his set (five "R" valves and a horn loud speaker!) was capable. At first I thought that one of my neighbours had installed some atrocity and was giving it a trial "all out" run. Then I realised that a fair was being held in a field about a quarter of a mile from me. The modern showman has discarded the steam organ in favour of pick-up, turntable and a public-address amplifier with rather awful results. His clients like a lot of noise, so he turns the volume control right up and lets things rip. A distant steam organ did not sound beautiful; but it was sweetness itself in comparison with an overloaded PA outfit blaring out jazz!

# DIRECT RECORDING BLANKS

*Compiled by Donald W. Aldous*

**In the May 19th, 1938, issue of "The Wireless World" a Table of direct play-back blanks for sound-recording was published, which was prepared by the present writer. Below is a revised version of this Table of blanks which are all readily obtainable in this country. Details of foreign blanks are not included, but a list of the names and addresses of the principal blank manufacturers abroad is appended.**

Abbreviations: SS = Single-sided. DS = Double-sided.

| Name | Type: Base | Type: Surface Coating | Type: Processing | Diameter | Prices Retail Each. | Manufacturer or Main Stockists. |
|---|---|---|---|---|---|---|
| Decelith ... ... | Unbacked (flexible). | Non-inflammable material. | Polishing fluid only ... ... ... ... ... | 8in. (DS)<br>10in. ,,<br>12in. ,, | 2s. 0d.<br>2s. 6d.<br>4s. 0d. | Will Day, Ltd., 19, Lisle Street, W.C.2. |
| Electradix ... | Aluminium alloy | — | Before cutting a lubricant may be applied, e.g., paraffin oil or olive oil, or "Vaseline." | 6in. (DS)<br>10in. ,, | 3s. 3d. (doz.)<br>7s. 0d. ,, | Electradix Radios, 218, Upper Thames Street, E.C.4. |
| G. C. Master ... | Zinc ... ... | Cellulose acetate | None ... ... ... ... ... ... ... | 10in. (SS)<br>12in. ,,<br>10in. (DS)<br>12in. ,,<br>13in. ,, | 1s. 8d.<br>2s. 8d.<br>2s. 6d.<br>4s. 0d.<br>4s. 9d. | G.C. Electrical Recording Co., Ltd., 181, Wardour Street, W.1. |
| Neo-Cire ... | Metal ... | Cellulose compound | Electrolytic, as these blanks are primarily intended for use as masters when solid stock pressings required. | 11in. (SS)<br>13in. ,, | 4s. 0d.<br>5s. 0d. | V. G. Manufacturing Co., Ltd., Gorst Road, Park Royal, N.W.10, and Makers' Agents, Agents, Ltd., High Holborn House, High Holborn, W.C.1. |
| Phono-Disc ... | Aluminium ... | Non-fluid chemical lubricant impregnated in surface of aluminium. | None ... ... ... ... ... ... ... | 6in. (DS)<br>10in. ,,<br>12in. ,, | 5s. (doz.)*<br>10s. ,,<br>20s. ,, | Phono-Disc Ltd., 65, Bolsover Street, W.1. |
| Presto ... ... | Aluminium ... | — | Usual cutting lubricant, if desired ... ... | 6in. (DS)<br>8in. ,,<br>10in. ,,<br>12in. ,,<br>16in. ,, | Prices not available price schedule under revision. | A. C. Clifford, 17, Wigmore Street, W.1. |
| Presto ... ... | Aluminium Thick (Green Seal) | Cellulose compound | Preserving fluid, known as "Disclube" is available. | 6in. (DS)<br>8in. ,,<br>10in. ,,<br>12in. ,,<br>16in. ,, | | ,, ,, ,, ,, ,, |
| Presto ... ... | Aluminium Thin (Orange Seal) | ,, ,, ,, | ,, ,, ,, ,, ,, ,, | 6in. (DS)<br>8in. ,,<br>10in. ,,<br>12in. ,, | | ,, ,, ,, ,, ,, |
| Pyral ... ... | Cardboard ... | Cellulose compound | —— | 6in. (DS)<br>8in. ,, | 8d.<br>10d. | |
| Pyral ... ... | Zinc ... ... | Cellulose compound, plus black varnish | None, although a hardening or polishing fluid may be used if desired. | 8in. (DS)<br>10in. ,,<br>12in. ,, | 1s. 6d.<br>2s. 0d.<br>3s. 0d. | V. G. Manufacturing Co., Ltd., Gorst Road, Park Royal, N.W.10, and Makers' Agents, Ltd., High Holborn House, High Holborn, W.C.1. |
| Pyral ... ... | Aluminium ... | ,, ,, ,, | ,, ,, ,, ,, ,, ,, | 10in. (DS)<br>12in. ,,<br>16in. ,, | 2s. 6d.<br>4s. 0d.<br>8s. 0d. | |
| Simplat ... ... | Unbacked, flexible. | Gelatinous composition (non-flam.) | Chemical treatment, i.e., hardened and polished by fluids containing formaldehyde and waxy oils respectively. | 7in. (DS) | 1s. 0d. | V.G. Manufacturing Co., Ltd., Gorst Road, Park Royal, N.W.10. |
| Simplat ... ... | Glass ... ... | ,, ,, ,, | ,, ,, ,, ,, ,, ,, | 7in. (DS)<br>10in. ,,<br>12in. ,,<br>14in. ,,<br>16in. ,, | 2s. 0d.<br>3s. 0d.<br>4s. 0d.<br>6s. 0d.<br>8s. 0d. | ,, ,, ,, ,, ,, |
| Supercut ... | Aluminium ... | Cellulose acetate (Black coloured). | Chemical treatment, if desired, and very light oil applied before and after cutting will prolong useful playing life. | 10in. (SS)<br>12in. ,,<br>13in. ,,<br>10in. (DS)<br>12in. ,,<br>13in. ,, | 2s. 8d.<br>3s. 0d.<br>5s. 0d.<br>3s. 6d.<br>4s. 6d.<br>7s. 0d. | M.S.S. Recording Co., Ltd., 83, The Green Kew, Surrey. |
| W.D. ... ... | Metal ... ... | Cellulose acetate | Polishing fluid only ... ... ... ... ... | 8in. (DS)<br>10in. ,,<br>12in. ,, | 2s. 0d.<br>3s. 0d.<br>4s. 6d. | Will Day, Ltd., 19, Lisle Street, W.C.2. |

* (Phono-Disc) Smaller quantities are not supplied at proportionate prices.

**FOREIGN BLANK SUPPLIERS.**

(1) Allied Recording Products Co., 126, West 46th Street, N.Y.C., U.S.A.
(2) Cellutone Record & Mfg. Co., Los Angles, California, U.S.A.
(3) Mirror Record Corporation, 58, West 25th Street, N.Y.C., U.S.A.
(4) Presto Recording Corporation, 242, West 55th Street, N.Y.C., U.S.A.
(5) Rangertone Inc., 201, Verona Avenue, Newark, New Jersey, U.S.A.
(6) Recoton Corporation, 178, Prince Street, N.Y.C., U.S.A.
(7) Sound Apparatus Co., 150, West 46th Street, N.Y.C., U.S.A.
(8) Svenska Radioaktiebolaget, Alströmekgatan, 12, Stockholm, Sweden.
(9) Universal Microphone Co., Ltd., Recording Division, Inglewood, California, U.S.A.
(10) Wiener Gelatinewaren Industrie, XVII/3, Hernalser, Haupstrasse, 130, Vienna.

# Recent Inventions

***Brief descriptions of the more interesting radio devices and improvements issued as patents will be included in this section.***

### RELAYING TELEVISION SIGNALS

TO maintain the correct balance as between the high and low frequencies in a transmission line for relaying television signals, attenuation losses are compensated by deliberately increasing the amplitude of the high-frequency components at the input to the line, and then reducing them to their proper proportion at the output end of the line.

At the input, the signals are subjected to a process of double modulation and are passed through "distorting" circuits which make the desired frequency discrimination, the process being reversed as the currents are delivered from the far end of the line to the local amplifiers. The overall or resultant distortion is thus reduced to zero, both as regards phase and frequency.

*Standard Telephones and Cables, Ltd.; K. G. Hodgson; and W. N. Roseway. Application date July 21st, 1937. No. 499317.*

o o o o

### TUNING CONTROL

WHEN a receiver is fitted with automatic tuning control, it is difficult to tune in to a weak station that happens to be adjacent to a strong station, because the ATC action tends to "pull" the circuits into tune with the dominant station. One way of overcoming this difficulty is to provide a switch for cutting-out the ATC action when searching for a relatively weak signal.

The figure shows a convenient arrangement in which the ATC is maintained operative for relatively strong signals, but is automatically cut out of action when tuning the set to a weak signal. In the latter case, for instance, the normal AVC bias gives the IF valve V a low impedance, so that sufficient current flows through the cathode resistance R to energise a relay K. The lower pair of contacts C are thus closed to short-circuit the ATC voltage across the leads L. Tuning is then completed by hand control.

For a strong signal, the impedance of the valve V is increased by the AVC bias, the relay K is de-energised, and an upper contact C1 is closed to energise a winding W. This puts a braking action on the movement of the tuning spindle S through a disc D, and so warns the operator to release the tuning knob T, so that the ATC voltage can complete the tuning.

*E. K. Cole, Ltd., and A. W. Martin. Application date September 18th, 1937. No. 501934.*

o o o o

### LARGER PICTURES

RELATES to a cathode ray television receiver of the kind in which an image of the televised picture is projected through a screen of variable transparency on to a large viewing screen mounted outside the tube.

As shown, the electron stream from the gun G is made to scan a screen S in the usual way. Instead of being fluorescent the screen S is composed of a transparent substance capable of developing static charges under the action of a scanning stream. Mounted immediately behind it is a shallow disc-like chamber C filled with paraffin oil containing a large number of iron particles in solution.

Normally the iron particles arrange themselves indiscriminately, and in this condition they block the passage of a ray of light from a powerful lamp L. But under the action of the scanning beam—which sets up local static charges on the screen S—the iron particles are aligned "end-on" to the screen, and so permit the free passage of light from the lamp L to an extent varying with the intensity of each picture point.

This allows an image of the picture to be projected from the lamp L, through the paraffin, on to a large-sized viewing-screen which can be mounted outside the tube.

*F. J. G. Van den Bosch. Application date September 3rd, 1937. No. 501816.*

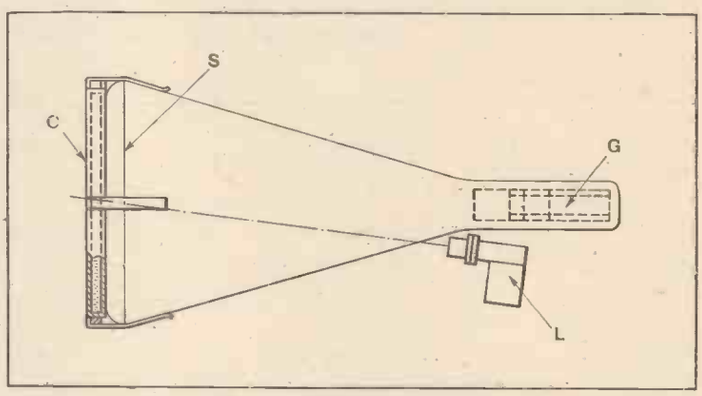


Projection-type cathode-ray tube for large television pictures.

o o o o

### DIRECTION FINDERS

IN an automatic direction-finder for "homing" on to a beacon station, the bearing-line is indicated by the point of intersection of two separate pointers which move over a dial marked with a series of radial lines diverging from a common centre. When the machine is flying "on course," the pointers intersect on the centre-line, the pointers gradually travelling down and along it as the machine approaches the transmitter.

This avoids having to use any critical degree of AVC to compensate for varying field strength in the course of the flight. The same kind of indication is given along an inclined radial line, when the beacon station is to port or starboard of the machine. Used in conjunction with a compass, the arrangement gives a reliable indication of wind drift. It can also be used for the "robot" control of an unmanned aeroplane.

The indicator is fed with signal voltage picked up on a frame aerial and combined alternately in and out of phase with the pick-up from a non-directional aerial. This gives a reversed cardioid curve, the necessary phase-changing being effected by a motor-driven switch.

*Marconi's Wireless Telegraph Co., Ltd.; and T. A. Vallette. Application date September 4th, 1937. No. 501550.*

o o o o

### MOSAIC SCREENS

A KNOWN method of producing television signals is to project a picture on to a mosaic screen of photo-sensitive cells, so that an electric image is formed, which is then discharged by scanning it with an electron beam. The strength of the picture signals so produced can be increased by increasing the beam current, but a limit is set by the production of dark patches. These are due to the liberation of secondary electrons, which set up a space-charge in front of the scanning stream. Owing to the scanning movement of the stream, the patches tend to "wander" and generally drift from the outer edges towards the centre.

According to the invention, this distortion effect is prevented by constructing the mosaic screen so that it has a variable instead of a uniform sensitivity, both as regards photo-electric response and the production of secondary electrons. The screen usually consists of a silver plate with an oxidised surface, and the required effect is obtained by shading-off the degree of oxidation from the centre towards the edges of the plate.

*W. Heimann. Convention date (Germany) September 10th, 1936. No. 502024.*

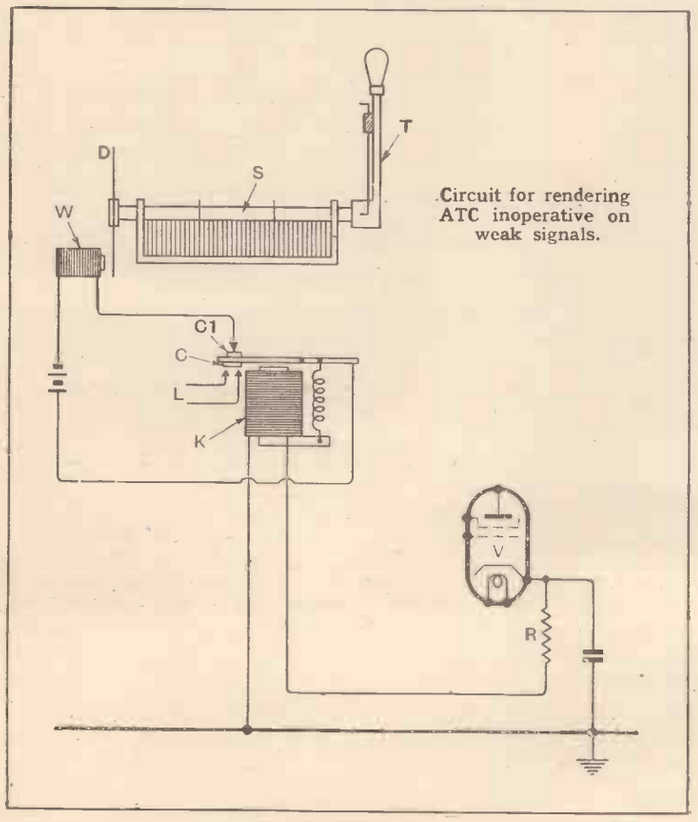


Circuit for rendering ATC inoperative on weak signals.

**The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.**

# ...and, of course, RED 'E' VALVES for QUALITY★

MULLARD RED 'E' VALVES, in whatever stage they are used, make a big contribution to Quality Reproduction.

Their extra reserve of efficiency is a safety margin for the designer. It means that he need never extract the last ounce from them. Where ordinary valves must work at the pitch of their performance, Mullard Red 'E' Valves carry out their functions with efficiency to spare.

That's the secret of the success of sets fitted with these valves. They are streets ahead of others on Performance PLUS Quality.

**★Extra Efficiency in the Frequency Changer Stage is an important contribution to Quality Reproduction**

Quality in the output stage is more easily obtained if the valves in the preceding stages afford that vital safety margin of reserve efficiency. In the superheterodyne receiver, therefore, quality really starts with the Frequency Changer. The new Mullard Triode-Hexode ECH3, in addition to its outstanding constructional improvements, has remarkably good characteristics. Its conversion conductance is 0.65mA/V (resulting in high conversion gain); mutual conductance of the triode oscillator section is 3.8 mA/V; optimum heterodyne voltage for maximum conversion gain is 8 volts R.M.S; and the cathode wattage is only 1.25 W.

| | |
|---|---|
| HEATER VOLTS | 6.3 V. |
| HEATER CURRENT | 0.2 Amp. |

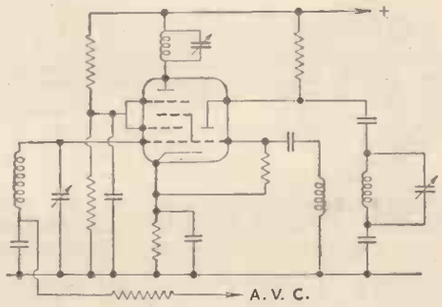


# Mullard
## RED 'E' VALVES

**THE MULLARD WIRELESS SERVICE COMPANY LTD.**
**VALVE SALES DEPARTMENT**
**225 TOTTENHAM COURT ROAD, LONDON, W.I.**

VOIGT PATENTS LTD.

## DEFERRED DELIVERY MADE EASY

Our "Deferred Delivery" system, advertised on February 23rd, elicited many requests for details. It meets the case of those who are unwilling to tie themselves down to the payment of regular amounts, and who wish their goods to be "bought and paid for" before delivery. Take a simple illustration. Imagine that whenever Mr. X buys a packet of cigarettes he puts aside an equal amount of cash and send us this money each month, plus £1 if he can manage it. He is tied down to nothing, and we give him a special "Deferred Delivery" credit on his money equal to 1/- per £ per annum. Mr. X gets his unit in less than a year. How? Very simply; look at the account below. He puts aside roughly 6/- a week; never pays more than £2 7s. in one month; pays nothing when he cares not to; submits to no compulsion; and receives credits totalling 7/1—thus saving this amount on the price of the unit.

| | Amount Recd. £ s. d. | Total £ s. d. | Credit |
|---|---|---|---|
| January | 18 0 | 18 0 | Nil |
| February | 1 14 0 | 2 12 0 | 2d. |
| March | 2 2 0 | 4 14 2 | 4d. |
| April | 2 7 0 | 7 1 6 | 7d. |
| May | 2 4 0 | 9 6 1 | 9d. |
| June | 1 19 0 | 11 5 10 | 11d. |
| July | 15 0 | 12 1 9 | 1/- |
| August (holidays) | Nil | 12 2 9 | 1/- |
| September | 1 17 0 | 14 0 9 | 1/2 |
| October (new suit) | Nil | 14 1 11 | 1/2 |
| November (to clear) | 16 11 | 15 0 0 | Unit supplied |

46 weeks—£14 12s. 11d.

So pay down any amount you like as a first deposit and your D.D. account is open. What an incentive to save! Get your Voigt Speaker some time soon. You will never regret it.

VOIGT PATENTS LTD., THE COURTS, SILVERDALE, LONDON, S.E.26

Tel.: SYDenham 6666 Regd. Office: 22, Castle Street, E.C.1.

## "100% BETTER than an ordinary GOOD AERIAL"

THIS is the verdict of one user who is enjoying first-class reception in a busy shopping centre surrounded by electrical interference. Testimonials are being received every week from radio dealers and private users in all parts of the country, telling how the Belling-Lee 'SKYROD' Aerial System is reducing electrical interference to negligible proportions, improving volume, bringing in far more stations and doubling listening enjoyment.

MONEY BACK GUARANTEE

Prove the 'Skyrod'—under any conditions—with your own set. If it fails to fulfil any claims we make, your money in full. See your dealer to-day—he'll gladly demonstrate—and, remember, hire purchase terms are available.

BELLING-LEE "B" TYPE TERMINALS specified for "WIRELESS WORLD" D.C. MAINS SUPER List No. 1001 Price each 8d.

'The BELLING-LEE SKYROD' AERIAL SYSTEM

TRADE MARK, REGT DESIGN & PATENTS APPLIED FOR

In four different mountings from £3.19.6 to £6.7.0 or on H.P. Terms from 1/3 weekly. Prices do not apply to Eire.

Belling & Lee Ltd., Cambridge Arterial Road, Enfield, Middlesex.

7417

## B.I. COPPER EARTHING RODS for WIRELESS APPARATUS

(U.K. Patent Nos. 438598, 423385, 430040.)

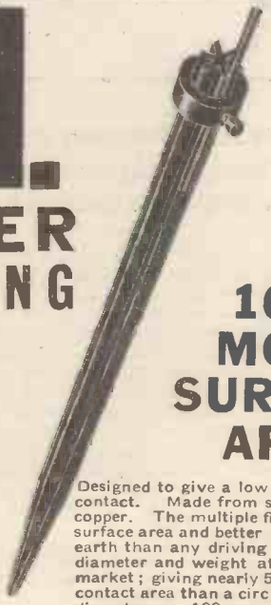

100% MORE SURFACE AREA

Designed to give a low resistance earth contact. Made from solid drawn H.C. copper. The multiple fins ensure larger surface area and better contact with the earth than any driving earth of similar diameter and weight at present on the market; giving nearly 50 per cent. more contact area than a circular rod of equal diameter, or 100 per cent. more than a solid rod of equal weight.

About 1½" of the rod is left exposed and the earth lead is simply clamped against the rod by means of the copper clamp ring and screw. No sweating or soldering is required. Supplied in two standard sizes, 18" and 24". Longer rods of similar type can be supplied, if desired, to meet special requirements.

BRITISH INSULATED CABLES LTD.,

CABLE MAKERS AND ELECTRICAL ENGINEERS,

PRESCOT, LANCS. Tel. No. PRESCOT 6571

## FLIGHT

## Royal Air Force Number

DATED MAY 18th

A comprehensive review of the work and machine equipment of the R.A.F. and Fleet Air Arm. Also many pictorial features, including striking air photographs by "Flight" photographers.

Guide to Empire Air Day displays

GREATLY ENLARGED

SPLENDIDLY ILLUSTRATED

ALL THE REGULAR FEATURES 6d. AS USUAL

Flight Publishing Co. Ltd., Dorset House, Stamford Street, London, S.E.1

# CATHODE RAY TUBE

## TYPE 4096 A

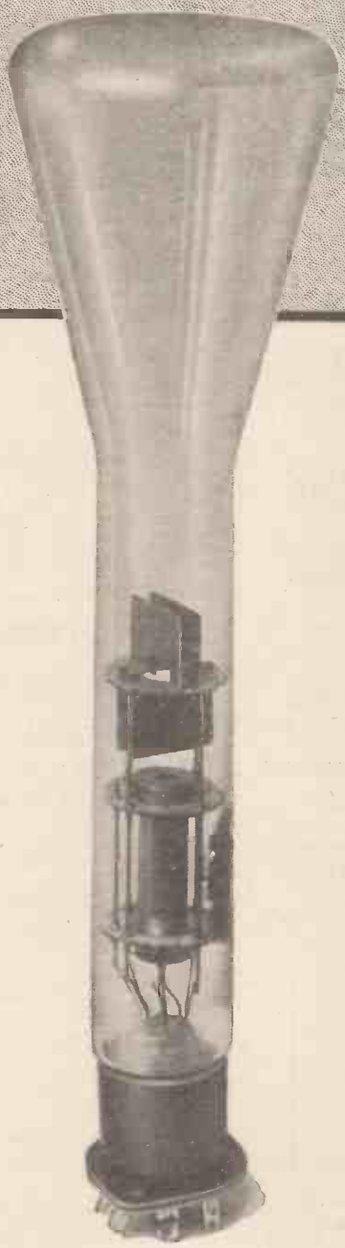

THE 4096 A Cathode Ray Tube is a hard vacuum tube suitable for use with anode voltages from 800 to 2,000 volts and has a screen diameter of 3 inches. The screen provides a blue spot of high actinic value necessary for photographic purposes and, in addition, owing to its intense brilliance, is suitable for visual work.

Efficient electrostatic screening is ensured by the internal coating of the tube with aquadag while the connections to the "Y" plates are brought out to separate pins, thereby facilitating the use of balanced circuits and providing for improved focussing.

The cathode is indirectly heated and thus the heater may be supplied with raw A.C. This tube is fitted with an American type octal base.

**The popularity of this tube has now enabled us to offer it at the attractive price of**

**£2.10.0 NETT**

**Delivery in Gt. Britain or Northern Ireland within 2 days of receipt of order.**

*Standard Telephones and Cables Limited*

**NORTH WOOLWICH, LONDON, E.16**

Telephone: Albert Dock 1401

BRANCHES AND REPRESENTATIVES THROUGHOUT THE WORLD

# CLASSIFIED ADVERTISEMENTS

## NOTICES

THE CHARGE FOR ADVERTISEMENTS in these columns is

12 words or less, 3/- and 3d. for every additional word.

Each paragraph is charged separately and name and address must be counted.

SERIES DISCOUNTS are allowed to Trade Advertisers as follows on orders for consecutive insertions, provided a contract is placed in advance, and in the absence of fresh instructions the entire "copy" is repeated from the previous issue: 13 consecutive insertions 5%, 26 consecutive, 10%; 52 consecutive, 15%.

ADVERTISEMENTS for these columns are accepted up to FIRST POST on MONDAY MORNING (previous to date of issue) at the Head Offices of "The Wireless World," Dorset House, Stamford Street, London, S.E.1, or on SATURDAY MORNING at the Branch Offices, 8-10, Corporation Street, Coventry; Guildhall Buildings, Navigation Street, Birmingham, 2; 260, Deansgate, Manchester, 3; 26B, Renfield Street, Glasgow, C.2.

Advertisements that arrive too late for a particular issue will automatically be inserted in the following issue unless accompanied by instructions to the contrary. All advertisements in this section must be strictly prepaid.

The proprietors retain the right to refuse or withdraw advertisements at their discretion.

Postal Orders and Cheques sent in payment for advertisements should be made payable to ILIFFE & SONS Ltd., and crossed & Co. Notes being untraceable if lost in transit should not be sent as remittances.

All letters relating to advertisements should quote the number which is printed at the end of each advertisement and the date of the issue in which it appeared.

The proprietors are not responsible for clerical or printers' errors, although every care is taken to avoid mistakes.

## IMPORTANT NOTICE.

Owing to the Whitsun Holidays the issue of "THE WIRELESS WORLD" for June 1st must be closed for press earlier than usual.

MISCELLANEOUS ADVERTISEMENTS for insertion in that issue can be accepted up to

**FIRST POST FRIDAY, MAY 26th.**

## NEW RECEIVERS AND AMPLIFIERS

*

*

DEGALLIER'S "Challenger Radio Corporation."

SEND 2d. stamp for Handsome Illustrated Catalogues Telling of our Superb Range of Receivers; direct public sales policy (saves you 40%), most exceptional value on the market, from a T.R.F. Midget at £3/5 to a 19-valve general purpose receiver, 6 bands, with two P.A. speakers, at 30 gns.; 6-page brochure of *Wireless World* report on this set is available; car radio; any known American valve, all 5/6 each; also American P.A. speakers, cabinets, and the Challenger 6-valve A.C. tuning unit, 5 bands 6-10, 12.8-50, 65-200, 190-550, 900-2,000 metres. Hours business 11 a.m. until 9.30 p.m.

DEGALLIER'S, 31, Craven Terrace, London, W.2. Paddington 6492. Nearest point Lancaster Gate Tube Station. [8443

R

RADIO CLEARANCE, Ltd.

ALL Lines Previously Advertised Still Available.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1. Holborn 4631. [8471

## RECEIVERS AND AMPLIFIERS

### CLEARANCE, SURPLUS, ETC.

1939 Midwest 15-valve A.C./D.C. Allwave, 6 wavebands, 5-1,500 metres, brand new, in handsome walnut console cabinet; listed £36/15. £20; two only.

1939 Midwest 9-valve A.C. Radiogram, 6 wavebands, 5-1,500 metres, brand new, in massive walnut cabinet; £18/10.

HENRY'S, 72, Wellington Ave., Stamford Hill, N.15. Stamford Hill 2907. [8438

## ARMSTRONG's NEW HEADQUARTERS

After many years at our old premises in Camden Town we have moved our Offices, Show rooms and Development Department to a modern building centrally situated in

**WARLTERS ROAD, HOLLOWAY, N.7**
(Adjoining Holloway Arcade).

Send for Illustrated Catalogue of our full range, which includes the following outstanding chassis.

**MODEL AW125PP . . Price £17.17.0**
**12-V. ALL-WAVE RADIOGRAM CHASSIS**
5 wavebands, 12-550 continuous, 1,000-2,000 m., R.F. Pre-Amplifier, 2 I.F. stages with Variable Selectivity. Manual R.F. gain control and 10 watts R.C. coupled Triode P.P. output.

**MODEL AW93PP . . . Price £10.10.0**
**9-V. ALL-WAVE RADIOGRAM CHASSIS**
3 wavebands, R.F. Pre-Amplifier, 3 stages of A.V.C. and 8 watts R.C. coupled Triode P.P. output.

**MODEL RF96 . . . . . Price £8.0.0**
**6-V. ALL-WAVE RADIOGRAM CHASSIS**
(Incorporating R.F. Amplifier).
3 wavebands, 17.9-50, 200-550, 1,000-2,000 m., 3 stages of A.V.C., corrected 3½ watts output. Complete with Matched M.C. Speaker.

*All communications to be addressed to*

**ARMSTRONG MANUFACTURING CO.,**
**WARLTERS ROAD, HOLLOWAY, LONDON, N.7**
(Adjoining Holloway Arcade).

*Telephone: NORth 3213.*

## SIGN OF PSEI PRECISION

ELECTRICAL INSTRUMENTS

- Geared slow-motion dials.
- Metal Chassis.
- Racks and Panels.
- Turned and Machined Parts.
- Short-Wave.
- Ultra S/Wave.
- Dia-thermy.
- Electro-Medical.

. . . and all allied equipment.

—For MANUFACTURERS only—

We specialise in the production of equipment and parts to individual needs and gladly offer our long experience in the design of special requirements.

*Send your enquiries to—*

**P.S.E.I.** (Holdings) Limited, Pilot House, Stoke Newington, Church Street, London, N.16. *'Phone: Clissold 9875.*

—CONTRACTORS TO H.M. GOVERNMENT—

| | |
|---|---|
| 8-Way Battery Looms | 7d. each |
| 4-Way Looms, with two 27in. screened leads | 8d. each |
| Phone Cords | 6d. each |
| Speaker Transformers, 70 to 1 Ratio | 2/6 each |
| Power Pack Metal Chassis (cut out for Transformer and Valve) | 7d. each |
| 2 Gang Condensers with Trimmers, .0005 | 2/- each |
| 3 Gang Condensers with Trimmers, .0005 | 3/6 each |
| Tubular Condensers, .0001, .0002, .0003, .002, .003, .01, .03, .05 | 6d. each |
| Resisters, All Values | 6d. each |
| 5 ohm Mains Filter Chokes | 6d. each |

*ALL POST FREE.*

We shall be glad to send quotations for anything in Radio on receipt of enquiries. We do NOT issue a catalogue.

**UNIVERSAL, 8 & 10, Brown Street,**
*'Phone: Deansgate 5009.* MANCHESTER, 2.

## NUMBERED ADDRESSES

For the convenience of private advertisers, letters may be addressed to numbers at "The Wireless World" Office. When this is desired, the sum of 6d. to defray the cost of registration and to cover postage on replies must be added to the advertisement charge, which must include the words Box 000, c/o "The Wireless World." All replies should be addressed to the Box number shown in the advertisement, c/o "The Wireless World," Dorset House, Stamford Street, London, S.E.1. *Readers who reply to Box No. advertisements are warned against sending remittances through the post except in registered envelopes: in all such cases the use of the Deposit System is recommended, and the envelope should be clearly marked "Deposit Department."*

### DEPOSIT SYSTEM

Readers who hesitate to send money to advertisers in these columns may deal in perfect safety by availing themselves of our Deposit System. If the money be deposited with "The Wireless World," both parties are advised of its receipt.

The time allowed for decision is three days, counting from receipt of goods, after which period, if buyer decides not to retain goods, they must be returned to sender. If a sale is effected, buyer instructs us to remit amount to seller, but if not, seller instructs us to return amount to depositor. Carriage is paid by the buyer, but in the event of no sale, and subject to there being no different arrangement between buyer and seller, each pays carriage one way. The seller takes the risk of loss or damage in transit, for which we take no responsibility. For all transactions up to £10, a deposit fee of 1/- is charged; on transactions over £10 and under £50, the fee is 2/6; over £50, 5/-. All deposit matters are dealt with at Dorset House, Stamford Street, London, S.E.1, and cheques and money orders should be made payable to Iliffe & Sons Limited.

**SPECIAL NOTE.**—Readers who reply to advertisements and receive no answer to their enquiries are requested to regard the silence as an indication that the goods advertised have already been disposed of. Advertisers often receive so many enquiries that it is quite impossible to reply to each one by post. When sending remittances direct to an advertiser, stamp for return should also be included for use in the event of the application proving unsuccessful.

## BATTERY CHARGING PLANT

TUNGAR Charger. 5 circuits, 30 cells circuit, 1½-1½-2-2-7 amps, trade £21/10, practically new; £14.—Morris, 2, Cottersloe Rd., Norton-on-Tees. [8462

## USED SETS FOR SALE

### SCOTT

SCOTT Imperial, 23-valve, auto-radiogram, improved type, 13-2,000 metres, three speakers, new valves, Garrard record-changer, in magnificent mahogany and ebony Milton Grande cabinet, cost 185 gns.; £55.—Bedson, Tower House, 78, Westmoreland Rd., Bromley, Kent. [8455

### W.W. STRAIGHT SIX

W.W. Straight Six and Push-pull Quality Amplifier, with valves, speaker, excellent condition; £10.—Kellaway, 67, Park Drive, Colne. [8460

## CAR RADIO

A

ANGLO-AMERICAN RADIO (and MOTORS), Ltd.

NEW Trav-Ler Car Radio, 1939 models.

£7/17/6.—Model 620, distinctive Trav-Ler features, press button tuning, can be set up and changed at will, no tools required, shielded power supply, full A.V.C. energised moving coil speaker, illuminated slide rule dial, improved superheterodyne circuit in brown steel container, 17in.×6in.×6in.

£8/17/6.—Model 620L, for long and medium wave bands, same specifications as model 620, except that it covers the 900-2,000 and 200-600 meter bands.

ANGLO-AMERICAN RADIO (and MOTORS), Ltd., Albion House, 59, New Oxford St., London, W.C.1. 'Phone: Tem. 3231. [8473

CROSLEY Push-button 1939 10-guinea Models, 5½ gns.; aerials overheads, police type, etc., from 8/6; trade enquiries solicited.—Shippers, 18, Corporation St., Manchester. [0622

FINEST American Twin Running-board, Aerials, completely rubber covered, maximum signal pick-up, minimum noise, easy mounting, now only 17/6 pair complete; handsome chromium roof aerials, to mount straight or "vee," complete, 15/-; immediate despatch, carriage paid; cash with order or c.o.d.

WIRELESS SUPPLIES UNLIMITED, Essex House, Stratford, E.15. Maryland 3191. [0577

### Wanted

CHEAP Car Radio, in good condition, 12v.—Box 9770, c/o *The Wireless World*. [8456

*"Radio Data Charts," A Series of Abacs Post free 4/10*

## PUBLIC ADDRESS

V

VORTEXION P.A. Equipment.

IMITATED, but unequalled.

WE Invite You to a Demonstration.

A.C.-D.C. Dance Band Amplifier, 10 watts output, complete in case, with moving coil microphone, speaker and cables, weight 22lb.; 12 gns.

A.C.-20 15-20-watt Amplifier, 38-18,000 cycles, independent mike and gram., inputs and controls, 0.037 volts required to full load, output for 4, 7.5, and 15 ohms speakers or to specification, inaudible hum level; ready for use; 8½ gns., complete.

C.P. 20, 12-volt battery and A.C. mains model, as used by R.A.F., output as above; 12 gns.

A.C.-20, in portable case, with Collaro motor, Piezo pick-up, etc., £14; C.P.20 ditto, £17/17.

50-WATT Output 6L6s, under 60-watt conditions, with negative feed back, separate rectifiers for anode screen and bias, with better than 4% regulation, level response, 20-25,000 cycles, excellent driver, driver transformer, and output transformer matching 2-30 ohms impedance electronic mixing for mike and pick-up, with tone control, complete with valves and plugs; £15.

COMPLETE in Case, with turntable B.T.H. Piezo pick-up and shielded microphone transformer; £20.

80-WATT Model, with negative feed back; £25, complete.

120-WATT Model, with negative feed back; £40, complete.

250-VOLT 250 m.a. Full Wave Speaker, field supply unit; 25/-, with valve.

ALL P.A. Accessories in Stock; trade supplied.

VORTEXION, Ltd., 182, The Broadway, Wimbledon, S.W.19. 'Phone: Lib. 2814. [8241

"PARTRIDGE P.A. Manual," free to trade, from N. Partridge, B.Sc., A.I.M.E.E., King's Buildings, Dean Stanley St., London, S.W.1. [0631

QUALITY Amplifiers and Microphone Equipments for Hire or Permanent Installation.—Harmony House, 116, Cambridge Rd., Southport. [8307

AMPLIFYING Equipment, P.A. vans for sale or hire. Booklet on request.—Alexander Black, Ltd., 55, Ebury St., S.W.1. Sloane 6129. [0599

PUBLIC Address Contractors Can Hire P.A. Vans, loud speakers, microphones and equipments of all types from Hire Dept., Grampian Reproducers, Ltd., Kew Gardens, Surrey. Tel.: Richmond 1175-6-7. [0618

## NEW MAINS EQUIPMENT

V.

VORTEXION Supply G.P.O., B.B.C., L.P.T.B. Why not you?

ALL Models Super Shrouded, primaries screened and tapped, 200-250v., filaments C.T.

ANY Model Fitted 5v. or 6.3v. Filaments if Required.

500-0-500 150 m.a., 4v. 4a., 2.5a., 4v. 2a., 4v. 2a., 4v. 2a., 35/-; 400 or 350v., same price.

500-0-500 120 m.a., 4v. 4a.. 4v. 2.5a., 4v. 1-2a., 4v. 1-2a., 28/-; 400v. or 450v., same price.

425-0-425 150 m.a., 4v. 8-10a., 4v. 2.5a., 4v. 1a.. 4v. 1a., 32/-.

350-0-350 120 m.a., 4v. 4a., 4v. 2.5a.. 4v. 1-2a., 21/-; with extra 4v. 6a., 25/-.

350-0-350 75 m.a., 4v. 2.4a., 4v. 1-2a.; 18/-.

250-0-250 60 m.a., 4v. 2-4a., 4v. 1-2a.; 15/-.

AUTO Transformers, 100-120 to 200-240v., 80 watts, 11/-; 120 watts, 14/6; 200 watts, 21/-; 250 watts, 25/-; 300 watts, 28/-; 500 watts, 47/6.

W.W. Q.A. Output Transformer; 21/-.

MICROPHONE Transformers. in heavy magnetic shielding; 12/6.

CHOKES.—30h. 60 m.a., 7/6; 7-13h. 120 m.a., 12/6; 30h. 150 m.a., 15/-; 25h. 150 m.a., 21/-.

TRANSFORMERS and Chokes to Any Specification.

CAR Battery Charger, 6 and 12v., 1½ to 2 amperes; 30/- complete.

VORTEXION, Ltd., 182, The Broadway, Wimbledon. London, S.W.19. Telephone: Liberty 2814. [8469

## NEW LOUD-SPEAKERS

SINCLAIR Speakers for All Types.—Alma Grove, Copenhagen St., N.1. [0603

BAKERS' New Corner Horn Speakers, surplus bargains and triple cone conversions, from 29/6. —Leaflets free from Bakers Selhurst Radio, 75, Sussex Rd., South Croydon. [8434

## LOUD-SPEAKERS

### SECOND-HAND, CLEARANCE, SURPLUS, ETC.

ROLAS for 6/11; G12's, 47/6; ½d. stamp for lists.—Shippers, 18, Corporation St., Manchester. [0606

VAUXHALL UTILITIES, 163a, Strand, W.C.2.—Rola G12 P.M. speakers, 62/6; G12 energised, 50/-; with transformers, brand new. [8467

3,000 Speakers from 5/6 each, P.M. and energised, 4in. to 14in., including several Epoch 18in. —Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0591

EPOCH 18in., rebuilt, any field, £5; with A.C. equipment, £2 extra; Epoch 14in. mains energised, 70/-; fitted A.C., 30/- extra; several 10in., 12in., and 15in. energised and P.M.s, from 20/-.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0628

*About M.C.L.S. in P.A.*

# MOVING COIL LOUDSPEAKERS

are important factors in successful Public Address. The large Grampian range of M.C. Speakers includes types for all purposes. They all employ powerful Permanent Magnets of Nickel aluminium. The cone, of Curvilinear design, prevents the generation of sub-harmonics up to high outputs. The response curve is very smooth. The gently rising characteristic gives an essential clarity.

Two types particularly useful for Public Address are the K.80 and K.11. The former is a 12" Speaker which handles 12 watts. Magnetic flux of 10,000 lines. Impedance 15 ohms. Price 95/-. The K.11 is a 9" Speaker handling 6 watts. High flux of 9,500 lines gives extremely high conversion efficiency. Price 45/-.

Cabinets for these units can be supplied for any purpose. The two cabinets illustrated here for use in churches, are an example.

We are also manufacturers of Microphones of all kinds, Amplifiers, and all forms of P.A. equipment—portable and permanent.

**STOP PRESS**

Latest Grampian Public Address Installations include:—

F.A. AND RUGBY LEAGUE CUP FINALS
Wembley Stadium

LAUNCHING OF H.M.S. PRINCE OF WALES
at Birkenhead by H.R.H. the Princess Royal

**GRAMPIAN**

ACTUAL MANUFACTURERS OF
*"Everything in P.A."*

GRAMPIAN REPRODUCERS LTD.
Kew Gardens, Surrey. *Tel.: Richmond 1175.*

## LOUD-SPEAKER CONVERSIONS

EPOCH Domino Loudspeakers can Now be Converted to the Famous "NEW" Super Cinema Speaker with 14in. Cone, replacement for all Epoch speakers, also output transformers; a genuine Epoch hand-made cone for any speaker.

HALFORD DISTRIBUTORS, Ltd., 31, St. George St., W.1. Sole manufacturers of Epoch loudspeakers and the famous Halford Phantom radio set. [0632

## TRANSMITTING APPARATUS

BARGAINS.—Clearance of surplus stock, valves, components, transmitters, receivers; stamp for lists.—Fox Radio, Thrussington, Leicester. [8461

A.C.S. RADIO, specialists in short-wave apparatus, communication receivers, including Hallicrafters, National and R.M.E. transmitting equipment, valves and components.—Send for free catalogue to A.C.S. Radio, 16, Gray's Inn Rd., W.C.1. Holborn 9894-5. G2NK. Technical Manager. [0550

G5NI.—The oldest and largest distributors of amateur equipment, transmitting and receiving; short-wave catalogue, 1½d.; G5NI 70-page Manual, 7½d., post free; authorised direct distributors for Collins, National, R.M.E., Thordarson, Hammerlund, Bliley, Taylor, Eimac, etc., etc.—44, Holloway Head, Birmingham. [0531

## CABINETS

A CABINET for Every Radio Purpose.

CONVERT Your Set into a Radiogram at Minimum Cost; surplus cabinets from noted makers under cost of manufacture (undrilled); 30/- upwards; motors at wholesale prices.

"FIT-A-GRAM" Cabinet, 31 × 17 × 15; 21/-.

UNDRILLED Table Console and Loud-speaker Cabinets, from 3/6.

INSPECTION Invited; photos loaned to country customers.

H. L. SMITH and Co., Ltd., 289, Edgware Rd., W.2. Tel.: Pad. 5891. [0485

CLEARANCE Sale!! — Radiogram and television cabinets; prices slashed! 10 gns. worth for 50/-! 5 gns. worth for 20/-!—Write, wire, 'phone or call. Cameo Co., 23, Denmark St., W.C.2. (Tem. 5900.) [8353

## DYNAMOS, MOTORS, ETC.

D.C.-A.C. Convertors, motors, all voltages, for sale and wanted.—Easco, 18w, Brixton Rd., S.W.9. [0558

ALL Types of Rotary Converters, electric motors, battery chargers, petrol-electric generator sets, etc., in stock, new and second-hand.

A.C.-D.C. Conversion Units for Operating D.C. Receivers from A.C. Mains, 100 watts output, £2/10; 150 watts output, £3/10.

WARD, 46, Farringdon St., London, E.C.4. Tel.: Holborn 9703. [0518

ELECTRADIX Rotary Converters for A.C. Radios on D.C. mains; alternators 50 to 500 cycles; mains motors and motor generators for 1 to 600 cells; petrol engines and switchgear.—218, Upper Thames St., London, E.C.4. [0619

## RECORDING EQUIPMENT

ALL Recording Discs and Materials in Stock; tracker units, £4/7/6; recording motors, £3/17/6.—Write for further details, Will Day, Ltd., 19, Lisle St., W.C.2. [0595

PROFESSIONAL Recording Block, ribbon microphone, 14 watt amplifier, mixing panel, polished recording desk with V.G. tracker recording motor and switching, guaranteed perfect; £45.—Liverpool Sound Studios, 83a, Bold St., Liverpool. [8463

## VALVES

ALL Types of American Tubes in Stock of Impex and Arcturus makes at competitive prices.

WE Can Also Supply a Full Range of Guaranteed Replacement Valves for Any British non-ring, American or Continental type at an appreciably lower price.

SEND for Lists of These, and also electrolytic condensers, line cords, resistances, etc.

CHAS. F. WARD, 46, Farringdon St., London, E.C.4. Tel.: Holborn 9703. [0452

AMERICAN Valves, first grade, by leading makers, guaranteed, popular types; standard base 5/6; octal base 6/6; 6L6G, 7/6—General Radio Distributors, 309, Falloden Way, N.W.11. [0626

2/9 R.C.A. American Valves, 50 popular types; also National Union, Hytron; also British non-ring valves, cheapest in Britain; ½d. stamp for revised lists.—Shippers, 18, Corporation St., Manchester. [0607

METROPOLITAN RADIO SERVICE.—Special offer: American valves, in makers' cartons, 3/- each; Octals, 3/6 each; American valves, first grade, in all types; trade supplied.—1021, Finchley Rd., N.W.11. Speedwell 3000. [0436

## COMPONENTS

### SECOND-HAND, CLEARANCE, SURPLUS, ETC.

R

RADIO CLEARANCE, Ltd.

ALL Lines Previously Advertised Still Available.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1. Holborn 4631. [8470

## COMPONENTS—SECOND-HAND, CLEARANCE, SURPLUS, ETC.

PREMIER SUPPLY STORES

PLEASE See Our Displayed Advertisement on this page. [0400

RADIO SUPPLIES, 22, Faraday Av., Manchester, 8. Tel.: Col. 1261.

JUST Arrived from America, the latest "Automatic" 5-valve car radio, tone control, 3 watts output, one-hole fixing, complete with all accessories, in sealed carton, 6-volt; £4/8/6.

A FEW Only, 5-valve, medium and long wave car radios, with 5 push buttons, all accessories, in sealed carton, 6-volt; £5.

THE Latest "Travler" 6-valve High Fidelity Car Radio, Triode output, 6 push buttons, easy installation, complete with all accessories, all in sealed carton; £5/7/6.

OVERHEAD Car Aerials, heavily chromium plated, 11/- each; 12-6-volt dropping resistors, 3/6 each.

BRAND New Belmont 1st Grade American Valves, boxed, types available, 75, 78, 606, 43, 42 and 18E; 2/9 each, 2/6 each in dozen lots.

BRAND New Philco Boxed Valves, O1A and 38E; 2/6 each, 2/3 in dozens.

RECORD Rectifiers, 350-0-350 volt, 120 ma., boxed; 2/9 each, 2/6 each in dozen lots.

MIDGET Type Band Pass Coils, medium and long wave; 9d. each, 6/- a dozen.

AMERICAN Goat Cans, complete with base; 2/6 a dozen.

RADIO Record H.F. Pentodes, equivalent to Mazda AC/VP1, boxed, 3/- each, 2/9 each in dozens.

BRAND New Large Decca Mains Transformers, 200-250-volt primary, secondary 350-0-350 volt 120 ma., 4-volt 2.5-amp., 4-volt 6-amp., 13-volt 2-amp.; 3/- each, 2/6 each in dozens.

BRAND New Magnavox and Blue Spot Mixed Output Transformers; 2/- each, £1/2/6 a dozen.

MIDGET Tubular 8 mfd. Condensers, 500 volt working, finest make; 1/- each, 10/6 a dozen.

ROLA G12 P.M., with large multi ratio output transformer, boxed, £2/12/6; Rola 8in. P.M.s, with large matching transformer, boxed, 9/- each.

THREE Only, G.E.C. A.C. All-wave 5, 1938 model, shop soiled only, listed at £11/2/6; for £4 each.

THREE Only, Ever Ready 5-valve A.C. All-wave, 1938 model, shop soiled only, listed at £11/11/5; for £4 each.

CENTRALAB Pots, long spindle, less switch, sizes available 10,000, 50,000 and ½ meg.; 1/- each, 11/- a dozen.

B.I. 50 mfd. 50-volt Condensers, 1/- each, 10/- a dozen; Plessey cardboard cased electrolytics, 6+6+4+2+25 mfd., 450 volt working, 1/- each, 10/6 a dozen.

A SUITABLE Amount Must be Included to Cover Postage.

SPECIAL Trade List for Dealers Radio Supplies.

SIX Only, Ever Ready Band Pass 3 battery sets, 1937-38 model, complete, in perfect order, slightly shop soiled; £1/10. [8464

RYALLS RADIO, 280, High Holborn, London, W.C.1, offer new goods, post free.

ELLIPTICAL Speakers, Celestion, suitable Ekco replacements, 750 and 1,250 ohms, less transformers, speech 25 ohms, new, handle 8 watts, carry up to 120 m.a.; 5/6 each.

SPECIAL Offer of New Ferranti Transformers, AF5, OMP6, AF6c, OPM16c, 8/9; AF17c, B2 chokes, 6/9; OPM8 (15-1), AF10, B8 chokes, OPM1c, 4/9; all each.

GARRARD AC Induction Type AC7a Gramophone Motors, with pick-ups complete, 200-250v., 12in. turntable and unit plate, auto. stop, speed regulator, new; 32/6 each.

WEARITE 110 k.c. I.F.'s with Top Trimmers, 1/6 each; sets band pass air core superhet coils, ex Halycon, screened chassis type, 4/9 set five; 110 kc. with coil details.

B.I. Tubular 4mf. 200v., 6d. each or 4/- dozen; B.I. 0.05, 1/3 dozen, 7/9 gross; B.I. 0.25 mf. tubulars, 2/- dozen, 4/6 per three dozen.

SPEAKERS, pairs, brand new, elliptical cone speakers, made by first class firm, quality of reproduction outstanding, push-pull pentode transformer, fields 325 ohm for smoothing choke, 8,600 as bleeder, circuit available, handle 10-15w.; 14/- pair.—Ryalls Radio, see above. [8374

VAUXHALL UTILITIES, 163a, Strand, W.C.2.—Ask for free list; metal rectifiers, HT10, 10/-; HT9, 9/-.

VAUXHALL.—Hivac valves, all types; full range of pick-ups, from 11/-.

VAUXHALL.—T.C.C. dry, 8 mfd., 2/6; 600v. aluminium containers; T.C.C. 600v. dry, cardboard containers, 8 mfd., 1/9. [8468

LONDON'S CENTRAL RADIO STORES.—See last two issues for bargains still available. New lines this week.

"WAVE-CLIPPER Products" Television Aerials in copper or special metal alloy, 25/-; special anti-interference radio aerial, copper rod model, 12/6; both complete with fixing brackets.

MORSE Keys, made to A.R.P. reserves specification, 3/6; Senior model, chrome finish, 7/6; Ferranti meters; moving coil, 2½in. type, 1 m.a., 25/-; other ranges also, cheap; call and see above and many other bargain clearance lines. London's only walk round radio shop.

LONDON'S CENTRAL RADIO STORES, 23, Lisle St., Leicester Sq., London, W.C. Gerrard 2969. [8472

# PREMIER
## ★ RADIO ★

### PREMIER L.T. TRANSFORMERS

All Primaries tapped 200-250 volts. Between winding insulation 1,000 volts.

| | | | |
|---|---|---|---|
| 2.5 v., 8 amps CT | 8/6 | 2.5 v., 3a+6.3 v., 3a | 10/- |
| 4 v., 5 „ CT | 9/6 | 2.5 v., 3a2.+5 v., 8a | 14/6 |
| 5 v., 3 „ CT | 8/6 | **3,000 volt Test Type** | |
| 6.3 v., 3 „ CT | 8/6 | 2.5 v., 5a CT ... | 11/6 |
| 7.5 v., 3 „ CT | 8/6 | 2.5 v., 10a CT. ... | 12/6 |
| 10 v., 3-4 „ CT | 11/6 | 10 v., 4a CT. ... | 14/6 |
| 12 v., 4-5 „ CT | 11/6 | | |

**Auto Transformers.** Step up or down A.C. Mains between 100—250 volts. 60 watts, 9/-; 100 watts, 11/6.

### PREMIER SHORT-WAVE KITS

Complete to the last detail including all Valves and coils, as well as theoretical and wiring diagrams and lucid instructions for building and working. Each kit is supplied with a steel Chassis and Panel and uses plug-in coils to tune from 13 to 170 metres.

| | |
|---|---|
| 1 Valve Short-Wave Receiver or Adapter Kit ... | 17/6 |
| 1 Valve Short-Wave Superhet Converter Kit ... | 20/- |
| 1 Valve Short-Wave A.C. Superhet Converter Kit | 22/6 |
| 2 Valve Short-Wave Receiver Kit ... ... ... | 25/- |
| 3 Valve Short-Wave Screen Grid and Pentode Kit | 58/6 |

### PREMIER 3-BAND S.W. KITS

11-86 metres without coil changing. Complete Kits of Parts with Valves and Circuits. One Valve, 12/6; Two Valver, 19/6.

**PREMIER U.S.A. QUARTZ TRANSMITTING CRYSTALS.** 7 mc. Band, 10/- each, with Calibration Certificate. Enclosed holder and Base, 3/-.

**PREMIER SHORT-WAVE COILS,** 4- and 6-pin types, 13-26, 22-47, 41-94, 78-170 metres, 1/9 each, with circuit. Special set of S.W. Coils, 14-150 metres, 4/- set, with circuit. Premier 3-band S.W. coil, 11-25, 19-43, 38-86 metres. Suitable any type circuit, 2/6.

**UTILITY** Micro Cursor Dials, Direct and 100.1 Ratios, 3/9.

**PREMIER** Short-Wave Condensers, all-brass construction, with Trolitul insulation. 15 mmf., 1/6; 25 mmf., 1/7; 40 mmf., 1/9; 100 mmf., 2/-; 160 mmf., 2/3; 250 mmf., 2/6.

**TROLITUL DOUBLE SPACED TRANSMITTING CONDENSERS.** 15 mmf., 2/9; 40 mmf., 3/6; 100 mmf., 4/-; 160 mmf., 4/6.

**NEW TROLITUL SPLIT STATOR CONDENSERS,** 50×50 mmf., 10/6.

**COIL FORMERS,** 4- or 6-pin low-loss, 1/- each.

**AMERICAN VALVES.** We hold the largest stocks of U.S.A. tubes in this country and are sole British Distributors for **TRIAD** High-grade American Valves. All types in stock. Standard types, 5/6 each. All the new Octal Base tubes at 6/6 each, 210 and 250, 8/6 each.

**EUROPA MAINS VALVES,** 4 v. A.C. Types, A.C./H.L., A.C./L., A.C./S.G., A.C./V.M.S.G., A.C./H.P., A.C./V.H.P., A.C./P., and 1 watt D.H. Pentodes, all 4/6 each. A.C./Pens., 1.J., 5/6; A.C./P.X.4, 6/6; Oct. Freq. Changers, 8/6; Double Diode Triodes, 7/6; Triode H. ex. Freq. Ch., 8/6; Tri. Grid Pen., 10/6; 3½-watt D.H. Triode, 7/6. 350 v. and 500 v. F.W. Rect., 5/6. 13 v. 2 amps. Gen. Purpose Triodes, 5/6; H.F. Pens. and Var.-Mu. H.F. Pens., Double Diode Triodes, Oct. Freq. Changers, 7/6 each. Full-wave and half-wave Rectifiers, 5/9 each.

### MATCHMAKER UNIVERSAL MODULATION TRANSFORMERS

Will match any modulator to any R.F. load. 50 watts, 17/6; 150 watts, 29/6; 300 watts, 49/6.

**MATCHMAKER UNIVERSAL OUTPUT TRANSFORMERS.** Will match any output valves to any speaker impedance. 11 ratios from 13 : 1 to 80 : 1. 5-7 watts, 13/6; 10-15 watts, 17/6; 20-30 watts, 29/6. Send for full details.

**PREMIER AC/DC MOVING IRON METRES.** 2½in. diam. Flush Mounting. All ranges. 10 m.a., 30 m.a., 50 m.a., 100 m.a., 250 m.a., 500 m.a., 5/9 each.

**AMMETERS.** 1, 3, 5, 10 or 30 amps., 5/9 each.

### PREMIER 1939 HIGH FIDELITY AMPLIFIERS

**A New Complete Range of 7 High Fidelity P.A. Amplifier for A.C. or A.C./D.C. Mains operation.**

| | Kit of Parts with Valves. | Completely Wired and Tested. |
|---|---|---|
| 3-watt A.C. Amplifier ... | £2 0 0 | £2 15 0 |
| 3-watt A.C./D.C. „ ... | £2 0 0 | £2 15 0 |
| 6-watt A.C. „ ... | £5 5 0 | £6 0 0 |
| 8-10-watt A.C./D.C. „ ... | £4 10 0 | £5 5 0 |
| 15-watt A.C. „ ... | £5 15 0 | £7 0 0 |

Black Crackle Steel Cabinet 15/- extra.

**NEW PREMIER SELF-POWERED RF TUNING UNIT,** incorporating a Var.-Mu pentode amplifier followed by a power grid detector. Designed for high-fidelity reception. Wave range 200-500 and 800-2,000 metres. £4 - 9 - 6 complete with valves.

**IGRANIC** insulated midgets jacks 1/6 each. Plugs 1/3.

**CONDENSERS. CARDBOARD ELECTROLYTIC,** 4 mf. or 8 mf. 500 v., 1/6 each; 8+4 mf. 500 v., 2/3; 8+8 mf. 500 v., 2/6; 4+4+4 mf. 500 v., 2/6; 16+8 mf. 500 v., 3/6.

**TUBULAR METAL CAN ELECTROLYTICS** by famous makers. 4 or 8 mf. dry, 500 v., 2/6 each. 8 mf. wet, 450 v., 2/3. 8 mf. 650 v., Peak dry, 4/-.

Orders 5/- and over sent Post Free. Under 5/- please add 6d. postage.

**Have you had our 1939 Catalogue, Handbook and Valve Manual? 90 pages of Radio Bargains and Interesting Data. Price 6d.**

**ALL POST ORDERS TO: Jubilee Works, 167, Lower Clapton Road, London, E.5.** *Amherst 4723.*

**CALLERS TO: Jubilee Works, or our NEW PREMISES, 169, FLEET STREET, E.C.4.** *Central 2833*

**or 50, High Street, Clapham, S.W.4.** *Macaulay 2331*

## COMPONENTS—SECOND-HAND, CLEARANCE, SURPLUS, ETC.

COLLARO A.C./D.C. Record changers, 200-250, plays eight 10in. or 12in. records, mixed, also incorporates repeater and rejector; limited quantity, £5/5, in sealed cartons.

HENRY'S, 72, Wellington Ave., Stamford Hill, N.15. Stamford Hill 2907. [8216

SOUTHERN RADIOS Bargains.—Sale now proceeding of hundreds of bargain lines, goods previously advertised still available.—Southern Radio, 46, Lisle St., London, W.C.1. Gerrard 6653. [8236

MAINS RADIO DEVELOPMENT COMPANY Offer immediate delivery, carriage paid; call mornings; telephone Tudor 4046; stamp for list 227; Transatlantic all-wave tuning packs now available from stock, stamp for details.

DUBILIER Mica Tag Condensers, 0.00005, 0.0001, 0.0002, 0.0003, 0.0005 mfd.; 3d., 2/6 dozen.

AMAZING Resistor Bargain, N.S.F. ½, 1 and 2 watt, new, marked, colour coded resistors, 20 different useful sizes in parcel; 50 for 2/6 only.

CLIX Unused Chassis V-holders, 5-pin, 7-pin, 3d. each; all American sizes, 6d. each; best sleeving, 1½d. yd.; T.C.C. metal can 8 mfd., 600v. dry electrolytics, 2/3.

TUBULAR Condensers, 400 volt working, wire ends, best make, 0.0001-0.05 mfd., 4d.; 0.1 mfd., 4d.; 0.25, 0.5 mfd., 6d.

CENTRALAB Latest Potentiometers, long standard spindle, unused, all sizes, 5,000 ohms, 2 megohm., 2/-; with mains switch, 2/3.

POLAR Midget Latest Three-gang Condensers, screened, trimmers, ¼in. spindle, 0.0005 mfd., 110 k/c tracker, unused; 2/6.

ERIE One Watt, colour coded, unused resistors, any size, 50 ohms to 5 megohms, your selection, 3d., 2/6 dozen; two watt, 6d.

MAINS RADIO DEVELOPMENT COMPANY, 4-6, Muswell Hill Rd., London, N.6. Tudor 4043. [8457

FOLT Disposal Below Cost, quantity of new receivers, amplifiers, feeder units, chokes, condenser banks, Ferranti and other transformers, etc.; state requirements; write, 'phone or call.—W. T. Rickards, 17, Heathfield Rd., King's Heath, Birmingham. Highbury 1804. [8390

## REPAIRS AND SERVICE

"SERVICE With a Smile."

AMERICAN Valves, spares, linecords, rewinds; repairers of all types of American and British receivers.—F.R.I., Ltd., 22, Howland St., W.1. Museum 5675. [0434

HIGH Class Radio Service, any model, collected and delivered; quotations per return; finest components only used.

ANGLO-AMERICAN RADIO (and MOTORS), Ltd., Albion House, 59, New Oxford St., London, W.C.1. 'Phone: Tem. 3231. [8474

BAKERS.—Send your next speaker repair, any make, to the pioneer manufacturers, Bakers Selhurst Radio, South Croydon. [8435

LOUD-SPEAKER Repairs, British, American, any make, 24-hours service; moderate prices.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0590

GUARANTEED Repairs Any Transformers, choke, motor armature, converter, dynamo, etc.; keenest prices, immediate quotation, prompt dependable service.—See below.

L.T.P. (LONDON TRANSFORMER PRODUCTS, Ltd.), Willesden, N.W.10. Willesden 6486 (3 lines). [6892

MAINS Transformer Service. Repairs, rewinds, or construction to specification of any type, competitive prices and prompt service.—Sturdy Electric Co., Dipton, Newcastle-on-Tyne. [0516

METROPOLITAN RADIO SERVICE.—Guaranteed repairs to American and British receivers; American valves, service parts and rewinds; trade supplied.—1021, Finchley Rd., N.W.11. Speedwell 3000. [0435

SCOTT-SESSIONS REPAIR SERVICE.—All types of receivers overhauled, rebuilt, repaired, including American communication sets, W.W. Monodials, All-wave Super-Seven, Variable Selectivity IV., etc.

SCOTT-SESSIONS REPAIR SERVICE, popular for 15 years from Land's End to John-o-Groats; van collection London area; immediate, courteous and skilled attention to every instruction.

SCOTT-SESSIONS REPAIR SERVICE. Exchange Works, Muswell Hill, N.10. Tudor 4101-2. [7497

REPAIRS to Moving Coil Speakers a Speciality; cones and coils fitted, fields altered; prices, including eliminators, quoted; loud speakers, 4/-; L.F. and output transformers, 4/-, post free; guaranteed satisfaction; trade invited, estimates free; prompt service.—Loud-Speaker Repair Works, 5, Balham Grove, London. Battersea 1321. [0394

## SITUATIONS VACANT

AIR MINISTRY.

CIVILIAN Wireless Instructors Required.

VACANCIES Exist for Civilian Wireless Instructors at the Electrical and Wireless School, Royal Air Force, Cranwell, Lincs. The commencing rate of pay is £4 a week inclusive which may be increased to £4 5s. a week after a short period of satisfactory service. Candidates must be capable of lecturing and must have a sound knowledge of electrical principles and their application to radio and low-power electrical engineering. Applications should be addressed to the Commanding Officer, Electrical and Wireless School, Cranwell, Lincs, giving full particulars as to previous experience, age, etc. Candidates will be required to appear before a Selection Board at the School for interview and test. The test will include the giving of a lecture on any subject which may be chosen by the candidate, involving the principles of modern radio. Lecturing sequence and style are most important. [0571

*"Radio Laboratory Handbook." Price 8s. 6d. net. Post free 9s.*

# ELECTRADIX

KEYS. Govt. Morse Keys. Type KBSL. Polished wood base, massive brass pivot bar, tungsten spring-mounted contacts and base lamp. Do your training on one of these, only 7/6. Walters Service bakelite enclosed transmit Key, for high voltage, 10 amp. contacts, good bridge key, 10/6. Super Keys. Brown's Car-Patrol, double acting, beautifully made and balanced totally enclosed, cast Ali. cover, for H.T. 21/-. Massive Navy type Ship Keys, 25/-.

A.R.P. WARDENS and Others.—Portable Army Field 'Phones in case, transmits code and speech. Unbreakable Govt. Cable, 55/- mile. Portable Day and Night Signal Lamps. Aldis Trigger or Lucas Key. Army type, battery only. Hand or tripod. Mains Bells for warnings, D.C. or A.C. Hand Generators for field or emergency transmitters (D.C.), 800 volts and 1,500 volts. Morse Inker Recorders for use when 'phone unsuitable, makes code message record on paper tape. Walnut cased, as new, portable type, spring driven, with tapper key and meter indicator, £7. Open G.P.O. type with tape reel in base, £5/10/-. A few soiled and incomplete, with perfect spring drive, 35/-. Dry cells work Inkers, no radio needed. G.P.O. Sounders, 7/6. 3-colour light switch box with Morse Key fitted for code signals, 4/6. D.C. Generators. 500, 800 and 1,500 volts. Electric Motor Pumps, will deliver 120 galls. per hour 6ft. on a 12 v. car battery or mains, A.C. or D.C., £3/7/6. Electric Blowers, Foul Air Exhausters and Porthole Fans.

BELLS! BELLS! for all purposes. House, wall and table 'phone bells for battery and mains. Single stroke per push Works Bells. Call Buzzers. Fire Alarm Bells and Pushes. First-class British, cheap.

D.C. GENERATORS, 120 watt 12 volts 10 amps., with vee pulley, 35/-. ¼ Kw. 12/16 volts 30 amps., with vee pullet, 45/-. Shunt wound.—110 volts 1 amp., 15/-; 200 volts ½ amp., 17/6; 200 volts 1½ amp., 26/-.

D.C. WINDMILL GENERATORS, totally enclosed, ball-bearing, start charging at 300 revs., 6 to 12 volt, 8 amps., 35/-. 25 amps., 45/-.

AS NEW E.D.C. ROTARY CONVERTERS.—For A.C. Receivers, on D.C. 230 v. A.C. output. In silence cabinet, with filter. All sizes in stock from 50 watts to sets for televisors of 450 watts.

D.C. MAINS MOTOR GENERATORS. D.C./D.C. 220 v. to 30 v. 10 amps., £7/10/-. M.G. Crompton, D.C./D.C., 100 volts to 17 volts 6 amps., £4/7/6. 200 v. to 16 v. 5 amps., £5. Estro M.G. ditto to 6 volts ½ amp., 45/-. Motor Generators for all outputs up to 60 amps.

MOTORS FOR A.C. MAINS. Midget 3lbs. 220 volts, 10/6. 1/60 H.P. with pulley, Type 50, 1,500 revs., 18/6. Enclo. Induction 1/10 H.P. Motors, 2,500 revs., 35/-. Self-starting, ¼ H.P., 1,425 revs., 55/-, etc., etc. D.C. Mains Motors, 1/40 H.P., 110 v., 12/6; 220 v. series Type K.B., 1,750 revs., 15/-. Ditto, G.E.C., 230 v., 2,000 revs., 16/-. Croydon 1/12 H.P., 110 v., 18/-. 220 v. shunt, 1,700 revs., 22/6.

AIR COMPRESSORS for Spraying, Cleaning, Inflation, etc. Foot operated, 37/6. Electric, No. 1 size, £5/15/-. No. 2. Twin-cyl., £7/10/-. Refrig. Compressors, 35/-.

BATTERY CHARGING ON A.C. MAINS.

The A.C. NITNDAY will keep your battery fit without attention. Model N/A6, 100/250 volts A.C. and D.C., 6/8 volts ½ amp., 15/-. Model N/B6, 100/250 volts to D.C., 6/8 volts 1 amp., 25/-. Model N/C6, 100/250 volts to D.C., 6/8 volts 2 amps., 35/-. Model N/D12, 100/250 volts to 12 volts 1 amp., 32/-. Ditto, 12 volts 2 amps., with 6-volt tap, 55/-. 5 amp., £4/10/-.

MICRO-AMMETERS for Valve Voltmeters, etc. 0 to 50 micro-amps, full scale 50 mV. moving coil. 1,000 ohms flush panel, 2½in. dial, 40/-.

METERS. Genuine Weston model 354. Central zero 1 to 15 amps., pol. mag. dead beat. Flush panel, 2½in. dial, nickel or black. Sale price 5/6. Mounted in solid mahog., 2in. sq., 9/-. Hoyt CZ mov. coil milliammeters. 25-0-25 m.a., 10/-. Weston 5, 30 and 50 m.a. mov. coil milliammeters, 17/6. Turner 100 m.a. panel meter for transmitters with shunt switch, 18/6. 2,000 Switchboard Meters, all sizes and ranges, from 5/6.

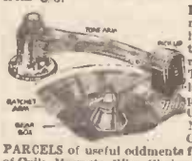


LOW COST SOUND RECORDING. Blanks now 3/3 per dozen. Electric FEIGH set has ball-bearing centre gear box and geared traverse rod. Set with Tracking Gear, Pick-up and Tone-arm fitted diamond, 37/6. Tracker gear only, less Pick-up and Tone-arm, £1 21/6. Diamond Cutter Needles fit all pick-ups, 7/6. 6in. Blank Discs, 3/3 dozen. Complete Acoustic Sets de Luxe, 18/-; No. 2, 10/6; Junior Type, 5/6 each. Complete.

PARCELS of useful oddments for the Experimenter who wants a junk-box of Coils, Magnets, Wire, Chokes, Condenser, Switches, etc., mostly ex-W.D. parts worth a lot more than 10 lbs., 7/-, or 7 lbs. for 5/-, post free. British Isles only.

**Dynamos, Alternators, Rotaries & Motors all Sizes.**

*Send for Radio-Electrical-Scientific Illus. "W."*

**ELECTRADIX RADIOS**

**218, UPPER THAMES STREET, LONDON, E.C.4**

*'Phone: Central 4611*



**THE INSTITUTE OF WIRELESS TECHNOLOGY**

(Founded in 1925. Incorporated).

**PROFESSIONAL MEMBERSHIP**

**The advantages of professional membership are open to all qualified wireless engineers.**

*Full information, with syllabus, may be obtained from the Secretary, Institute of Wireless Technology, 4, Vernon Place, Southampton Row, London, W.C.1. 'Phone: Holborn 4879.*



# WELBURN 12 WATT AMPLIFIER

Designed and built for consistent hard work. Reliability and first-class performance on both speech and music were our first consideration.

NOTE THESE POINTS:

No distortion; No hum; Cool running; Small Input (only 0.008v); Output 12 watts; Overall Gain 116dBs; No pre-amplifier required. Linear Amplification combined with Level Response; Mike-Gramo-Mixer; Mazda Valves; Self-contained in dust-proof steel case.

**A SOUND JOB FOR ALL *SOUND* PURPOSES**

***Write for 12 pp. descriptive brochure***

RETAIL PRICE **£14**

**WELBURN RADIO LTD.**

QUEENSWAY TEAM VALLEY

GATESHEAD-ON-TYNE


## SITUATIONS VACANT

AIR MINISTRY.

DIRECTORATE of Signals (Civil Aviation).

APPLICATIONS are invited for appointments as Civilian Wireless Operators at Air Ministry Civil Aviation Wireless Stations.

APPLICANTS, who should not have reached their 40th birthday on June 1st, 1939, should preferably possess the First Class Postmaster-General's Certificate or the Air Operator's Certificate in Wireless Telegraphy and have had experience of radiotelephony, direction-finding and maintenance work. Operators will be required to serve at any Air Ministry Civil Aviation station at home or abroad. At present there is only one station situated outside the United Kingdom manned temporarily by Air Ministry staff.

SALARY is at the rate of 67/- a week, rising by annual increments for approved service to 112/- a week inclusive. Should candidates be required to serve abroad, appropriate additional allowances would be paid.

THE first two years of service will constitute a probationary period and confirmation of appointment will be contingent on an operator passing an examination in all phases of his work.

POSTS will be Unestablished, i.e., non-pensionable in the first instance. A proportion of the total staff is pensionable, however, and subject to the existence of vacancies in the permanent staff operators may be considered for establishment according to their seniority, conduct and ability, provided that the probationary period has been satisfactorily completed.

REQUESTS by Postcard for Forms of Application should be addressed so as to reach the Under-Secretary of State, Air Ministry (S.1.e.), Kingsway, London, W.C.2, not later than May 24th, 1939.

SELECTED Applicants will be required to attend at the Air Ministry for interview on June 12th and 13th, 1939.

NO application will be considered unless the applicant states that he will be able to attend on either of these dates.

NO other arrangement regarding interview can be entertained. [8425

AIR MINISTRY.

AERONAUTICAL Inspection Directorate.

VACANCIES Exist for Unestablished Appointments as Examiners in the W.T. and Instrument Branches. Qualifications:—

APPLICANTS for Vacancies in Instrument Branch must have Good General Education, theoretical knowledge of physics, and training in light engineering or instrument making. Candidates should be able to read drawings, understand specifications, and use micrometers and other types of measuring instruments. If necessary, preference will be given to candidates having a good knowledge of thermometry and optical and pressure measuring instruments.

APPLICANTS for Vacancies in W.T. Branch having the Following Qualifications will receive Preference: Good general education, sound technical knowledge of high-frequency engineering equal to City and Guilds Final Examination in Radio Communications, practical knowledge of modern W.T. and electrical equipment. Candidates should be able to read drawings, understand specifications, and use micrometers and other measuring instruments.

SUCCESSFUL Candidates will be given a Period of Training in Inspection, as applied to these subjects, not exceeding three months.

DURING Training, candidates will be regarded as on probation and paid at the rate of £184 a year; on satisfactory completion of the training course they will be appointed as Examiner and paid at £246 a year, rising by increments of £12 if service is satisfactory to £337, except that the starting salary for entrants below the age of 24 years will be reduced by £12 for each year below that age.

SUBSISTENCE Allowance, at the rate of £1/5 weekly, is payable whilst under training to married men (and others with certain dependents) who normally reside outside the training centre.

SALARIES are paid Monthly in Arrear.

CANDIDATES Must be Prepared to Serve in Any Part of the United Kingdom, and be willing to fly as observers in connection with their duties.

NORMAL Age Limits, 21-50 years; candidates between 50-55 years will be considered if they have had previous inspection experience.

CANDIDATES who, on interview, fail to qualify for the Examiner Grade may be considered for:—

ASSISTANT Examiner.—Salary scale, £184-£10-£246.

ASSISTANT Examiners do not undergo Training, but are appointed direct to an A.I.D. station; they may later become eligible for promotion to Examiner on attaining the requisite standard of efficiency, provided they are willing to undertake the obligations required of Examiners as above.

APPLICATION Must Be Made on Form 786, copies of which can be obtained on application (by postcard only) to:—

THE UNDER-SECRETARY OF STATE, Air Ministry (1,C.S./Rec.40), Berkeley Sq. House, Berkeley Sq., W.1. [8466

WIRELESS Operator Seeks Relief Voyages, direct employ, experienced.—Box 9745, c/o *The Wireless World*. [8452

SHORTHAND-TYPIST, familiar wireless technical terms, wanted in London; quick and accurate.—Apply Box 9712, c/o *The Wireless World*. [8449


# BULGIN
## QUALITY PRODUCTS

# VIBRATORS

| | |
|---|---|
| L.T. | H.T. |
| L.T. | H.T. |
| L.T. | H.T. |
| L.T. | H.T. |
| L.T. | H.T. |
| L.T. | HT |
| L.T. | H.T. |
| L.T. | H.T. |
| L.T. | H.T. |

4,6,12 V. INPUT OUTPUT 250 V.

12/6 FOR CAR-RADIO TRANSMITTERS MOBILE P.A. etc. 15/-

Products of modern unending research, these new Vibrators have long working life and high efficiency in every way, yet both prices and size are reduced. A Bulgin H.T.-from-L.T. Vibrator for all requirements.

**RANGE OF *NEW* HIGH-QUALITY LOW-PRICE MODELS**

| *List No.* | *Input* | *Watts* | *Base* | *Price* |
|---|---|---|---|---|
| HTV16 | 4V. | 15-18W. | 5 pin ‡ | 12/6 EACH |
| HTV18 | 6V. | ,, | ,, ‡ | |
| HTV20 | 12V. | ,, | ,, ‡ | |
| HTV22 | 24V. | ,, | ,, ‡ | |
| HTV24 | 32V. | ,, | ,, ‡ | |
| HTV15 | 4V. | ,, | 5 pin + | 15/- EACH |
| HTV17 | 6V. | ,, | ,, + | |
| HTV19 | 12V. | ,, | ,, + | |
| HTV21 | 24V. | ,, | ,, + | |
| HTV23 | 32V. | ,, | ,, + | |

+ Synchronous—U.S.A.-type 5-pin base.
‡ Non-Synchronous. Base as above.

TRANSFORMERS for all voltages, to give 150V. or 250 V. max. output, and up to 60mA., are available, from 10/6 to 17/6.

AND ALL ACCESSORIES:

HOLDERS for above Vibrators, chassis type, List No. V.H.55, 6d. each.

**ALL SERVICE REPLACEMENTS:**

Stock types (other than those above), and Special Types at a few days' notice, meet all needs. Fit BULGIN *RELIABLE* REPLACEMENT VIBRATORS

**COUPON**

CUT OUT & SEND THIS *NOW*

To: A. F. BULGIN & CO. LTD.,
ABBEY ROAD,
BARKING, ESSEX.

Please send me a selection of leaflets of new products *with all details of, and circuits for, new Vibrators.* 1½d. stamp encl.

NAME .....

ADDRESS .....

W.W.18539 .....

A. F. BULGIN & CO. LTD., BARKING, ESSEX
RIPpleway 3474-5-6


*"Wireless Direction Finding," Third Edition. Price 25s. net. Post free 25s. 9d.*

## SITUATIONS VACANT

TELEPHONE and Radio Testers or Servicemen Required.—Write, stating age, education, experience and salary required, to Siemens Brothers & Co., Ltd., Telephone Installation Section, Woolwich, S.E.18. [8459

WAYLEAVE Officer Required, undertake reorganisation of feeders, must have practical knowledge wiring, able take charge, supervise, instruct wiremen; knowledge wayleave office procedure; experienced obtaining wayleaves.

RELAY Wiremen, thoroughly experienced, required.—Write fully, Western Wireless Relay Co., City Rd., Bristol. [8451

RADIO Engineer With Experience in Design and Construction of Modern Super Heterodyne Receivers, capacle of working without supervision. All applications will be replied to.—Box 9769, c/o *The Wireless World*. [8454

RADIO Valve Engineer (Junior) Required by Radio Valve Manufacturers in North London, some knowledge of valves and set circuits essential.—Write, stating age, experience, training and salary required, to Box 9765, c/o *The Wireless World*. [8453

VACANCY Exists for a Television Engineer, experienced in the design and production of modern Television Receivers, good prospects for the right man.—Apply in confidence, stating age, experience and salary required, to Box 9786, c/o *The Wireless World*. [8465

DRAUGHTSMAN (Male, Aged 18-26 years) required, with some experience in detail work and knowledge of workshop practice.—Write, stating nationality, age, education, experience and salary expected, to Siemens Brothers and Co., Ltd., 715, Telephone Department, Woolwich, S.E.18. [8450.

VACANCIES Exist for Civilian Wireless Instructors at the Electrical and Wireless School, Royal Air Force, Yatesbury, Wilts. The commencing rate of pay is £4 a week inclusive. which may be increased to £4 5s. a week after a short period of satisfactory service. Candidates must be capable of lecturing and must have a sound knowledge of electrical principles and their application to Radio and low-power electrical engineering. Applications should be addressed to the Commanding Officer, No. 2 Electrical and Wireless School, Yatesbury, Wilts, giving full particulars as to previous experience, age etc. Candidates will be required to appear before a Selection Board at the School for interview and test. The test will include the giving of a lecture on any subject which may be chosen by the candidate involving the principles of modern radio. Lecturing sequence and style are most important. [0616

## ELECTRIC DRY SHAVERS

REMINGTON. Rand, Shavemaster, Packard and Casco. —Trade enquiries to Leonard Heys, 36, Henry St., Blackpool. [0633

ELECTRIC Dry Shavers, A.C./D.C., 200-50 volts. "Minute Man," list price £2/10, our price £1/10. complete with leatherette case, one year's guarantee; send for details; trade supplied.
HENRY'S, 72 Wellington Ave., Stamford Hill, N.15. 'Phone: Stamford Hill 2907. [8441

## MISCELLANEOUS

PHOTO-ELECTRIC Cells, brand new; 15/- each.—Universal, 221, City Rd., London, E.C.1. [8370

G.P.O. Engineering Dept (no experience required); commencing £3/13 per week; age 18-23; excellent prospects; free details of Entrance Exam. from B.I.E.T. (Dept. 574), 17-19, Stratford Place, London, W.1. [8396

EVERY Radio Dealer Who is Not a Regular Reader of "The Wireless and Electrical Trader" should send his trade card at once for a specimen copy and full details of the "Trader" Services. "The Wireless and Electrical Trader" has the widest influence, the largest weekly circulation, and is read by all the leading manufacturers and traders. Trade only, 15/- per annum, post free.—Published at Dorset House, Stamford St., London, S.E.1. [0615

"ENGINEER'S Guide to Success" Shows How to Qualify in Television Radio Engineering and Servicing, sound recording, wireless communication, etc., by studying at home with the T.I.G.B. Write to-day for this Great Guide—free—which gives full particulars, contains the world's widest choice of engineering courses—over 200—and alone gives the regulations for qualifications such as A.M.I.E.E., A.M.I.R.E., A.M.I.T.E., A.M.I.W.T., C. and G., etc. Training until successful guaranteed.—The Technological Institute of Great Britain, 82, Temple Bar House, London, E.C.4. (Founded 1917. 20,000 successes.) [8409

## PATENTS

"PRACTICAL Hints on Patents," free on application. —The Imperial Patent Service, First Avenue House, High Holborn, W.C.1. Preliminary consultation free. [0481

THE Proprietor of the Patents Nos. 461128, for "Scanning Device for Television," and 461417, for "Improvements in or relating to a system for facsimile transmission and reception," is desirous of entering into arrangements by way of licence and otherwise on reasonable terms for the purpose of exploiting the same and ensuring their full development and practical working in this country.—All communications should be addressed in the first instance to Haseltine Lake and Co., 28, Southampton Buildings, Chancery Lane, London, W.C.2. [8420

## BUSINESSES AND PROPERTY FOR SALE, TO BE LET, OR WANTED

"THE Wireless and Electrical Trader" is an essential part of the equipment of every Wireless Trader; its pages reflect the very latest turn of trade events, and it is read by all the leading dealers and manufacturers, for particulars of businesses offered or wanted. By subscription to the trade only, 15/- per annum, post free.—Send your trade card for specimen copy to Dorset House, Stamford St., London, S.E.1. [0614

*Said Peter Augustus De Wet,*

*"I've found out what's wrong with this set.*

*For all it's requiring*

*Is just a rewiring.*

*And this time, with FLUXITE you bet!"*

**See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for 30 years in Government works and by leading engineers and manufacturers. Of Ironmongers—in tins, 4d., 8d., 1/4 and 2/8.**
**Ask to see the FLUXITE SMALL-SPACE SOLDERING SET—compact but substantial—Complete with full instructions, 7/6.**
**Write for Free Book on the art of "SOFT" SOLDERING—and ask for leaflet on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE.**

TO CYCLISTS! Your wheels will NOT keep round and true unless the spokes are tied with fine wire at the crossings AND SOLDERED. This makes a much stronger wheel. It's simple—with FLUXITE—but IMPORTANT

# THE FLUXITE GUN

is always *ready* to put *Fluxite* on the soldering job instantly. A little pressure places the right quantity on the right spot and one charging lasts for ages.
**Price 1/6 or filled 2/6**

ALL MECHANICS *WILL* HAVE

# FLUXITE

IT SIMPLIFIES *ALL* SOLDERING

FLUXITE LTD., Dept. W.W., DRAGON WORKS BERMONDSEY ST., S.E.1

# RADIOMART

G5NI (HAM) LTD.

## THE SHORT-WAVE SPECIALISTS

**SPECIAL OFFER!!!**
Fully shrouded Transformers by America's largest manufacturer. While they last.
All 230 v. primary and fully impregnated.

| | |
|---|---|
| T28708—375/375 v. 150 m/A., 6.3V5A. 2.5V5A. 5V3A. | 15/- |
| T19610—350/350 v. 150 m/A., 2.5V6A. 2.5V2A. 5V3A. | 12/6 |
| T7236—375/375 v. 120 m/A., 6.3VCT. 4A. 5V3A | 10/6 |
| T7326—350/350 v. 100 m/A., 6.3VCT. 3A. 5V3A | 8/6 |
| T7307—350/350 v. 80 m/A., 6.3VCT. 3A. 5V3A | 7/6 |
| T7000—320/320 v. 80 m/A., 6.3V4A. 5V3A | 7/6 |
| T6926—320/320 v. 80 m/A., 2.5V6A. 5V3A | 7/6 |
| T46919—10V4A Primary Tapped 110—250 v. | 5/6 |
| T1113AB—110/230 v. 500 watt Auto Transformer | 29/6 |

The following chokes are interleaved and impregnated.

| | |
|---|---|
| T7007—250 m/A., 135 ohms, 20-8 Hy., cadmium shrouded | 12/6 |
| T7007A—150 m/A., 250 ohms, 30-12 Hy., cadmium shrouded | 12/6 |
| 100 m/A., 20 Hy., 500 ohms, unshrouded | 4/11 |
| 60 m/A., 15 Hy., 250 ohms | 1/11 |

HEAVY DUTY TRANSFORMER for models, bells, etc., 6 v. 3 a., 2/3.
4 mf., 1,500 v. test 500 v. wkg. oil filled condensers, 2/-.
HEAVY DUTY Mains Transformer, worth 45/-. 350-350. 150 m/A. 4 v. 2.5 a. CT. 4 v. 6 a., CT, 12/6; 300-300 v. 80 m/A., 4 v. 3 a., CT. 4 v. 2 a., CT, 6/6. Moving Coil Speech Transformers, 1/11.
GANG CONDENSERS with Airplane Dial, 8 and 80-1. Cost 35/-. Few only. 4/11. Utility, 7/6. Microdials, 3/9.
W.B. 8in. PERMANENT MAGNET SPEAKERS AT ONE-THIRD COST Extension Type (no Transformer), 8/11. Standard Type (with Transformer), 10/6. Energised 8", 1,200 ohms with Transformer, 6/11.
PUSHBACK Wire, 6 yds., 6d., heavy, 9d. Resin-cored Solder, 6ft., 6d.; Screened Flex, single, 6d. yd.; twin 9d. yd. Assorted Solder Tags, 6d. packet. Humdimmers, 6d. each.
Centralab pots, all sizes, 1/6; switched, 2/-; tubular glass fuses, 2d.
Milliammeters, 0.25 m.a., upwards, 5/9; Super, 6/9.
OUR NEW 66-PAGE MANUAL, packed full of valuable information. Post Free, 7½d.
THE NEW RAYMART CATALOGUE shows dozens of New Short-wave Components and is yours for 1½d. post free.
VALVES.—A complete range of replacements, showing a saving of over 50 per cent. Quotations on receipt of types required. Quantity Discounts to Service Engineers. TRADE enquiries for communication equipment solicited.

**RADIOMART** *Telephone: MIDland 324*
G5NI (Birmingham) Ltd.
44, HOLLOWAY HEAD, BIRMINGHAM

Mains Transformers as specified for *The Wireless World* High Quality Communication Receiver Type WW51—45/-.

**W. BRYAN SAVAGE LTD.**
*Westmoreland Rd., London, N.W.9. 'Phone: Colindale 7131*

## TUITION

RADIO Training.—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0611

WIRELESS.—Complete training, Marine, Broadcast and Television. Posts waiting. Mod. fees. Boarders taken. Approved college, prosp.—Dept. W., London Radio College, Grove Park Rd., London, W.4. (Chi. 3244.) [0580

## BOOKS, INSTRUCTION, ETC.

AMERICAN Valve Data.—The new 200-page Raytheon Valve Data Book gives full characteristics and applications of all types of American valves; invaluable to all servicemen; post free, 2/3; abroad, 3/-.—Leonard Heys, 36, Henry St., Blackpool. [0594

"THE Wireless World" Diary for 1939 contains 77 pages of facts, formulæ and general information of the kind that is always wanted but is difficult to follow. Also a list of the most important European Broadcasting Stations and short-wave stations of the world. Twelve pages of circuit diagrams of receivers, amplifiers and units. —By post 1/7 from Iliffe & Sons, Ltd., Dorset House, Stamford St., London, S.E.1.

"FOUNDATIONS of Wireless." By A. L. M. Sowerby, M.Sc. Second edition. An elementary textbook on receivers. Deals fully with the construction of wireless sets, valves, and the process of detection. Price 4/6 net. By post 4/11, from Iliffe and Sons, Ltd., Dorset House, Stamford Street, London, S.E.1.

"RADIO Data Charts." By R. T. Beatty, M.A., B.E., D.Sc. Second edition. A series of Abacs providing most of the esential data required in receiver design and enabling problems to be solved without having recourse to complicated mathematical formulæ. Price 4/6 net. By post 4/10, from Iliffe and Sons, Ltd., Dorset House, Stamford St., London, S.E.1.

"ELEMENTARY Principles of Wireless Telegraphy and Telephony." By R. D. Banguay. Revised by O. F. Brown, B.Sc. Third edition (1930). The standard textbook for wireless students and beginners. Deals with the whole subject of wireless telegraphy and telephony, avoiding too technical a treatment of the problems involved. Well illustrated. Price 7/6 net. By post 8/-, from Iliffe and Sons, Ltd., Dorset House, Stamford St., London, S.E.1.

# Pamphonic
## AMPLIFIERS

Pamphonic Reproducers Ltd. (*Associated with PYE Ltd.*)
45, St. Pancras Way London, N.W.1.
'Phone: EUSton 1727.

## AUSTRALIA

**RADIO AND SOUNDFILM ENGINEER** (now in London) with long experience in construction and sales-organisation of Radio and Soundfilm Apparatus, will co-operate with important firm.—Box 295, STRAND HOUSE, W.C.2.

## INDEX TO ADVERTISEMENTS


| | PAGE |
|---|---|
| Air Ministry | |
| Air Service Training, Ltd. | |
| Ambassador Radio Works | |
| Armstrong Manufacturing Co. | 4 |
| Automatic Coil Winder Co., Ltd. .... Inside Front Cover | |
| Belling & Lee, Ltd. | 2 |
| Birmingham Radiomart G5N1 | 8 |
| Box 295 | 8 |
| British Institute of Engineering Technology | |
| British Insulated Cables, Ltd. | 2 |
| British Rola, Ltd. | |
| British Thomson-Houston Co., Ltd. | |
| Bulgin, A. F., & Co., Ltd. | 7 |
| Edison Swan Electric Co., Ltd. | |
| Electradix Radios | 7 |
| Fluxite, Ltd. | 8 |
| Grampian Reproducers, Ltd. | 5 |
| Institute of Wireless Technology | 7 |
| London Radio Supply Co. | |
| McClure, John, Ltd. | |
| Mullard Wireless Service Co., Ltd. | 1 |
| Pamphonic Reproducers, Ltd. | 8 |
| Partridge, N. | |
| Peto-Scott Electrical Instrument (Holdings), Ltd. | 4 |
| Premier Supply Stores | 6 |
| Salford Electrical | |
| Savage, W. Bryan, Ltd. | 8 |
| Sound Sales, Ltd. .... Inside Front Cover | |
| Standard Telephones and Cables, Ltd. | 3 |
| Stratton & Co. | |
| Taylor Electrical Co., Ltd. | |
| Universal Electric | 4 |
| Volgt Patents, Ltd. | 2 |
| Webbs Radio | |
| Welburn Radio, Ltd. | 7 |
| Westinghouse Brake & Signal Co. | |


Printed in England for the Publishers, ILIFFE AND SONS LTD., Dorset House, Stamford Street, London, S.E.1, by The Cornwall Press Ltd., Paris Garden, Stamford Street, London, S.E.1. "The Wireless World" can be obtained abroad from the following: France: W. H. Smith & Son, 248, Rue Rivoli, Paris; Hachette et Cie, Réaumur, Paris, and branches; Messageries Dawson, 4, Rue de Faubourg Poissoniere, Paris. BELGIUM: W. H. Smith & Son, 74-75, Boulevard Adolphe Max, Brussels. AUSTRALIA: Gordon & Gotch, Ltd., Melbourne (Victoria), Sydney (N.S.W.), Brisbane (Queensland), Adelaide (S.A.), Perth (W.A.), and Launceston (Tasmania). NEW ZEALAND: Gordon & Gotch Ltd., Wellington Auckland, Christchurch and Dunedin. INDIA: A. H. Wheeler & Co., Bombay, Allahabad and Calcutta. CANADA: Imperial News Co., Toronto, Winnipeg and Vancouver; Benjamin News Co., Montreal; Gordon & Gotch, Ltd., Toronto. SOUTH AFRICA: Central News Agency, Ltd.; Wm. Dawson & Sons (S.A.), Ltd., Cape Town. UNITED STATES: The International News Co., New York.

*SIXTH EDITION—REVISED AND ENLARGED*

# HANDBOOK of TECHNICAL INSTRUCTION for WIRELESS TELEGRAPHISTS

by H. M. DOWSETT
(M.I.E.E., F.Inst.P., M.Inst.R.E.)

***This standard handbook, completely revised and enlarged, is planned primarily for the use of wireless operators, whether prospective or actual. It is virtually a complete theoretical course for students wishing to qualify for the Postmaster-General's Certificate of Proficiency***

CONTENTS INCLUDE:

**The Electric Charge and the Condenser—The Condenser in Practice—Direct Current and Ohm's Law—Scalar and Vector Quantities and Curve Plotting—Primary Batteries—Accumulators—Magnetism—Electro Magnetism—Self-Induction—Dynamo Electric Machines—Measuring Instruments—Switchboards and Switchgear—Alternating Current Effects, and Vector Diagrams—Alternating Current Fundamental Formulae—Alternating Current Generators—Alternating Current Motors and Transformers—Damped Oscillations—Commercial Types of Spark Transmitter—Aerials and Radiation—Simple Receiver Circuit and Crystal Detector—Thermionics and the Various Applications of the Valve—Depth Sounding—Valve Transmitters—Wavemeter and Transmitter Adjustment—Theory of Valve Receiver Circuits—Valve Receivers—Short Wave Aerials and Apparatus—Marine Direction Finders—Marine Audio Relay Service—Distress Call Apparatus—Lifeboat and Emergency Outfits—Trawler Apparatus—Maintenance of Marine Radio Installations and Possible Faults.**

618 *pages, including Comprehensive Index and* 578 *Illustrations.*

## NOW ON SALE

PRICE 21/- By post 21/9

**Foreign Postage 22/-**

*Obtainable from leading booksellers or direct from the Publishers:*

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

# Inside Information

The international chessboard is now presenting such a complicated series of problems that no one brain can follow all its ramifications. INSIDE INFORMATION is designed to enable you to keep in touch.

This feature is conducted with the strictest regard for the responsibility that attaches to it. It is not planned from a sensational angle, but at a time when there is so much intrigue, so many forces that work in different directions, it is essential to have someone in control of the most reliable sources of information—through diplomatic channels and its own intelligence department.

INSIDE INFORMATION plays no part in communicating *rumour*. Its purpose is to give people a really reliable set of facts from which they can draw their own deductions and to set out those facts in such a form that their relation to each other is easily seen.

*Every day in the*

# DAILY SKETCH

DESIGN FOR C-R OSCILLOSCOPE

# The Wireless World

6D.

## THE PRACTICAL RADIO & TELEVISION JOURNAL

Thursday, May 25th, 1939.

No. 1,030. Vol. XLIV. No. 21.

Copyright. Registered as a Newspaper for transmission in the United Kingdom.
Entered as Second Class at the New York, U.S.A., Post Office.

# GECALLOY

## RADIO CORES

GREATER MAGNIFICATION

ROBUST CONSTRUCTION

HIGHER SELECTIVITY

SIMPLE ADJUSTMENT

REDUCED COSTS

SMALL SIZE

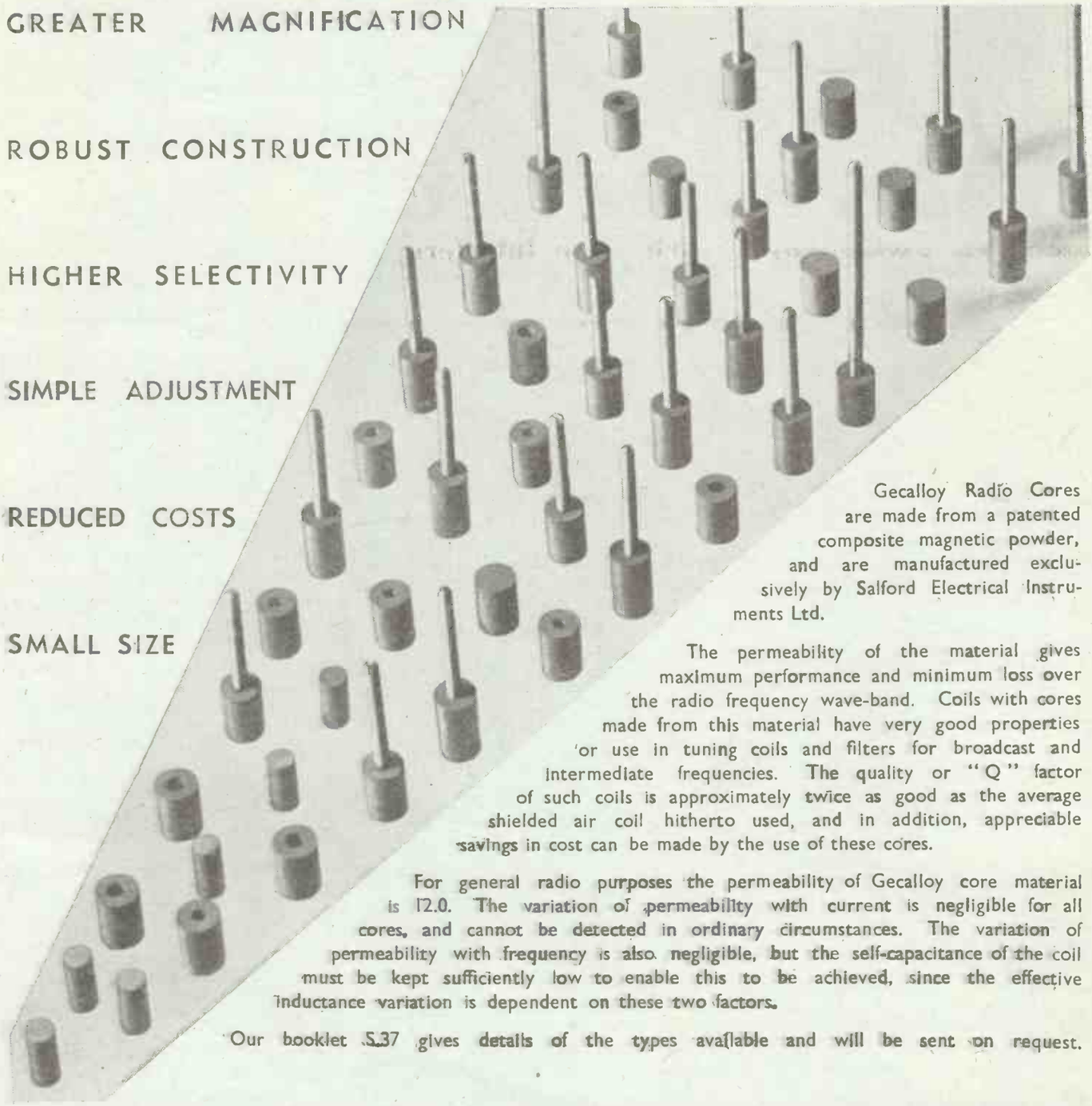

Gecalloy Radio Cores are made from a patented composite magnetic powder, and are manufactured exclusively by Salford Electrical Instruments Ltd.

The permeability of the material gives maximum performance and minimum loss over the radio frequency wave-band. Coils with cores made from this material have very good properties for use in tuning coils and filters for broadcast and intermediate frequencies. The quality or "Q" factor of such coils is approximately twice as good as the average shielded air coil hitherto used, and in addition, appreciable savings in cost can be made by the use of these cores.

For general radio purposes the permeability of Gecalloy core material is 12.0. The variation of permeability with current is negligible for all cores, and cannot be detected in ordinary circumstances. The variation of permeability with frequency is also negligible, but the self-capacitance of the coil must be kept sufficiently low to enable this to be achieved, since the effective inductance variation is dependent on these two factors.

Our booklet S.37 gives details of the types available and will be sent on request.

## SALFORD ELECTRICAL INSTRUMENTS LTD.

PEEL WORKS, SALFORD, 3 Telephones: BLAckfriars 8888 (3 lines) Telegrams and Cables: "SPARKLES, MANCHESTER"

PROPRIETORS: THE GENERAL ELECTRIC Co. Ltd., OF ENGLAND

The Wireless World

THE PRACTICAL RADIO JOURNAL

29th Year of Publication

No. 1030. THURSDAY, MAY 25TH, 1939. VOL. XLIV. No. 21.

Proprietors : ILIFFE & SONS LTD.

Editor :
HUGH S. POCOCK.

Editorial,
Advertising and Publishing Offices :
DORSET HOUSE, STAMFORD STREET,
LONDON, S.E.1.

Telephone : Waterloo 3333 (50 lines).
Telegrams : "Ethaworld, Sedist, London."

COVENTRY : 8-10, Corporation Street.
Telegrams : "Autocar, Coventry." Telephone : 5210 Coventry.

BIRMINGHAM :
Guildhall Buildings, Navigation Street, 2.
Telegrams : "Autopress, Birmingham." Telephone : 2971 Midland (5 lines).

MANCHESTER : 260, Deansgate, 3.
Telegrams : "Iliffe, Manchester." Telephone : Blackfriars 4412 (4 lines).

GLASGOW : 26B, Renfield Street, C.2.
Telegrams : "Iliffe, Glasgow." Telephone : Central 4857.

PUBLISHED WEEKLY. ENTERED AS SECOND CLASS MATTER AT NEW YORK, N.Y.

Subscription Rates :
Home and Canada, £1 10s. 4d. ; other countries, £1 12s. 6d. per annum.

*As many of the circuits and apparatus described in these pages are covered by patents, readers are advised, before making use of them, to satisfy themselves that they would not be infringing patents.*

## CONTENTS

| | Page |
|---|---|
| *Editorial Comment* | 479 |
| *Aerial Masts : Practical Hints on Design and Construction* | 480 |
| *Cathode-ray Oscilloscope* | 483 |
| *Problem Corner* | 486 |
| *Television Programmes* | 486 |
| *Footless Valves* | 487 |
| *News of the Week* | 489 |
| *AF Transformers Simplified* | 491 |
| *"The Wireless World" DC Mains Super : Construction and Adjustment* | 493 |
| *McMichael Model 382 : Test Report* | 496 |
| *Club News* | 497 |
| *Unbiased* | 498 |
| *The B.B.C.'s German News Bulletins* | 499 |
| *Letters to the Editor* | 500 |
| *Random Radiations* | 501 |
| *Recent Inventions* | 502 |

# *EDITORIAL COMMENT*

## Suppression of Television Interference

### *"We've Got to be Prepared"*

THE British Standards Institution has recently issued a "Specification for Radio-interference suppression for Automobiles and Stationary Internal-combustion Engines." This is the fifth technical specification dealing with radio interference to be issued by this Institution. The preparation of all these publications represents an enormous amount of time and effort devoted not only by the Institution itself but by the representatives of the numerous co-operating organisations.

In issuing this new specification, the B.S.I. states that "it must not be inferred from the publication of the specification that all motor cars will immediately be fitted by the makers with suppression devices. In the event of relevant legislation coming into force, however, the guidance given in the specification will be of considerable assistance to the industry, and in the meantime car owners and designers will find much in the specification to interest them."

### *Wasted Effort*

It seems to us an extraordinary state of affairs that so much work should have been undertaken before there was any guarantee that it would ultimately serve a useful purpose. At present it is to be regarded as of "interest" to car owners and designers but it will only become of practical value "in the event of relevant legislation coming into force."

We have often expressed the view that it would be expecting too much to hope that manufacturers generally would go to the trouble and cost of fitting suppressing devices to interfering sources unless it becomes compulsory to do so, nor do we think it fair that any manufacturer should be asked to take such action on a voluntary basis whilst his competitors may decline to do so.

If suppression is to be effective it must be made compulsory, yet the years go by and no progress in this direction is apparent. As time goes on the complexity of the problem of legislation increases.

Is it not time that the matter should be reviewed to see if it is not possible to introduce some simple form of legislation which will render interference in principle illegal without waiting for the evolution of an ideal and comprehensive statute? We should then justify the work of the B.S.I. on the principle that "we've got to be prepared."

## B.B.C. Statements

### *Quote the Authority*

ON another page we print a letter from a correspondent who, though not completely in agreement with our views, expressed in a recent issue, on B.B.C. news bulletins, is clearly with us in believing that the source of Government-inspired statements should be given. In this matter we would indeed go farther than our correspondent, and urge that the origin of every statement should be made clear. This rule should apply even to the admittedly trivial and often innocuous items that are often broadcast in such a way as to suggest that they emanate from the B.B.C. itself. The fact that the Corporation appears sometimes to assume the responsibility of admonishing its listeners has surely done much to incalcate in simple minds the idea that it is speaking with Government authority.

# Aerial Masts

## PRACTICAL HINTS ON DESIGN AND CONSTRUCTION

By R. H. WALLACE

WHEN one has taken considerable trouble in the erection of mast and aerial, it is very disappointing to find the whole brought down by some extra-strong gale, yet there are many points to be considered if this is to be avoided. In the present article only the more ordinary types of receiving aerial and mast will be considered, and the formulæ and calculations will be omitted, enough data being given to enable reasonable alterations to be made to the typical designs set out, while at the same time the various factors affecting the strength and endurance of the mast will be indicated.

The first step in the actual design of an installation is a decision on the type and dimensions of the conductor; this may seem to be the wrong end to start at, but, in fact, it is only when this has been done that it is possible to evaluate the horizontal pull on the mast, which must be known before the necessary strength of the top section in particular, and the structure as a whole, can be determined. Since the more ordinary types are here being discussed, there will in general be one or two wires only, the total length being limited by the G.P.O. regulations and by the space at one's disposal. There will not usually be more than 70ft. or so of single, or about half this length of double, conductor, so that the weight and wind loading will be about the same for the two. This length is accordingly the longest that will be considered, and it can be taken that where double wire is used it will be precisely equivalent to twice the length of single wire so far as the effect on the pole is concerned.

### Choice of Wire

The size and material of which the conductor is made do not admit of much variation, as for such short spans the strength of hard-drawn copper wire is more than sufficient. This will, therefore, be the obvious choice on the grounds of its superior conductivity. The minimum cross-sectional area is fixed by the tensile stress it may be called on to bear, which should not be allowed to exceed 30,000 lb. per sq. in. The stresses are dependent on several factors; one not often recognised as important by the amateur being actually the most likely to cause failure, namely, the stress due to the weight of the wire. Some readers may call to mind the well-worn maxim, "No power on earth, however great, can stretch a cord, however fine, into an horizontal line which shall be absolutely straight. The stress increases very rapidly as the sag becomes small, and, unless a sufficient amount of this is left when erecting, the wire may break should temperature changes or ice formation cause additional stress.

A good practice is to leave a sag of from two to four per cent. of the span, the smaller figure if the erection be performed on a cold, frosty day, and the latter if the day be warm. With a sag of two per cent. the pull on the supports will be about six times the actual weight of the wire. This is not an over-cautious figure; indeed, if this were all, the design would be a very simple matter. Actually, if this figure alone were taken into consideration when designing the mast, then it would almost certainly collapse when sleet and frost produced a coating of ice on the conductor. The weight of such a coating is not easy to estimate, but, fortunately, we can profit by the experience of others with transmission and telephone lines. These are usually designed on the assumption that they may have to bear an additional loading equal to that due to a radial thickness of ¼in. of solid ice. Coatings much thicker than this do occur, but they are rarely as dense as solid ice, and this figure makes all the allowance that is necessary. This extra loading due to ice may make the pull on the mast several times greater than before, and the necessary allowance must be made, together with those for the other stresses. It should be noted, however, that by increasing the sag sufficiently it is possible to reduce the stress to any desired value above the weight of the wire, but this is hardly worth while, as the side pressure on the mast due to gales may reach as high a figure as the stress due to ice loading at two per cent. sag.

*WHILE most readers are likely to possess a good knowledge of the electrical properties of aerials, it is probably true to say that comparatively few have full knowledge of mechanical design and construction. This article treats of this aspect of the subject, and deals with the erection of both steel and wooden masts. Detailed constructional information is given for masts of various heights and diameters.*

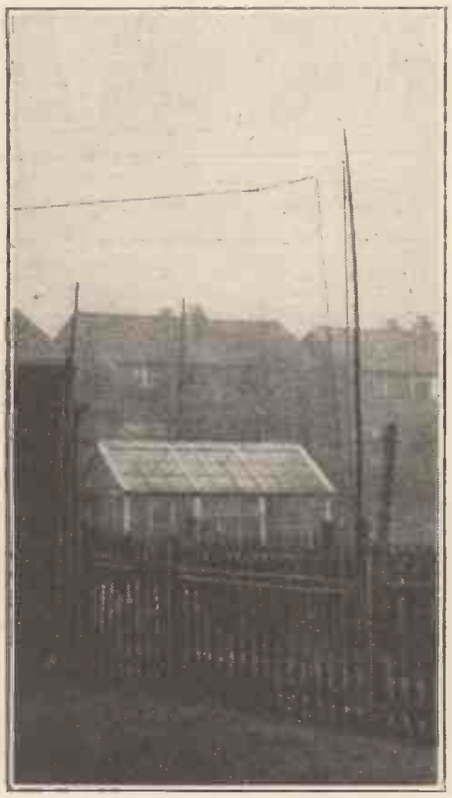

The effect of using an unduly thin mast without guys to counteract the wire pull is clearly visible in the case of the foreground mast.

### Wood or Steel?

Table I, showing the pull due to a sag of this amount, with different spans, and for two common sizes of wire, is included to show the great effect this factor has on the design of the mast. Calculations show that, for a span of 70ft., the tensile stress approaches the safe maximum for 7/26 copper wire; there is, however, no reason why this should not be used, though the use of 7/22 will give a greater factor of safety, and is recommended by the writer for all spans over 40ft. It should be noted that the use of insulated wire will result in the stress under ice conditions becoming much greater than is the

TABLE I

Horizontal Pull with Various Spans of Copper Wire with a sag of 2 per cent. (in lb.)

| Size of wire | Span of Conductor 30ft. | 40ft. | 50ft. | 60ft. | 70ft. | Remarks |
|---|---|---|---|---|---|---|
| 7/22 | 3.1 | 4.1 | 5.2 | 6.2 | 7.3 | Normal. |
| 7/22 | 22.8 | 30.6 | 39.2 | 45.8 | 53.6 | With ¼in. radial thickness of ice. |
| 7/26 | 1.3 | 1.7 | 2.1 | 2.5 | 2.9 | Normal. |
| 7/26 | 19.6 | 26.4 | 33.6 | 39.4 | 46.2 | With ¼in. radial thickness of ice. |

**Aerial Masts—**

case with bare wire, as, among other things, the diameter is larger. In practice it has been found that the use of 7/26 insulated wire cannot be advocated for spans over 30ft., and it is, in the writer's opinion, just as satisfactory to use bare wire.

In this article attention is being confined to tubular steel masts and their wooden equivalents, and the first point to be decided is which to use. There is not any overwhelming advantage possessed by one or the other, and the question has to be settled mainly on the score of relative cost and availability. The wooden pole is cheaper and often more easily available, it has grown to withstand much the same sort of stresses as are now required of it, and has a naturally correct taper; also its ability to bend through considerable angles without damage is in its favour. On the other hand, wood has undoubtedly a shorter life than a properly protected steel mast, and larger factors of safety have to be allowed in the case of the former, since the presence of defects of uncertain magnitude is always probable. The steel mast is capable of an indefinite life if properly protected, and there is less uncertainty about its strength, nor will this be likely to depreciate greatly during its life, as is the case with wood. Steel tubes are not readily available in the lengths which are likely to be required, however, and there is the problem of jointing to be considered; also tapered tubes are not within the realm of economical manufacture for this purpose, and two or more diameters will have to be used, since the bending moment increases as the base of the pole is reached.

### Methods of Staying

Self-supporting masts have the merit of neatness, and, if properly erected, are very attractive, but they have the disadvantage that they need to be much stronger, and also there is no means of counteracting the pull of the wire, with the result that they can never be quite straight at the top. The greatest difficulty lies in their erection and in the maintenance of vertical alignment. In general, they are more costly and more difficult to erect, but there are many circumstances where their other good points outweigh these drawbacks, and they may be adopted with success.

A compromise between the entirely unstayed and the fully guyed mast can be made by using spreaders at the middle of the pole, guy wires being attached at the top and brought over these to the foundation of the mast. This arrangement avoids the necessity of a large piece of ground, and, since in many cases it is desired to take advantage of the full length of garden available, enables the use of a longer aerial without having to fix stays on other people's property.

The pull on the top is not the only stress the mast has to bear; it must be strong enough not to break in erection, when the weight is largely borne by the section nearest the base, while there is the wind pressure on the pole itself to be allowed for, besides that on the wire. Calculations show that, in the sizes likely to be used for receiving installations of the domestic sort, the service stresses will be greater than those encountered in the course of erection, so that if it is strong enough to bear the former under the worst conditions, there will be no likelihood of failure. It might be added that the weather conditions envisaged in the designs that follow are those probable in the British Isles, but it must not be forgotten that there are some places where these assumptions will not be valid and would result in too low a factor of safety.

TABLE II

Recommended Maximum Lengths of "Steam Quality" Tube, free and with various Spans of 7/22 copper wire at 2 per cent. sag, and with ¼in. radial thickness of ice.

| Nominal size of tube, in. | Outside diam. of tube, in. | Maximum length in feet | Tube lengths with aerial spans as under: 30ft. in feet | 40ft. in feet | 50ft. in feet | 60ft. in feet | 70ft. in feet | Length of lower tube in feet (see note) |
|---|---|---|---|---|---|---|---|---|
| 1 | 1.309 | 17 | 8 | 6½ | 5½ | 4½ | 4 | — |
| 1¼ | 1.650 | 22 | 13½ | 11½ | 10 | 9 | 8 | — |
| 1½ | 1.882 | 24 | 16 | 14 | 12 | 11 | 10 | — |
| 1¾ | 2.116 | 25 | 18 | 16 | 14½ | 13 | 12 | — |
| 2 | 2.347 | 26 | 18½ | 17 | 16 | 15 | 14 | 12 |
| 2¼ | 2.587 | 28 | — | — | — | — | — | 13 |
| 2½ | 2.960 | 32 | — | — | — | — | — | 14 |

Note.—Length when carrying the maximum length of tube ½in. smaller in diameter.

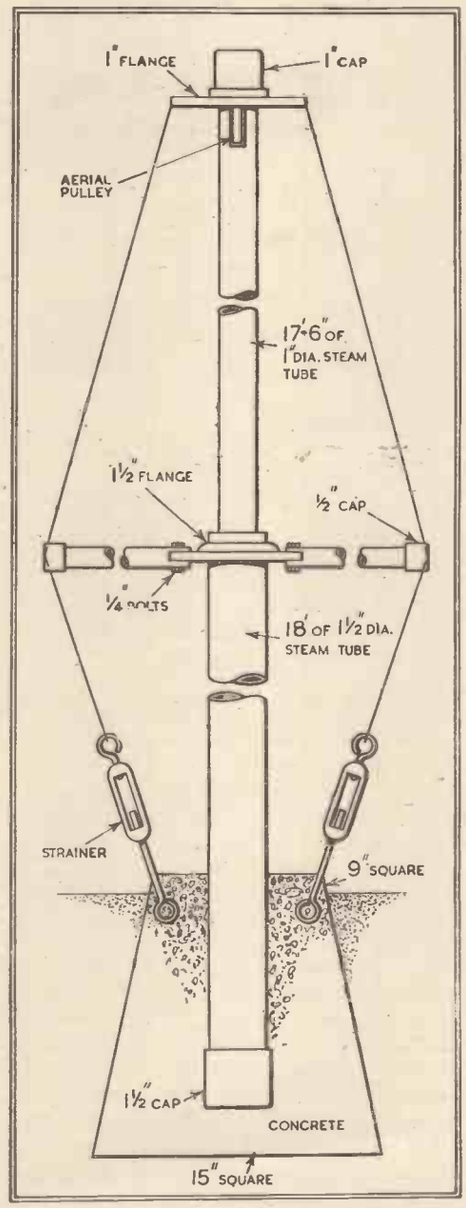


A compromise between the unsupported and the fully-stayed mast can be made by stretching stays of 7/20 SWG galvanised steel wire from the top of the mast to the base, passing *en route* through a slot cut in the outer end of spreaders attached radially to the centre of the mast. Three spreaders and stays, spaced at an angle of 120 degrees to each other, are used.

### Jointing Steel Masts

The wind pressure, at normal heights, may be as high as 50 lb. per sq. ft. of projected section, but an allowance is usually made for round objects by taking half of this, and since the above conditions are very exceptional it will be sufficient if the maximum pressure on a round spar is taken as 15 lb. per sq. ft. This makes the total side-thrust on a pole, 30ft. high and 2in. in diameter, equal to 75 lb. weight, a very considerable value indeed, and one that cannot be neglected.

In the design of a steel mast one is usually restricted to the standard sizes obtainable from stock, and it may be useful to give some indication of these; seamless tubes are expensive and not normally available, and the most convenient source of supply is those welded tubes, which are made for gas, water and steam, and are used for plumbing installations and the like. Those intended for carrying steam usually have thicker walls than gas or water pipes. Standard fittings, such as coupling sockets, caps, flanges and various pieces for joining several tubes together, are readily bought, and from these can be assembled most of the necessary types of mast; at a slight additional cost these may all be had in a galvanised finish, which is well worth while even if the whole is to be painted, and is essential if this is not the case.

The jointing, which will be necessary at least once in the height, may be done either by driving one tube into the other so that they overlap about 6in., using a piece of sheet metal to make the fit correct, or by the use of screwed couplings. The latter method is easier, but has the disadvantage that the section of the tube at the joint is reduced by the threading, and it is therefore necessary to use one thickness greater in order to allow for this. In either case it is wise to sweat over the joint

Aerial Masts—

with solder so that no moisture can gain admittance and cause corrosion and subsequent failure. This is especially necessary with galvanised tubes, where there exists the possibility, in certain circumstances, of electrolytic action. This may be prevented by a coat of paint. Steam and water tubes are sometimes not readily obtainable galvanised, and these should have at least one coat of good paint over the somewhat indifferent coating put on by the manufacturers. This painting should naturally be done after assembly of the mast and before erection.

The full calculations necessary to ascertain the stresses in the mast and guys are out of place here, and, instead, tables are given which will facilitate the adoption of designs other than the standard. Table II gives the maximum recommended lengths of the various sizes of steam tube, both without any pull due to the wire and also with different spans of 7/22 copper. The probable wind pressures on pole and wire with the additions for ice loading have been taken into account and a reasonable factor of safety allowed. These figures refer to an unsupported mast, and give the permissible length of the top section. To cover the requirements of the lower parts the last column is included; this shows the length of tube which can safely support the full length of a top section ½in. smaller in diameter than itself, *i.e.*, if the top part is 1in. nominal, then the next one should be 1½in., and the length may be 12ft. Similarly, if three sections are required, then the lowest of them may be a 12ft. length of 2in. diameter. It should be noted that the part in the ground is not included in the above, and this may be added to the bottom tube without increasing the stress.

### Securing the Base

Where lengths greater than those thus shown are needed, it is clear that stays will have to be used; also, if more than two sections are included it is wise to run guys to each junction. In these cases the lengths may safely be increased to the figures given for a free tube of the appropriate size. The amount of the tube that should be below the ground is a great deal affected by the nature of the latter; it is smallest for good clay and greatest for sandy soils. It is also dependent on the size of the mast, and is greater for steel than wooden poles, as the latter have a smaller diameter at the base. A very usual allowance is a depth of setting equal to one-fifth of the height above ground; somewhat less than this may be permitted for guyed masts in good soil, but where the unsupported and small-base types are used, the full amount should be allowed. Even for wood masts in poor ground this will be insufficient, and a concrete foundation, at least six inches square at the top, should be provided to distribute the pressure better. Unless these precautions are taken the mast will, sooner or later, begin to lean, and there are few things more unsightly than this. Alternatively, in the case of wood poles, kicking blocks may be used. These are blocks fitted crosswise to the mast at the butt and just below ground level so that they help to take the bending action of the wire-pull, and thus prevent movement. For steel masts which are not guyed in the conventional manner, it will be necessary to use a concrete base, and in soft soil it would be a wise precaution even with a well-stayed mast; it has, too, the advantage that it protects the base of the tube from corrosion.

Where normal guying is adopted the wires must be anchored in the ground and, though this may be done by driving stakes into the earth and attaching the stays to these, a much better way is to fasten them to plates or boards buried in the soil at a depth of, say, 4ft.; at this depth a plate 1ft. square will hold any pull that is likely to be experienced. In order to ensure that the guys are tight it is best to fit screwed strainers a short distance above ground; the slack may then be taken up with precision. For the small-base type of construction it is necessary to fix the stays near, but not to, the base of the mast, and since this type will have a concrete foundation, it is easy, when pouring the latter, to arrange to embed suitable hooks, or the lower end of each strainer, therein. When attaching the guys to steel masts a standard flange is useful. This may be drilled to take the aerial pulley also, and then screwed on to the top of the pole before fitting the cap. Where stays have to be fixed to the joint of the tubes this is also the neatest way of doing the job. A flange is also useful at the bottom of the mast to increase the area where this would otherwise sink in soft ground. If a concrete foundation is not used the bottom of the tube should be closed with a cap to lessen corrosion.

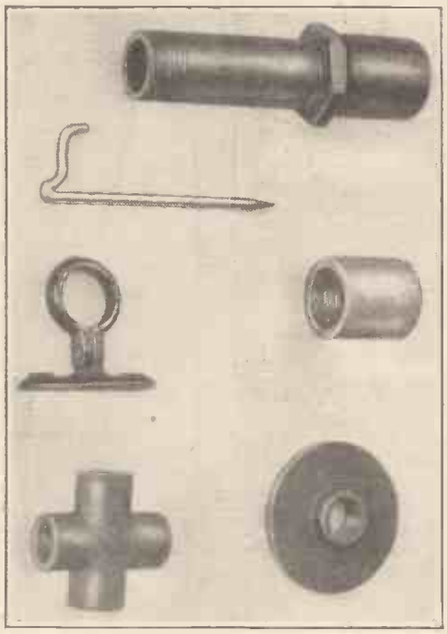

Fittings for masts showing tube with coupling sleeve and locking nut, wall hook, cap, clip for screwing on wood, crosspiece and flange.

Where it is required to fit spreaders at the centre of the mast, this may be done by the use of a flange having lengths of, say, ½in. tube fixed to it as shown in the diagram. As these are always in compression there is little tendency for them to slip even if the bolts shown are omitted, but these are an additional precaution and are recommended; a cap should be fitted to the ends of these pieces of tube and a groove filed in this to locate the wire. In the case of wooden masts such struts should be at least 1½in. square and may be secured to the pole by small rectangular brackets, such as are used to support shelves.

The number of guys may vary from the single one, used where it is desired merely to counteract the bending of the top section in an unsupported mast, to four or more, but the writer advises the use, where possible, of three, set at an angle of 120 degrees to each other and with the aerial wire opposite to one of them. By the adoption of this construction the mast is fully stayed and does not depend on the aerial, which may break, to offset wind pressure. The stays should be strained a little when erection is complete, but not to an excessive amount, or the whole system will be too rigid; if they are so tight that they "sing" nicely at a low pitch the stress will be about right. This also gives a means of ensuring that all are equally loaded as, being the same length, they should give the same note.

(*To be concluded.*)

## In Next Week's Issue

**SHORT-WAVE COILS.** Design and constructional data for efficient windings.

**VOLTAGE-CURRENT RELATIONSHIPS.** Simplifying points in AC theory that often cause confusion.

**TRANSMITTER MEASUREMENTS.** Constructional details of a valve voltmeter and methods of using it.

## BOOKS RECEIVED

**Building a Television Receiver at Home,** Pp. 112. Published by Bernard Jones Publications, Ltd., 37-38, Chancery Lane, London, W.C. Price 2s. 6d.

Constructional details are given in this booklet of television receiving apparatus for 1-in., 4-in., and 12-in. tubes of the electrostatic type. The contents are reprinted, with revisions, from *Television and Short-wave World.*

**Radio Marketing Trade Annual, 1939.** The information contained in this book of reference is grouped under three main headings: Directory, Technical, Commercial and Legal. It contains a list of wireless firms, a "Who's Who," business information for dealers and others, while, in the technical part of the book, there is a new television servicing section. The annual costs 5s., post free, and is published by *Radio and Electrical Marketing,* 29, Bedford Street, Strand, London, W.C.2.

# Cathode-ray Oscilloscope

## SIMPLE UNITS EMPLOYING A 2½in. TUBE

THE modern trend is more and more towards the use of the cathode-ray tube for testing purposes, and an oscilloscope is undoubtedly an extremely versatile and robust piece of apparatus. Its great advantage is that it gives a two-dimensional response so that it indicates the combined effect of two voltages.

For many purposes the cathode-ray tube with its power supply is sufficient, but for others a linear time-base is necessary. The apparatus described in this article is consequently built in two units, thus giving a maximum of flexibility. Before discussing the applications of the apparatus, it is advisable to have some idea of what it is, and we shall accordingly deal with this first.

The circuit of the CR tube unit is shown in Fig. 1. The tube used is the Osram 4081 with a diameter of 2½in. The screen colour is green. It is a two-anode tube with an indirectly-heated cathode, and all four deflector plates are brought out for external connection.

The HT supply is provided by a full-wave rectifier in the conventional manner, the reservoir condenser C1 having a capacity of 8μF. Owing to the low current consumption it is possible to dispense with a smoothing choke and to use a 10,000-ohm resistance R1 instead. The smoothing condenser C2 is 8μF.

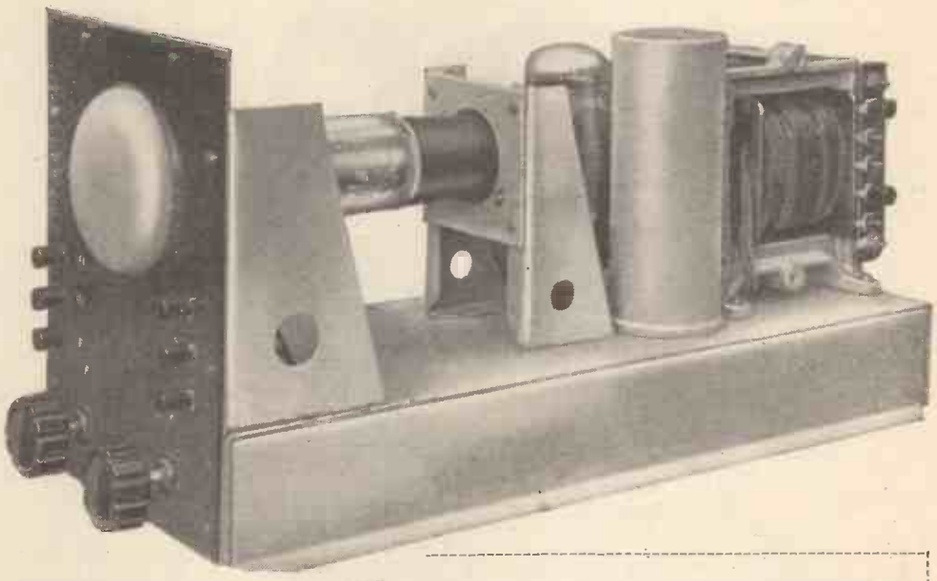

A view of the tube unit; the mains equipment is at the rear.

*THIS versatile equipment meets the basic applications of the small CR tube for test purposes. It is easy to build and, being arranged in unit form, construction need only be carried as far as the particular requirements demand. Many industrial applications of the CR tube preclude the use of a ready-built unit and trouble may be saved by working to this clearly set out design.*

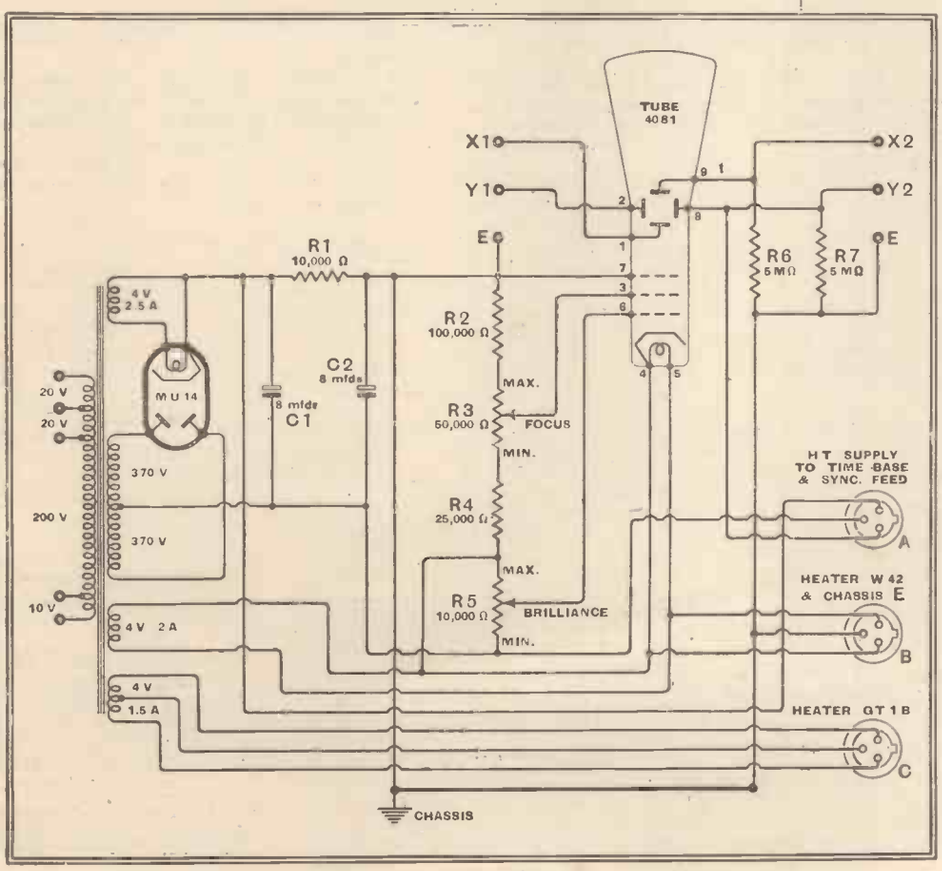


Fig. 1. — This diagram shows the circuit of the tube unit with its HT supply.

Positive HT is taken directly to the second anode of the tube, and the other electrodes are connected to tappings on a potentiometer across the HT supply. This comprises R2, R3, R4 and R5. The first anode is fed from the slider on R3 since the potential required is critical for focusing. R3 thus forms the focusing control. The cathode is connected to the junction of R4 and R5, and the grid is taken to the slider on R5, so that it is negative with respect to the cathode. The bias is adjustable to form a brilliance control.

The HT supply is taken to an output socket so that it can be fed to the time-base unit if this is employed. Heater windings are also provided on the mains transformer for this unit.

It is important to note that the *positive* HT lead is earthed to the chassis. This is done because the deflector plates must be returned to the second anode, and they are at earth potential since they must be available for connection to external circuits.

Two of the deflector plates are taken to the terminals X1, Y1, and the other two are taken to the terminals X2, Y2, and are

**Cathode-ray Oscilloscope—**

also connected to the second anode through the 5-megohm resistances R6 and R7. In use there must always be a conductive path between X1, Y1 and E. Normally these three terminals are connected directly together, and if they are not, then resistances must be interposed between X1 and E and between Y1 and E.

The output of the rectifier is some 400 volts, and the potentiometer across the HT supply takes 2.2 mA. The first anode potential is variable from about 50 volts to 160 volts, and up to 22 volts bias is available. The second anode potential with respect to cathode is 378 volts.

The deflection sensitivity is approximately 0.397 mm. per volt or 0.156 in. per volt. For a deflection of one inch some 64 volts is thus needed, or for one centimetre 25 volts. This is for a steady potential applied between X1, X2 or Y1, Y2. With an alternating potential the deflection depends on the peak-to-peak voltage which is 2.828 times the RMS value for a sine waveform. In terms of RMS voltages, therefore, the sensitivity is 22.6 volts per inch and 8.9 volts per cm.

These figures are, of course, approximate only, for they will vary somewhat with different tubes and depend on the precise second anode voltage. It is, however, an easy matter to calibrate the tube with a battery and voltmeter.

To do this connect X1, Y1 and E and join Y2 to E. Switch on, and when the tube has been given time to warm up advance the brilliance control gradually. A fuzzy spot will appear in the centre of the screen. Then adjust the focus control for the smallest and most sharply outlined spot. While doing this it may be necessary to reduce the brilliance. With a stationary spot great care should be taken to avoid excessive brilliance, otherwise the screen may be burnt.

Having obtained the focused spot, connect a battery between X2 and E. The spot will move horizontally to left or right, depending on the polarity of the battery. Measure the amount of the displacement and also the battery voltage. Repeat, this time using the Y2 plate; the spot will now move vertically. The sensitivity is approximately the same in this direction, but may not be exactly so.

Connected in this way the tube can be used as a voltmeter of high input impedance, and it is as accurate at audio- and low radio-frequencies as it is to steady potentials. At the highest radio frequencies errors may occur, but not within the commonly used range.

It is worthy of note that while the application of a steady potential to the deflector plates merely results in a shifting of the position of the spot, the application of an alternating potential results in the appearance of a line. The length of this line, which is due to the spot moving rapidly to and fro, indicates the peak-to-peak value of the applied voltage.

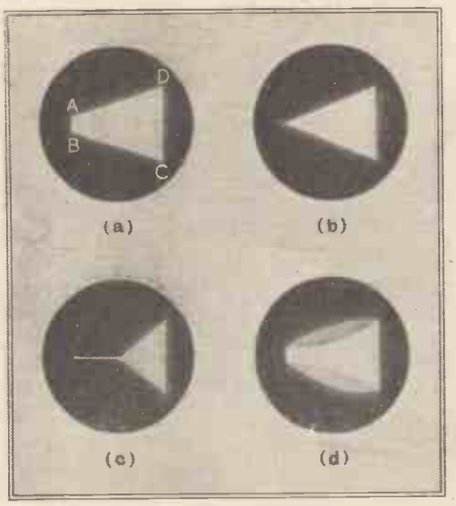


Fig. 2.—Modulation depth can be determined with the CR tube as explained in the text. Modulation less than 100 per cent. produces a picture such as (a), while 100 per cent. modulation gives (b). Over-modulation gives the effect of (c), and phase shift of (d).

While the ability of the tube to function as a voltmeter is useful, it would not alone justify its use, and in most cases both sets of deflector plates are employed. When alternating potentials are applied to both sets of plates, the position of the spot at any instant depends on the instantaneous values of both potentials, and with the usual repetitive waveforms a pattern appears on the screen.

One particularly useful application lies in the determination of distortion. The amplifier under test is fed from the usual fixed frequency source, and the output is applied to one pair of plates, say between Y2 and E. The source must be of fairly high voltage and only a fraction of it applied to the amplifier, for it must also be connected to the other pair of plates, say, between X2 and E. Alternatively, a separate and distortionless amplifier can be used between the source and the X-plates.

If the adjustments are made so that the voltages on the X and Y plates are equal, and the amplifier is free from distortion, a straight line inclined at an angle of 45 degrees to the vertical will appear on the screen. Inequality in the voltages will be shown as a change from this angle.

Amplitude distortion results in the line being no longer straight, and phase distortion makes it turn into an ellipse. In an extreme case where the voltages are 90 degrees out of phase the trace becomes a circle.

The tube can also be used for comparing frequencies. A known frequency, such as a potential from the 50 c/s mains, is applied to one set of plates and the unknown to the other. From the resulting figure the ratio of the frequencies can be deduced, provided that the ratio is such that a stationary figure is obtained. The figures obtained are known as Lissajous' figures, and are given in most textbooks dealing with cathode-ray apparatus.

One case where this may be very useful is in the calibration of a beat-frequency

## List of Parts

### TUBE UNIT

1 **Mains transformer**, 370-0-370 v., 40 mA. 4 volts 2.5 amps, 4 volts 1.5 amps C.T., 4 volts 2 amps — **Haynes TB64**
1 **Condenser**, 8-8 mfds., electrolytic, common negative lead, case isolated, **C1, C2** — **Dubilier 9203E**
**Resistances:**
2 5 megohms, ½ watt, **R6, R7** — **Dubilier F½**
1 10,000 ohms, 1 watt, **R1** — **Dubilier F1**
1 25,000 ohms, 1 watt, **R4** — **Dubilier F1**
1 100,000 ohms, 1 watt, **R2** — **Dubilier F1**
1 **Potentiometer**, 10,000 ohms, wire wound, **R5** — **Haynes**
1 **Potentiometer**, 50,000 ohms, wire wound, **R3** — **Haynes**
3 **Connectors**, plug and socket — **Bulgin P73**
1 **Valve holder**, 5-pin — **W.B.**
1 **Valve holder**, 9-pin — **W.B.**
2 **Knobs**, black, ¼-in. hole, 2 grub screws
**Aluminium Chassis**, comprising baseplate, 2 side pieces, front plate and engraved paxolin panel, 2 large brackets, 2 small brackets, small plate for tube holder, fitted with grommets and insulated terminals — **Haynes**
6 **Feet Flex**, triple 5-amp
**Miscellaneous:**
Screws, wire, sleeving.
**Valves:**
MU14, Tube 4081 — **Osram**

### TIME BASE AND AMPLIFIER

1 **Mains Transformer**, 375-0-375 v., 4 volts 2.5 amps, 4 volts 1 amp — **Haynes T2714**
1 **Volume control**, 1 megohm, **R5** — **Dubilier "A"**
1 **Volume control**, 0.5 megohm, **R9** — **Dubilier "A"**
1 **Volume control**, wire wound, 25,000 ohms, **R13** — **Haynes**
1 **Volume control**, wire wound, 50,000 ohms, **R11** — **Haynes**
**Condensers:**
1 0.0001 mfd., mica, **C10** — **Dubilier 691**
1 0.002 mfd., mica, **C15** — **Dubilier 690**
1 0.01 mfd., mica. **C14** — **Dubilier 690**
4 0.02 mfd., mica, **C4, C6, C9, C11** — **Dubilier 680**
1 0.1 mfd., tubular, **C13** — **Dubilier 4603S**
2 0.5 mfd., tubular, **C12** (two in parallel) — **Dubilier 4608S**
1 Triple 1 mfd., paper block condenser. **C3** — **Dubilier BE379**
2 8-8 mfds., electrolytic condensers, common negative lead, case isolated **C1, C2, C7, C8** — **Dubilier 9203E**
1 25 mfds. electrolytic condenser, **C5.** — **Dubilier 3016**
**Resistances:**
1 300 ohms, ½ watt, **R17** — **Dubilier F½**
1 350 ohms, ½ watt, **R6** — **Dubilier F½**
1 5,000 ohms, ½ watt, **R14** — **Dubilier F½**
2 10,000 ohms, ½ watt, **R7, R8** — **Dubilier F½**
3 25,000 ohms, ½ watt, **R2, R10, R12** — **Dubilier F½**
4 100,000 ohms, ½ watt, **R3, R4, R15, R16** — **Dubilier F½**
1 25,000 ohms, 1 watt, **R1** — **Dubilier F1**
2 **Valve holders**, 5-pin — **W.B.**
2 **Valve holders**, 7-pin — **W.B.**
1 **Switch**, 4-way (or 5-way) with condenser-holding plate and 2 spacers — **Peto-Scott**
5 **Knobs**, black, ¼-in. hole, 2 grub screws
**Aluminium Chassis**, comprising baseplate, 2 brackets, front plate and engraved paxolin panel with insulated terminals — **Haynes**
**Miscellaneous:** Screws, wire, sleeving.
**Valves:**
1 MU14, 1 MSP4, 1 W42, 1 GT1B — **Osram**

**Cathode-ray Oscilloscope—**

oscillator, for with a little care and ingenuity it is possible to carry out an accurate calibration based on the 50 c/s mains. Using the CR tube as an indicator a direct calibration against the mains is possible up to about 500 c/s. From this a separate oscillator can be fixed exactly at 500 c/s, and then used to take the calibration up to 5,000 c/s. Another fixed oscillator can then be calibrated and the main calibration extended indefinitely.

As an indicator of modulation depth in a transmitter the tube is particularly useful. The modulated RF output is applied to one pair of plates, and the AF output of the modulation amplifier to the other pair. The result is a figure which depends on the modnlation depth.

With perfect modulation the figure takes the form of Fig. 2 (a) and the modulation depth is given by $\frac{CD - AB}{CD + AB}$ 100. With 100 per cent. modulation AB is zero and the figure is a triangle (b). When the modulation exceeds 100 per cent. the figure is a triangle with a line extending from the apex (c). A phase difference between the modulation and the modulation voltage will modify the figure to the form shown at (d).

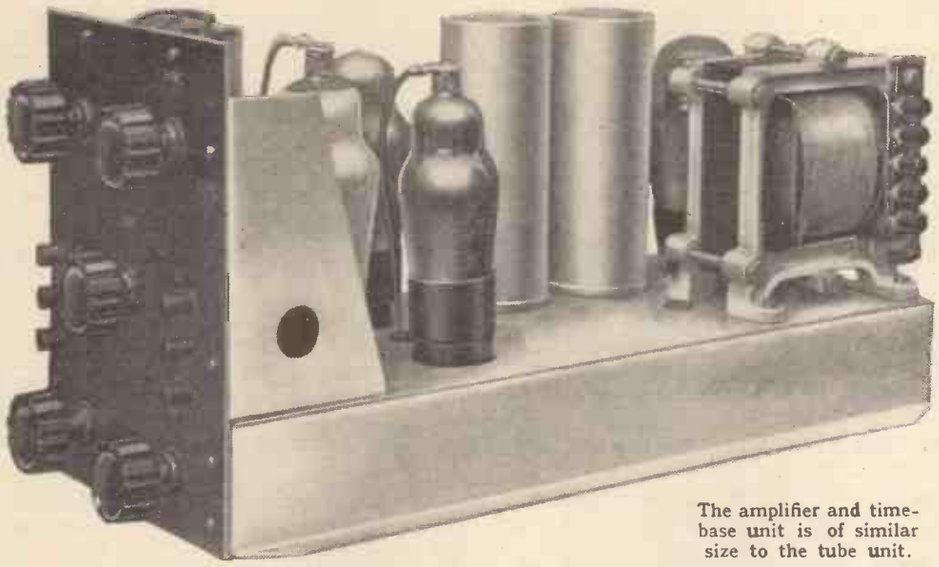

The amplifier and time-base unit is of similar size to the tube unit.

Although the CR tube unit alone is very useful, there are many cases where a linear time-base is desirable. This is an oscillator delivering an output voltage which rises steadily with time until a certain maximum is reached, when it falls back very rapidly to its initial value and starts to rise again, and so on.

The output is applied to the X-plates to give the horizontal deflection, and the waveform under examination is applied to the Y-plates. The pattern on the tube is then that which would be obtained by plotting as a graph the voltage variations against time with linear scales. A direct picture of the waveform is obtained.

The circuit of the time-base unit is shown in Fig. 3, and it also includes an amplifier for the waveform to be observed. The saw-tooth oscillator is operated from the tube HT supply in the tube unit, and the mains equipment in this unit is provided solely for the amplifier.

Additional smoothing of the time-base HT supply is provided by the 10,000-ohm resistances R7 and R8 in conjunction with the 8-$\mu$F. condensers C7 and C8. The saw-tooth oscillator is a gas-triode with a 300-ohm resistance R17 in its anode circuit to limit the anode current to a safe value. The charging condensers are C12 to C15, the required value being selected by the switch S1.

In order to obtain a linear waveform a charging valve is used, the W42; it is

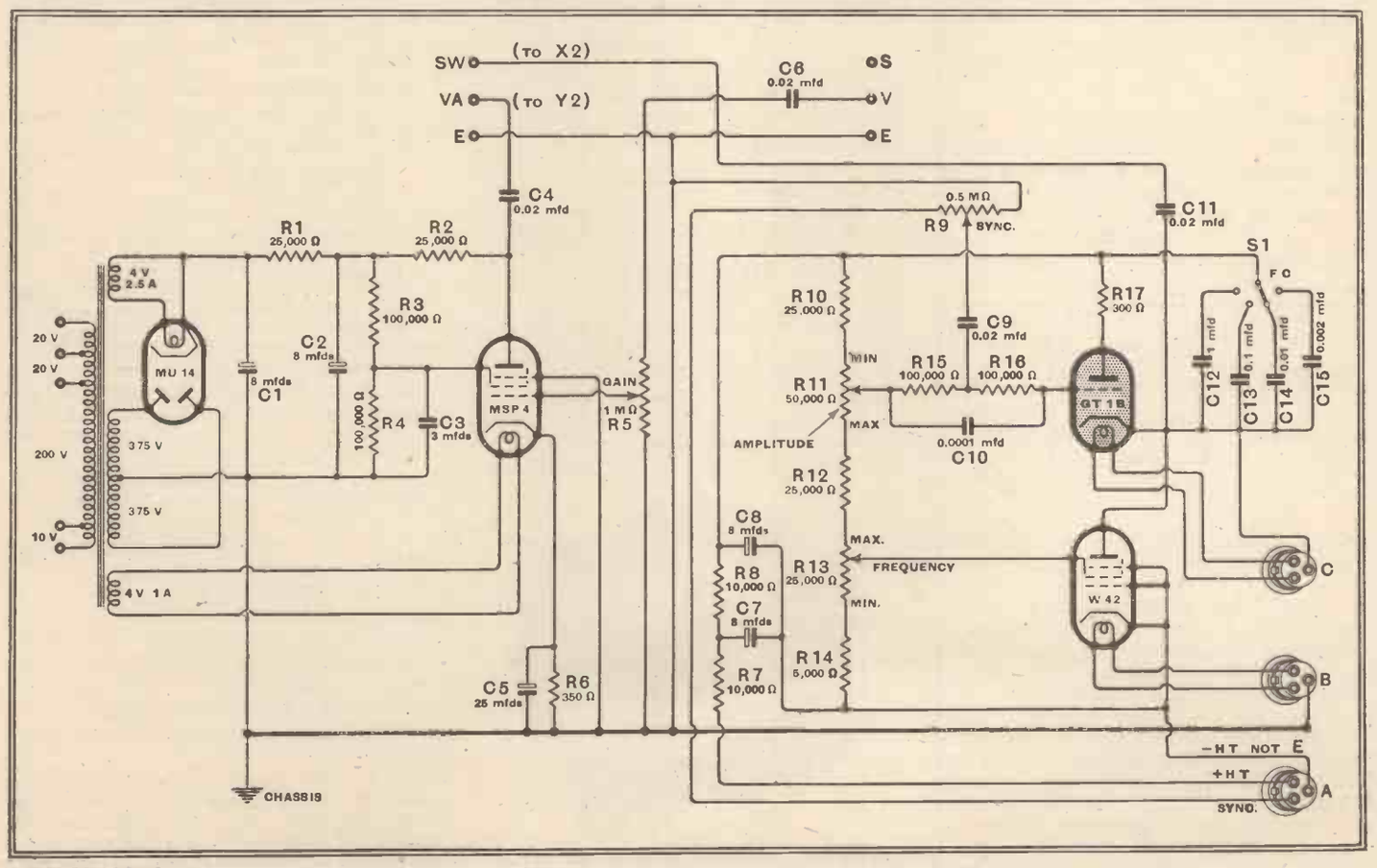


Fig. 3.—Circuit diagram of the time-base unit incorporating an amplifier for the observation of waveform.

**Cathode-ray Oscilloscope—**

operated with zero grid bias, and has its anode joined to the cathode of the gas-triode. The screen is fed from a voltage-divider across the HT supply, and its voltage is adjustable by R13. This is the main frequency control. The saw-tooth frequency is adjustable in steps by S1 and precisely by R13.

The grid of the gas-triode is also taken to the voltage divider, and the setting of R11 determines its grid bias, and hence the amplitude of the sweep. Synchronising is obtained by applying a portion of the voltage to be examined to the grid of this valve, and this is done with the aid of R9.

In operation the gas-triode is non-conductive, and the charging condenser, say C12, charges from the HT supply through the charging valve. The rate of charge depends on the screen potential of this valve. As it is a pentode, the anode current, which constitutes the charging current, is substantially independent of anode voltage. The voltage across C12 consequently rises at a uniform rate.

At length the voltage is sufficient to operate the gas-triode. The gas ionises and the valve becomes conductive and very rapidly discharges C12. The cycle then recommences. When the generator is synchronised a portion of the work voltage is applied to the grid. The change of grid voltage in a positive direction, occurring just before the gas-triode would normally strike of itself, causes it to fire at a definite point of the signal cycle every time, with the result that successive traces are superimposed and a steady picture is obtained.

The amplifier is provided so that a reasonable deflection can be secured with a small input and is extremely useful in many applications. An RF pentode is used with an input gain control. It is biased by R6, shunted by the 25 $\mu$F. electrolytic condenser C5, and the screen is fed from the voltage divider R3 R4. Resistance coupling to the tube is adopted.

As it is inconvenient to operate the amplifier from the same HT supply as the tube, because the supply for the latter has its positive earthed, separate mains equipment is provided. Resistance smoothing is again adequate, and is provided by R1 in conjunction with C1 and C2.

When using the amplifier it is important to note that it reverses the phase of the "signal" voltage. This means that if a certain waveform produces a pattern on the tube when the amplifier is not used and it is then inserted, the pattern will be upside down. In most cases this does not matter, but if it is forgotten misleading results may occasionally be obtained.

*(To be concluded.)*

# PROBLEM CORNER–21

**An extract from Henry Farrad's correspondence, published to give readers an opportunity of testing their own powers of deduction :—**

90, Fays Way,
Vectorford.

Dear Henry,

We have been having a bit of an argument, and as it has reached a deadlock I am hoping you will be able to clear it up. It cropped up while discussing how to arrange for several loud speakers to be worked from one output transformer. Suppose A represents a secondary winding cor-

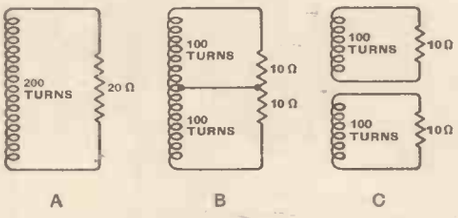


rectly designed to supply a load of 20 ohms as shown, and for the sake of argument let the number of turns be 200. Then according to the well-known rule that the ratio of turns is proportional to the *square root* of the ratio of impedances, it looks as if a 100-turn winding ought to be correct for supplying a quarter of the load resistance—5 ohms.

But now suppose that a centre tap on the winding is joined to a centre tap on the load, as at B, it ought (according to the Wheatstone bridge principle) to make no difference, because it joins two points that are at the same potential. But now we have 10 ohms across 100 turns. In fact, the two halves of the winding could be separated, as shown at C, and this disagrees with the rule mentioned above.

There must be a fallacy somewhere, I suppose, but none of us can see just where it lies.

Yours sincerely,
Fred New.

*How can the above result be reconciled with the "square-root-of-the-impedances" rule?—Solution on p. 501.*

# The New Murphy Portable

**Superheterodyne Circuit with an RF Stage**

THE first Murphy receiver designed for quantity production was a battery portable and now after nearly 10 years the firm has introduced a new model, the B81.

First consideration has been given to performance and to judge from the specification this should be of a high order. Adequate volume for an economical use of HT current is assured by the use of a QPP stage and a most unusual feature is the inclusion of an RF stage before the frequency-changer in the five-valve superheterodyne circuit. This should give sensitivity comparable with a four-valve table model on a medium-sized aerial and better signal-to-noise ratio than is usually available in portable receivers.

A black rexine case with green trimmings has been adopted for the B81 Murphy portable.

The entire chassis is mounted on rubber supports and quick-fitting rubber straps hold the batteries in place. The weight is about 25 lb. with batteries, and the price (less batteries) £8 15s.

# Television Programmes

Sound 41.5 Mc/s Vision 45 Mc/s

**An hour's special film transmission intended for demonstration purposes will be given from 11 a.m. to 12 noon each weekday. The National or Regional programme will be radiated on 41.5 Mc/s from approximately 7.45 to 9 p.m. daily.**

THURSDAY, MAY 25th.

**3,** "Lonesome Like," a short play by Harold Brighouse. **3.30,** Gaumont-British News. **3.40,** 245th edition of Picture Page.

**9,** 246th edition of Picture Page. **9.30-10.45,** Boxing O.B. from Harringay Arena. The World's Welterweight Championship; Armstrong v. Roderick.

FRIDAY, MAY 26th.

**3,** Adelaide Hall in "Dark Sophistication," the coloured cabaret from the Old Florida Club. **3.30,** British Movietonews. **3.40,** "Smiling at Grief," a play by Walter Hudd.

**9,** Naunton Wayne in Cabaret. **9.30,** Cartoon Film. **9.35,** "Looking for a House," Pearl Binder describes the successful outcome of her trials. **9.45,** Gaumont-British News. **9.55,** Vanity Fair—modern dress design. **10.10,** Film. **10.20-10.30,** Music Makers—Dorothea Aspinall, pianoforte.

SATURDAY, MAY 27th.

**3,** C. H. Middleton, "In Our Garden." **3.15,** Gaumont-British News. **3.25,** Cartoon Film. **3.30,** The Vic-Wells Ballet present the third act of "The Sleeping Princess."

**9-10.30,** "Behind the Schemes," by G. H. Grimaldi. The action takes place in the publicity office of "The Daily Quiver," Fleet Street.

SUNDAY, MAY 28th.

**3,** The Hotchkiss Marionettes. **3.15,** Cartoon Film. **3.20,** Cartoons by Harry Rutherford. **3.30,** Mabel Constanduros in "Zoo and You." **3.40,** Marcella Salzer in a One-Woman-Entertainment. **3.55,** British Movietonews.

**8.50,** News. **9.5-10.35,** Edmund Knight in "First Stop North," a new play by Nicholas Phipps.

MONDAY, MAY 29th.

**3,** Ray Ventura et ses Collegiens. **3.35,** Gaumont-British News. **3.45-4.10,** Polo O.B. from Hurlingham.

**9,** "Fantastic Garden," No. 3. **9.30-10.30,** "The Fighting Texan"—Film.

TUESDAY, MAY 30th.

**3-4.30,** D. A. Clarke-Smith in "The Great Adventure," by Arnold Bennett.

**9-10.30,** "The Insect Play," by Karel Capek; adapted by Nigel Playfair and Clifford Bax.

WEDNESDAY, MAY 31st.

**3-4.30,** "Behind the Schemes" (as on Saturday at 9 p.m.).

**9,** Cabaret Cruise, with Commander A. B. Campbell. **9.45,** British Movietonews. **9.55,** Sunday in the Country. **10.15,** Cartoon Film. **10.20,** Pouishnoff, playing Grieg's pianoforte concerto in A minor with the B.B.C. Television Orchestra. **10.50,** News.

# Footless Valves

## NEW TUNGSRAM RANGE FOR SHORT WAVES

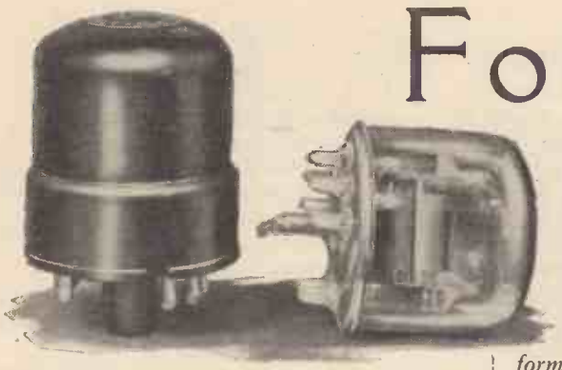

*VALVE development proceeds very rapidly nowadays and the changes are more often than not in the mechanical form in order to obtain increased efficiency on short waves. One of the latest trends—the abolition of the pinch and top cap—is described in this article.*

ONE of the greatest disadvantages of the conventional form of valve construction is the length of the internal connecting leads between the base pins and the electrodes The promixity of these leads adds very considerably to the interelectrode capacities, and their length makes their inductance appreciable at high frequencies.

The inductance of the cathode lead is probably the most important, for it makes proper decoupling of the circuits impossible. One serious result is that on short waves the input resistance of the valve is considerably lower than would be the case if the electron transit time were the only factor to be taken into account. The inductance of the screen-grid lead is also disadvantageous, since it makes the effective capacities rise with frequency.

Recent valve development has lain very largely in the direction of reducing the length of the internal leads, and considerable improvement in valve performance has resulted. This process was carried to its logical conclusion some years ago in the well-known acorn, in which the very small electrode clearances also greatly reduced electron transit time effects.

While the acorn is the only suitable type of valve for some applications, it is too difficult to manufacture and too fragile for general use. Recent development, therefore, has had for its aim the attainment of electrical characteristics approaching those of the acorn combined with a mechanical construction which is not inferior to that of ordinary valves.

This was first approached by adopting conventional forms of construction, but reducing the length of the valve and using a special form of base to reduce the length of the internal leads. One example of this development is the well-known "E" series with the side-contact base.

The next stage was to abandon the use of the glass pinch for supporting the electrodes and to substitute for it a glass ring of the same diameter as that of the circle of base pins. This ring forms part of the glass wall of the bulb, and not only gives a considerable reduction in the length of the leads, but the leads themselves are much more widely spaced in the glass support. This results in a reduction of the inter-electrode capacities and at the same time gives greater mechanical rigidity. In addition, it makes it possible to bring both anode and grid connections out to the base, instead of having to take one of them to a top-cap, because there is now room to introduce internal screening between the leads.

This in itself is by no means an unimportant development, because it permits a considerable reduction in the length of the connecting leads external to the valve. The top-cap has long been a nuisance in receiver design.

Valves of this type with an all-glass construction have been described in *The Wireless World*, and the practice has been to retain the usual vertical electrode assembly.[1] In Germany, however, Telefunken have produced a range of valves with the electrodes arranged horizontally and use an all-metal construction with glass beads for insulating the leading out wires.[2] The horizontal construction is claimed to give increased rigidity, because the electrodes can readily be anchored at each end.

A new range has now been introduced by Tungsram. The valves are in some ways similar to the Telefunken, for they have a horizontal electrode assembly and have the same arrangement of the base pins, but they are of all-glass construction with an external metal cover for screening and protection.

The base is a modified octal, but with a larger pin circle to increase the spacing; the pins are provided with a waist to give a locking action in the socket.

In this way mechanical rigidity and easy assembly are combined with the desirable electrical properties of the footless valve, and at the same time the advantage of the well-tried evacuation technique of a glass valve is retained.

The makers claim that in a comparison

[1] *The Wireless World*, February 16th, 23rd, 1939.
[2] *The Wireless World*, November 10th, 1938.

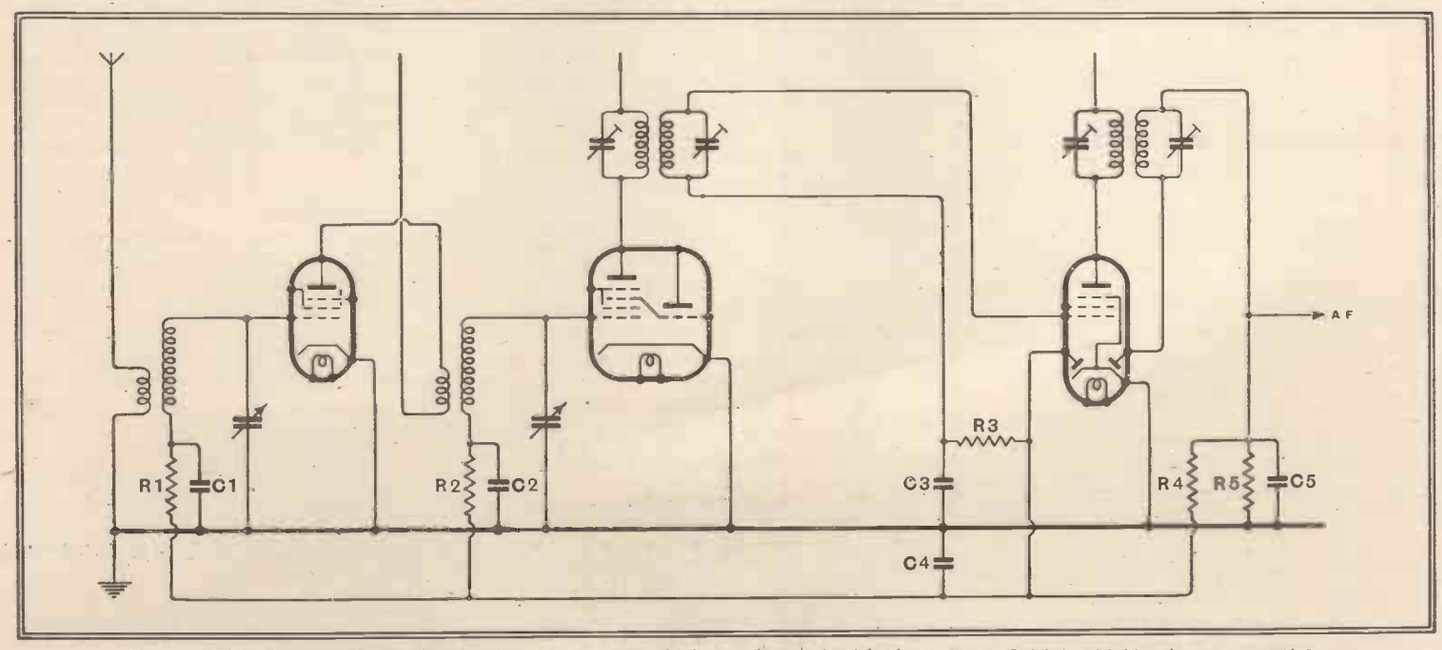


Fig. 1.—This diagram shows the simple arrangement which can be used with the valves. Initial grid bias is not essential.

**Footless Valves—**

of these new valves with the usual types with a pinch construction the following advantages are gained:—

Lower inter-electrode capacities and reduced internal lead length, giving improved performance on short- and ultra-short-waves.

Grid and anode connections at the same end, thus reducing external lead lengths.

Greater mechanical rigidity (every electrode has a three- or four-point suspension instead of the usual two-point).

Smaller physical dimensions.

Greater reliability because of the simpler construction.

Reduced leakage, due to the absence of the pinch and the use of fewer mica spacers, thus giving quieter operation.

The valves so far produced in this range are a variable-mu RF pentode EF11, a straight abrupt cut-off RF pentode EF12, a duo-diode-RF pentode EBF11, a triode-hexode frequency-changer ECH11, an output pentode EL11N, and a rectifier AZ11. Further valves to be produced are a cathode-ray tuning indicator EM11, and an AC/DC output pentode and rectifier CL11N and CY11.

The EF11 is rated for 250 volts and 100 volts anode and screen potentials, and at the normal bias of −2.2 volts the anode and screen currents are 6 mA. and 2 mA. respectively. When the screen potential is fixed, a bias of 17 volts is needed to reduce the mutual conductance from its normal value of 2.2 mA/v. to 0.022 mA/v. If the screen is fed from the 250-volt line through a dropping resistance of 75,000 ohms, however, 45 volts bias is needed to obtain this value of mutual conductance. The valve can thus be arranged to have either a short or a long grid base, as desired. The maximum cathode current is 10 mA. and the input and output capacities are 6.1 μμF. and 6.5 μμF. respectively with a grid-anode capacity of 0.002 μμF. The straight RF pentode EF12 has similar general characteristics, but the mutual conductance is 2.8 mA/v.

### The Triode-hexode

The triode-hexode ECH11 is rated for 250 volts anode and 100 volts screen potentials on the hexode section with currents of 2.3 mA. and 3 mA. at 2 volts grid bias. With fixed screen potential, 13 volts bias is needed to reduce the conversion conductance from 0.65 mA/v. to 0.00325 mA/v., whereas if the screen is fed through 50,000 ohms a bias of 21 volts is necessary to bring the conversion conductance down to 0.0016 mA/v.

The triode section, which is used as the oscillator, should have a 50,000-ohm grid leak, and with the correct amplitude of oscillation the grid current is 200 μA. The anode should be fed through 30,000 ohms from the 250-volt line and it takes a current of 3.3 mA. This section has a mutual conductance of 2.8 mA/v. with an amplification factor of 20.

The hexode section has input and output capacities of 5.3 μμF. and 9.1 μμF. respectively; the triode grid-cathode capacity is 4.3 μμF., the anode-cathode capacity 2.5 μμF. and the grid-anode capacity 1.5 μμF. The capacity between the hexode grid and anode is 0.001 μμF., between the hexode grid and the triode grid 0.2 μμF., and between the hexode grid and heater 0.001 μμF.

The characteristics of the pentode section of the EBF11 duo-diode-RF pentode are very similar to those of the EF11. The anode and screen currents are 5 mA. and 1.8 mA. respectively, however, and if a dropping resistance is used for the screen supply it should have a value of 85,000 ohms.

The particular feature of this valve is the extremely low inter-electrode capacities. The input and output capacities are 4.9 μμF. and 6.2 μμF. respectively with a grid-anode capacity of less than 0.002 μμF. The diode capacities are D1-cathode 2.3 μμF., D2-cathode 2.7 μμF. and D1-D2 0.5 μμF. The capacity between

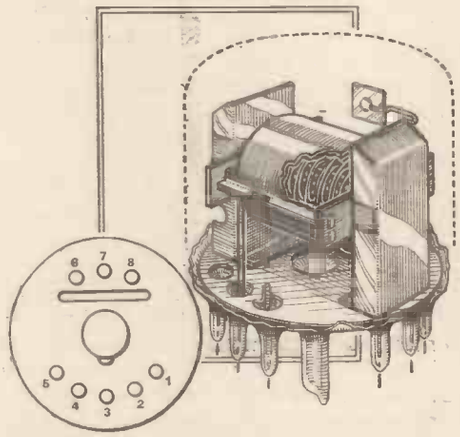


A sketch of the electrode system of an RF pentode is shown here, together with the arrangement of the base pins.

the pentode anode and either diode anode is less than 0.015 μμF. and between the pentode grid and either diode anode it is less than 0.001 μμF.

These four valves all have heaters rated at 6.3 volts 0.2 ampere, but the output pentode EL11N takes 0.9 ampere at this voltage. The similar CL11N will have a heater rated at approximately 40 volts 0.2 ampere.

The EL11N is rated for 250 volts anode and 275 volts screen potentials with 6 volts grid bias, the currents being 36 mA. and 4 mA. respectively. The bias resistance should be 150 ohms and the load impedance 7,000 ohms. The output is given as 4.5 watts for 10 per cent. total harmonic distortion and the input as 4.2 volts RMS. The mutual conductance is 9 mA/v. and the AC resistance 50,000 ohms.

The AZ11 rectifier has a 4-volt 1.1-amp. filament and is of the full-wave directly-heated type. At 300 volts RMS input the maximum output current is 100 mA., but at 500 volts input it is rated at 60 mA. only.

BASE CONNECTIONS

| Pin | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 |
|---|---|---|---|---|---|---|---|---|
| EF11 | — | H | H | — | A | SG | G | C, M, Sup. |
| EBF11 | A | H | H | DA | DA | SG | G | C, M, Sup. |
| ECH11 | A | H | H | OG | OA | SG | G | C, M |
| EL11N | — | H | H | — | A | SG | G | C, Sup. |
| AZ11 | — | F | F | — | A | A | — | —— |

The base connections for these valves are given in the accompanying table, and it will be noted that the metal shell is internally connected to the cathode pin. Partly because of this, and partly to reduce the length of the external common cathode connection to the valve, the use of cathode bias is not recommended in the early stages.

Bias by means of a resistance in the negative HT lead can be used, but is usually inconvenient. The makers recommend the omission of any initial bias and that the circuit be arranged in the form shown in Fig. 1, where R1C1, R2C2, R3C3, R4C4 are the usual AVC filters. In the EBF11 one diode is used as the detector with R5 for the load resistance and C5 for the by-pass condenser. The other diode is connected after R4 to give a small measure of delay on AVC.

Owing to the fact that the diode passes current up to about −1 volt anode potential, the normal no-signal anode potential is about −0.9 volt, and the controlled valves consequently have a slightly negative grid potential which prevents their cathode currents from becoming excessive. On any normal signal, of course, bias is provided by the AVC system.

This method of operation considerably simplifies the receiver, and its only disadvantage is some reduction in the initial sensitivity. This may not always be considered a disadvantage, however, for the effect is that of a QAVC action.

The EF11, EF12, EL11N and CL11N are provisionally priced at 10s. 6d.; the ECH11 and EBF11 at 11s. 6d.; the AZ11 and CY11 at 9s., and the EM11 at 8s. 6d.

## The "Princely" Portable

***Model 905M, for Operation from Mains or Batteries***

THE valves used in this receiver, which is available in this country through the Princely Radio and Television Corporation (of Gt. Britain) Ltd., 5 and 6, Clipstone Street, London, W.1, are of the latest 1.4-volt type, and when used as a battery set the LT is derived from dry cells. The HT battery is divided into two 45-volt units.

There are four valves in the superheterodyne circuit, with a fifth as rectifier when the set is connected for mains operation.

The Model 905M costs £10 17s. 6d., and there is a model (904B) for battery operation only at £8 18s. 6d.

## The Electric Gramophone

IN the article in the May 11th issue under the above heading reference was made to the Varley BP26 Nicore HF choke. For the convenience of readers who are contemplating the construction of this equipment, Varley, Cambridge Row, Woolwich, London, S.E.18, are arranging to manufacture a special centre-tapped choke at a list price of 5s.

Special models of the push-pull output transformer range are also being produced, with split primary windings, at the standard price of 18s. These will be known as the types DP46SP, DP47SP and DP48SP.

# NEWS OF THE WEEK

## HIGH-POWER TRANSMITTERS

### Decision of the F.C.C.

SOME interesting sidelights on the refusal of the Federal Communications Commission to renew the 500-kW licence of the Crosley Radio Corporation's station WLW, as announced in *The Wireless World* of March 2nd, are revealed by our American correspondent.

Originally a 50-kW station, WLW's power has been 500 kW for nearly five years under the experimental licence granted by the F.C.C. Since the commencement of the high-power transmissions there has been almost continual controversy on the advisability of the granting of the licence—the only one in existence.

At 500 kW WLW's field at Connecticut, about 700 miles away, was said to be precisely that arrived at in the theoretical calculations which prompted the request for the increase of power. Advocates of high-power transmitters desired to have perhaps a dozen similar stations in the States to work in broad clear channels for the purpose of high-fidelity transmission in the hope of covering the entire nation.

#### *Service Areas*

This system, our correspondent says, was suggested as possibly capable of replacing the present tangle of hundreds of stations each spoiling more territory than it covers.

Perhaps the best argument of the opposition was that in a country more than 2,500 miles wide even a reasonable number of 500-kW stations could not be certain of producing dependable service areas covering all States. It is, however, difficult to say definitely what consideration finally governed the F.C.C.'s decision.

It is perhaps of interest to mention that the Federal Communications Commission of the United States Government is composed of political nominees who acquire their appointments after examination by a committee from the Congress, and are therefore not necessarily radio engineers.

Whether an aerial power of 500 kW is desirable or not, it is still fairly easy to conclude that technical considerations alone did not sway the F.C.C. in its decision to refuse the renewal of WLW's 500-kW licence. However, high-power transmitters have apparently passed from the American radio picture.

## TELEVISION INTERFERENCE

### British Standards for Suppression

AS the result of co-operative effort on the part of the Society of Motor Manufacturers and Traders, the B.B.C., the Electrical Research Association, and the G.P.O., the British Standards Institution has issued a specification which deals with the suppression of radio interference caused by ignition systems.

This new specification relates to the suppression of interference of various kinds, including that caused by the sundry electrical equipment of cars. It is primarily concerned with the protection of reception at points not in the immediate vicinity of the sources of interference, and the degree of suppression required has been specified with this end in view.

The causes and characteristics of the interference have been exhaustively investigated by the B.S.I. Committee, and certain methods of suppressing the interference to an adequate extent without appreciable detriment to the operation of the machinery involved have been arrived at and are described and illustrated in the specification.

The publication of this specification must not be taken as inferring that motor cars fitted by the makers with suppression devices will soon be on the market. In the event of relevant legislation coming into force, however, the guidance given in the specification should be of considerable assistance to the motor car industry, and in the meantime car owners and designers will find much to interest them in the specification B.S. No. 833-1939. This can be obtained from the British Standards Institution, 28, Victoria Street, London, S.W.1, price 2s. 2d. post free.

## PROPAGATION OF RADIO WAVES

### Amateurs Help in Investigations

BETWEEN the Quinquennial International Telecommunications Conferences, the last of which was held at Cairo in February, 1938, are held technical conferences which are officially known as Comité Consultatif International des Radiocommunications meetings. In preparation for the next C.C.I.R. meeting, which is to be held in Stockholm during 1940, a committee has been set up by the G.P.O. to investigate the problems emerging from the last meeting, held in Bucharest.

Great Britain is responsible for three questions at the Stockholm meeting. In the current issue of *The T. & R. Bulletin* it is pointed out that one of the questions to be discussed, that on the propagation of radio-electric waves, provides the amateur with an opportunity of making a practical contribution to the next C.C.I.R. meeting.

Data relating to horizontally polarised waves is wanted by the R.S.G.B., which has again been invited to send representatives to serve on the G.P.O. Committee. Information covering amateur observations on all frequencies above 28 Mc/s will be appreciated, and in particular practical data dealing with work on frequencies around 60, 120, and 240 Mc/s.

A Technical Sub-Committee has been set up by the R.S.G.B. to correlate the information submitted by members, and the data provided is asked to be put under eleven general headings, which are tabulated in *The T. & R. Bulletin*.

The amount of information procurable on the propagation of the ultra-high frequencies will doubtless be lessened by the recent decision of the G.P.O. not to issue further licences for transmission above 56 Mc/s.

## NEW RADIO TELEPHONE

### Post Office Experiments Between Great Britain and Norway

THE growth of telephone communication between the United Kingdom and Norway has taxed the submarine cable beyond its capacity. In order to avoid the rather formidable expense involved by the laying of a new cable, a series of experiments is being carried out to investigate the practicability of a beam radio-telephony service between the Orkney Islands and the west coast of Norway. Daily transmissions from a G.P.O. experimental station have been successfully received by the Bergen Radio engineers.

Our correspondent states that the Norwegian Post Office is likely to construct a similar beam telephony transmitter, and Mr. Flanagan, a G.P.O. radio engineer, recently arrived in Bergen to inspect a site at Ulrikken close to that town.

## CONCERT PITCH

### World Standard Fixed

AT the recent Conference called by the British Standards Institution at Broadcasting House, it was decided that the international standard of musical pitch should be fixed at 440 c/s per second for the note A in the treble clef. The Conference was attended by experts of five nations and subject to the approval of their recommendations by members of the International Standards Association, the standard will be universally adopted.

It is suggested that musicians should be able to receive the note by wireless and by telephone. It was the International Broadcasting Union which urged the I.S.A. to endeavour to bring about an international agreement.

## 7-Mc/s BROADCASTING

### A Protest from British Amateurs

THE Radio Society of Great Britain has registered a protest with the G.P.O. regarding the unjustified and illegal opera-

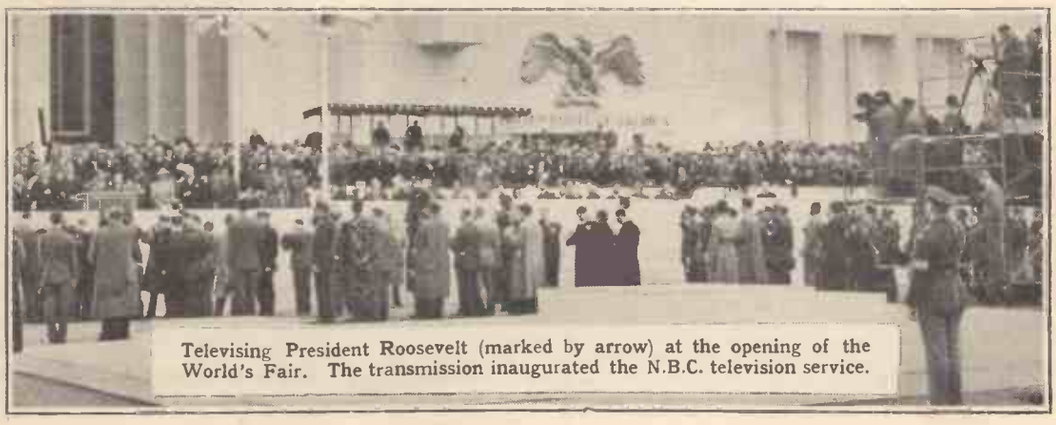

Televising President Roosevelt (marked by arrow) at the opening of the World's Fair. The transmission inaugurated the N.B.C. television service.

**News of the Week—**

tion of the French colonial station, Paris Mondial, on 7.28 Mc/s. The reason that prompted this protest, and that recently lodged by the A.R.R.L. with the American authorities, is that whilst the Cairo Telecommunications Conference agreed that from September 1st, 1939, broadcasting stations could transmit on frequencies between 7.2 and 7.3 Mc/s, Paris Mondial is already using 7.28 Mc/s.

The importance of the 7-Mc/s band to amateurs is stressed by the R.S.G.B., and the bi-annual occupancy figures of transmitters in this country using the band show that whereas in the second half of 1935 there were 716 amateurs transmitting on this frequency, the number in the same period last year was 1,263.

## "AERADIO" TRAINING SCHOOL

AT Wallington, Surrey, about one mile from the Croydon Airport, Marconi's Wireless Telegraph Company has opened an air-radio training school, the chief instructor at which is himself a qualified operator and engineer.

In addition to the practical and theoretical training required for the Aircraft Wireless Telegraph Operator's Certificate, instruction is provided for the signalling sections of pilots' and navigators' examinations, embracing Morse lamp signalling, radio direction finding, blind-approach guidance, etc.

As there are no fixed sessions instruction is arranged to suit students' individual requirements, and subject to the existence of vacancies students may be enrolled at any time.

The school is under the local management of the manager of the Marconi Aircraft Wireless Establishment, Wandle Road, Hackbridge, Surrey, to whom applications for admission should be addressed.

## 40-METRE D.F. COMPETITION

SOUTHALL RADIO SOCIETY captured the first and second prizes in the 40-metre open direction finding competition which the Golders Green and Hendon Radio Scientific Society organised in the St. Albans-Harpenden area last Sunday, May 21st. The transmitter, which was operated by Mr. Corfield, G5CD (P) of the organising society, took up four different positions.

More than 60 members of the various participating wireless clubs spent a very enjoyable day. Mr. Rapsey was the winner, with Mr. Swan a close second, whilst third place was taken by Mr. Black, of the Golders Green Society.

## *FROM ALL QUARTERS*

### Television and the Cinema

LAST Thursday the Postmaster-General received a deputation which included representatives of the Cinematograph Exhibitors' Association and the Kinematograph Renters' Society to discuss the effect of the development of television on the cinema industry. The deputation undertook to submit a written statement of their considered views on the subject, which the P.M.G. promised to bring to the notice of the Television Advisory Committee.

### Anti-German Broadcasts

A PIRATE broadcasting station which has been transmitting anti-German propaganda in Belgium was discovered by the police last week in a house at Berchem, near Antwerp.

### Pictures by Wireless

THE new system of picture transmission by wireless, now operating between Montreal and London, and New York and London, provides for the transmission of an $8\frac{1}{4} \times 4\frac{1}{4}$in. picture in less than eight minutes, a third of the time previously taken. As a result, finished pictures of the King and Queen's landing in Canada began to arrive at the offices of Cable and Wireless in Electra House, Moorgate, within a few minutes of the event.

### Sabotage

THE Arabic and Hebrew broadcasts on the Palestine White Paper, due to have been given from Jerusalem at 8 p.m. on May 17th, were not heard. It is reported in *The Times* that a breakdown was caused by the cutting of the telephone wires between the Jerusalem studio and the Ramallah transmitter. The staff went to Ramallah and the programme was resumed at 9.30 p.m.

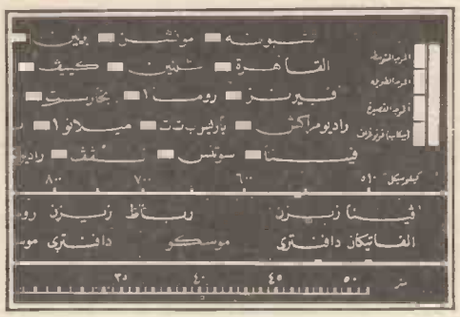


GERMAN ENTERPRISE. Perhaps the secret of the expansion of the German radio industry's over-sea market lies in the care taken to provide every facility for the listener abroad. Part of the tuning dial of a Telefunken receiver inscribed in Arabic is illustrated.

### B.B.C. Foreign Service

AN extended service of B.B.C. transmissions for listeners in Latin-America will start on July 3rd. The programmes, which are to take place from 11.25 p.m. to 2.20 a.m. (G.M.T.) daily, will be announced in Spanish and Portuguese. They will be radiated on GSO in the 19-metre band and GSC in the 31-metre band.

### The B.B.C. in Europe

MR. H. R. CUMMINGS, former London representative of the League of Nations Secretariat, has taken up the post of B.B.C. Public Relations Officer for Europe. He was in the Wireless News Department of the Ministry of Information in the Great War, and the News Department of the Foreign Office. He joined the Secretariat in 1920.

### Political Intrigue

NEWS of political intrigue and wireless comes from the port of Piræus, Greece, where an Athenian architect erected a mortuary chapel to the memory of his deceased wife. Headed by the Bishop of Athens, a procession bearing the corpse made its way to the chapel, where subsequently the architect spent long periods of mourning shut up with the coffin. The police became suspicious, and during the mourner's absence conducted a thorough search. It was revealed that the coffin contained a complete short-wave transmitter, which was being used for nefarious political purposes. The mourner's meditations were curtailed abruptly.

### I.E.E. Wireless Section

THE Committee of the I.E.E. Wireless Section has made the following nominations to fill the vacancies which will occur on the committee at the end of September: Chairman, E. B. Moullin, M.A. (Oxford University); Vice-chairman, Dr. R. L. Smith-Rose (N.P.L.); ordinary members, W. L. McPherson, B.Sc. (Eng.), (Standard Telephones and Cables), J. A. Ratcliffe, M.A. (Cambridge University), and M. G. Scroggie, B.Sc. (a consulting radio engineer and frequent contributor to *The Wireless World*).

### Amateur Awards

WILSON E. BURGESS, of Westerley, U.S.A., will be presented with the William S. Paley amateur radio award for 1938. He receives this distinction for his work during the hurricane which swept large areas of New England. When power was cut off and telephone lines wrecked he kept a battery-operated transmitter working, and was for forty-six hours the only link between Westerley and the outside world.

The Hiram Percy Maxim award for 1938 goes to Owen J. Dowd, of Brooklyn, New York. The prize is awarded to the amateur under twenty-one years of age whose radio work is voted by his confrères to be the most outstanding of the year.

### Car Radio Banned

A NEW regulation has been included in the Calcutta Motor Vehicle Rules by which wireless and gramophones are not to be permitted in motors in the city.

### National Field Day

THE seventh annual National Field Day organised by the R.S.G.B. will be held on June 3rd and 4th. A complete list of the stations, totalling over 100, which will be operating in 28 districts, is given in the May issue of *The T. & R. Bulletin*. In each district, with the exception of one, there will be transmissions in the 1.7-, 3.5-, 7-, and 14-Mc/s band.

### Extending Television

FOLLOWING the Manchester address by Mr. C. O. Stanley, Chairman of the R.M.A. Television Development Committee, in which he stressed the need for television facilities in the provinces, the Hon. Lionel Berry referred to the harmonious contact which his company, Allied Newspapers, had always had with wireless manufacturers. "We have not said 'television is coming to the North,'" he continued, "we have been careful, while advocating television, not to mislead the public by wild, rash statements."

### At Imperial Airways

AMONG those affected by the extensive reorganisation of the staff of Imperial Airways is Sqdn. Ldr. E. F. Turner, former Radio Superintendent. He will now become Communications Officer, in which capacity he will be responsible for all the Company's wireless and telephone equipment, as well as the meteorological services. Sqdn. Ldr. Turner was a Signal Officer in the R.F.C. and R.A.F. from 1915 to 1935. He joined the staff of Imperial Airways in 1936.

### Cost of World Convention

THE World Radio Convention, held at Sydney from April 4th to 14th, 1938, cost just over £6,300, of which sum £2,500 was granted by the N.S.W. Government. The actual cost to the organisers, the Institution of Radio Engineers (Australia), was a little over £100, the bulk being provided by contributions.

### Australian I.R.E.

THE growth of the Institution of Radio Engineers (Australia), which commenced its present activities in May, 1932, is given in a recent Proceedings of the Institution. This shows that, whereas in March, 1933, the number of members was 108, the membership at the end of November last year was 441.

### Enthusiasm Carried Too Far

RAIDERS drove up to a wireless dealer's shop in Spencer Street, E.C., shattered the window with a coal-hole cover, and carried away a television set. Are stolen peeps the sweetest?

### Miscellaneous Advertisements and Whitsun

ALTERATIONS in our printing arrangements are necessitated with the approach of the Whitsun holidays, and miscellaneous advertisements intended for the issue of June 1st must, therefore, be received not later than first post to-morrow, Friday, May 26th.

# AF Transformers Simplified

## COMPARISONS WITH OTHER TYPES

By N. PARTRIDGE, B.Sc., A.M.I.E.E.

*AS the author of this article points out, the belief seems to have grown up that speech-frequency transformers have little in common with power or similar types designed for constant operating conditions. A knowledge of the many points of similarity that actually exist is a great help towards a proper understanding of transformer operation.*

TRANSFORMERS as employed for radio purposes fall into two well-defined groups: (a) mains or power transformers and (b) audio or speech transformers. The two types have drifted farther and farther apart until nowadays each possesses its own technical jargon and it has become traditional to treat them as distinct and separate.

This duplicity of theory is liable to puzzle the novice and to make him wonder if there is or is not a basic principle governing transformers as a whole. How is it that in the one case voltage ratios are so important, while in the other the square root of the impedance ratio takes priority? Why is the no-load current never mentioned in connection with audio transformers and primary inductance totally ignored in the power type? What is the difficulty about bass response when a power transformer can be designed to work on 25 c/s without the slightest trouble?

The relationship between the mains and audio branches of the transformer family is a little analogous to that existing between the imaginary Smiths of Eastown and the hypothetical Smythes of Westown. In reality both are very human individuals, guided by the same emotions and striving towards the same end. The apparent difference is to be found in the technique of living and is entirely superficial as far as the zoologist, anthropologist, or whatever - ologist studies these things, is concerned.

For example, our Smythes might indulge in an apéritif before dinner, whereas our Smiths would undoubtedly prefer half a pint at the local hostelry prior to their equivalent of the aforesaid meal. Note how unlike are the technical terms! Nevertheless, a few simple experiments with apéritifs and half-pints will reveal certain points of similarity to the scientific enquirer. Likewise the procedures of "indulging in" the former and "having one" of the latter possess much in common.

Mains and audio transformers are fundamentally the same, but the widely different applications have made it convenient to approach design problems in technically different ways. Allowing a brief interval subsequent to the "half-pint" experiments, we will proceed to show how the two modes of thought may be correlated.

Electricity for power and lighting is distributed by means of a constant voltage system. This does not necessarily imply that one's supply voltage is, in fact, rigidly constant, but simply that all the houses in one district have the same mythical number stamped upon their meters. Should this be, say, 230 V, then we make a special point of buying lamps, cookers, etc., that are constructed to operate on 230 V. Hence one of the first things a purchaser wishes to know is that the nominal voltage of the equipment in view agrees with that of his supply. The next thing is, how much will it cost to run? Power is sold by the kilowatt-hour, and therefore the cost per hour or per day will be proportional to the watts. It follows that the current practice of rating things in volts and watts, such as a 230-V, 60-watt lamp or a 210-V, 3-kW fire, is very convenient and is sufficiently simple to be of use to the non-technical public.

TABLE 1

| Appliance | Watts | Volts | Amps | Ohms |
|---|---|---|---|---|
| Lamp... ... | 60 | 100 | 0.600 | 167.0 |
| | | 110 | 0.545 | 202.0 |
| | | 200 | 0.300 | 666.0 |
| | | 230 | 0.260 | 885.0 |
| | | 250 | 0.240 | 1,040.0 |
| Lamp... ... | 100 | 100 | 1.000 | 100.0 |
| | | 110 | 0.910 | 121.0 |
| | | 200 | 0.500 | 400.0 |
| | | 230 | 0.435 | 528.0 |
| | | 250 | 0.400 | 625.0 |
| Bowl Fire ... | 500 | 100 | 5.00 | 20.0 |
| | | 110 | 4.54 | 24.2 |
| | | 200 | 2.50 | 80.0 |
| | | 230 | 2.17 | 106.0 |
| | | 250 | 2.00 | 125.0 |
| Radiator ... | 2,000 | 100 | 20.0 | 5.0 |
| | | 110 | 18.2 | 6.05 |
| | | 200 | 10.0 | 20.0 |
| | | 230 | 8.7 | 26.4 |
| | | 250 | 8.0 | 31.3 |

All apparatus taking constant watts at a stated voltage must draw a fixed current which can be calculated by dividing the watts by the voltage. Thus the 230-V, 60-watt lamp will pass 0.26 amp. and it might well be called a 230-V, 0.26-amp. lamp, which is electrically just as specific. Again, the lamp has got a resistance or impedance which is found by dividing the voltage by the current and is, in this case, 885 ohms. Hence we might call it a 230-V, 885-ohm lamp, or perhaps a 0.26 amp., 885-ohm lamp or, indeed, a 60-watt 885-ohm lamp. Any one of these specifications is complete in itself and all of the others can be derived from it. Table 1 sets out the watts, volts, current and impedances of several typical pieces of domestic apparatus.

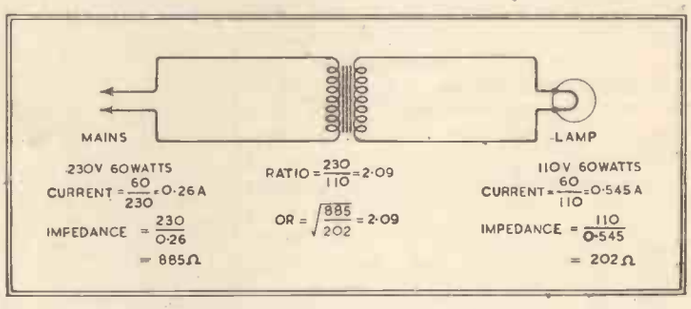


Fig. 1.—Illustrating the functioning of a power transformer working under constant operating conditions.

In order to get back to transformers, we will assume that Mr. Brown has had a 110-V, 60-watt lamp bequeathed to him and that he wishes to use it in his home, which is connected to the 230-V, 50-cycle system. Any ordinary individual can see that a transformer with a 230-V primary and an output of 110 V, 60 watts will do the job admirably. The ratio of the transformer would be 230 ÷ 110 = 2.09 to 1 step-down, and from a knowledge of small transformers the no-load current would be about 0.06 amp.

### Designing by "AF" Rules

But suppose Mr. Brown is not an ordinary individual. Imagine him to be an ardent designer of audio-frequency gear, whose life is one long round of decibels and impedances. Referring to Table 1, it will be seen that an impedance of 202 ohms, *i.e.*, that of a 110-V, 60-watt lamp, has got to be matched to, or made to behave like, 885 ohms, *i.e.*, impedance of a 230-V, 60-watt lamp (see Fig. 1). Therefore Mr.

**AF Transformers Simplified—**

Brown might absentmindedly say that the transformer ratio should be

$$\sqrt{\frac{885}{202}} = \sqrt{4.38} = 2.09$$

and, extraordinary as it may seem, he will get the correct answer. Actually there is nothing extraordinary about it, because the voltage ratio and the root of the impedance ratio are one and the same thing. The two calculations are just two different ways of arriving at the same answer.

Having determined the transformer ratio, Mr. Brown will probably ponder upon the frequency of the supply. Being as low as 50 c/s, the transformer must have a good bass response. The upper register is unimportant, so he can afford to make the primary impedance, say, four times that of the load (885 ohms), and the required primary inductance comes out at around 12 H, which is the same as that of a 230-V mains transformer drawing 0.06 amp. no-load current.

Our newly acquired friend gets accurate results even if he does go a long way round the houses to get them. But why should he choose so cumbersome a scheme when our own volts-watts mode of working is so delightfully simple? The answer is that an optimum load or a loud speaker cannot usefully be rated in volts and watts.

Consider a 15-ohm speaker engaged upon the task of emitting a typical radio programme. Between items there is silence and, therefore, no audio-frequency volts across the speech coil and no audio-frequency current through the winding. A little later massed trombones and tympani may be rendering Wagner, and there will be an abundance of volts and amps. around the speech coil. Clearly the speech volts, current and watts delivered to the speaker will vary from instant to instant throughout the entire transmission. There is only one thing that can, with justification, be regarded as constant and that is the nominal impedance of the speech coil, namely, 15 ohms.

The above reasoning applies equally to

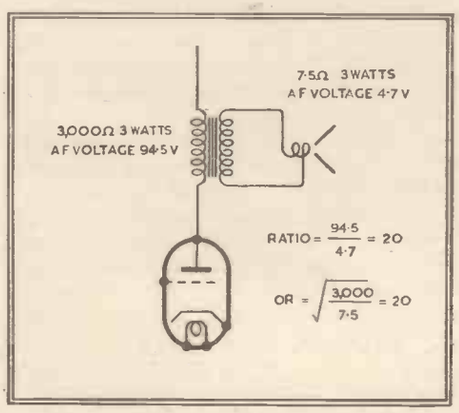


Fig. 2.—This diagram, representing a speech-frequency transformer in an output stage, should be compared with Fig. 1.

pick-ups, sound-heads, microphones, speech lines, valve anode circuits, etc. One is compelled to talk in terms of impedances instead of volts and watts. Thus we say that a certain valve has an optimum load of 6,000 ohms. Sometimes the maximum output, perhaps 5 watts, may be added. But the latter is strictly a statement of maximum power and does not compare with the watts specification of a lamp which relates to the power taken continuously.

Table 2 is the equivalent of Table 1, but deals with optimum loads and speakers instead of household appliances. The first group of volts and amps shows the voltages and currents that would result if a steady 3 watts were being dissipated. The remaining columns give similar information for powers of 6, 9 and 12 watts.

TABLE 2

| Impedance Ohms | 3 Watts | | 6 Watts | | 9 Watts | | 12 Watts | |
|---|---|---|---|---|---|---|---|---|
| | Volts | Amps. | Volts | Amps. | Volts | Amps. | Volts | Amps. |
| 10,000 | 173.0 | 0.0173 | 246.0 | 0.0244 | 300.0 | 0.0300 | 347.0 | 0.0346 |
| 8,000 | 155.0 | 0.0193 | 219.0 | 0.0274 | 268.0 | 0.0336 | 310.0 | 0.0386 |
| 6,000 | 134.0 | 0.0224 | 190.0 | 0.0316 | 232.0 | 0.0388 | 268.0 | 0.0448 |
| 4,000 | 109.0 | 0.0275 | 155.0 | 0.0386 | 189.0 | 0.0476 | 219.0 | 0.0550 |
| 3,000 | 94.5 | 0.0317 | 134.0 | 0.0447 | 164.0 | 0.0549 | 189.0 | 0.0634 |
| 2,000 | 77.5 | 0.0387 | 109.5 | 0.0548 | 134.0 | 0.0670 | 155.0 | 0.0774 |
| 1,000 | 55.0 | 0.0545 | 78.0 | 0.0770 | 95.0 | 0.0948 | 110.0 | 0.1090 |
| 30 | 9.4 | 0.32 | 13.4 | 0.45 | 16.4 | 0.55 | 18.9 | 0.64 |
| 15 | 6.7 | 0.45 | 9.5 | 0.63 | 11.6 | 0.77 | 13.4 | 0.90 |
| 10 | 5.5 | 0.55 | 7.8 | 0.77 | 9.5 | 0.95 | 11.0 | 1.10 |
| 7.5 | 4.7 | 0.64 | 6.7 | 0.90 | 8.2 | 1.10 | 9.4 | 1.28 |
| 4 | 3.5 | 0.86 | 4.4 | 1.36 | 6.0 | 1.50 | 7.0 | 1.72 |
| 2 | 2.45 | 1.22 | 3.46 | 1.73 | 4.25 | 2.12 | 4.9 | 2.44 |

An example or two will make clear what this table is about. Suppose a push-pull pair of valves has an anode-to-anode load of 10,000 ohms. If a steady voltage is fed to the grids of these valves and the volume adjusted so that an output of 3 watts is obtained, then the audio-frequency voltage across the 10,000-ohm load will be 173 V and the audio-frequency current will be 0.0173 amp. Similarly, if the volume is increased until the output reaches 9 watts the figures will become 300 V and 0.030 amp. Corresponding values for 6 watts and 12 watts are shown in the table to be 246 V, 0.244 amp. and 347 V, 0.0346 amp. respectively. The lower impedances mentioned in the table correspond to those frequently employed for speakers. Thus a 15-ohm speaker fed with a steady 6 watts will draw 0.63 amp. at 9.5 V and a 2-ohm speaker 1.73 amp. at 3.46 V.

Having held up the programme in order temporarily to fix the volts, current and watts we may as well see if our elementary ideas of voltage matching hold good. Suppose we try to match a 7½-ohm speaker to a valve requiring a load of 3,000 ohms. At 3 watts the corresponding voltages are 4.7 V and 94.5 V, hence a transformer with a primary wound for 94.5 V and a secondary output of 4.7 V should be correct, *i.e.*, the ratio would be 94.5 ÷ 4.7 = 20 : 1 (see Fig. 2). At a volume corresponding to 6 watts the values are 6.7 V and 134 V, which again give a ratio of 20 : 1. And still the same ratio is arrived at by taking the figures given for 9 or 12 watts.

The more orthodox calculation for determining the output transformer ratio would be:—

$$\sqrt{\frac{3000}{7.5}} = \sqrt{400} = 20$$

Once again the same answer is obtained, whichever of the two methods of working are used. It should be noted, however, that in order to use the simple volts ratio we had to devise Table 2, which involved a lot of juggling with Ohm's Law and several arithmetical processes. Mr. Brown's idea of taking the root of the impedance ratio avoids this inconvenience and gives the answer in one step.

A good transformer, mains or audio, should have a high efficiency, and the watts put into the primary should be substantially equal to the watts given out from the secondary. Hence all a transformer does is to increase or reduce the voltage and current in such a way that the product of the two, *i.e.*, the watts, remains unaltered. The apparent impedance of the primary and the impedance across the secondary can be calculated from Ohm's Law (volts divided by the amps.) and the root of the ratio of these impedances always comes out to be the same as the voltage ratio, which in turn is the same as the reciprocal of the current ratio. When converting one voltage to another the transformer ratio is most easily calculated direct from the voltage ratio, when working in currents it is best determined from the reciprocal of the current ratio, and when dealing with audio circuits, where neither voltage nor current is constant, the quickest method in the long run is to employ the root of the impedance ratio.

## Conclusions

The foregoing revelation does not entirely reduce the audio-frequency transformer to the level of the power transformer. Neither does it suggest that they are equally simple to manufacture. The power transformer works on a fixed frequency and at a constant flux density, *i.e.*, constant voltage. It is not difficult to design a transformer to operate at 10 cycles or at 20,000 cycles, but it is rather a task to make it work well at both of these frequencies. Again, flux density has a strong bearing upon iron loss and iron distortion. The output transformer must be satisfactory in this respect at any density from the maximum downwards and at any frequency. The power transformer can be regarded as a special case of the output transformer in which the frequency and primary voltage are fixed.

The Wireless World

# DC Mains Super

## THREE-BAND RECEIVER FOR THE DC QUALITY AMPLIFIER

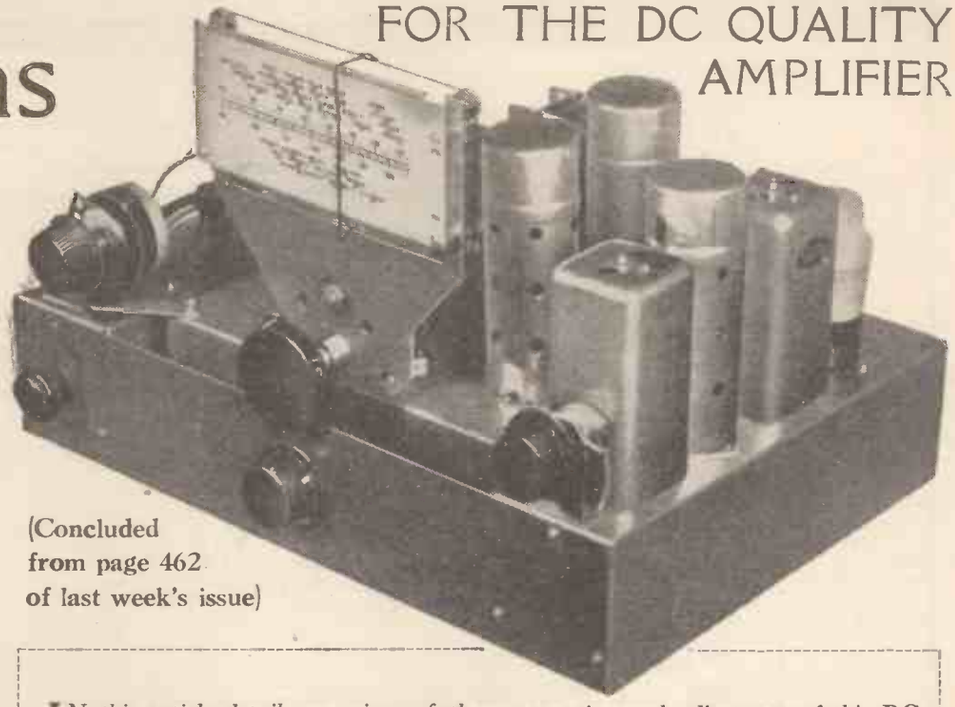

## CONSTRUCTION AND ADJUSTMENT

(Concluded from page 462 of last week's issue)

*IN this article details are given of the construction and adjustment of this DC mains set. A description of its performance is also given when tested in conjunction with the DC Quality Amplifier.*

THERE is nothing difficult in the construction and wiring of the receiver, for all parts are reasonably accessible, and the details are shown in the drawings which accompany this article. Care should be taken to see that the switches are mounted correctly in the tuner. This is chiefly a matter of ensuring that the centre rotating discs carrying the contact studs are all in the same relative positions before inserting the operating shaft. This point should be watched, since it is possible for the shaft to be inserted with the switch discs turned 180 degrees from their correct positions. Naturally, the contact studs do not then fall on the contact arms.

Check this carefully while assembling the components, for it is then easy to put it right if a mistake has been made. If it is only discovered when the coils and wiring are in place a lot of dismantling will be needed.

The coils are identifiable by their appearance, but the long, medium and short-wave coils also bear the numbers 1, 2, and 3 respectively, stamped on the brass mounting strips. The aerial coils are unmarked otherwise, the RF transformers carry a red spot on the former, and the oscillator coils a blue spot. In every case the long pair of solder tags is for the tuned winding. For the medium and short-wave coils, the grid end of the coil is remote from the primary winding and can readily be traced to its tag; the identification of the other tags then follows from the drawings. On the long waveband it does not matter which of the long tags is used for the grid connection.

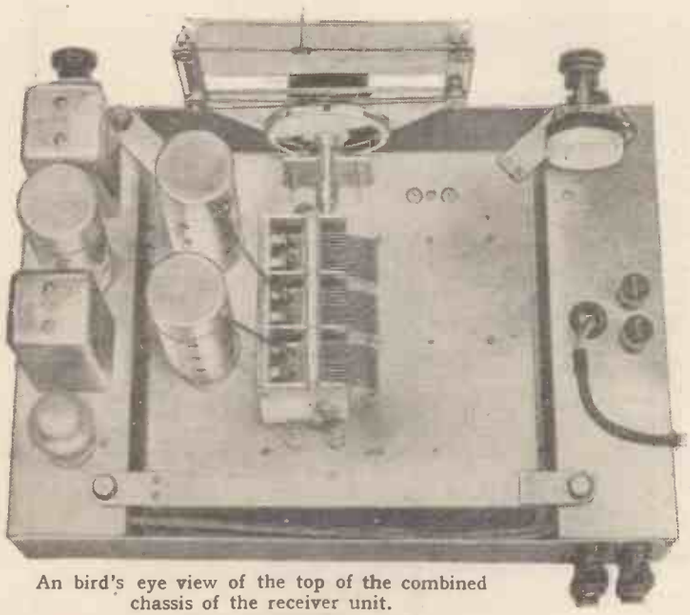

An bird's eye view of the top of the combined chassis of the receiver unit.

It must be remembered when using the apparatus that the chassis and all metal parts are live to the mains. Adequate insulation must thus be provided both from earth and from accidental contact. When the apparatus is installed in a cabinet, do not forget to see that the grub screws in the control knobs are adequately sunk so that they cannot be touched.

In order to avoid hum pick-up a screened lead should be used for the AF connection between the receiver and the amplifier, and "chassis" terminals are provided on each unit for connection to the screening. The connection should not, of course, be longer than necessary, but a yard length has been used.

The initial adjustments needed are only the usual and are best made with a modulated test oscillator. This oscillator should be set to 465 kc/s and its output clipped to the grid of the IF valve. The two trimmers in T2 are then to be adjusted for maximum output. The oscillator output is then transferred to the grid of the frequency-changer and the two trimmers in T1 similarly adjusted for maximum response—of course, with the switch S7 set for high selectivity. Then check over all four IF trimmers carefully.

### Ganging

Next connect the test oscillator to the aerial and earth terminals and set the waveband switch for the medium waves. If the oscillator is capable of a fairly large output, as most are, set it to 1,500 kc/s (200 metres) and the gang condenser to its minimum capacity. Short-circuit the medium-wave oscillator coil by a short lead terminating in crocodile clips and connect a low range voltmeter across R2. With the test oscillator at full output, tune to it by the trimmers C7 and C17. As the circuits come into resonance the meter reading will fall slightly if the oscillator output is adequate.

Then set the oscillator to 1,400 kc/s and tune the receiver to it by the gang condenser and readjust C7 and C17 at this frequency. Then remove the short-circuit from the set oscillator and reduce the output of the test oscillator considerably. Follow this by adjusting C27. Its setting will be very critical.

The next steps are to reapply the short-

# The Wireless World DC MAINS SUPER : Wiring Diagram

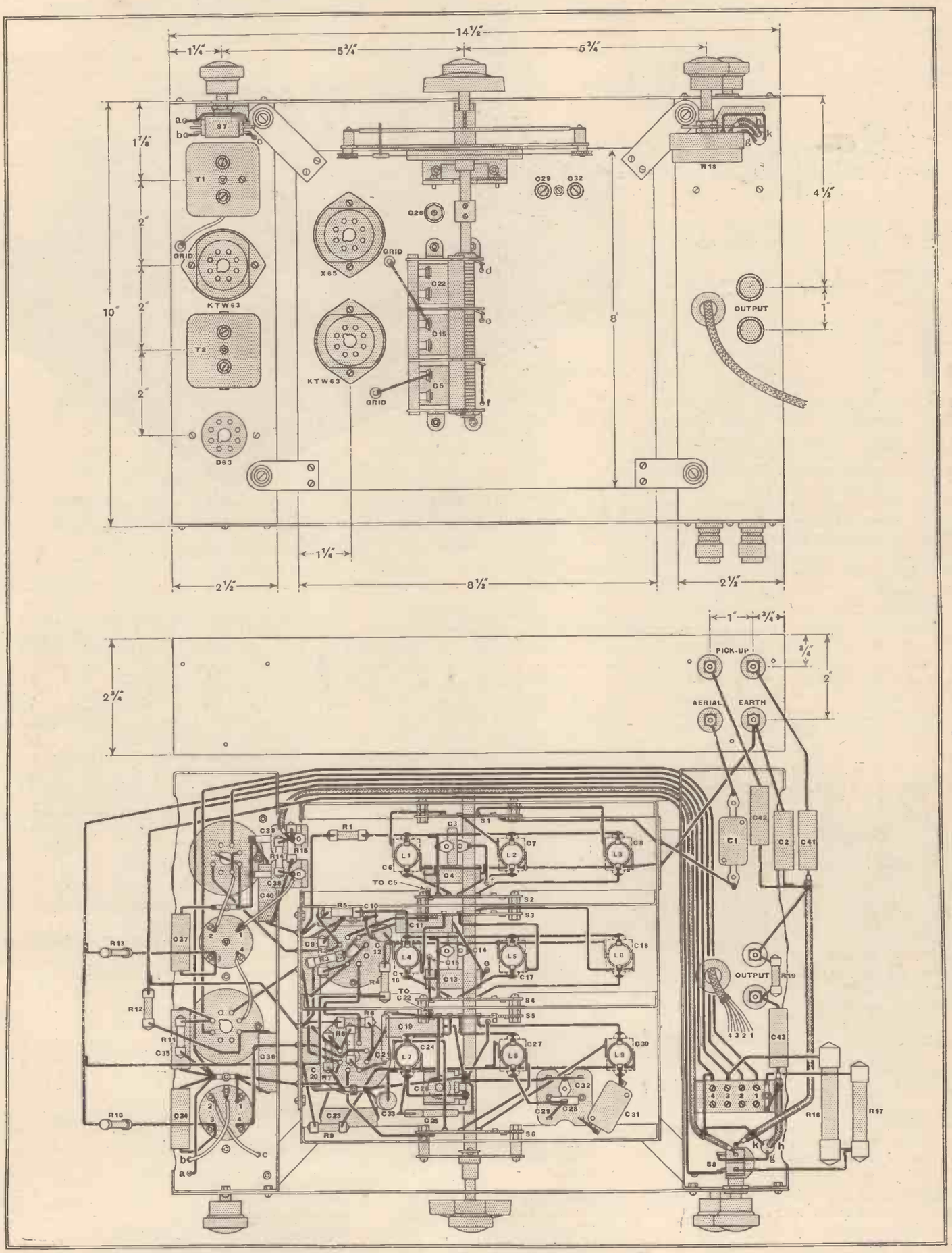


The identification of the components is readily carried out with the aid of the reference letters and the circuit diagram printed last week.

**DC Mains Super—**

circuit to the set oscillator, to set the test oscillator to full output at 600 kc/s and to tune the set to it by the gang condenser, again using the voltmeter as an indicator. Then remove the short-circuit, reduce the output of the test oscillator, and adjust the padding condenser C29. A return to 1,400 kc/s should then be made for a probable slight readjustment to C27.

On the long waveband the procedure is exactly the same, but the trimmers are C8 and C18 for the signal-frequency circuits and C30 and C32 for the oscillator. The first three are adjusted in exactly the same way as the medium wave ones, but at 260 kc/s instead of 1,400 kc/s. Then C32 is adjusted at 170 kc/s.

This procedure is theoretically possible also on short waves, but in practice rarely works very well. Set the gang condenser with the vanes about one-quarter enmeshed, and screw up C6 and C16 about half way. Then adjust C24. Even if no signal is found, there will usually be a point at which some hiss or local interference becomes audible. This affords an opportunity to adjust the signal circuits roughly.

Then connect the test oscillator to the aerial and earth terminals and swing its tuning control so that its frequency coincides with the receiver tuning. There will be two settings and one will give a stronger signal than the other. They will be found round about 12-15 Mc/s (20-25 metres).

Choose the stronger setting, and then adjust C6 and C16 for maximum signal strength. Next bring the test oscillator over to the other weaker setting and note whether it corresponds to a lower or a higher *frequency* than the stronger. If the weaker setting is at a higher frequency (lower wavelength) of the test oscillator than the strong one, all is well.

If it is at a lower frequency, however, the receiver has been lined up on the wrong beat. Increase the capacity in C6 and C16 and reduce that in C24, while retuning by the main control to keep the signal. Then carry out the adjustments in the manner already described.

The padding condenser C26 should be adjusted at the other end of the band, while rocking the tuning control backwards and forwards. It is not usually very critical, however, and is generally nearly fully screwed up.

On test the receiver was found to give a very good account of itself, being sensitive and selective, while capable of a very high standard of reproduction. The quality, in fact, was up to the best AC standards and far superior to most DC equipment.

On the mains employed in the tests hum was inaudible. There is no reason why hum should be expected in any district, but DC mains undoubtedly do vary greatly and it is impossible to be certain that hum will be absent in every case. Individual treatment is sometimes necessary with a DC supply.

The receiver covers the usual medium and long waves and is capable of receiving most worth-while transmissions on these bands. When interference conditions permit, advantage can be taken of the variable selectivity to improve the quality to a really high standard, but for general distant listening the use of high selectivity is advised.

The aerial is not unimportant and an outdoor aerial of reasonable efficiency is to be recommended, not necessarily because the receiver will not give a good signal with a poor aerial, but because the signal-noise ratio is always better with a good one.

On short waves the band of about 16-45 metres is covered so that the more important stations are included. Tuning here

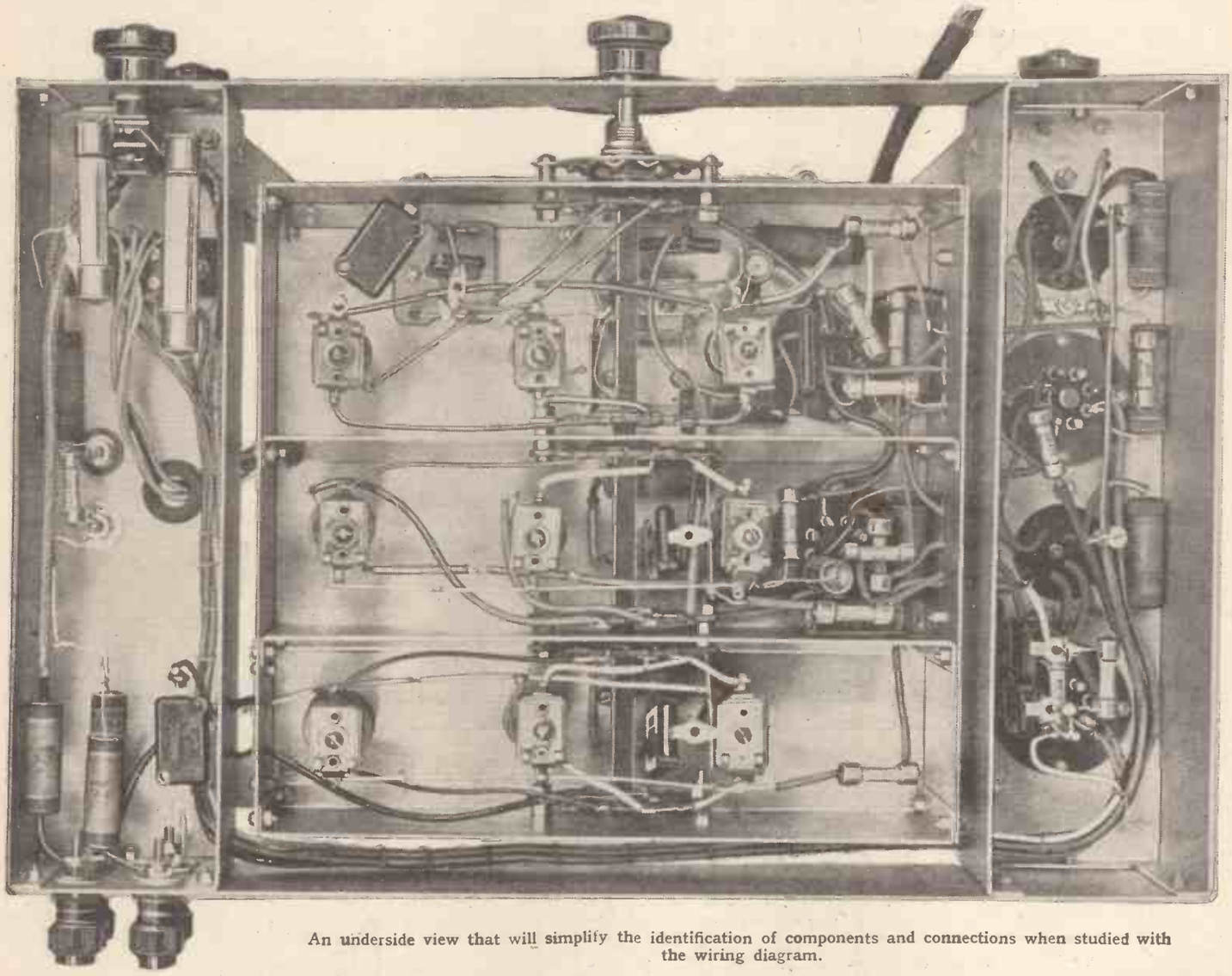

An underside view that will simplify the identification of components and connections when studied with the wiring diagram.

**DC Mains Super—**
is quite critical and the control should be rotated quite slowly or all but the strong signals will be passed over unnoticed. At suitable times, signals on the 16-metre, 19-, 25-, and 31-metre broadcast bands can usually be found, as well as the 20- and 40-metre amateur bands. In between these bands there are hosts of commercial transmissions employing CW or ICW morse, or "scrambled" speech.

In conclusion, it should be pointed out that two errors occurred in the circuit diagram in last week's issue. The padding condensers C31 and C32 were shown in parallel instead of in series, and the two leads to the centre and top contacts on the left-hand side of S8 should be reversed.

---

**Test Report**

# McMICHAEL MODEL 382

## Table Model AC Superheterodyne (8 Valves + Rectifier) and Tuning Indicator

**Price 18½ guineas**

IN designing this receiver the makers have first of all established a radio performance adequate for present receiving conditions and have then concentrated on refinements in the controls and automatic tuning arrangements which will improve the ease of handling without affecting performance. In particular, quality of reproduction has been carefully nursed throughout the circuit, and the performance in this respect is outstandingly good. An efficient motor tuning mechanism gives push-button selection of eleven stations.

*Circuit.*—The valves in the direct line of amplification from aerial to loud speaker comprise a triode hexode frequency-changer with band-pass input on medium and long waves, pentode IF amplifier, diode-triode signal rectifier and first AF amplifier and a beam tetrode output valve.

The control voltage for the tuning indicator is taken from the diode load resistance and an untuned third winding on the output IF transformer goes to the auxiliary IF amplifier supplying the AVC and automatic tuning (AFC) circuits. The use of this extra valve as a separate IF amplifier instead of as an RF stage before the frequency-changer has the advantage that signals below the AVC delay level which may be of good programme value are still capable of operating the AFC circuits. Of equal importance is the complete isolation of the AVC diode from the signal circuits and the consequent elimination of AVC distortion.

The AFC discriminator is the conventional balanced diode arrangement and the control bias is applied to a separate screened pentode valve which alters the reactance of the oscillator section of the frequency-changer valve in the appropriate direction to correct the tuning of the incoming signal.

A very effective tone control system incorporating both selectivity in the IF stage and negative feedback in the AF circuits has been adopted. There are four positions. In the first ("Fidelity") the band-width in the IF amplifier is increased by tighter coupling in the input transformer, and negative feedback incorporating tone correction which increases low-note response is introduced in the AF circuits. For the remaining positions the selectivity is returned to maximum and the second ("Normal") setting gives negative feedback at all audio frequencies, *i.e.*, less bass as well as a reduction of top from the increased selectivity. In the third ("Bass") position, one correction is re-introduced in the feedback restoring the relative lift in the bass and a by-pass condenser is connected across the volume control to increase the cut top. Finally, in the fourth position ("Foreign") the top cut is left as it is and the bass boost removed by once again applying negative feedback at all frequencies.

Negative feedback is taken from the secondary of the output transformer and introduced into the grid circuit of the triode first AF amplifier via a tapping on the volume control. The effect is to increase the ratio of bass response at low volume levels and so to compensate for the subjective raising of pitch.

As in most receivers with motor tuning it is necessary to verify the setting of the waverange switch before (or after) pressing one of the station buttons, but in all other respects the mechanism has been rendered foolproof by a comprehensive switching system. Automatic frequency control is made inoperative when the manual tuning button is pressed and also while the motor is running during automatic tuning. In this way, "trailing" of a powerful local station which might take charge up to the point where the motor came to rest is avoided. If two buttons are pressed simultaneously the contacts are so arranged that only one takes effect and the motor cannot "lock."

| *WAVERANGES* | |
|---|---|
| *Short* | *18.6—50 metres* |
| *Medium* | *200—550 metres* |
| *Long* | *850—2,000 metres* |

*Performance.*—Among the many attractive features of this set we would put first the quality of reproduction. A cabinet on the large side for a table model, a 10-inch loud speaker and a powerful output stage all contribute to the impression of console rather than table model quality. In the "Fidelity" position of the tone control switch the set does not require any special type of programme to show off its paces, a sure sign that the frequency range is wide and free from resonances. Both bass and treble show a considerable extension beyond the limits usually set in commercial receivers, and it is interesting to see that the makers regard the now almost forsaken band-pass input circuit as a worth-while refinement. The volume is unusually full, and there is little doubt that the output tetrode is giving the 5 watts at which it is rated with the minimum generation of harmonics. The tone compensated volume control works well, and maintains a good foundation of bass at low levels, and the four-position tone control with its multiple functions in various parts of the circuit is a great improvement over the simpler types.

The set makes no pretence to a "hot stuff" performance, but, never-

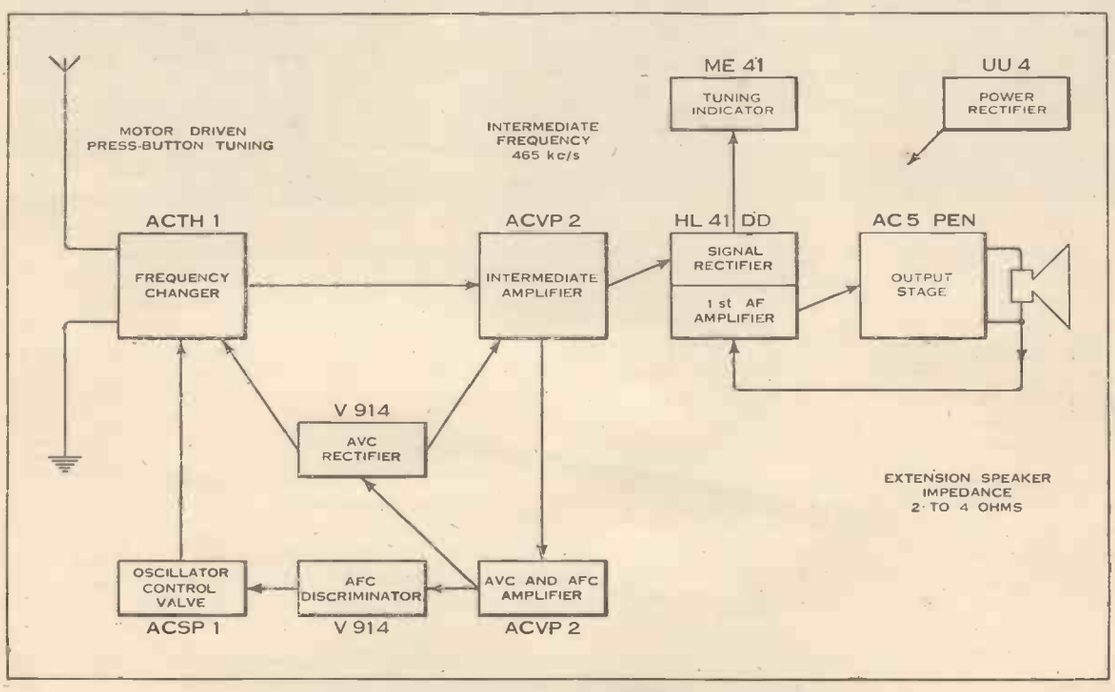


Schematic circuit diagram of the McMichael Model 382.

McMichael Model 382—

theless, brings in everything worth listening to with unobtrusive efficiency and the minimum of background noise. This is especially true of the medium and long waves which are clear of self-generated whistles, and sufficiently selective to satisfy all normal requirements. London Regional at a distance of 15 miles spreads the usual 1½ channels each side of its normal tuning point, and on long waves the Deutschlandsender programme can be well received with the tone control in the "Normal" position.

The good entertainment value of the receiver owes much to its efficient amplified AVC system, the advantages of which are nowhere more apparent than on the short-waves. Instead of flitting from station to station we found much more incentive to settle down to the enjoyment of full length programmes.

***Constructional Details.***—The chassis is a straightforward engineering job without gadgets, and is finished to the standard which McMichael have always set themselves. The cabinet design is simple and dignified with a large rectangular tuning scale bordered by two vertical rows of push buttons. Indicators show the settings of the waverange and volume controls, and a pilot light coloured to match the tuning indicator shows when the controls are set for automatic tuning. The tuning indicator is illuminated only when the "Manual" button is pressed.

A concentric two-speed tuning control is fitted, the outer ring of which gives motor "cruising" or "scanning" from one part of the scale to another, and the small centre knob final manual adjustment with a high reduction ratio. If the "scanning" control is operated while the set is under automatic control, a loud hum from the receiver warns the user "not to touch."

***Summary.***—This receiver gives a refreshing change from the stereotyped performance of the small table model superheterodyne. The extra cost is more than justified by (1) the exceptionally good quality of reproduction, (2) the general smoothness and ease of handling imparted by a good motor tuning device backed by efficient AFC and AVC systems.

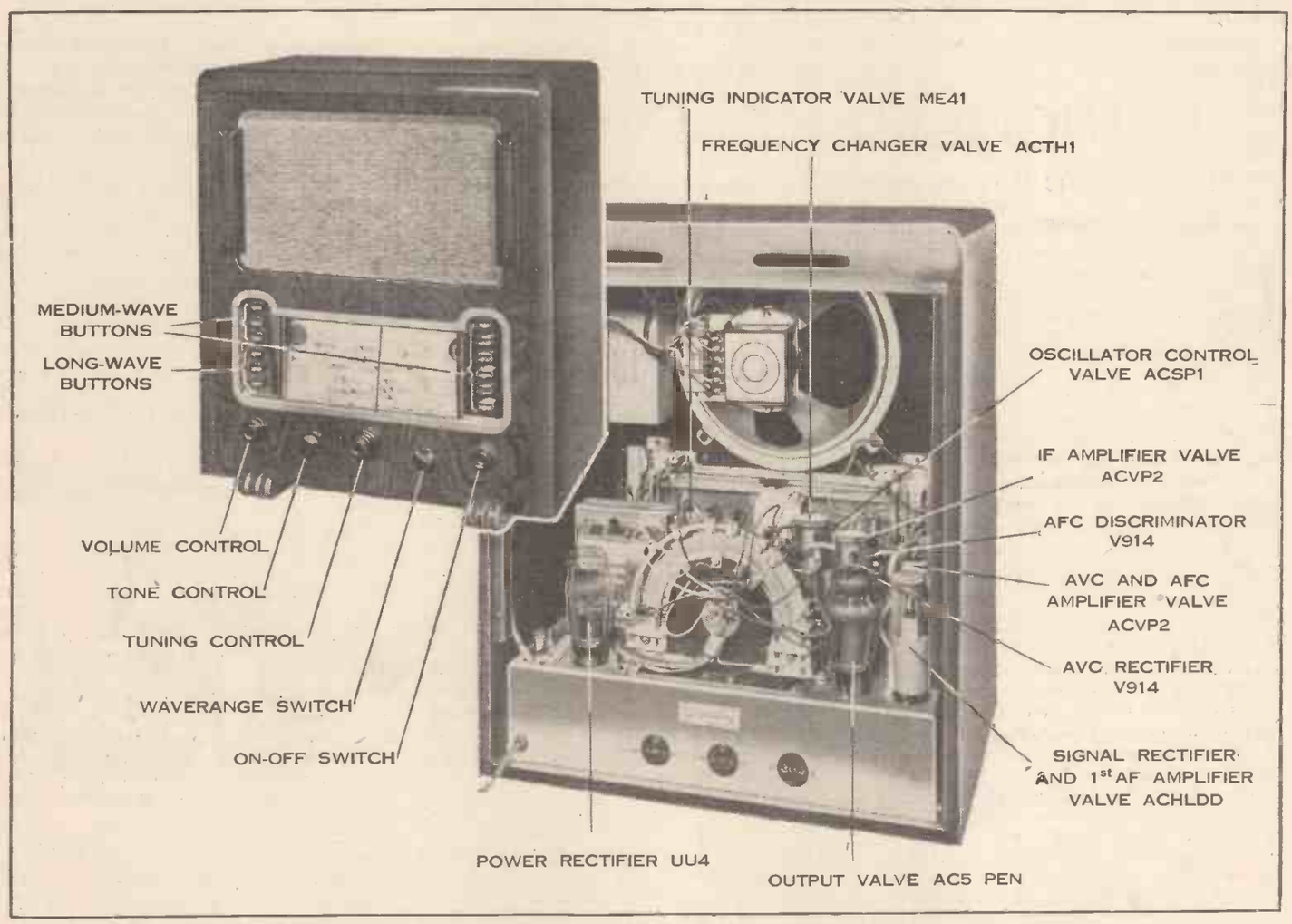


Layout of valves and controls in the McMichael 382. As sent out from the works three buttons are set for long and eight for medium-wave stations. The bottom right-hand button changes the circuits for manual operation.

# Club News

### *Edgware Short-wave Society*

**Headquarters:** Constitutional Club, Edgware.
**Meetings:** Wednesdays at 8 p.m.
**Hon. Sec.:** Mr. F. Bell, 118, Colin Crescent, Hendon, London, N.W.9.

Three more members have now obtained transmitting licences, making a total of 18 fully licensed members of the club. Several other members are applying for licences. At the debate held on May 10th on "Phone *v.* CW" it was agreed by all that CW and phone should occupy separate parts of the amateur waveband, CW having two-thirds of the available ether space.

Future activities include a lecture by Dr. Smith on "Telcon Cables," a 5-metre field day and the R.S.G.B. field day.

### *Hoddesdon and District Radio Society*

**Headquarters:** Blairgowrie, Station Road, Broxbourne, Herts.
**Meetings:** Second and fourth Wednesdays in the month at 8 p.m.
**Hon. Sec.:** Mr. T. Knight, Caxton House, High Street, Hoddesdon, Herts.

On May 10th Mr. Jackson, of Bishop's Stortford, gave a talk on television and demonstrated his home-constructed receiver. On May 21st there was a 1.7-megacycle field day. There have also recently been talks on USW and DF apparatus. Several field days are to be held during the summer.

### *Maidstone Radio Society*

**Headquarters:** 244, Upper Fant Road, Maidstone, Kent.
**Meetings:** Tuesdays at 7.45 p.m.
**Hon. Sec.:** Mr. P. M. S. Hedgeland, 8, Hayle Road, Maidstone, Kent.

A party of members spent an enjoyable evening at the Medway Society's "hamfest" on May 10th.

On June 3rd and 4th Mr. S. A. G. Cook will be operating his portable transmitter as an unofficial NFD station. A DF field day will be held on June 18th.

### *Medway Amateur Transmitters Society*

**Headquarters:** The Navy Wives' Club, Dock Road, Chatham, Kent.
**Meetings:** Tuesdays at 8.15 p.m.
**Hon. Sec.:** Mr. S. A. C. Howell, "Veronique," Broadway, Gillingham, Kent.

The "hamfest" held on May 10th was attended by amateurs from many parts of Kent. G2IG gave a talk on television, and G6WY dealt with the use and misuse of the amateur bands.

The transmitter is now complete and it is hoped that the Society's licence will be granted very soon.

### *Sale and District Radio Society*

**Headquarters:** St. Mary's School, Barkers Lane, Sale, Lancs.
**Meetings:** Thursday evenings.
**Hon. Sec.:** Mr. S. C. O. Allen, 31, Ennerdale Drive, Ashton-on-Mersey, Lancs.

At the last meeting a letter was read from Sir Edward Grigg, the M.P. for the Altrincham division, replying to the recent resolution passed by the Society calling for an extension of the television service to the north. Sir Edward promised to do all he could to support the resolution.

### *Slough and District Short-wave Club*

**Headquarters:** 35, High Street, Slough, Bucks.
**Meetings:** Alternate Thursdays at 7.30 p.m.
**Hon. Sec.:** Mr. K. A. Sly, 16, Buckland Avenue, Slough, Bucks.

At the last meeting the main item of interest was a demonstration by a member of high-voltage electrical phenomena. Three members have enlisted in the Territorial Army, including Mr. R. J. Sly, who has, therefore, been forced to resign the position of hon. secretary. A successful junk sale has been held. The next meeting will take place this evening (May 25th).

# UNBIASED

By FREE GRID

## A Raw Recruit

I AM, as you well know, always willing and ready to help readers in their wireless troubles to the best of my ability, and nothing pleases me more than to see my breakfast table stacked high with technical queries, although I may say that these feelings are not always shared by Mrs. Free Grid, more especially when, as sometimes happens, the whole pile topples over on her as she is consuming her morning portion of filleted frogs, a new reducing diet which I am told is all the rage in certain circles at present.

There are, however, limits to my patience, and sometimes I must admit the queries irritate me very greatly, as many of them betray a crass ignorance of the elementary principles of radio to a degree which I could hardly believe possible in these enlightened days. One letter which I found in my postbag the other morning betrayed exceptional lack of knowledge, and although it was not of a technical nature it revealed such amazing ignorance of the ways of the world of wireless in general that I feel constrained to mention it to you.

Briefly, my correspondent told me that he was engaged in the construction of a new receiver, and had duly ordered all the components, most of which had arrived, but that he was completely hung up in his constructional work by the fact that a

Toppled over on her.

certain tuning condenser had not yet turned up. "It is now ten whole days since I ordered this component," he wrote, "and not only has it failed to arrive but I have not received one word of explanation from the manufacturers concerning this unheard-of delay. I trust, therefore, that you will not only write to this manufacturer on my behalf but will give due publicity to this monstrous state of affairs in the pages of *The Wireless World*."

I think I need hardly say that I was amazed at the contents of this letter, and it was not until I came to the postscript that I was vouchsafed an explanation. "I think I ought to mention," my correspondent wrote, "that I am a newcomer to wireless." This, of course, explains everything. "To know all is to forgive all," as the old wisecrack has it, and I freely forgive him.

My correspondent has a lot to learn yet of the weird ways of our wireless manufacturers. Ten days, indeed! Perhaps it will help him if I tell him that I am still awaiting delivery of a marvellous new crystal which I saw favourably mentioned in the editorial columns of *The Wireless World* as far back as 1926. "Ananite," it was called, and when I ordered it I was told that the demand exceeded the supply with the result that the whole factory output was sold for some time to come and I might, therefore, have to wait a considerable time for delivery. I am still waiting!

## A Fishy Story

I DARESAY that most of you noticed the picture published recently in this journal (p. 421, May 4th) of a dog with a small receiver and loud speaker strapped to his back. However far the dog strays from home, its owner has only to speak into the microphone of his home-built transmitter and he can summon the animal home. According to the reading matter underneath the picture, the dog and its owner reside in Sydney, but as the four towns of this name are situated many thousands of miles apart, and the writer very skilfully omitted to say which one he meant, I was prevented from sending a telegram of protest to the authorities of the place concerned.

If this sort of thing is allowed to go unchecked abroad it will not be very long before it spreads to this country, and we shall have a new source of interference to contend with. It was not for some considerable time that it dawned on me that several of the cats wandering about my neighbourhood and belonging to a rather vinegary-looking spinster carried suspicious-looking bundles on their backs, bundles which I had always taken to be merely superfluous clothing which some spinsters insist on inflicting on their unfortunate pets.

Needless to say, I lost no time in impounding one of the cats which I found wandering about in the neighbourhood and quickly removed its bundle of clothing, expecting to find a miniature battery portable and loud speaker. To my surprise, however, I came across something very much more serious which puzzled me for a long time. It was nothing more nor less than a miniature flea-power USW transmitter. I use the expression flea-power in a purely figurative sense, of course, in order to convey an idea of the smallness of the power employed and not to indicate that, by some ingenious system, power was obtained from the fauna in the cat's fur.

I was very puzzled for a long time, and even more so when I found out by listening in on my USW receiver that a long dash was being sent out automatically every few seconds. I lost no time in impounding all the other similarly clad cats in the neighbourhood and it was due, I suppose, to the fact that some tittle-tattling neighbour must have seen me that eventually I found a policeman on my doorstep.

It appears from the explanations that were given that the transmitters were the property of a scientific investigator who is lodging in the spinster's household, and is carrying out DF research work in connection with A.R.P. The cats have been chosen because they are first-class nocturnal wanderers, and it was just this sort

Suspicious-looking bundles.

of thing that was wanted to enable the investigator to check up on his DF experiments. For the life of me I cannot think what DF has got to do with A.R.P.; in fact, it all seems very fishy to me, almost as much so as the state of my laboratory after my feeding the cats on their favourite diet during their few days' enforced stay with me.

## After 17 Years

I AM delighted to learn that after all these years of radio exhibitions it has been decided that this year there shall be a technical section. Apparently the matinée idols are still to be retained on the ordinary stands in order to give the women and children something to look at while father is having a quick one in the technical section. I fully realise that we do not want the technical part of the show jammed up with people who have come merely to see the fat lady and other sideshows, but if the technical section is to be made a *sanctum sanctorum* of men, as I learn, it will only lead our womenfolk to think that the technical experts whom we go to consult about our mixer problems are brassy blondes, more used to drink-mixing than frequency-mixing.

# The B.B.C.'s German News Bulletins

## ARE THEY RECEIVABLE ON THE "VOLKSEMPFÄNGER"?

*AS the average German broadcast receiver is well known to be of lower sensitivity and selectivity than its British counterpart, most readers will have wondered whether the B.B.C.'s broadcasts in the German language have been successful in "getting over." A correspondent in Germany has, therefore, been commissioned to make a test under ordinary conditions with the two most popular German sets.*

The Volksempfänger and the Kleinempfänger compared. Both are straightforward detector AF receivers.

SOME doubt has been expressed in certain quarters as to whether the B.B.C.'s news broadcasts in the German language are really serving their purpose in putting the British point of view before the German man-in-the-street. It is not a question of whether the text of the bulletins is suited to the particular psychological make-up of the ordinary German citizen—that is another matter rather outside our province—but whether they can be heard at all having regard to the simple type of receiver commonly used by many of the inhabitants of Germany. It was in order to answer this question that a special correspondent of *The Wireless World* was commissioned to conduct certain receiving tests in Germany, the results of which we detail herewith.

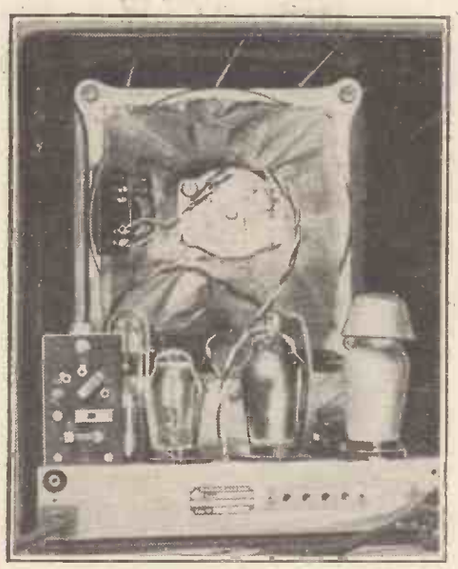

The Volksempfänger, shown here, has many refinements not found in the Kleinempfänger, including a separate output valve.

Probably everybody has heard of the Volksempfänger or "People's Receiver," and the reason why it was put on the German market, namely, to bring wireless reception within the limited means of the great majority of the population. From the fact that it was found necessary to market this cheap receiver, which for mains operation costs only £3 15s., it may be safely assumed that there was a crying need for it, or, in other words, that many Germans could not, or would not, pay any more. That this assumption is more than justified is proved by the fact that it has been necessary to produce a still cheaper receiver, which is called the Kleinempfänger, or "little receiver," and can be obtained for thirty-five shillings.

Now it needs very little effort of the imagination to realise that, at the prices mentioned, the Volksempfänger and the Kleinempfänger must be very simple instruments indeed, without any pretentions to sensitivity and selectivity, but nevertheless adequately fulfilling the purpose for which they were mainly intended, namely, to enable the population to listen in to the political pronouncements of the German authorities. These are, of course, always simultaneously broadcast by all stations on important occasions, thus enabling them to be heard even by the owners of the Kleinempfänger, which is intended to be very little more than a local-station receiver. These receivers, being of the simple regenerative detector-AF type, cannot be used for foreign-station listening without a certain amount of juggling with the reaction control.

### The Sets on Test

There are, of course, a large number of ordinary superhets sold every year in Germany, but there is rather a big gap between the £3 15s. Volksempfänger, and the cheapest superhet which costs nearly £11, and, although there is evidence to show that an astonishing number of the German working class do possess these more sensitive receivers, there must be a far greater number who do not, otherwise the Volksempfänger and the Kleinempfänger would not be necessary. Within their obvious limitations, these sets are effective enough from the sensitivity and selectivity points of view, but they are, of necessity, far behind the ordinary superhet in these respects.

With regard to the actual tests, both sets were tried out in a Berlin flat, using an indoor aerial; conditions which are fairly representative of those under which town-dwellers in Germany have to use wireless. The Kleinempfänger, although surprisingly sensitive, failed to bring in any British station during normal broadcasting hours. An outdoor aerial would probably have remedied this so far as actually hearing British stations was concerned, but the background from the local transmitter, which was rather annoying even when using the indoor aerial, would have rendered reception impracticable, without careful adjustment of an external wave-trap. After the German stations had closed down, Droitwich and one medium-wave transmitter were the only worthwhile transmissions heard from this country.

The Volksempfänger, as might be expected, did somewhat better. The North Regional station was received during the time that the German stations were on the air, but our correspondent points out that,

Fig. 3.—The Kleinempfänger employs one multiple valve and a mains rectifier.

on any set, the reception obtainable from this station varies greatly from day to day. Late at night the London and Northern Ireland Regional stations were heard. Droitwich was also picked up, but this station's transmissions were, as they

**The B.B.C.'s German News Bulletins—**

usually are, marred by considerable morse interference.

The important point to remember is, however, that tuning was done by somebody who has had considerable experience in using many types of wireless receiver for several years past, although, on the other hand, our correspondent reports that the necessary tuning was well within the capabilities of the average completely non-technical citizen. He also states that, as might be expected in the case of these cheap sets, the various stations do not always come in at the same spot on the dial but vary with the adjustment of the reaction control.

Bearing all these facts in mind, therefore, we have to ask ourselves whether the average German citizen would bother to tune in the British transmissions? The ordinary British listener of to-day certainly would not do so in the same circumstances, but we must remember that the average German is far more painstaking than ourselves and, in addition, has not been pampered with a surfeit of superhets and push-buttons as we have. Also it must not be forgotten that there is a considerable number of country-dwellers in Germany who, by reason of their remoteness from a powerful local transmitter, and their facilities for erecting a good outdoor aerial, would have little difficulty in receiving the British transmissions.

Even making these allowances, however, we are reluctantly drawn to the conclusion that the B.B.C. broadcasts do not "get across" to the bulk of the German population as well as they might do.

# Letters to the Editor

The Editor does not necessarily endorse the opinions of his correspondents

### *Condenser Impedance*

I WAS very glad to notice Mr. M. G. Scroggie's letter in your issue of May 18th concerning my article in the preceding number.

A careful check on the calculated inductance of straight wires did not indicate the discrepancy in the resonant frequencies as suggested by Mr. Scroggie, but a further search revealed that the formula used included a printing error which accounted for the discrepancy. I must apologise for this unforeseen error and hasten to append herewith a corrected family of curves with which I trust Mr. Scroggie will agree.

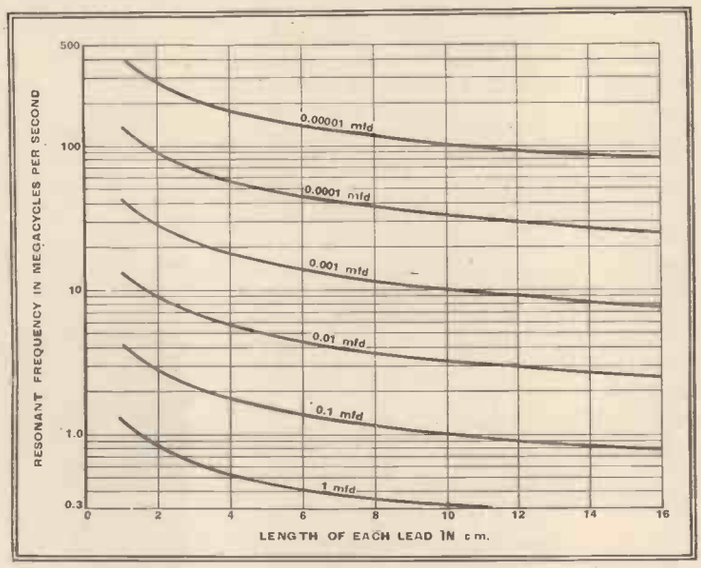


Revised graph showing the resonant frequency of various capacities with 20-SWG leads of lengths up to 20 cm.

For his and readers' information they are computed on the base of negligible mutual inductance between the wires, which are assumed to lie along the longitudinal axis of the condenser itself. The main object of the article was to point out that the so-called non-inductivity of a tubular condenser is unimportant, since the connecting leads themselves are by far the greatest contributors to this property.

F. R. W. STRAFFORD.

Enfield, Middx.

### *Relaying Television: Use of Frequency Modulation*

THE articles by "Cathode Ray" and by your New York Correspondent on frequency modulation or, as it is sometimes called, phase modulation are of great interest.

While the operation of frequency-modulated broadcasting stations may not be practicable at the present time, an immediate use for this system suggests itself. I refer to the provision of a radio link between Alexandra Palace and the television transmitter which it is proposed shall be erected in the Midlands immediately the Television Advisory Committee have concluded their deliberations.

There are many advantages in using frequency as opposed to amplitude modulation for this purpose. The installation and running costs are likely to be minimised owing to the low power and greater range of the former type of transmitter. Secondly, the quality is likely to show a considerable improvement, due to the absence of atmospherics and interference. Thirdly, the greater range might easily reduce the number of relay stations or "repeaters" required between any two points.

It may be said that there is no record of frequency modulation having been used for television purposes and that there is not sufficient time available to develop it. To this I would reply there is probably ample data available in America for the asking; and, further, that the television station to be erected in the Midlands will not by any means be the last. I would therefore suggest that there is no time to be lost in examining a form of communication of which little is yet known in this country.

HOWARD HEATON,
Radio Correspondent,
*Sunday Mercury*, Birmingham.

### *Voice of the State*

I HAVE read with interest your remarks in *The Wireless World* of May 11th, and regret you should find yourself advocating a form of censorship. As things stand, the B.B.C. provides the only news service without partisan politics. A Press review, although desirable, would not adequately replace the present news service.

You allege that the average man thinks that the B.B.C. speaks for the Government, but are not you yourself labouring under a worse misconception? The Government under the British Constitution is *not* the State. Furthermore, the B.B.C., to my mind, is, and rightly, the voice of the State.

Its job is to speak for every section of society in this country and to provide an unbiased foreign news service on the spot, not six or twelve hours late in the shape of a Press review. The average man does not want the B.B.C. to become the voice of the Government, as is the case in the totalitarian States.

If confusion does exist, it would be a simple matter to broadcast official communiqués separate from general news.

Uxbridge, Middx. JOHN GREGORY.

### *Shaver Interference*

YOUR correspondent in *The Wireless World* of May 11th, Mr. W. H. Pierce, has my sympathy. I am keen on ultra-short wave reception and I use a Philips 362A. Recently I was given an electric shaver, and it certainly caused a lot of interference. I have since found that a migdet 0.01-mfd. condenser across the points completely eliminated all interference.

My razor was fitted with a small condenser, but it is not connected across the points.

If my next-door neighbour was using an electric shaver I should volunteer to fit a condenser free. It would be well worth it.

Southampton. J. A. YEARSLEY.

### *Designing a School Receiver*

I SUBMIT the following comments on the design for a school receiver as proposed by "Assistant Master" in your issue of May 11th:—

(a) Arrange each section of the set on separate metal baseboards. (I have used with success thin sheet metal, either aluminium or zinc, fitted to wood bases ¾in. thick, the thin metal being easy to work by hand, either drilling or punching.) As ventilation is necessary, the glass covers would have to be removed when the equipment is used, or, alternatively, the front and top could be of glass, with metal gauze (for free air circulation) for the sides.

(b) The circuit suggested should be very suitable, especially for high-quality reproduction, and the tone-control stage most desirable. For the resistance capacity-coupled amplifier *The Wireless World* one, described in the issue of April 3rd, 1936, should form a suitable basis.

(c) As the accuracy desired is not always easy to obtain, except in well-equipped workshops devoted to the manufacture of radio apparatus, it would be more desirable

to purchase the inductances than to wind them.

(d) Good soldered joints should be made where possible.

(e) The valves should be 4-volt types, all indirectly heated, except the power valves in the audio-frequency output stage, which might be directly heated 4-volt types.

(f) Heater current obtained from large-capacity accumulators is quite suitable.

(g) High tension from large-capacity cells is very good, if attention is paid to them. Interference (mains-borne) is greatly reduced by their use.

(h) The output suggested would enable good-quality reproduction to be obtained, without working the equipment near "full-out" position. Also, several loud speakers could be used, with adequate volume per speaker, if this was required, as it sometimes may be.

The use of metal baseboards (not chassis) not only leaves the set open for inspection and demonstration as desired, but also cost is reduced, and construction is easier for persons not accustomed to this kind of work.

The tone-control unit described in *The Wireless World* of January 6th, 1938, should be a suitable type. KEN. G. PAYTON.

West Bromwich.

### *Paper Records*

SIR JOHN FALSTAFF said: "I can find no remedy for this consumption of the purse." His wail must be echoed by many nowadays who like to have good gramophone records. The announcement about "Paper Records" in your issue of May 11th gives one hope. They seem to be just what the doctor ordered. Let us hear more of the "Paper Phonogram." It ought not only to provide the remedy Falstaff sought, but do much more, to wit: (1) cure needle scratch; (2) allow a full bass; (3) and full-range treble; (4) save the exasperating changing of records and needles in the longer pieces of music and for speech recording.

Think also of the gain to schools, lecturers and for instructional purposes of all sorts. W. McKECHNIE (Lt.-Col.).

Hastings.

# Random Radiations

By "DIALLIST"

## Concert Pitch

WELL, one thing at any rate has at last been standardised the world over, and the B.B.C. can claim a large share of the credit. At a conference between experts forming a committee of the International Standards Association, held recently at Broadcasting House, it was decided that the "A" of the treble clef, used by orchestras as a tuning note, shall have a frequency of 440 cycles a second. Up to now different countries have had their own standards, varying from 435 to 442. With the A at 440 c/s, middle C becomes 262, D 294, E 331, F 350, G 392, and B 495. Once the standardised tuning comes into force, as presumably it will almost immediately, those with good ears will be able without trouble to assign an exact frequency to loud speaker and cabinet resonances that they track down. Resonance hunting has always been rather fun; it will be still more interesting with a standard pitch for concert transmissions. I wonder, though, whether the next series of measurements made with the cathode-ray oscillograph of Drs. van der Pol and Addink[1], will show that orchestras are strictly keeping the new pitch!

## Whiskrospherics

MY deepest sympathy goes out to Mr. Pierce, of Beckenham, Kent, who reported in a recent issue of *The Wireless World* that a neighbour's electric razor was completely blotting out morning reception of the 14 Mc/s Australian and New Zealand stations. I have heard that the motors used in razors are very difficult to suppress. One wonders why those who make the things didn't have a bit of research done before putting them on to the market with a view to seeing whether an innocuous motor couldn't be evolved. Couldn't a small induction motor be designed to do the job quite well? One thing I do know is that the use of interference-causing motors is having some adverse effect on sales. Several people who refuse, in the interests of wireless, to have radiating appliances in their homes, have told me that they have sent them back after trial. My own good deed, as a practical contribution to the anti-interference campaign, was to turn down my better half's suggestion of giving me one for a birthday present.

## Adverse Conditions

A PITY—wasn't it?—that bad radio conditions accompanied the relay from Quebec of the landing of the King and Queen from the *Empress of Australia*. I hadn't been listening to it long before I began to congratulate myself that it wasn't my job to work the controls at the receiving end. That must have been a ticklish business, for there was a nasty little morse signal that kept on drifting in and out. Luckily the fading and the various forms of interference were not bad enough to spoil the relay. When the signal went right out just as the commentator announced that the King and Queen were about to step on to the gangway, I feared the worst. Luckily it came back again in time and we were able to hear the cheering and the twenty-one gun salute as His Majesty's foot touched Canadian soil. Later I tuned in direct the N.B.C. commentary on the 15-Mc/s band. It was weak, fading badly and also suffering from the unwelcome visits of a morse signal. What a nuisance those morse transmissions are on the higher-frequency short-wave bands! There don't seem to be many of them as a rule; but as sure as eggs are eggs if there's one about it will be on the station that you most want to hear.

[1] "Orchestral Pitch," by van der Pol and Addink, *The Wireless World*, May 11th, 1939.

## More Power to Their Elbows

THE R.M.A., I observe, has appointed a small committee of its members to conduct a campaign against interference. I am all in favour of small committees: with larger ones it's always difficult to "cut the cackle and come to the 'osses"; small ones can get things done. I hope that this committee will take the line that the best way to get rid of undesirable things is to strike at their roots. With that end in view they might well launch their campaign by bringing home to manufacturers and others connected with the radio industry the folly (to put it mildly!) of turning out domestic electrical appliances that produce interference and then of urging wireless shops to sell them. It's of little use for the man-in-the-street to be encouraged at one moment to do his bit against intereference if at the next he is urged to buy and to use in his home apparatus that is certain to cause it in his own house, and very likely in those of his neighbours as well. Nor will other manufacturers give much heed to any protests that the R.M.A. may make unless it can show that it has already cleaned up its own stables.

## Theatres of the Future

THE present position of television in the ciné theatre programmes, in which it provides more or less brief interludes between films, rather reminds one of what used to be done in the early days of the cinematograph. Those whose memories stretch back into the early nineteen hundreds may remember that before there were any regular ciné theatres, the "bioscope" was often used to provide one or more turns in music-hall programmes. Television entertainment is a bit better than that and on the big screen it is not just a turn. I shouldn't be surprised if the television theatre, with full-length programmes, is one day as common as the ciné theatre is now.

### HENRY FARRAD'S SOLUTION

(See page 486)

FRED NEW'S equivalent rearrangements from A to C are quite sound so far as they go, but they do not go far enough. C can be redrawn as D here, and as each winding generates the same voltage there is no reason why their ends should not be joined (E). So far as anybody knows, the two 100-turn windings may be wound close together, perhaps in the same outer covering. In fact, they may just be two strands in one piece of flexible wire, so can now be regarded as one and the same winding, having 100 turns. Meanwhile the two 10-ohm loads, being in parallel, are equivalent to one 5-ohm load. So finally we arrive at F, which justifies the square root rule, for compared with A there is a quarter the load impedance across half the number of turns.

The fallacy consisted in considering the two halves of C separately. One half, with 10 ohms across 100 turns, is, of course, not equivalent to any of the arrangements A-F.

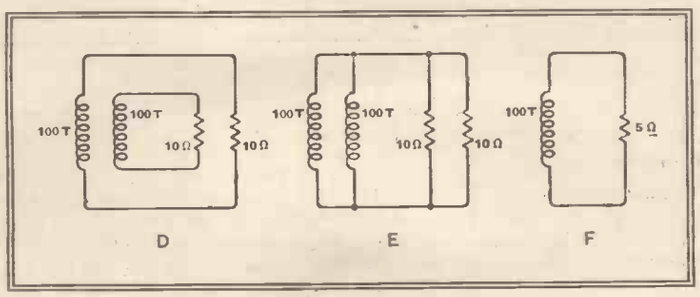

# Recent Inventions

The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from Specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.

***Brief descriptions of the more interesting radio devices and improvements issued as patents will be included in this section.***

### TELEVISION SCREENS

IN order to intensify the output from a cathode-ray tube, it has been proposed to use a relay arrangement in which the light produced on a fluorescent screen is subsequently projected on to a light-sensitive screen, preferably of the mosaic-cell type, so that the resulting electric image forms the source of a new stream of electrons.

The Figure shows the construction of a double screen used for this purpose. It consists of a group of small glass or quartz rods R, which are laid side by side in parallel formation and bound together by waterglass. The near end or face A of each rod is coated with fluorescent material F, whilst the opposite end B is covered with light-sensitive material M, so that collectively they form a mosaic screen.

In this way the fluorescent light

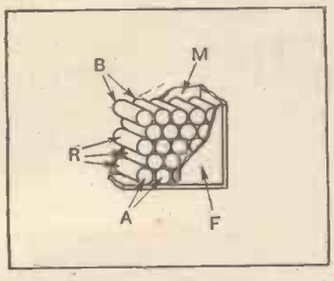


Method of increasing the intensity of the visual output of a cathode-ray tube.

produced at F by the impact of the original stream of electrons is conveyed to the mosaic cells B by total internal reflection inside each of the rods, and the usual dispersion losses are minimised.

*Baird Television, Ltd.; V. A. Jones and K. A. R. Samson. Application date July 29th, 1937. No. 499785.*

o o o o

### RADIOGONIOMETERS

A CONVENIENT arrangement is described for finding the "sense" as well as the direction of a distant beacon station on a radiogoniometer. After the bearing line has been ascertained in the ordinary way, it is usual to apply the pick-up voltage from a vertical or non-directional aerial, so as to convert the figure-of-eight curve given by the frame aerial into a cardioid curve. The latter, having only one critical "minimum," instead of two, then serves to show on which side of the bearing line the distant transmitter is located.

According to the invention, the usual search coil of the radiogoniometer is replaced by two "crossed" coils. One of these is used when the bearing line is being taken, and is then switched out and replaced by the second coil (which is coupled to a vertical aerial) for "sense" determination. The control switches are conveniently mounted on the hand wheel used for rotating the search coil, the phase of the auxiliary "vertical" aerial being reversed by a press ring of the kind used on the steering wheel of a motor car for sounding the horn.

*C. Lorenz Akt. Convention date (Germany), May 14th, 1937. No. 499708.*

o o o o

### RECEIVING ULTRA-SHORT WAVES

A RECTIFYING circuit for handling very short waves is designed to avoid any perceptible damping effect on the tuned input circuit. With very short waves, the transit time taken by the electrons to pass from the cathode to the control grid sets up an out-of-phase relationship with the incoming signals, and so produces a grid current which tends to damp the selectivity of the tuned RF circuit.

According to the invention, a two-grid valve V is operated on the Barkhausen-Kurz principle of a negative anode and positive grid. The tuned input circuit LC is connected across the cathode and anode, the latter being negatively biased through a resistance R. The grid nearer the anode is positively biased through a resistance R1, and the rectified signals are tapped off from a resistance R2 connected to the second grid. The resistance R2 presents a considerable impedance to the rectified current.

The only damping effect which can occur is that due to the absorption of the energy required to accelerate the electrons flowing through the valve, and this is extremely small.

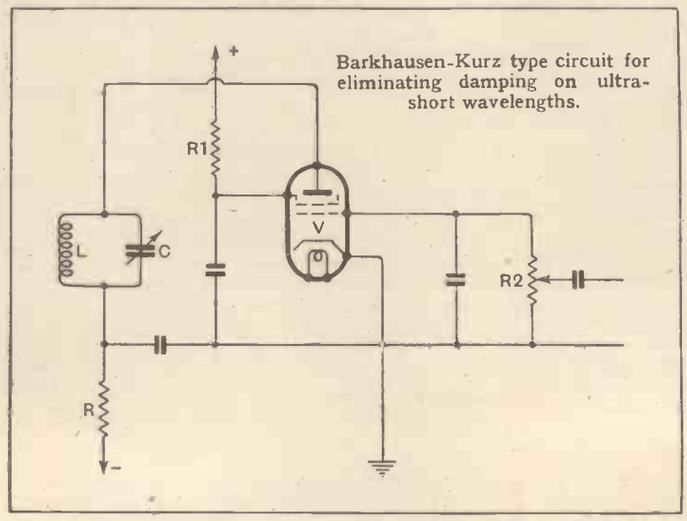


Barkhausen-Kurz type circuit for eliminating damping on ultra-short wavelengths.

*N. V. Philips' Gloeilampenfabrieken. Convention date (Germany) July 10th, 1937. No. 501890.*

o o o o

### USW FILTER CIRCUITS

A HIGH-FREQUENCY "transmission line" such as a pair of parallel or coaxial conductors, a quarter-wave long, presents a high impedance to frequencies corresponding to that wavelength, as well as to odd multiples of it.

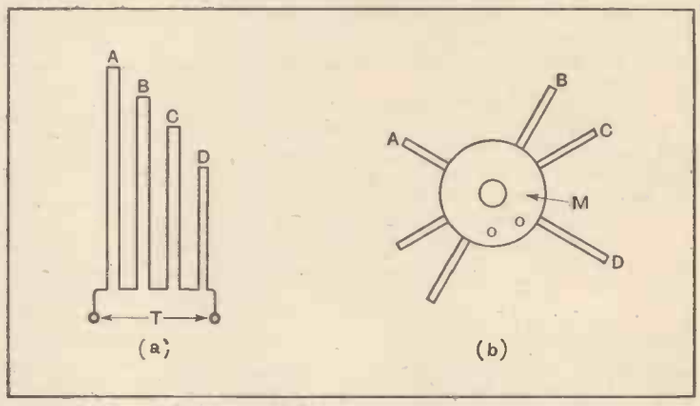


Use of quarter-wave coaxial or parallel conductors as rejectors for waveband filtering.

This principle is utilised to construct a filter circuit covering a selected band of wavelengths.

As shown in Figure (a), a number of quarter-wave units A, B, C, D are connected in series across a pair of terminals T. Each is short-circuited at the far end, and each acts as a resonant choke or rejector circuit at the frequency for which it is designed, so that the combined unit serves as a waveband filter. A similar arrangement of half-wave elements with open ends can be used for alternating currents when no D.C. component is present. Fig. (b) shows a practical arrangement in which the different units A, B, etc., are mounted to project radially from a pair of clamping discs M.

*Belling and Lee, Ltd., and F. R. W. Stafford. Application date July 21st, 1937. No. 499590.*

### MUTING CIRCUITS

A MUTING circuit is used to keep a receiver silent until a worth-while signal, of predetermined threshold strength, removes the bias and brings the loud speaker into operation. The object of the invention is to carry out this operation in a more clear-cut manner than usual.

For this purpose, a glow-discharge tube is inserted in series with the impedance across which the incoming signal builds up the voltage required to remove the muting bias. At the threshold point, the signal voltage reaches a strength sufficient to cause the discharge tube to strike. This removes the muting bias in a clean and effective manner, and allows the incoming signal to be promptly reproduced.

*Marconi's Wireless Telegraph Co., Ltd. and O. E. Keall. Application date, July 28th, 1937. No. 499774.*

o o o o

### SHORT-WAVE GENERATORS

ANY variation in the mains-supply voltage to an ultra-short-wave generator valve tends to make the frequency of the output fluctuate. The invention is concerned with ways and means of preventing this.

It is pointed out that such frequency variations are due to changes in the space charge set up around the control grid of the valve. A rise in the voltage applied to the cathode, for instance, results in increased emission and a higher density of space charge. On the other hand, an increase in the positive voltage on the grid nearest the control grid tends to draw away the accumulated electrons, and so lowers the space charge.

A circuit arrangement is described in which one of these effects is made to counterbalance the other, thus keeping the capacity between the control grid and cathode constant at all times. This stabilises the generated frequency in spite of variations in the supply voltage.

*NV. Philips Gloeilampenfabrieken. Convention date (Germany) March 8th, 1937. No. 499546.*

# Are our Condensers & Resistances the most reliable?

IF we said quite simply, "Yes, they are," and left it at that, you probably wouldn't believe us—and we wouldn't blame you. Then, what proof can we give you? Well, our range of fixed and variable resistances is probably the largest of ny British manufacturer—we've been making Condensers for every electrical purpose for many, many years now—through all those years we have concentrated above all on reliability. Are you convinced? If not, may we add this—"The Wireless World" have specified 16 Dubilier Condensers and 18 Dubilier Resistances for their Cathode Ray Oscilloscope. And you know as well as we do that you can't take chances with condensers and resistances in Electronic Apparatus. Convinced now?

**DUBILIER**

CONDENSERS AND RESISTANCES

DUBILIER CONDENSER CO. (1925) LTD.
DUCON WORKS, VICTORIA ROAD, NORTH ACTON, LONDON, W.3.

C. R. Casson 148

# G.E.C.

## CATHODE RAY MONITOR TUBE

**TYPE 4081**
2¾ inch Screen

The handy and efficient Tube for all general oscillographic purposes.

- **Low operating voltages.**
- **High spot brilliance.**
- **Fine Focus.**
- **High sensitivity for short length.**

PRICE 55/- each

*Write for Technical leaflet OV.8698*

*Advt. of The General Electric Co. Ltd., Magnet House, Kingsway, London, W.C.2.*

HAYNES RADIO

## THE CATHODE RAY OSCILLOSCOPE

| | |
|---|---|
| **TUBE UNIT TB64** | |
| Mains Transformer | £1.13.0 |
| Potentiometer 50,000 ohms | 5.0 |
| Potentiometer 10,000 ohms | 5.0 |
| Aluminium chassis comprising baseplate, 2 side pieces, front plate and engraved paxolin panel, 2 large brackets, 2 small brackets, small plate for tube holder, fitted with grommets and insulated terminals | £1. 3.6 |
| **TIME BASE and AMPLIFIER** | |
| Mains Transformer T2714 | £1.10.0 |
| Potentiometer 25,000 ohms | 5.0 |
| Potentiometer 50,000 ohms | 5.0 |
| Aluminium chassis comprising baseplate, 2 brackets, front plate and engraved paxolin panel with insulated terminals | £1. 5.0 |
| Knobs | 4d. each. |

**HAYNES QUALITY RECEIVERS, AMPLIFIERS and FILTERS.**

*List free on application to*

**HAYNES RADIO LTD.**

QUEENSWAY, ENFIELD, MIDDX.

(Howard 1171)

★ ANNOUNCING A NEW

# MARCONI SERVICE!

**THE MARCONI AERADIO TRAINING SCHOOL.**

*The practical experience of Marconi experts is now placed at the disposal of pilots, navigators, wireless operators, and others requiring training in radio, direction finding, blind approach, flag, lamp, semaphore and all signalling requirements for the various Air Ministry Certificates. In addition to the complete courses the School provides REVISION AND QUALIFYING COURSES, and instruction arranged to special requirements.*

*1. Radiotelephone Certificate. 2. W/T Operators Certificate. Revision Courses. Special qualifying course for ex-R.A.F. operators and others. 3. 1st and 2nd Class Navigators' Certificates: (Visual Signalling section, radio direction-finding and blind approach)*

**THE MARCONI AERADIO TRAINING SCHOOL**

(ONE MILE FROM CROYDON AIRPORT)

*Prospectus from Marconi's Wireless Telegraph Co. Ltd., Aircraft Wireless Establishment, Hackbridge, Surrey.*

Covers CONTINUOUS fundamental frequency band from 95 Kc. to 40 Mc.

BRITISH MADE.

The ALL-WAVE

# Avo-Oscillator

*Regd. Trade Mark*

Battery Model 9 Gns. (Complete with Batteries)

A.C. Mains Model 10 Gns. (Leather Carrying Case 35/-)

DEFERRED TERMS IF DESIRED.

Covers complete band from 95 Kc. to 40 Mc. by six fundamental ranges. Extended to 80 Mc. by harmonic calibration. Directly calibrated throughout. Externally modulated, internally modulated, or R.F. signal obtained at will. Internal modulation is 30% at 400 cycles, the L.F. signal being available for external use. Double attenuation enables signals to be varied from a few microvolts to 50 millivolts, with a force output of 1 volt.

• *Write for fully descriptive leaflet.*

*Sole Proprietors & Manufacturers*
**The Automatic Coil Winder & Electrical Equipment Co., Ltd.,**
Winder House, Douglas Street, London, S.W.1. *'Phone: Victoria 3404/7.*

# POLAR

...specified for the "WIRELESS WORLD" D.C. MAINS SUPER

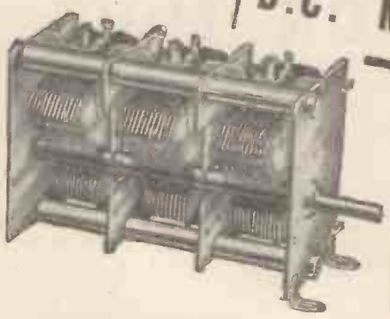

**1 BAR 3-GANG CONDENSER**
3 x ·0005 fitted ceramic rod insulations. Without trimmers. Type C.1703. Price - - **17/6**

**1 MICRO HORIZONTAL DRIVE**
Provides two reduction ratios of 10-1 and 50-1 operated by a single knob. Station Name Scale. Calibration for 0-180° or wavelengths only, supplied to order. Lampholders supplied. Price **9/6**

**1 MICA DIELECTRIC 2-GANG TRIMMER** Ceramic base. Brass vanes. Capacity range 150-550 mmf. Type 55. Price **2/-**

**WINGROVE & ROGERS LTD.**
**12, DARTMOUTH STREET, LONDON, S.W.1.**
POLAR WORKS, OLD SWAN, LIVERPOOL.

POLAR

7625 A12

# 'HIGH FIDELITY'— *and its achievement!*

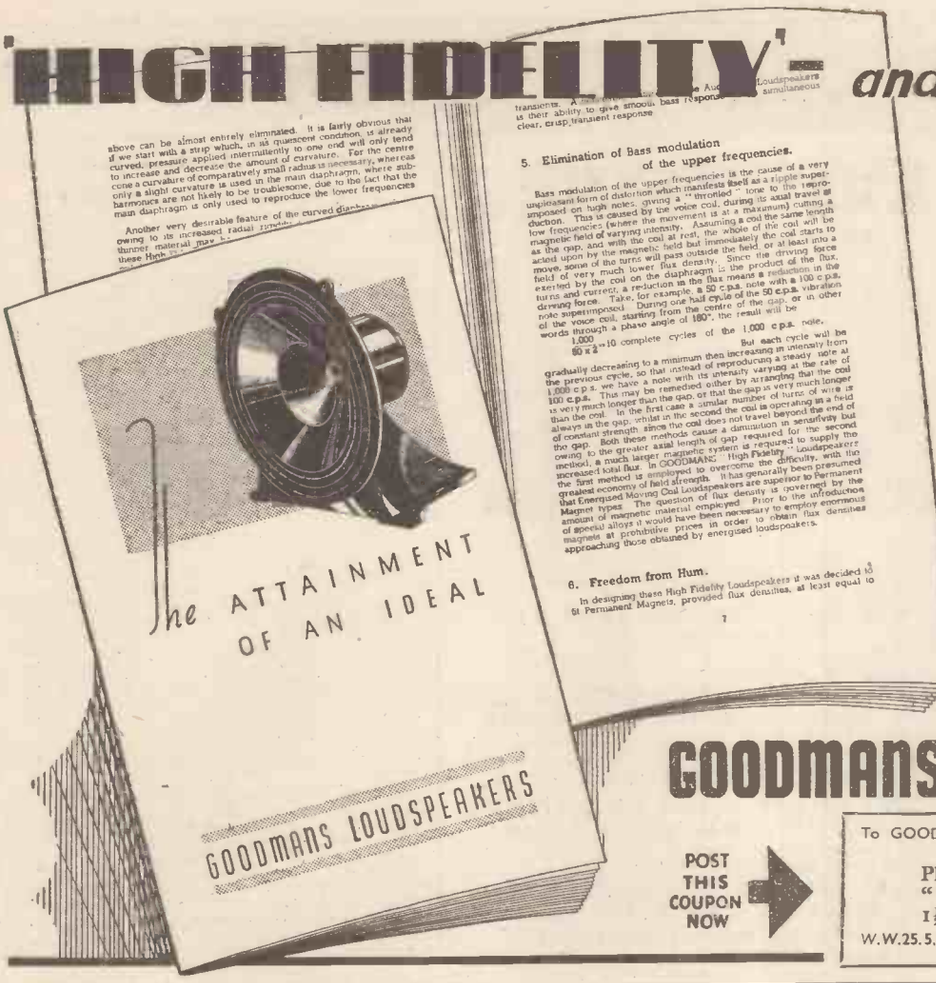


**AN AUTHORITATIVE 20-Page BROCHURE—YOURS FOR THIS COUPON**

This Brochure, acclaimed by the technical press as the most informative of its kind, describes the problems met with in the quest for "high fidelity" reproduction. The difficulties encountered in the attainment of level response, wide frequency range, and the reduction of sub-harmonics, etc., are fully described, together with the results of many tests and methods employed to overcome these difficulties.

This Brochure, of valuable technical data on the fundamental principles of loudspeaker design and with typical response curves, will be sent to you on receipt of the coupon below. Post it now!

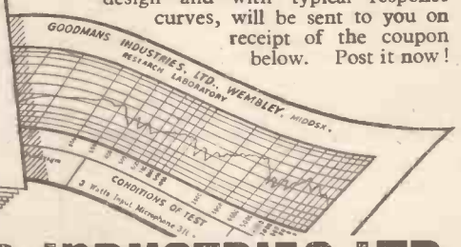


## GOODMANS INDUSTRIES, LTD.

POST THIS COUPON NOW

To GOODMANS INDUSTRIES LTD., Lancelot Road, Wembley, Middx.
*Phone: Wembley 4001/5*

Please send me a copy of your Brochure—"The Attainment of an Ideal." I enclose 1½d. stamp to cover postage.

W.W.25.5.39 **ATTACH TO YOUR CARD OR LETTERHEADING.**

---

## SWITCH ON TO *Faster* SOLDERING!

**READY IN 4 MINUTES**
No troublesome heating up with the Solon **Electric** Soldering Iron! Simply plug it in to your electric supply. Constant heat means there's no need to rush your work. Element clamped within the bit, concentrates all heat at the point.

**EFFICIENT**
Easier to solder—all the heat where you want it.
**CLEAN**
No flames, no dirt.
**ECONOMICAL**
15 hours' use for 1 unit.
**CONVENIENT**
All wearing parts easily replaceable.

*With solder, flex and lamp adaptor 8/6.*

*Electric* SOLDERING IRON
W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.,
(DEPT. 112/E) HOLBORN VIADUCT, LONDON, E.C.1

---

# RADIO LABORATORY HANDBOOK

**By M. G. SCROGGIE, B.Sc., A.M.I.E.E.**
*Issued in conjunction with "The Wireless World"*

"Radio Laboratory Handbook" gives the serious wireless worker complete information from first-hand experience about laboratory equipment, the instruments which are necessary and the correct methods of operating them.

The fundamental principles are fully discussed, as well as the sources of power and signals, instruments and measurements. Ultra-high-frequency work, the working out of results, and reference data are also dealt with. There is a collection of the most useful symbols, abbreviations, formulae, laws, curves, tables and other data.

A complete index, numbered sections and cross references enable the reader to find what is required without loss of time.

384 pp. 211 illustrations

PRICE 8/6 NET By Post 9/-

*From Bookstalls and Booksellers or direct from the Publishers*

ILIFFE & SONS LTD.,
DORSET HOUSE, STAMFORD ST., LONDON, S.E.1

---

# Varley

## I.F. TRANSFORMERS for the W.W.D.C. MAINS SUPER

**B.P.122 I.F. Transformer 465 Kc. .... Price 7/9**
**B.P.124 I.F. Transformer 465 Kc. .... Price 8/6**
**(with variable coupling).**

These I.F. Transformers have again been selected by the designer of W.W. Receivers. Fitted with Litz wound iron cored coils with high "Q" and best quality Mica Di-electric trimming condensers. B.P. 124 has auxiliary coupling winding allowing single peak curve for selectivity or double peaked curve for quality.

★ ★ ★

## VARLEY BATTERY RECEIVERS

Blue prints of three Battery Receivers are available for the Amateur Constructor. All receivers have been designed for easy construction and full instructions are supplied with Blue prints. Extremely suitable for emergency use if electricity mains should be disconnected.

**B.P.112 Battery Superhet Receiver 465 Kc. Price 6d.**
**B.P.114 3-Valve S.G. Battery Receiver ..... „ 6d.**
**ARP. 2. 2-Valve Battery Receiver ..... „ 4d.**

**VARLEY** (Props.: Oliver Pell Control Ltd.),
CAMBRIDGE ROW, WOOLWICH, S.E.18.

# CLASSIFIED ADVERTISEMENTS

## NOTICES

THE CHARGE FOR ADVERTISEMENTS in these columns is

12 words or less, 3/- and 3d. for every additional word.

Each paragraph is charged separately and name and address must be counted.

SERIES DISCOUNTS are allowed to Trade Advertisers as follows on orders for consecutive insertions, provided a contract is placed in advance, and in the absence of fresh instructions the entire "copy" is repeated from the previous issue: 13 consecutive insertions 5%, 26 consecutive, 10%; 52 consecutive, 15%.

ADVERTISEMENTS for these columns are accepted up to FIRST POST on MONDAY MORNING (previous to date of issue) at the Head Offices of "The Wireless World," Dorset House, Stamford Street, London, S.E.1, or on SATURDAY MORNING at the Branch Offices, 8-10, Corporation Street, Coventry; Guildhall Buildings, Navigation Street, Birmingham, 2; 260, Deansgate, Manchester, 3; 26B, Renfield Street, Glasgow, C.2.

Advertisements that arrive too late for a particular issue will automatically be inserted in the following issue unless accompanied by instructions to the contrary. All advertisements in this section must be strictly prepaid.

The proprietors retain the right to refuse or withdraw advertisements at their discretion.

Postal Orders and Cheques sent in payment for advertisements should be made payable to ILIFFE & SONS Ltd., and crossed & Co. Notes being untraceable if lost in transit should not be sent as remittances.

All letters relating to advertisements should quote the number which is printed at the end of each advertisement and the date of the issue in which it appeared.

The proprietors are not responsible for clerical or printers' errors, although every care is taken to avoid mistakes.

## IMPORTANT NOTICE.

Owing to the Whitsun Holidays the issue of "THE WIRELESS WORLD" for June 1st must be closed for press earlier than usual.

MISCELLANEOUS ADVERTISEMENTS for Insertion in that issue can be accepted up to

**FIRST POST FRIDAY, MAY 26th.**

## NEW RECEIVERS AND AMPLIFIERS

R.

C.

TELEPHONE: Holborn 4631.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1, by offering brand new receivers, maintain their reputation as the leading Mail Order House for surplus radios.

BRITISH Belmont 8-valve Plus Magic Eye All-wave A.C. Superhet Chassis, 4 wave bands, 2 short medium and long, fitted latest Mullard octal base American type valves. Brief specification: Short wave 6-18 metres (covers television sound), short wave 2, 18-50 metres, medium band 200-550 metres, long 900-2,000 metres; valve combination 6K7 Pre H.F., 6J7 oscillator, 6J7 mixer, 6K7 I.F., 6Q7 (DDT) detection, A.V.C. and first L.F., two 6F6s, parallel output, 5Y3 rectifier, plus 6G5 Magic Eye visual tuning, handsome dial, station names etched on glass, controls 2-speed tuning, volume and on-off, combined variable tone control and selectivity switch, wave change plus gramo. switch; size of chassis 13½in.×10in.×3in.; supplied complete with valves, escutcheon, knobs, but less speaker, £5/19/6 each; complete receiver in handsome walnut cabinet, details as above, complete with speaker, £7/7.

DECCA 6-valve 3-waveband Battery Chassis, fitted complete with Mazda and Osram valves, QPP output; these chassis give a sparkling performance on all wavebands, and are the product of a well-known manufacturer, complete with valves, £3/3 each; complete receiver in handsome walnut cabinet, details as above, complete with speaker, £3/19/6 each.

ALL the Above Fitted Ring Valves Throughout.

SEE Our Advertisement under Components.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1. Telephone: Holborn 4631. [8502

## ARMSTRONG'S NEW HEADQUARTERS

After many years at our old premises in Camden Town we have moved our Offices, Showrooms and Development Department to a modern building centrally situated in

**WARLTERS ROAD, HOLLOWAY, N.7**
(Adjoining Holloway Arcade).

Send for Illustrated Catalogue of our full range, which includes the following outstanding chassis.

**MODEL AW125PP . . Price £17.17.0**
**12-V. ALL-WAVE RADIOGRAM CHASSIS**
5 wavebands, 12-550 continuous, 1,000-2,000 m., R.F. Pre-Amplifier, 2 I.F. stages with Variable Selectivity. Manual R.F. gain control and 10 watts R.C. coupled Triode P.P. output.

**MODEL AW93PP . . . Price £10.10.0**
**9-V. ALL-WAVE RADIOGRAM CHASSIS**
3 wavebands, R.F. Pre-Amplifier, 3 stages of A.V.C. and 8 watts R.C. coupled Triode P.P. output.

**MODEL RF96 . . . . . Price £8.0.0**
**6-V. ALL-WAVE RADIOGRAM CHASSIS**
**Complete with Matched M.C. Speaker.**
Incorporating R.F. Amplifier. 3 wavebands, 17.9-50, 200-550, 1,000-2,000 m., 3 stages of A.V.C., corrected 3½ watts output.

*All communications to be addressed to*

**ARMSTRONG MANUFACTURING CO.,**
**WARLTERS ROAD, HOLLOWAY, LONDON, N.7**
(Adjoining Holloway Arcade).
*Telephone: NORth 3213.*

## For PROMPT DELIVERY of High Quality

LOUDSPEAKERS, LOUDSPEAKER CONES LOUDSPEAKER COMPONENTS, TRANSFORMER LAMINATIONS, TRANSFORMER HOUSINGS, TRANSFORMER WINDINGS, CHOKE WINDINGS, FIELD COIL WINDINGS, PERMANENT MAGNETS, PRESS TOOLS AND PRESSINGS, JIG BORING. AUTOMATIC SCREW MACHINE PARTS UP TO 2" DIAMETER.

Contractors to the Admiralty, War Office and Air Ministry.

**Call on BRITISH ROLA LTD.**
MINERVA ROAD, PARK ROYAL, N.W.10.
'PHONE: WILLESDEN 4322-3-4-5-6

## NUMBERED ADDRESSES

For the convenience of private advertisers, letters may be addressed to numbers at "The Wireless World" Office. When this is desired, the sum of 6d. to defray the cost of registration and to cover postage on replies must be added to the advertisement charge, which must include the words Box 000, c/o "The Wireless World." All replies should be addressed to the Box number shown in the advertisement, c/o "The Wireless World," Dorset House, Stamford Street, London, S.E.1. *Readers who reply to Box No. advertisements are warned against sending remittances through the post except in registered envelopes: in all such cases the use of the Deposit System is recommended, and the envelope should be clearly marked "Deposit Department."*

### DEPOSIT SYSTEM

Readers who hesitate to send money to advertisers in these columns may deal in perfect safety by availing themselves of our Deposit System. If the money be deposited with "The Wireless World," both parties are advised of its receipt.

The time allowed for decision is three days, counting from receipt of goods, after which period, if buyer decides not to retain goods, they must be returned to sender. If a sale is effected, buyer instructs us to remit amount to seller, but if not, seller instructs us to return amount to depositor. Carriage is paid by the buyer, but in the event of no sale, and subject to there being no different arrangement between buyer and seller, each pays carriage one way. The seller takes the risk of loss or damage in transit, for which we take no responsibility. For all transactions up to £10, a deposit fee of 1/- is charged; on transactions over £10 and under £50, the fee is 2/6; over £50, 5/-. All deposit matters are dealt with at Dorset House, Stamford Street, London, S.E.1, and cheques and money orders should be made payable to Iliffe & Sons Limited.

SPECIAL NOTE.—Readers who reply to advertisements and receive no answer to their enquiries are requested to regard the silence as an indication that the goods advertised have already been disposed of. Advertisers often receive so many enquiries that it is quite impossible to reply to each one by post. When sending remittances direct to an advertiser, stamp for return should also be included for use in the event of the application proving unsuccessful.

## RECEIVERS AND AMPLIFIERS

### CLEARANCE, SURPLUS, ETC.

DYNATRON RADIO Annual Clearance Sale of Recently Obsolete and Reconditioned High Fidelity Radiogramophones, receivers, and chassis, at extremely attractive prices: Ether Empress Radiogramophone, 115 gns. list, 65 gns.; Ether Knight Radiogramophone, 29 gns., receivers from £4; all-wave tuners with straight-superhet. feature, model T1014, £15; surplus chassis, record changers, speakers and components; send for list.—Perfecta Works, Ray Lea Rd., Maidenhead. [8493

## USED SETS FOR SALE

### DENCO

DENCO U.H.F. Superhet, 5-65 Mc., Acorn valves; 6 gns.—26, Moor Park Rd., Northwood, Middlesex. [8489

### MISCELLANEOUS

A NUMBER of Reconditioned Sets in Good Order; from £5 upwards.—Halford Radio, 31, St. George St., W.1. [0617

SOUND SALES Quality H.F. Tuner, 6w. amplifier, G12P.M., H.M.V. record player, suitable radiogram cabinet, new Christmas; offers; demonstration.—Box 9816, c/o *The Wireless World*. [8473

## CAR RADIO

NEW Caradios from £4/10; used caradios from £3.—41, Glebe Avenue, Kenton. [8482

CROSLEY Push-button 1939 10-guinea Models, 5½ gns.; aerials overheads, police type, etc., from 8/6; trade enquiries solicited.—Shippers, 18, Corporation St., Manchester. [0622

FINEST American Twin Running-board Aerials, completely rubber covered, maximum signal pick-up, minimum noise, easy mounting, now only 17/6 pair complete; handsome chromium roof aerials, to mount straight or "vee," complete, 15/-; immediate despatch, carriage paid; cash with order or c.o.d.

WIRELESS SUPPLIES UNLIMITED, Essex House, Stratford, E.15. Maryland 3191. [0577

## PUBLIC ADDRESS

"PARTRIDGE P.A. Manual," standard handbook on electro-acoustics, amplifiers, and audio circuits; price 2/6 (free to trade).

"PARTRIDGE Amplifier Circuits," describes many modern constructional amplifiers, 2w. to 45w. output, battery, A.C.-D.C., etc.; price 2/- (no free copies).

PARTRIDGE, N., B.Sc., A.M.I.E.E., King's Buildings, Dean Stanley St., London, S.W.1. [0630

*"Radio Data Charts," A Series of Abacs Post free 4/10*

# VORTEXION 15W

## Type CP20 AC and 12-VOLT DC AMPLIFIER

THIS small Portable Amplifier, operating either from AC mains or 12-volt battery was tested by "THE WIRELESS WORLD," October 1st, 1937, and has proved so popular that at Customers' demand it remains unaltered except that the output has been increased to 17.2 watts and the battery consumption lowered to 6 amperes. Read what "The Wireless World" said :—

"During tests an output of 14.7 watts was obtained without any trace of distortion so that the rating of 15 watts is quite justified. The measured response shows an upper limit of 18,000 c/s and a lower of 30 c/s. Its performance is exceptionally good. Another outstanding feature is its exceptionally low hum level when AC operated even without an earth connection. In order to obtain the maximum undistorted output, an input to the microphone jack of 0.037 volt was required. The two independent volume controls enable one to adjust the gain of the amplifier for the same power output from both sources, as well as superimpose one on the other, or fade out one and bring the other up to full volume. The secondary of the output transformer is tapped for loudspeakers or line impedances of 4, 7.5 and 15 ohms."

AC and 12-volt CHASSIS with valves, etc. **£12 12 0**

Or in Rexine Case with Collaro Motor, Piezo P.U. and Mike Transformer..... **£17 17 0**

AC only CHASSIS with valves, etc. ..... **£8 18 6**

Or in Rexine Case with Collaro Motor, Piezo P.U. and Mike Transformer..... **£14 0 0**

Gauze Case for either chassis 12/6 extra.

**SEND NOW FOR FULL DETAILS.**

***Vortexion Ltd., 182, The Broadway, Wimbledon, S.W.19. 'Phone: LIBerty 2814.***

# RADIOMART

G5NI (BHAM) LTD.

## THE SHORT-WAVE SPECIALISTS

**SPECIAL OFFER ! !!**
Fully shrouded Transformers by America's largest manufacturer. While they last.
All 230 v. primary and fully impregnated.

| | |
|---|---|
| T28708—375/375 v. 150 m/A., 6.3V5A. 2.5V5A. 5V3A. | 15/- |
| T19610—350/350 v. 150 m/A., 2.5V6A. 2.5V2A. 5V3A. | 12/6 |
| T7236—375/375 v. 120 m/A., 6.3VCT. 4A. 5V3A | 10/6 |
| T7326—350/350 v. 100 m/A., 6.3VCT. 3A. 5V3A | 8/6 |
| T7307—350/350 v. 80 m/A., 6.3VCT. 3A. 5V3A | 7/6 |
| T7000—320/320 v. 80 m/A., 6.3V4A. 5V3A | 7/6 |
| T6025—320/320 v. 80 m/A., 2.5V6A. 5V3A | 7/6 |
| T464919—10V4A Primary Tapped 110—250 v. | 5/6 |
| T1113AB—110/230 v. 500 watt Auto Transformer | 29/6 |

The following chokes are interleaved and impregnated.

| | |
|---|---|
| T7007—250 m/A., 135 ohms, 20-8 Hy., cadmium shrouded | 12/6 |
| T7007A—150 m/A., 250 ohms, 30-12 Hy., cadmium shrouded | 12/6 |
| 100 m A., 20 Hy., 500 ohms, unshrouded | 4/11 |
| 60 m/A., 15 Hy., 250 ohms | 1/11 |

**HEAVY DUTY TRANSFORMER** for models, bells, etc., 6 v. 3 a., 2/3. 4 mf., 1,500 v. test 500 v. wkg. oil filled condensers, 2/-.
**HEAVY DUTY** Mains Transformer, worth 45/-. 350-350, 150 m/A. 4 v. 2.5 a. CT, 4 v. 6 a., CT, 12/6 ; 300-300 v., 80 m/A., 4 v. 3 a., CT, 4 v. 2 a., CT, 6/6. Moving Coil Speech Transformers, 1/11.
**GANG CONDENSERS** with Airplane Dial, 8 and 80-1. Cost 35/-. Few only. 4/11. Utility, 7/6. Microdials, 3/9.
**W.B. 8in. PERMANENT MAGNET SPEAKERS AT ONE-THIRD COST** Extension Type (no Transformer), 8/11. Standard Type (with Transformer), 10/6. Energised 8", 1,200 ohms with Transformer, 6/11.
**PUSHBACK** Wire, 6 yds., 6d., heavy, 9d. Resin-cored Solder, 6ft., 6d. ; Screened Flex, single, 6d. yd. ; twin 9d. yd. Assorted Solder Tags, 6d. packet. Humdimmers, 6d. each.
Centralab pots, all sizes, 1/6 ; switched, 2/- ; tubular glass fuses, 2d. Milliammeters, 0.25 m.a., upwards, 5/9 ; Super, 6/9.
**OUR NEW 66-PAGE MANUAL,** packed full of valuable information. Post Free, 7½d.
**THE NEW RAYMART CATALOGUE** shows dozens of New Short-wave Components and is yours for 1½d. post free.
**VALVES.**—A complete range of replacements, showing a saving of over 50 per cent. Quotations on receipt of types required. Quantity Discounts to Service Engineers. TRADE enquiries for communication equipment solicited.

**RADIOMART** *Telephone: MIDland 324*
G5NI (Birmingham) Ltd.
**44, HOLLOWAY HEAD, BIRMINGHAM**

We don't claim to make the cheapest transformers but we *do* claim to make good ones. Most of the professional P.A. men seem to think so, too.

**W. BRYAN SAVAGE LTD.**
*Westmoreland Rd., London, N.W.9. 'Phone: Colindale 7131*

## PUBLIC ADDRESS

VORTEXION P.A. Equipment.

IMITATED, but unequalled.

WE Invite You to a Demonstration.

A.C.-D.C. Dance Band Amplifier, 10 watts output, complete in case, with moving coil microphone, speaker and cables, weight 22lb.; 12 gns.

A.C.-20 15-20-watt Amplifier, 38-18,000 cycles, independent mike and gram., inputs and controls, 0.037 volts required to full load, output for 4, 7.5, and 15 ohms speakers or to specification, inaudible hum level; ready for use; 8½ gns., complete.

C.P. 20, 12-volt battery and A.C. mains model, as used by R.A.F., output as above; 12 gns.

A.C.-20, in portable case, with Collaro motor, Piezo pick-up, etc., £14; C.P.20 ditto, £17/17.

50-WATT Output 6L6s, under 60-watt conditions, with negative feed back, separate rectifiers for anode screen and bias, with better than 4% regulation, level response, 20-25,000 cycles, excellent driver, driver transformer, and output transformer matching 2-30 ohms impedance electronic mixing for mike and pick-up, with tone control, complete with valves and plugs; £15.

COMPLETE in Case, with turntable B.T.H. Piezo pick-up and shielded microphone transformer; £20.

80-WATT Model, with negative feed back; £25, complete.

120-WATT Model, with negative feed back; £40, complete.

250-VOLT 250 m.a. Full Wave Speaker, field supply unit; 25/-, with valve.

ALL P.A. Accessories in Stock; trade supplied.

VORTEXION, Ltd., 182, The Broadway, Wimbledon, S.W.19. 'Phone: Lib. 2814. [8241

QUALITY Amplifiers and Microphone Equipments for Hire or Permanent Installation.—Harmony House, 116, Cambridge Rd., Southport. [8307

ALEXANDER BLACK, Ltd., Established 1925.—For microphone equipment when quality counts. Booklet on request.—55, Ebury St., S.W.1. Sloane 6129. [0596

PUBLIC Address Contractors Can Hire P.A. Vans, loud speakers, microphones and equipments of all types from Hire Dept., Grampian Reproducers, Ltd., Kew Gardens, Surrey. Tel.: Richmond 1175-6-7. [0618

RIBBON Microphone, 7 models, from £3/19/6, list free; 15-watt, high gain, high fidelity, 4-stage amplifier for ribbon microphones, £12/10; 30-watt ditto, £18.—Holiday and Hemmerdinger, Ltd., 74, Hardman St., Manchester. [8475

## NEW MAINS EQUIPMENT

V.

ALL Transformers at Last Week's Prices.

VORTEXION, Ltd., 182, The Broadway, Wimbledon, S.W.19. 'Phone: Lib. 2814. [8500

## NEW LOUD-SPEAKERS

SINCLAIR Speakers for All Types.—Alma Grove, Copenhagen St., N.1. [0603

BAKERS' New Corner Horn Speakers, surplus bargains and triple cone conversions, from 29/6.—Leaflets free from Bakers Selhurst Radio, 75, Sussex Rd., South Croydon. [8434

## LOUD-SPEAKERS

### SECOND-HAND, CLEARANCE, SURPLUS, ETC.

EPOCH 18in., energised, new; bargain, £3.—Fawcett, 707, Barking Rd., London, E.13. [8492

ROLAS for 6/11; G12's, 47/6; ½d. stamp for lists.—Shippers, 18, Corporation St., Manchester. [0606

VAUXHALL UTILITIES, 163a, Strand, W.C.2.—Rola G12 P.M. speakers, 62/6; G12 energised, 50/-; with transformers, brand new. [8499

HARTLEY-TURNER Duode De Luxe, 2,500 ohm field, PPLL transformer, new condition, cost £8/15; nearest £4.—96, Vicarage Lane, Stratford, E.15. [8497

HARTLEY-TURNER Duode De Luxe, mains energised, with push-pull output transformer, condition perfect, cost £7/10; sacrifice, £3/15.—Gerry, Bank St., Newquay. [8491

3,000 Speakers from 5/6 each, P.M. and energised, 4in. to 14in., including several Epoch 18in.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0591

EPOCH 18in., rebuilt, any field, £5; with A.C. equipment, £2 extra; Epoch 14in. mains energised, 70/-; fitted A.C., 30/- extra; several 10in., 12in., and 15in. energised and P.M.s, from 20/-.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0628

## LOUD-SPEAKER CONVERSIONS

EPOCH Domino Loudspeakers can Now be Converted to the Famous "NEW" Super Cinema Speaker with 14in. Cone, replacement for all Epoch speakers, also output transformers; a genuine Epoch hand-made cone for any speaker.

HALFORD DISTRIBUTORS, Ltd., 31, St. George St., W.1. Sole manufacturers of Epoch loudspeakers and the famous Halford Phantom radio set. [0632

# PREMIER

## ★ RADIO ★

### PREMIER MOVING COIL METERS

**Guaranteed Accuracy within ± 2 per cent.**

| Model No. 21. 3in. square case. | | Model No. 311. 3½in. diameter round case. | |
|---|---|---|---|
| 0-1 m/A. | 18/6 | 0-1 m/A. | 22/6 |
| 0-10 m/A. | 17/6 | 0-10 m/A. | 20/- |
| 0-50 m/A. | 17/6 | 0-50 m/A. | 20/- |
| 0-100 m/A. | 17/6 | 0-100 m/A. | 20/- |
| 0-250 m/A. | 17/6 | 0-250 m/A. | 20/- |

**Model 311.** 0-1 m/A. movement, with calibrated scale, volts-ohms-m/A., 25/-.

**VOLTAGE MULTIPLIER RESISTANCES.** guaranteed accuracy ± 2 per cent. All standard ranges, 1/3 each.
**TAPPED SHUNT** to provide readings of 5 m/A., 25 m/A., 250 m/A., and 1,000 m/A., 5/6.

### PREMIER SHORT-WAVE KITS

Complete to the last detail including all Valves and coils, as well as theoretical and wiring diagrams and lucid instructions for building and working. Each kit is supplied with a steel Chassis and Panel and uses plug-in coils to tune from 13 to 170 metres.

| | |
|---|---|
| 1 Valve Short-Wave Receiver or Adapter Kit | 17/6 |
| 1 Valve Short-Wave Superhet Converter Kit | 20/- |
| 1 Valve Short-Wave A.C. Superhet Converter Kit | 22/6 |
| 2 Valve Short-Wave Receiver Kit | 25/- |
| 3 Valve Short-Wave Screen Grid and Pentode Kit | 58/6 |

### PREMIER 3-BAND S.W. KITS

11-86 metres without coil changing. Complete Kits of Parts with Valves and Circuits. One Valver, 12/6 ; Two Valver, 19/6.

**PREMIER U.S.A. QUARTZ TRANSMITTING CRYSTALS.** 7 mc. Band, 10/- each, with Calibration Certificate. Enclosed holder and Base, 3/-.
**PREMIER SHORT-WAVE COILS,** 4- and 6-pin types, 13-26, 22-47, 41-94, 78-170 metres, 1/9 each, with circuit Special set of S.W. Coils, 14-150 metres, 4/- set, with circuit. Premier 3-band S.W. coil, 11-25, 19-43, 38-86 metres. Suitable any type circuit, 2/6.
**UTILITY** Micro Cursor Dials, Direct and 100.1 Ratios, 3/9.
**PREMIER** Short-Wave Condensers, all-brass construction, with **Trolitul** insulation. 15 mmf., 1/6 ; 25 mmf., 1/7 ; 40 mmf., 1/9 ; 100 mmf., 2/- ; 160 mmf., 2/3 ; 250 mmf., 2/6.
**TROLITUL DOUBLE SPACED TRANSMITTING CONDENSERS.** 15 mmf., 2/9 ; 40 mmf., 3/6 ; 100 mmf., 4/- ; 160 mmf., 4/6.
**NEW TROLITUL SPLIT STATOR CONDENSERS** 50×50 mmf., 10/6.
**COIL FORMERS,** 4- or 6-pin low-loss, 1/- each.
**AMERICAN VALVES.** We hold the largest stocks of U.S.A. tubes in this country and are sole British Distributors for **TRIAD** High-grade American Valves. All types in stock. Standard types, 5/6 each. All the new Octal Base tubes at 6/6 each, 210 and 250, 8/6 each.
**EUROPA MAINS VALVES,** 4 v. A.C. Types, A.C./H.L., A.C./L., A.C./S.G., A.C./V.M.S.G., A.C./H.P., A.C./V.H.P., A.C./P., and 1 watt D.H. Pentodes, all 4/6 each. A.C./Pens., I.J., 5/6 ; A.C./P.X.4, 6/6 ; Oct. Freq. Changers, 8/6 ; Double Diode Triodes, 7/6 ; Triode H. ex. Freq. Ch., 8/6 ; Tri. Grid Pen., 10/6 ; 3½-watt D.H. Triode, 7/6. 350 v. and 500 v. F.W. Rect., 5/6. **13 v. 2 amps.** Gen. Purpose Triodes, 5/6 ; H.F. Pens. and Var.-Mu. H.F. Pens., Double Diode Triodes, Oct. Freq. Changers, 7/6 each. Full-wave and half-wave Rectifiers, 5/9 each.

### MATCHMAKER UNIVERSAL MODULATION TRANSFORMERS

Will match any modulator to any R.F. load. 50 watts, 17/6 ; 150 watts, 29/6 ; 300 watts, 49/6.
**MATCHMAKER UNIVERSAL OUTPUT TRANSFORMERS.** Will match any output valves to any speaker impedance. 11 ratios from 13 : 1 to 80 : 1. 5-7 watts, 13/6 ; 10-15 watts, 17/6 ; 20-30 watts, 29/6. Send for full details.
**PREMIER AC/DC MOVING IRON METERS.** 2½in. diam. Flush Mounting. All ranges. 10 m.a., 30 m.a., 50 m.a., 100 m.a., 250 m.a., 500 m.a., 5/9 each.
**AMMETERS.** 1, 3, 5, 10 or 30 amps., 5/9 each.

### PREMIER 1939 HIGH FIDELITY AMPLIFIERS

**A New Complete Range of 7 High Fidelity P.A. Amplifier for A.C. or A.C./D.C. Mains operation.**

| | Kit of Parts with Valves. | Wired and Tested. |
|---|---|---|
| 3-watt A.C. Amplifier | £2 0 0 | £2 15 0 |
| 3-watt A.C./D.C. „ | £2 0 0 | £2 15 0 |
| 6-watt A.C. „ | £5 5 0 | £6 0 0 |
| 8-10-watt A.C./D.C. „ | £4 10 0 | £5 5 0 |
| 15-watt A.C. „ | £5 15 0 | £7 0 0 |

Black Crackle Steel Cabinet 15/- extra.

**NEW PREMIER SELF-POWERED RF TUNING UNIT,** incorporating a Var.-Mu pentode amplifier followed by a power grid detector. Designed for high-fidelity reception. Wave range 200-560 and 800-2,000 metres. £4 - 9 - 6 complete with valves.
**OIL-FILLED HIGH VOLTAGE.** 1,000 volts working; 1 mf., 5/- ; 2 mf., 7/- ; 4 mf., 10/6. 2,000 volts working; 1 mf., 8/- ; 2 mf., 12/- ; 4 mf., 14/-.
**BIAS CONDENSERS,** 6 mf. 50 v., 6d. ; 50 mf. 12 v. 1/- ; 25 mf. 25 v., 1/- ; 50 mf. 50 v. 1/-.
**TUBULAR,** all values from .0001 to .5 mf., 6d. each.
Orders 5/- and over sent Post Free. Under 5/- please add 6d. postage.

**Have you had our 1939 Catalogue, Handbook and Valve Manual? 90 pages of Radio Bargains and Interesting Data. Price 6d.**

**ALL POST ORDERS TO: Jubilee Works, 167, Lower Clapton Road, London, E.5.** *Amherst 4723*
**CALLERS TO: Jubilee Works, or our NEW PREMISES, 169, FLEET STREET, E.C.4.** *Central 2833*
**or 50, High Street, Clapham, S.W.4.** *Macaulay 2381.*

*"Foundations of Wireless," Second Edition. 4s. 6d. net. Post free 4s. 11d.*

# Sez you!—

This Americanism expresses a strong doubt. We prefer the English version "You have said it"—equally strong, but with a very different meaning.

As producers of **Quality** Components, Radio Receivers and Amplifier Equipment, we have not hesitated to tell you, through our advertisements, how good our products are.

Substantiation of our statements reach us regularly from users in various parts of the World, and here is an extract from one of the many letters recently received.

Referring to his Customer's order a Dealer says :—

"He wants to make quite sure that the speaker is properly fed, and he could find nothing better or anything as good!"

Surely, if you are interested in **Quality Reproduction**, then you must be interested in SOUND SALES PRODUCTS.

May we send YOU a copy of our latest catalogue and technical manual . . . PRICE 6D

*Specified by the Experts*

**SOUND SALES**

MARLBOROUGH RD., UPPER HOLLOWAY, LONDON, N.19. LIMITED. (*Contractors to the G.P.O., etc.*) *Tel.: Archway* 1661/2/3

Hours of Business—
Monday to Friday, 8.30 a.m. to 6 p.m.
SATURDAYS CLOSED

# WELBURN 12 WATT AMPLIFIER

Designed and built for consistent hard work. Reliability and first-class performance on both speech and music were our first consideration.

NOTE THESE POINTS:
No distortion; No hum; Cool running; Small Input (only 0.008v); Output 12 watts; Overall Gain 116dBs; No pre-amplifier required. Linear Amplification combined with Level Response; Mike-Gramo-Mixer; Mazda Valves; Self-contained in dust-proof steel case.

**A SOUND JOB FOR ALL *SOUND* PURPOSES**

***Write for 12 pp. descriptive brochure***

RETAIL PRICE **£14**

**WELBURN RADIO LTD.**
QUEENSWAY, TEAM VALLEY
GATESHEAD-ON-TYNE

# ENGINEERS! ARE YOU EARNING LESS THAN £10 PER WEEK?

If so, you cannot afford to carry on without reading our 268-page Handbook. The book explains clearly and definitely many ways of carving out a successful career. Among other things it explains the Services of our unique Appointments Department; outlines Home-Study Courses in all branches of **Civil, Mechanical, Electrical, Motor, Aero, Wireless, "Talkie" Engineering, Building, Govt. Employment,** etc., and gives details of B.Sc., A.M.I.C.E., A.M.I.E.E., A.M.I.Mech.E., A.M.I.A.E. A.M.I.W.T., A.M.I.R.E., G.P.O., MATRIC., and all Exams. We Guarantee —"NO PASS—NO FEE." Whether you be an old hand or a budding apprentice get this book to-day. FREE and POST FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY,
337, Shakespeare House, 17/19, Stratford Place, London, W.1.

**BOOKS ON WIRELESS**
Write for complete list to
Iliffe & Sons Ltd., Dorset House, Stamford St., London, S.E.1
W.W.1


## TRANSMITTING APPARATUS

A.C.S. RADIO, specialists in short-wave apparatus, communication receivers, including Hallicrafters, National and R.M.E. transmitting equipment, valves and components.—Send for free catalogue to A.C.S. Radio, 16, Gray's Inn Rd., W.C.1. Holborn 9894-5. G2NK Technical Manager. [0550

G5NI.—The oldest and largest distributors of amateur equipment, transmitting and receiving; short-wave catalogue, 1½d.; G5NI 70-page Manual, 7½d., post free; authorised direct distributors for Collins, National, R.M.E., Thordarson, Hammerlund, Bliley, Taylor, Eimac, etc., etc.—44, Holloway Head, Birmingham. [0531

## CABINETS

A CABINET for Every Radio Purpose.

CONVERT Your Set into a Radiogram at Minimum Cost; surplus cabinets from noted makers under cost of manufacture (undrilled); 30/- upwards; motors at wholesale prices.

"FIT-A-GRAM" Cabinet, 31 × 17 × 15; 21/-.

UNDRILLED Table Console and Loud-speaker Cabinets, from 3/6.

INSPECTION Invited; photos loaned to country customers.

H. L. SMITH and Co., Ltd., 289, Edgware Rd., W.2. Tel.: Pad. 5891. [0485

CLEARANCE Sale!! — Radiogram and television cabinets, prices slashed! 10 gns. worth for 50/-! 5 gns. worth for 20/-!—Write, wire, 'phone or call, Cameo Co., 23, Denmark St., W.C.2. (Tem. 5900.) [8353

## DYNAMOS, MOTORS, ETC.

D.C.-A.C. Convertors, motors, all voltages, for sale and wanted.—Easco, 18w, Brixton Rd., S.W.9. [0558

ALL Types of Rotary Converters, electric motors, battery chargers, petrol-electric generator sets, etc., in stock, new and second-hand.

A.C.-D.C. Conversion Units for Operating D.C. Receivers from A.C. Mains, 100 watts output, £2/10; 150 watts output, £3/10.

WARD, 46, Farringdon St., London, E.C.4. Tel.: Holborn 9703. [0518

M.L. Convertor, 50-volt D.C. input, 230-volt 85-watt A.C. output, excellent condition; £2/15.—Cyco-Rado, Ltd., 3, Mill St., Maidstone. [8476

### Wanted

WANTED, rotary converter, 100 d.c. to 230 a.c. 150 watts.—Davies, The Grove, Stubbington, Hants. [8481

## RECORDING EQUIPMENT

ALL Recording Discs and Materials in Stock; tracker units, £4/7/6; recording motors, £3/17/6.—Write for further details, Will Day, Ltd., 19, Lisle St., W.C.2. [0595

PROFESSIONAL Recording Block, ribbon microphone, 14 watt amplifier, mixing panel, polished recording desk with V.G. tracker recording motor and switching, guaranteed perfect; £45.—Liverpool Sound Studios, 83a, Bold St., Liverpool. [8463

FEIGH Recording Sets are Within Reach of All; ball bearing gear box, worm drive traverse; records on any disc, Morse, speech or music; diamond cutter-pickup on tone arm, the set 37/6; 6in. blanks, 3/3 doz.; 10in. discs, 7/- doz.—Electradix, 218, Upper Thames St., London, E.C.4. [0620

## VALVES

ALL Types of American Tubes in Stock of Impex and Arcturus makes at competitive prices.

WE Can Also Supply a Full Range of Guaranteed Replacement Valves for Any British non-ring, American or Continental type at an appreciably lower price.

SEND for Lists of These, and also electrolytic condensers, line cords, resistances, etc.

CHAS. F. WARD, 46, Farringdon St., London, E.C.4. Tel.: Holborn 9703. [0452

AMERICAN Valves, first grade, by leading makers, guaranteed, popular types; standard base 5/6; octal base 6/6; 6L6G, 7/6—General Radio Distributors, 309, Falloden Way, N.W.11. [0626

2/9 R.C.A. American Valves, 50 popular types; also National Union, Hytron; also British non ring valves, cheapest in Britain; ½d. stamp for revised lists.—Shippers, 18, Corporation St., Manchester. [0607

METROPOLITAN RADIO SERVICE.—Special offer: American valves, in makers' cartons, 3/- each; Octals, 3/6 each; American valves, first grade, in all types; trade supplied.—1021, Finchley Rd., N.W.11. Speedwell 3000. [0436

## COMPONENTS

### SECOND-HAND, CLEARANCE, SURPLUS, ETC.

RADIO CLEARANCE, Ltd.

ALL Lines Previously Advertised Still Available.

RADIO CLEARANCE, Ltd., 63, High Holborn, W.C.1. Holborn 4631. [8470

PREMIER SUPPLY STORES.

PLEASE See Our Displayed Advertisement on page 5. [0488


*Third Edition of*

# WIRELESS DIRECTION FINDING

BY R. KEEN, B.Eng.

A BOOK OF INSTRUCTION AND REFERENCE FOR ENGINEERS, TECHNICIANS, TELEGRAPHISTS AND OTHERS ENGAGED OR INTERESTED IN THE USE OF DIRECTIVE WIRELESS TELEGRAPHY FOR THE NAVIGATION OF SHIPS AND AIRCRAFT.

The third edition of this well-known book deals with the principles of Wireless Direction Finding and gives an account of the circuits and apparatus used in its application to navigation. The Adcock Aerial has a separate chapter covering its principles together with much information on its installation and performance. Further chapters are included on Shore, Ship and Aircraft installations as well as a special section on the choice of a suitable site for the Aircraft Ground D.F., with Adcock Aerials.

Engineering students and research engineers will find useful references to a selected list of some 600 of the more important contributions to the literature of D.F.

800 pages 550 illustrations

PRICE:

25/- net By post 25/9

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

W.W. 60

## COMPONENTS—SECOND-HAND, CLEARANCE, SURPLUS, ETC.

RYALLS RADIO, 280, High Holborn, London, W.C.1, offer new goods, post free.

ELLIPTICAL Speakers, Celestion, suitable Ekco replacements, 750 and 1,250 ohms, less transformers, speech 25 ohms, new, handle 8 watts, carry up to 120 m.a.; 5/6 each.

NEW Ferranti Transformers, AF5, OPM16c (15/22/45-1), AF6c, OPM15c, OPM5 (4/7/10-1), AF15c, OPM6; all 6/9 each.

GARRARD AC Induction Type AC7a Gramophone Motors, with pick-ups complete, 200-250v., 12in. turntable and unit plate, auto. stop, speed regulator, new; 32/6 each.

WEARITE 110 k.c. I.F.'s with Top Trimmers, 1/6 each; sets band pass air core superhet coils, ex Halycon, screened chassis type, 4/9 set five; 110 kc. with coil details.

B.I. Tubular 4mf. 200v., 6d. each or 4/- dozen; B.I. 0.05, 1/3 dozen, 7/9 gross; B.L. 0.25 mf. tubulars, 2/- dozen. 4/6 per three dozen.

AMPLIFIERS, A.C.-D.C. type, output 13 watts, complete with valves and pair elliptical speakers, ready for use, push-pull output, 3-stage, 200-250v. input; 52/6 complete.

AMPLIFIERS, A.C. 200-250v. only, output 25 watts from pair 6L6 in push-pull, complete with speakers as above; 72/6.

SPEAKERS, pairs, brand new, elliptical cone speakers, made by first class firm, quality of reproduction outstanding, push-pull pentode transformer, fields 325 ohm for smoothing choke, 8,600 as bleeder, circuit available, handle 10-15w.: 14/- pair.—Ryalls Radio, see above. [8374

VAUXHALL UTILITIES, 163a, Strand, W.C.2.—Ask for free list; metal rectifiers, HT10, 10/-; HT9, 9/-.

VAUXHALL.—Hivac valves, all types; full range of pick-ups, from 11/-; screened iron-cored 2-gang coils, switch, circuit, 11/3.

VAUXHALL.—T.C.C. dry, 8 mfd., 2/6; 600v. aluminium containers; T.C.C. 600v. dry, cardboard containers, 8 mfd., 1/9. [8498

3 WAVE-BAND Tuning Packs for British Valves, aligned and tested; 3-gang H.F., F.C., 32/6 only; 465 K/C IFTs, for above, 2/6 each.—S.A. Radio, 293, Norwood Rd., S.E.24. [8495

COLLARO A.C./D.C. Record-changers, 200-250, plays eight 10in. or 12in. records, mixed, also incorporates repeater and rejector; limited quantity, £5/5, in sealed cartons.

HENRY'S, 72, Wellington Ave., Stamford Hill, N.15. Stamford Hill 2907. [8216

SOUTHERN RADIOS Bargains.—Sale now proceeding of hundreds of bargain lines, goods previously advertised still available.—Southern Radio, 46, Lisle St., London, W.C.1. Gerrard 6653. [8236

LONDON CENTRAL RADIO STORES.—All lines advertised in the last 3 issues still available; also endless bargains for callers.—London Central Radio Stores, 23, Lisle St., W.C.2. Gerrard 2969. [8504

STARTLING Improvement from Gramophone Reproduction Obtainable by the Use of the Famous Novotone Unit; used Novotones in stock at 1 gn.; also new units at 3 gns.—Halford Radio, 31, St. George St., W.1. [0635

MAINS RADIO DEVELOPMENT COMPANY Offer immediate delivery, carriage paid; call mornings, telephone Tudor 4046; stamp for list 227; Transatlantic all-wave tuning packs now available from stock, stamp for details.

DUBILIER Mica Tag Condensers, 0.00005, 0.0001, 0.0002, 0.0003, 0.0005 mfd.; 3d., 2/6 dozen.

AMAZING Resistor Bargain, N.S.F. ½, 1 and 2 watt, new, marked; colour coded resistors, 20 different useful sizes in parcel; 50 for 2/6 only.

CLIX Unused Chassis V-holders, 5-pin, 7-pin, 3d. each; all American sizes, 6d. each; best sleeving, 1½d. yd.; T.C.C. metal can 8 mfd., 600v. dry electrolytics, 2/3.

TUBULAR Condensers, 400 volt working, wire ends, best make, 0.0001-0.05 mfd., 4d.; 0.1 mfd., 4d.; 0.25, 0.5 mfd., 6d.

CENTRALAB Latest Potentiometers, long standard spindle, unused, all sizes, 5,000 ohms, 2 megohm., 2/-; with mains switch, 2/3.

POLAR Midget Latest Three-gang Condensers, screened, trimmers, ¼in. spindle, 0.0005 mfd., 110 k/c tracker, unused; 2/6.

ERIE One Watt, colour coded, unused resistors, any size, 50 ohms to 5 megohms, your selection, 3d., 2/6 dozen; two watt, 6d.

MAINS RADIO DEVELOPMENT COMPANY, 4-6, Muswell Hill Rd., London, N.6. Tudor 4046. [8457

### Wanted

WANTED, surplus electrical goods.—Description, quantity and price to Box 9866, c/o *The Wireless World*. [8497

WE Buy for Cash All Types of Modern Second-hand Radio Sets and Accessories, test meters, parts, etc. We pay more than any other dealer. Part exchanges. Bring, send or will call.—University Radio, Ltd., 238, Euston Rd., London, N.W.1. 'Phone: Euston 3810. [8494

## REPAIRS AND SERVICE

"SERVICE With a Smile."

AMERICAN Valves, spares, linecords, rewinds; repairers of all types of American and British receivers.—F.R.I., Ltd., 22, Howland St., W.1. Museum 5675. [0434

BAKERS.—Send your next speaker repair, any make, to the pioneer manufacturers, Bakers Selhurst Radio, South Croydon. [8435

LOUD-SPEAKER Repairs, British, American, any make, 24-hours service; moderate prices.—Sinclair Speakers, Alma Grove, Copenhagen St., N.1. [0590

# PETO-SCOTT

"Wireless World" Cathode Ray

## OSCILLOSCOPE

### TIME BASE and AMPLIFIER

**KIT "A"** *Cash or C.O.D. Carriage Paid.* **£7 : 3 : 6**

*or Deposit* 12/6 *and* 12 *monthly payments of* 12/5.

Comprising all parts for Time Base and Amplifier only, to "Wireless World" specification, including Haynes Mains Transformer, Aluminium Chassis, Peto-Scott switch, screws, wire and sleeving but less all valves.

**OSCILLOSCOPE KIT "A" £4 : 10**

*or Deposit* 8/- *and* 12 *monthly payments of* 7/10.

Comprises all components for Oscilloscope only, including specified Mains Transformer, Chassis Assembly, wire, flex and screws but less valve and Cathode Ray tube.

**COMPLETE KIT** *Cash C.O.D.* **£17:8:0**

*or Deposit* £4 : 10 : 0 *and* 12 *monthly payments of* £1 : 4 : 3

Comprising all parts supplied in above "A" Kits plus all specified valves and Cathode Ray Tube.

### W.W. DC SUPER

**RECEIVER KIT "A"** Cash C.O.D. **£9 : 7 : 9**

*or Deposit* 16/3 *and* 12 *monthly payments of* 16/3.

Kit "A" comprises all parts to "Wireless World" specification for the Receiver Kit only and includes Peto-Scott Switch Assembly, ready-drilled Tuner and Receiver Chassis, all wire, flex and screws but less valves.
4 specified valves 38/- or add 3/3 to Kit "A" deposit and monthly payments.

**KIT BITS.** Supplied in Kit "A."

PETO-SCOTT specified SWITCH ASSEMBLY ..... 17/6
PETO-SCOTT specified TUNER CHASSIS ..... 11/6
PETO-SCOTT specified RECEIVER CHASSIS ..... 17/6

**W.W. ALL-WAVE TEST OSCILLATOR.** Finished Instrument to recent "Wireless World" designer's circuit. Complete in Cabinet with calibrated scale. Price £6.10.0, less batteries. Trade supplied.

**PETO-SCOTT Co. Ltd.** *Established* 1919

77 (W.W.16), City Road, London, E.C.1 *Clissold* 9875-6-7.
*New Showrooms:* *Clerkenwell* 5911.
41 (W.W.16), High Holborn, London, W.C.1. *Holborn* 3248.

## THE INSTITUTE OF WIRELESS TECHNOLOGY

(Founded in 1925. Incorporated).

**PROFESSIONAL MEMBERSHIP**

**The advantages of professional membership are open to all qualified wireless engineers.**

*Full information, with syllabus, may be obtained from the Secretary, Institute of Wireless Technology, 4, Vernon Place, Southampton Row, London, W.C.1. 'Phone: Holborn 4879.*

# This John McClure

MODEL A.C.7.A.W.6. 6 waveband receiver chassis incorporates the famous ACT6 Tuning Unit, covering a wave range of 5.5—12.5 m., 12.5—35 m., 30—80 m., 75—200 m., 200—600 m. and 750—2000 m. Dual ratio drive H.F. stage on all bands, delayed AVC, undistorted beam power output of 5 watts.

**Our reputation for unrivalled performance is in every way upheld by this chassis.**

When we designed this model only a moderate demand was anticipated, but the sales have greatly exceeded our expectations. Producing in larger quantities enables us to buy material on a more economic basis with the result that the price, including valves, is now reduced from £18. 10. 0 to

**£16**

UNIVERSAL AC/DC Model U.7.A.W.6 (formerly £20) Price £17. 10. 0

*Particulars of other models on request.*

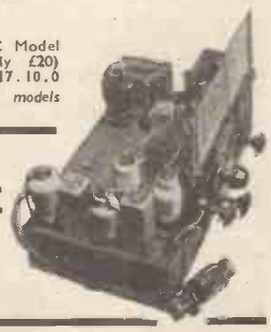

**JOHN McCLURE LTD.** (G6JM)
ERSKINE ROAD, LONDON, N.W.3.
*PRImrose 5435.*

## REPAIRS AND SERVICE

RADIO Service, all types receivers and amplifiers; aligning and testing constructors' sets a speciality; moderate rates.—S.A. Radio, 293, Norwood Rd., S.E.24. [8496

GUARANTEED Repairs Any Transformers, choke, motor armature, converter, dynamo, etc.; keenest prices, immediate quotation, prompt dependable service. —See below.

L.T.P. (LONDON TRANSFORMER PRODUCTS, Ltd.), Willesden, N.W.10. Willesden 6486 (3 lines). [6892

MAINS Transformer Service. Repairs, rewinds, or construction to specification of any type, competitive prices and prompt service.—Sturdy Electric Co., Dipton, Newcastle-on-Tyne. [0516

METROPOLITAN RADIO SERVICE.—Guaranteed repairs to American and British receivers; American valves, service parts and rewinds; trade supplied.—1021, Finchley Rd., N.W.1. Speedwell 3000. [0435

EPOCH Speaker Service.—Guaranteed replacement diaphragms, 20c., etc., 4/6; A2, B7, 99, etc., 10/-; Dominо, D4, etc., 15/-; auditorium and super cinema, 25/-; carriage paid; field coils, mains and output transformers rewound from 3/6.—L.S. and Radio Repair Services, 45, Crown St., Reading. [8490

REPAIRS to Moving Coil Speakers a Speciality; cones and coils fitted, fields altered; prices, including eliminators, quoted; loud speakers, 4/-; L.F. and output transformers, 4/-, post free; guaranteed satisfaction; trade invited, estimates free; prompt service.—Loud-Speaker Repair Works, 5, Balham Grove, London. Battersea 1321. [0394

## SITUATIONS VACANT

AIR MINISTRY.

DIRECTORATE of Signals.

APPLICATIONS are Invited for Appointment as an Assistant Signals Officer in the Civil Aviation Signals Service.

THE Commencing Salary will be Determined According to Qualifications and Experience, within the scale £350 rising by annual increments of £18 to £500 per annum.

THE Qualifications Required Are:—

EDUCATION to Degree Standard in Light Electrical Engineering. Experience in the design of modern radio transmitters and receivers.

PREFERENCE will be Given to Candidates who have not Reached their 45th Birthday, and who have the following additional qualifications.

EXPERIENCE in the Design, testing and installation of aircraft radio equipment.

A GENERAL Knowledge of the Application of Radio Aids in Aviation.

ADMINISTRATIVE Experience.

THE Officer will be Largely Concerned with Approval of New Types of Aircraft Radio Apparatus and his duties will be Mainly Administrative, but may involve occasional flying as an observer.

SUBJECT to a Period of Satisfactory Probation the Selected Candidate will be Eligible for Consideration for a Post on the Permanent Establishment when Vacancies Arise.

REQUESTS by Post-card for Forms of Application Should Reach the Under-Secretary of State, Air Ministry (S.1.e.), Adastral House, Kingsway, not later than 31st May, 1939, and the completed forms must be returned by 5th June, 1939. [8483

AMPLIFIERS.—Good opening for technician with factory experience; write in confidence, stating age and salary required.—Box 9847, c/o *The Wireless World*. [8485

VACANCY for Apprentices in Radio Manufacturer's Organisation, constructing transmitters and receivers for Government Departments; works situated in Surrey.—Write Box 9867, c/o *The Wireless World*. [8501

TELEPHONE and Radio Testers or Servicemen Required.—Write, stating age, education, experience and salary required, to Siemens Brothers & Co., Ltd., Telephone Installation Section, Woolwich, S.E.18. [8459

DRAUGHTSMAN (Junior), capable of producing finished radio circuit drawings from rough layouts, and chassis illustrations from photographs; no works experience necessary; permanent position.—"The Wireless and Electrical Trader," Dorset House, Stamford St., London, S.E.1. [8480

SERVICE Engineers.—A number of well-connected, first class, independent service engineers are required in all parts of the country to act as agents and service representatives for Scott-Radio Receivers; liberal commission paid and exclusive territory granted to successful applicants.—Write for details, enclosing particulars of your business to E. H. Scott Radio Laboratories, Ltd., 72a, Carlton Hill, N.W.8. [8488

## SITUATIONS WANTED

ENGINEER, University degree, good theoretical knowledge, 12 years' practice in radio and telephone design, seeks situation.—Write Radio Agency Tenser, Budapest, Szervitoter, Hungary. [8486

## ELECTRIC DRY SHAVERS

REMINGTON, Rand, Shavemaster, Packard and Gasco. —Trade enquiries to Leonard Heys, 36, Henry St., Blackpool. [0633

REPAIRS to All Makes of Electric Shavers, voltages changed.—Sinclair Speakers, Alma Grove, Copenhagen St., London, N.1. [0634

*"Wireless Direction Finding," Third Edition. Price 25s. net. Post free 25s. 9d.*

## ELECTRADIX BARGAINS!!!

**TRANSMITTERS SHIP KEYS** with massive contacts, 21/6. First-class Keys, balanced movement and heavy contacts of gold-silver, tungsten, etc. Panel Keys to fold up flat, 6/6. Fullerphone double acting Key, 6/6. 51KBSL R.A.F. Morse Key, solid lacquered brass on mahog. base, 7/6. Three-colour-light Switch Box with morse key for code signals, 4/6. Walter's enclosed Key, all bakelite, 10/6. Super Transmitting Radio Key, 51KE, 21/-.
**TAPE MORSE RECORDERS.** For radio to 30 w.p.m. or land line. New portable walnut case, very complete model with key and meter indicator. Standard G.P.O. type with tape reel on base. For experimenters we have a few incomplete with perfect spring drive. Paper tape reels, 6d.
**RELAYS.** Selector 25 way, 8 gang. Auto, 10/-. Single-blade No. 1 Relays, 1,000 ohms, 6/6. No. 2, 2,000 ohms, 8/-. C.O. Relays, No. 5, polarised 8/6 and so on. 16 distinct types in stock. Transmitters Relays, Sounder Type, 5 amps., 15/-. Yankee Ham Relays, 7/6. Ship Magnetic, 15/-. Creed Polarised, 2-way, 25/-. Ask for Relay brochure "S.W."
**SUPERSENSITIVE MOVING COIL RELAYS.** For operation from microamps. Small panel 2½" 50 m/ms. Relay W.1 for photo cells, 55/-. Lab. type Moving Coil Relays. Centre of 2 contacts. Paul & Weston cased. Fully guaranteed. Half price.
**5 METRE TRANSCEIVERS.** A.C. Mains type. Also eight portable battery type. 1½ metres Epoch with Lecher aerial with power pack. Cheap.
**TELESCOPES.** Navy Telescopes, hand spotters, 25/-. Gun type, 17/6.
**MAGNETIC 1½in. COMPASS** with Plain Scale. Bevel glass, brass body. A British Bargain for 9d. only.
**MOVING COIL MIKES.** Torpedo P.M. moving-coil mike, model T.M., needs no battery, directional correct frequency response, ideal for P.A. and recording, 55/-. Table stand, 7/6. Transf. 7/6. Epoch type ditto, a very robust and handsome P.M. M/C mike, 35/6; with table stand, 42/6. Transformer, 7/6.
**FLOOR STANDS,** 26in., 12/6; 37in., 15/-; 48in., 18/6.

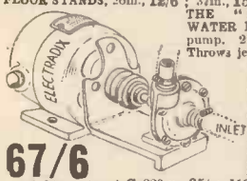


**67/6**

**THE "LESDIX BIJOU" ELECTRIC WATER PUMP** is a centrifugal, all-bronze pump. 2ft. lift. 120 gals. per hour. Throws jets 10ft. Runs for 20 hours for a unit. A.C. or D.C., any voltage supplied; or 12 or 50 volts D.C. Costs only 67/6. Supplied in hardwood case for 5/- extra. High lift Cesspool Pumps. Type "R" with electric motor, £5 10s.
**MOTOR BLOWERS. Fume Exhauster and Air Circulators.** Strong iron body, 2½in. fan, outlet, direct coupled to motor. A.C. 220-v., 65/-; 110-v. D.C., 45/-; D.C. 220-v., 55/-.
**BUZZERS.** Buzzers for Signals, Wave-meters or Testing. High Note Platinum contacts. List 10/-. Sale, 6/-. High Note "D.M." Buzzer in case, 3/6. Service Buzzer No. 24, 12/6. Dill Double Circuit Twin Buzzers, 10/-. 20 volt G.P.O. Buzzers, 3/6. Small Buzzer, 1/6. Large models, 2/6 and 3/-.
**BELLS. ALARM BELLS.** Mains, battery or magneto waterproof types. 1,000 British House Bells, wall and table. Priority for A.R.P. A.R.P. workers and especially Hams may want portable H.T. for emergency outdoor field transmitters. Portable Hand Generators in teak cases by Evershed. 800 and 1,600 volts D.C. Portable Field Emergency Telephone stations in leather case, light Army types. Battery type for key and speech. Not many left now. Light weight twin field cable unbreakable Army type, 55/- mile. Police and Fire Brigade, day and night Lucas and Aldis Army Signal lamps, telescopic sights, hand or tripod. Crystal sets, 7/6. Battery set kits, oak cabinet panel fitted 2 varia. condensers and range switch, terminal panel, etc., partly wired. Maker's surplus, 15/-.
**EMERGENCY ENGINE SETS.** Stuart petrol-electric sets, water-cooled, coupled to 30 volts 5 amp. dynamo, £12. 50 volts 10 amps, £17. Portable air-cooled engine sets, 2½ kW. for field charging.
**EDISON Steel Storage Cells. DYNAMOS** and Switchboards from 50 watts to 50 kW. Morse chains and wheels, 5/- set. Skewgear boxes, ½ h.p., 10/-. Gear boxes, 2-1 for ½ h.p., 4/6. Electric Governors, 7/6. Bowden R.A.F. Remote Controls, 18 points, 7/6.

**MERCURY**

**SWITCHES**

**S.P. MERCURY CONTACT TUBES,** 5 amps., 4/-; 10 amps., 5/-.
**THERMOMETERS.** Panel 2½in. dial, 5ft. ether tube, for distant indicating, reading 0 to 100 deg. Cent., 7/6. Cambridge ditto, 10/6.
**FOURNIER THERMOMETERS** by Cambridge Instrument Co., 4in. dial, 10-110 deg. Cent. Fitted adjustable electric contacts, 45/-. 12 in. right angle Immersion Thermom., to 150 Cent., 3/6.
**CINE PROJECTOR** 35 m.m. Powers No. 6, 35 mm. Dallmeyer lens and condenser, motor drive, on stand with lantern and arc, £7. Sound head with head Amplifier and spool box for talkies, £8.
**15-DAY TIME SWITCHES.** Venner 1 amp., 5 amps., 50 amps., 100 amps., 200 amps., cheap.

**LIGHT RAY CELLS.** Selenium, unmounted, 5/-, mounted 7/6 and 10/-. Raycraft outfit with relay, 45/-. Caesium Photo-cells, for Sound-on-Film and Ray Work, R.C.A., 25/-, as illus.; G.E.C., 25/- to £3/10/-. Beck Angle Prisms, mounted in carrier, 5/6.
**X-RAY TUBES.** Brand new W.D. pattern, cost 5 guineas, 12/6. Packing 2/6.
**MIRRORS.** 5½in. dia., Helio or Television, 1/6. Parabolic Concave, 20in., 25/-; 24in., 30/-. Carr. fwd. Neon Lamps, 2/6 and 3/- each with holder. Miniature Neons, 2/6.

*Send for the MAY BARGAIN LIST "W."*

**ELECTRADIX RADIOS**
218, UPPER THAMES STREET, LONDON, E.C.4
*'Phone: Central 4611*

**Pamphonic AMPLIFIERS**
Pamphonic Reproducers Ltd. (*Associated with PYE Ltd.*)
45, St. Pancras Way London, N.W.1.
'Phone: EUSton 1727.

**The Autocar** EVERY FRIDAY FOURPENCE
w.w16.


## MISCELLANEOUS

G.P.O. Engineering Dept (no experience required); commencing £3/13 per week; age 18-23; excellent prospects; free details of Entrance Exam. from B.I.E.T. (Dept. 574), 17-19, Stratford Place, London, W.1. [8396

EVERY Radio Dealer Who is Not a Regular Reader of "The Wireless and Electrical Trader" should send his trade card at once for a specimen copy and full details of the "Trader" Services. "The Wireless and Electrical Trader" has the widest influence, the largest weekly circulation, and is read by all the leading manufacturers and traders. Trade only, 15/- per annum, post free.—Published at Dorset House, Stamford St., London, S.E.1. [0615

"ENGINEER'S Guide to Success" Shows How to Qualify in Television Radio Engineering and Servicing, sound recording, wireless communication, etc., by studying at home with the T.I.G.B. Write to-day for this Great Guide—free—which gives full particulars, contains the world's widest choice of engineering courses—over 200—and alone gives the regulations for qualifications such as A.M.I.E.E., A.M.I.R.E., A.M.I.T.E., A.M.I.W.T., C. and G., etc. Training until successful guaranteed.—The Technological Institute of Great Britain, 82, Temple Bar House, London, E.C.4. (Founded 1917. 20,000 successes.) [8409

## PATENT AND TRADE MARK AGENTS

GEE and Co. (H. T. P. Gee, Mem. R.S.G.B., etc.), 51-52, Chancery Lane, London, W.C.2. Holborn 4547-8. Handbook free. [0001

## BUSINESSES AND PROPERTY FOR SALE, TO BE LET, OR WANTED

"THE Wireless and Electrical Trader" is an essential part of the equipment of every Wireless Trader; its pages reflect the very latest turn of trade events, and it is read by all the leading dealers and manufacturers, for particulars of businesses offered or wanted. By subscription to the trade only, 15/- per annum, post free.—Send your trade card for specimen copy to Dorset House, Stamford St., London, S.E.1. [0614

NEED for Radio and Cycle Dealer on Large New Estate. Main road position. Success assured. No premium.—Apply Fairway Homes, Mutton Lane, Potters Bar. Tel.: 931. [8477

## TUITION

RADIO Training.—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0611

WIRELESS.—Complete training, Marine, Broadcast and Television. Posts waiting. Mod. fees. Boarders taken. Approved college, prosp.—Dept. W., London Radio College, Grove Park Rd., London, W.4. (Chi. 3244.) [0580

## BOOKS, INSTRUCTION, ETC.

ALL Wireless and Radio Engineering Books Available on New Financial Terms, as low as 2/6 monthly.—Write a card for details from Phœnix, Chandos Place, W.C.2. [8484

CATHODE Ray Tubes.—40 pages of valuable practical data on "How to Use Them" (by J. H. Reyner, B.Sc., A.I.M.E.E.), 30 instructive photographs of waveforms, etc., 1/1 post free from Furzehill Laboratories, Boreham Wood, Herts. [8503

AMERICAN Valve Data.—The new 200-page Raytheon Valve Data Book gives full characteristics and applications of all types of American valves; invaluable to all servicemen; post free, 2/3; abroad, 3/-.—Leonard Heys, 36, Henry St., Blackpool. [0594

"THE Wireless World" Diary for 1939 contains 77 pages of facts, formulæ and general information of the kind that is always wanted but is difficult to follow. Also a list of the most important European Broadcasting Stations and short-wave stations of the world. Twelve pages of circuit diagrams of receivers, amplifiers and units.—By post 1/7 from Iliffe & Sons, Ltd., Dorset House, Stamford St., London, S.E.1.

"FOUNDATIONS of Wireless." By A. L. M. Sowerby, M.Sc. Second edition. An elementary textbook on receivers. Deals fully with the construction of wireless sets, valves, and the process of detection. Price 4/6 net. By post 4/11, from Iliffe and Sons, Ltd., Dorset House, Stamford Street, London, S.E.1.

"RADIO Data Charts." By R. T. Beatty, M.A., B.E., D.Sc. Second edition. A series of Abacs providing most of the esential data required in receiver design and enabling problems to be solved without having recourse to complicated mathematical formulæ. Price 4/6 net. By post 4/10, from Iliffe and Sons, Ltd., Dorset House, Stamford St., London, S.E.1.

"ELEMENTARY Principles of Wireless Telegraphy and Telephony." By R. D. Banguay. Revised by O. F. Brown, B.Sc. Third edition (1930). The standard textbook for wireless students and beginners. Deals with the whole subject of wireless telegraphy and telephony, avoiding too technical a treatment of the problems involved. Well illustrated. Price 7/6 net. By post 8/-, from Iliffe and Sons, Ltd., Dorset House, Stamford St., London, S.E.1.

### Wanted

WANTED, good second-hand copy Appleton's "Thermionic Vacuum Tubes."—Longstaff, Australia House, Strand, W.C.2. Tem. 1188. [8479


***Fourth Edition—Revised and Enlarged with 50 additional pages***

# WIRELESS SERVICING MANUAL

## By W. T. COCKING

(*of "The Wireless World"*)

**The most complete book of reference of its kind. A reliable practical guide for amateur and professional.**

***BOUND IN CLOTH BOARDS. SIZE 7½ ins. × 5 ins. 288 PAGES***

**5/- net. By post 5/5**

*Issued in conjunction with "THE WIRELESS WORLD" and Published by the Proprietors :—*

**ILIFFE & SONS LTD.**
**DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1**

W.W20.


## INDEX TO ADVERTISEMENTS


| | PAGE |
|---|---|
| A.C.S. Radio | |
| Air Ministry | |
| Armstrong Manufacturing Co. | 4 |
| Automatic Coil Winder Co., Ltd. | 2 |
| Belling & Lee, Ltd. | |
| Birmingham Radiomart G5N1 | 5 |
| British Institute of Engineering Technology | 6 |
| British Insulated Cables, Ltd. | |
| British McMurdo Silver Co., Ltd., The | |
| British Rola, Ltd. | 4 |
| British Thomson-Houston Co., Ltd., The | Inside Back Cover |
| Capstan Cigarettes | |
| Degalliers | |
| Dubilier Condenser Co., Ltd. | 1 |
| Edison Swan Electric Co., Ltd. | |
| Electradix Radios | 8 |
| Evrizone Radio & Television Co., Ltd. | |
| Galpin's Electrical Stores | |
| General Electric Co., Ltd. | 1 |
| Goodmans Industries, Ltd. | 3 |
| Hartley Turner Radio, Ltd. | |
| Haynes Radio, Ltd. | 1 |
| Henley, W. T., Telegraph Works Co., Ltd. | 3 |
| Institute of Wireless Technology | 7 |
| International Correspondence Schools | |
| Jackson Bros. (London), Ltd. | |
| London Radio Supply Co. | |
| Marconi's Wireless Telegraph Co., Ltd. | 2 |
| McClure, John, Ltd. | 7 |
| Pamphonic Reproducers, Ltd. | 8 |
| Peto-Scott Electrical Instruments (Holdings), Ltd. | 7 |
| Players Cigarettes | Inside Back Cover |
| Premier Supply Stores | 5 |
| Quartz Crystal Co. | |
| Salford Electrical Instruments, Ltd. | Inside Front Cover |
| Savage, W. Bryan, Ltd. | 5 |
| Sound Sales, Ltd. | 6 |
| Taylor Electrical Instruments, Ltd. | |
| Universal Electric | |
| Varley, Ltd. | 3 |
| Vortexion, Ltd. | 5 |
| Welburn Radio, Ltd. | 6 |
| Wingrove & Rogers, Ltd. | 2 |


Printed in England for the Publishers, ILIFFE AND SONS LTD., Dorset House, Stamford Street, London, S.E.1, by The Cornwall Press Ltd., Paris Garden, Stamford Street, London, S.E.1. "The Wireless World" can be obtained abroad from the following: France: W. H. Smith & Son, 248, Rue Rivoli, Paris; Hachette et Cie, Réaumur, Paris, and branches; Messageries Dawson, 4, Rue de Faubourg Poissoniere, Paris. BELGIUM: W. H. Smith & Son, 74-75, Boulevard Adolphe Max, Brussels. AUSTRALIA: Gordon & Gotch, Ltd., Melbourne (Victoria), Sydney (N.S.W.), Brisbane (Queensland), Adelaide (S.A.), Perth (W.A.), and Launceston (Tasmania). NEW ZEALAND: Gordon & Gotch Ltd., Wellington Auckland, Christchurch and Dunedin. INDIA: A. H. Wheeler & Co., Bombay, Allahabad and Calcutta. CANADA: Imperial News Co., Toronto, Winnipeg and Vancouver; Benjamin News Co., Montreal; Gordon & Gotch, Ltd., Toronto. SOUTH AFRICA: Central News Agency, Ltd.; Wm. Dawson & Sons (S.A.), Ltd., Cape Town. UNITED STATES: The International News Co., New York.

N.C.C.451E

# SOUND AMPLIFYING EQUIPMENT

B T-H

**Rack and Panel or Portable Equipments to suit particular requirements**

***AMPLIFIERS***—Units of 10 to 120 watts undistorted output. (Volume expansion and contraction when required).

***MICROPHONES***—Carbon, Ribbon, or Moving Coil.

***SPEAKERS***—
**Indoor:**— 6 ins. to 10 ins. Cone P.M. units.
**Outdoor:**— 3 ft. and 6 ft. Horns; metal diaphragm units.

*When sending in your enquiries, please state approximate area to be served, and power supply.*

***To Sound Reproducer Sales—***

**BTH RUGBY**

THE BRITISH THOMSON-HOUSTON COMPANY LIMITED, RUGBY, ENGLAND
A2710N

# LEARNING MORSE

AN EASY METHOD OF MASTERING THE INTERNATIONAL SIGNAL CODE

*Published from the Offices of* ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1

The **Wireless World** 6D NET BY POST 7d.

W.W.94

# The ELECTRICAL REVIEW

*The Complete Technical Journal*

Practical articles on all aspects of electricity supply and utilisation — industrial, commercial and domestic. Latest news of the electrical industry and developments. Advertisement pages form a comprehensive buyers' guide.

*Contents of May 26th Issue:—*

**NEW PLANT AT BRIMSDOWN**
High-pressure boiler and generating equipment installed by the North Metropolitan Company.

**BLENDED LIGHT**
The use of gas-filled and mercury-vapour lamps in combination for shop-window lighting.

**A SWISS VISIT**
A description of the Swiss National Exhibition and some leading electrical engineering works.

**THE E.T.U.**
One of the series "Organisations of the Industry," giving an account of the Union's history and activities.

EVERY FRIDAY 6d. Subscriptions: United Kingdom £1 14 8 Canada £1 12 6 Other Countries £2 1 6 per annum, post free.

**ELECTRICAL REVIEW LTD.**
**Dorset House, Stamford Street, London, S.E.1**

*THE*

# WIRELESS ENGINEER

**The Journal for Professional Engineers and Advanced Wireless Experimenters**

Monthly **2/6 net.** Annual Subscription **32/- post free.**

ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1

W.W.2

*What Does*

# BEVERLEY BAXTER

*say about it?*

The news is often confusing. One thing seems to contradict another, and events move too fast for a plain man to make up his mind.

That is why thousands of people turn to Beverley Baxter's article in the SUNDAY GRAPHIC. They know that his views are sound, clear and logical. They can rely upon Beverley Baxter, M.P.

*Every Sunday in the*

# SUNDAY GRAPHIC

*Best for News, Views and Pictures*